

CSE 2021

Computer Organization

Hugh Chesser, CSEB
1012U




W5-W

Combinational Logic: Design of a 1-bit adder (2)



Step 2: Derive the Boolean expression for each output from the truth table

INPUTS			OUTPUTS	
a	b	c (CarryIn)	CarryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$\text{Sum} = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$
$$\text{Carryout} = \bar{a}bc + a\bar{b}c + abc + abc$$




Combinational Logic: Design of a 1-bit adder (3)

Step 3: Simplify the Boolean expression

$$\text{Carryout} = \bar{a}bc + a\bar{b}c + abc\bar{c} + abc = bc + ac + ab$$

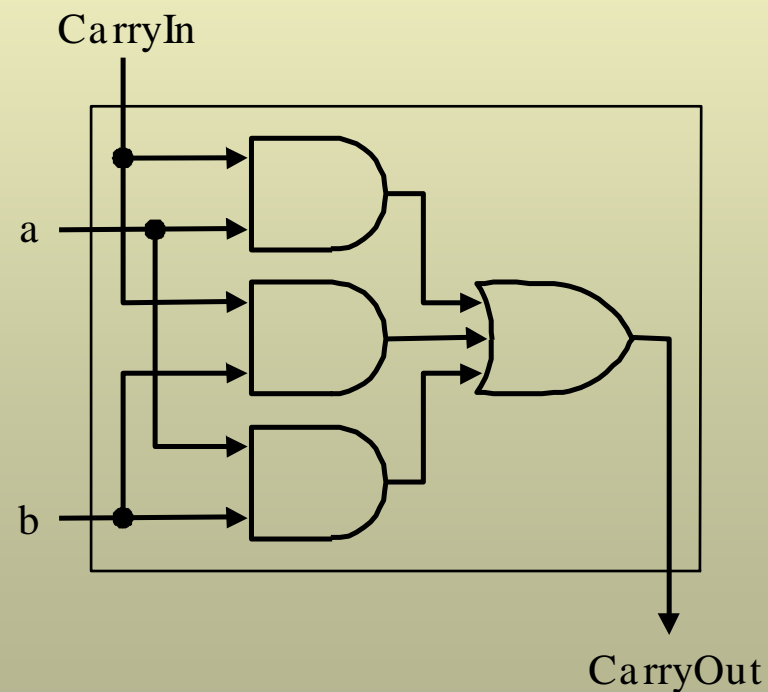Step 4: Implement the simplified Boolean expression using OR, AND, and NOT gates



Activity: Implement the hardware for the Sum output of the 1-bit adder



Agenda for Today



- Introduction to Hardware – Logic Design

Patterson: Appendix C



1-bit adder

 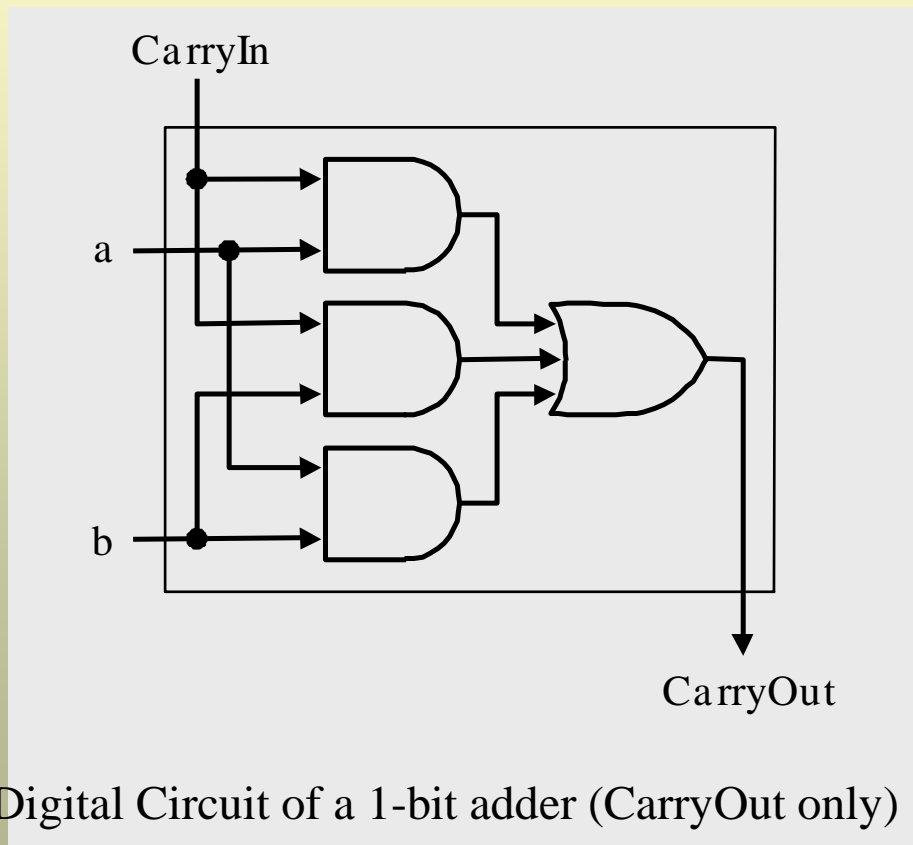
- Recall the digital circuit of a 1-bit adder
- We will enhance the 1-bit adder to develop a prototype ALU for MIPS






1-bit ALU with AND, OR, and Addition

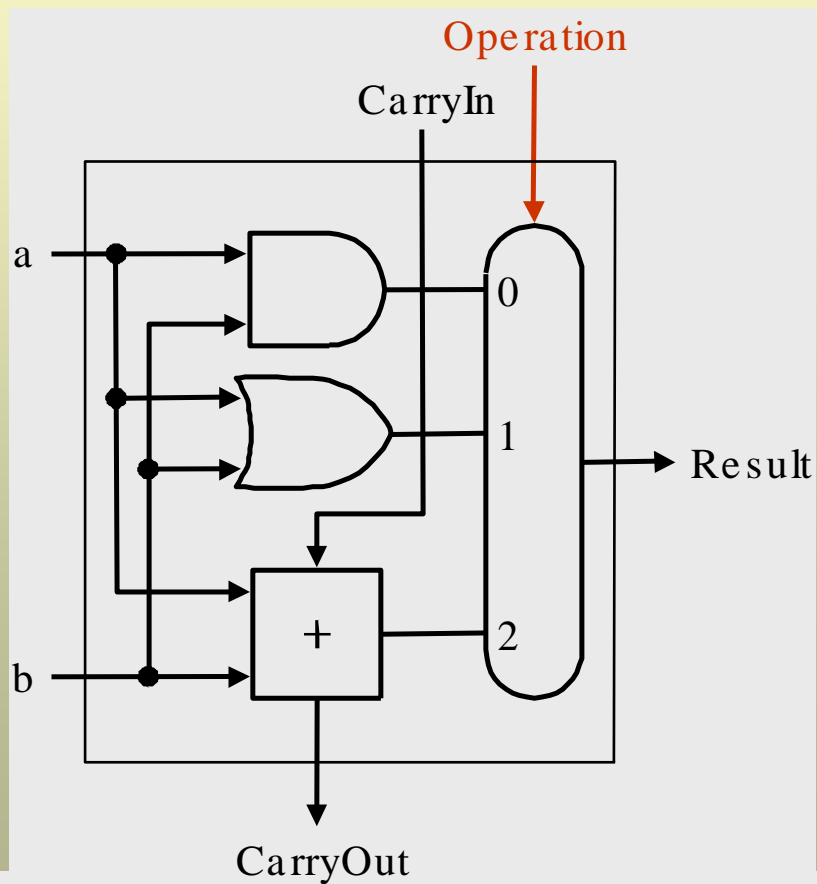- The 1-bit adder is supplemented with AND and OR gates
- A multiplexer controls which gate is connected to the output



1-bit ALU with AND, OR, and Addition capability

ALU Control Lines		Result
Carry In	Operation	
0	$0 = (00)_{\text{two}}$	AND
0	$1 = (01)_{\text{two}}$	OR
0	$2 = (10)_{\text{two}}$	add

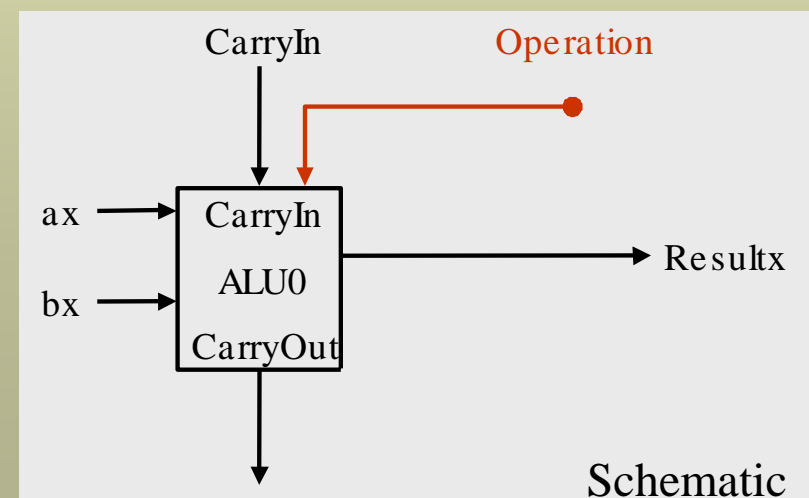


Schematic

32-bit ALU w/ AND, OR, and ADD

- The 1-bit ALU can be cascaded together to form a 32 bit ALU
- Which operation is performed is controlled by the Operation bus

ALU Control Lines		Result
Carry In	Operation	
0	0 = (00) _{two}	AND
0	1 = (01) _{two}	OR
0	2 = (10) _{two}	add

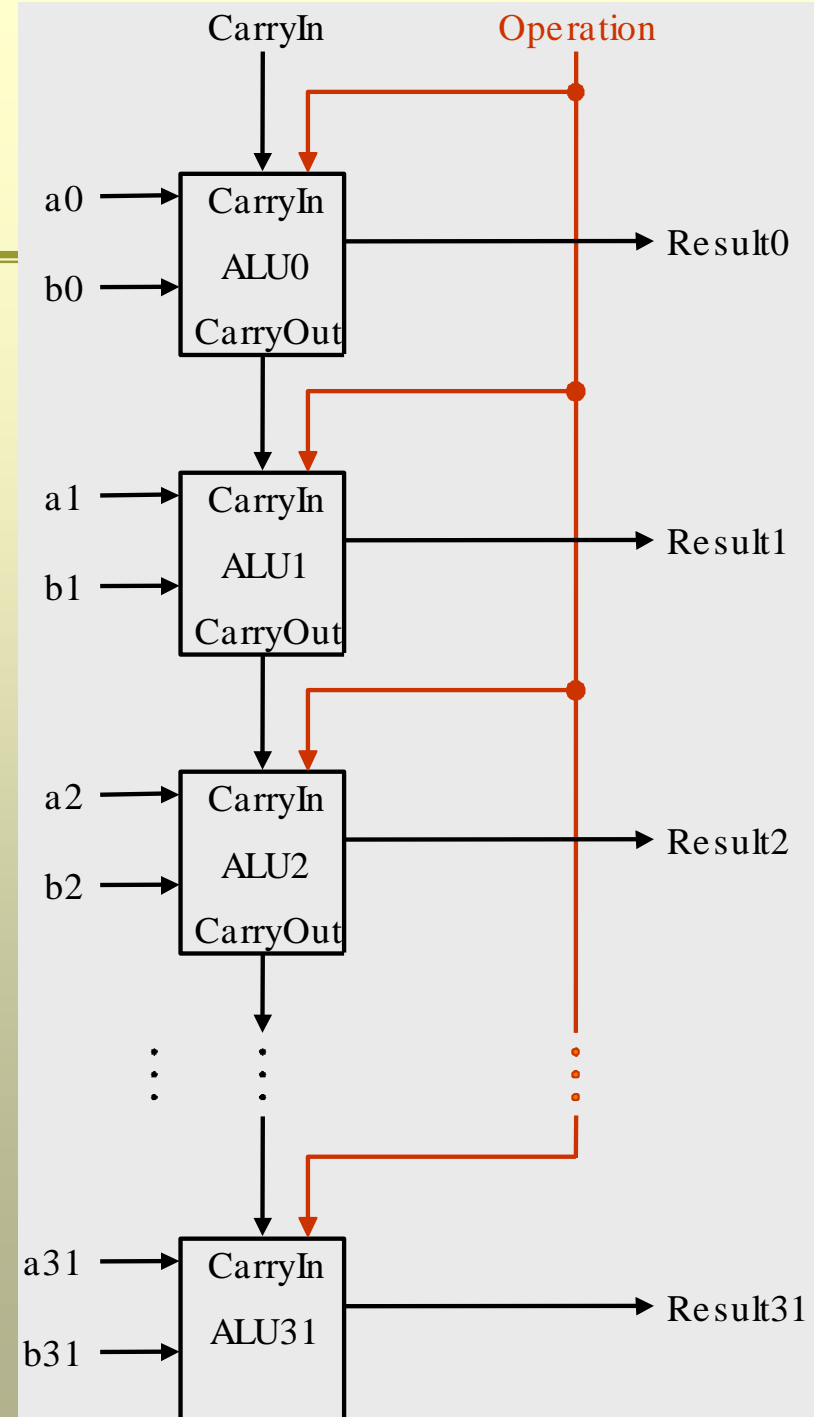
- The designed 32-bit ALU is still missing the subtraction, slt (set if less than), and conditional branch operations



1-bit ALU with AND, OR, Addition, and Subtraction



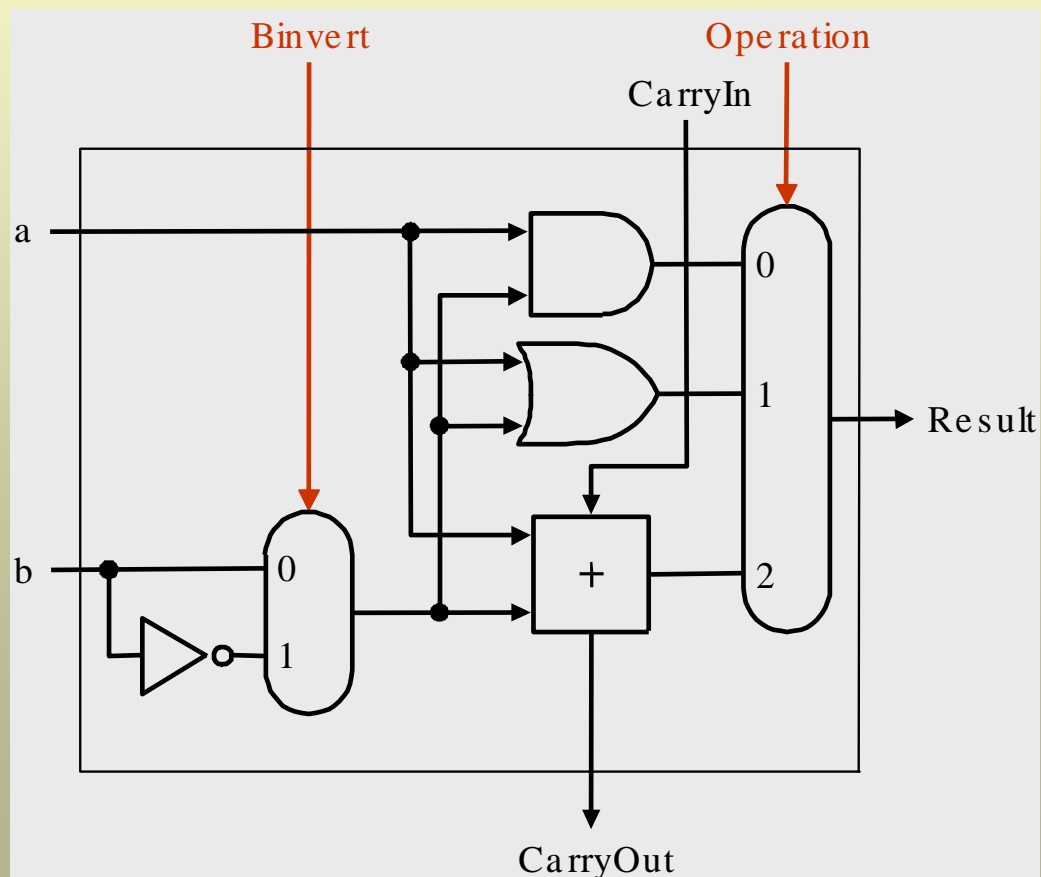- Recall that subtraction is performed using 2's complement arithmetic
- We calculate the 2's complement of the sub-operand and add to the first operand




ALU Control Lines			Result
Binvert	Carry In	Operation	
0	0	0 = (00) _{two}	AND
0	0	1 = (01) _{two}	OR
0	0	2 = (10) _{two}	add
1	1	2 = (10) _{two}	sub

1-bit ALU with AND, OR, Add, Sub, and SLT (1)



- Since we need to perform one more operation, we increase the number of inputs at the multiplexer by 1 and label the new input as **Less**
- **SLT operation:**
 - if $(a < b)$, set Less to 1
 - \Rightarrow if $(a - b) < 0$, set Less to 1
- SLT operation can therefore be expressed in terms of a subtraction between the two operands.
- If the result of subtraction is negative, set Less to 1.
- How do we determine if the result is negative?

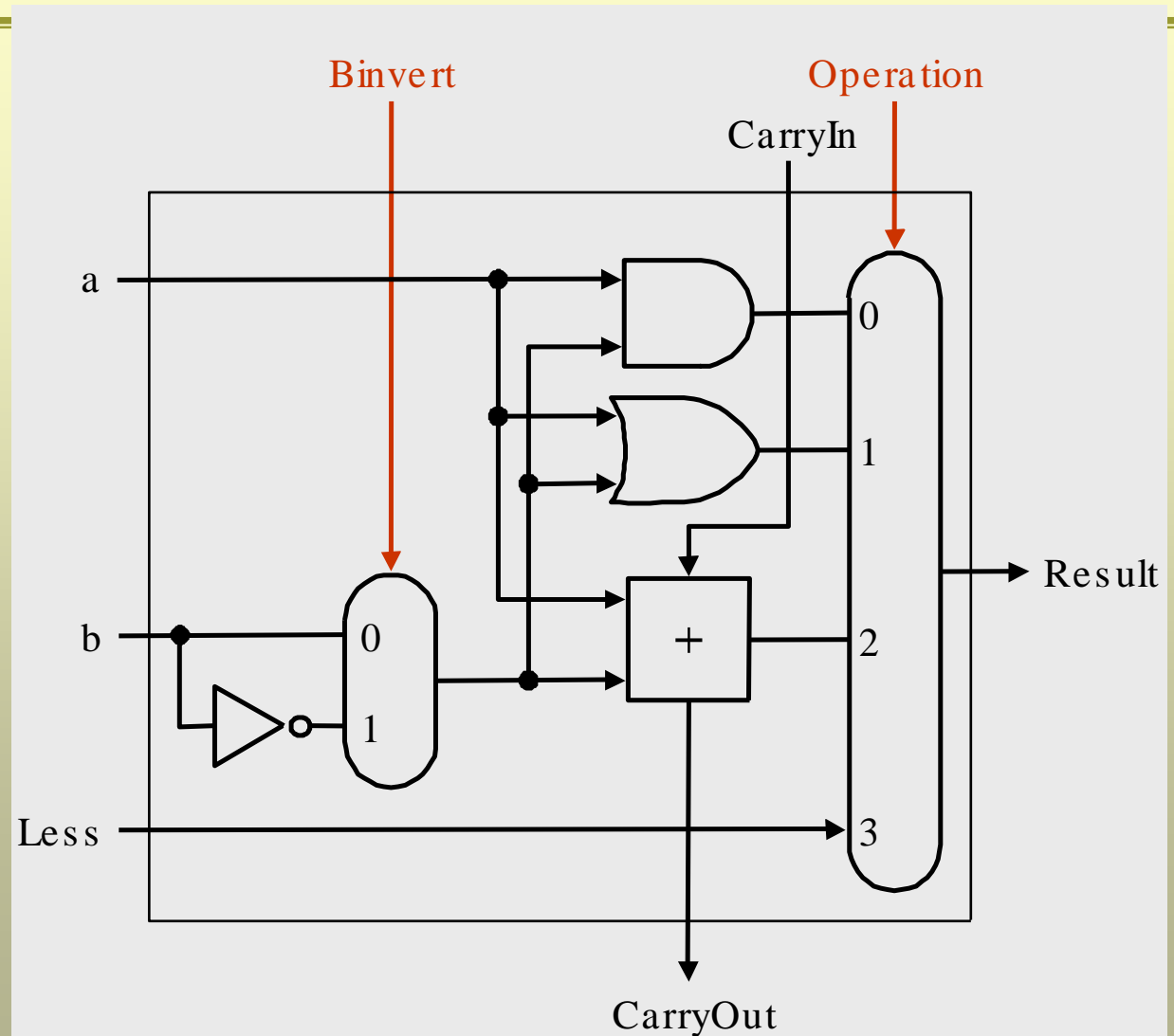


1-bit ALU with AND, OR, Add, Sub, and SLT capability

1-bit ALU with AND, OR, Add, Sub, and SLT (2)



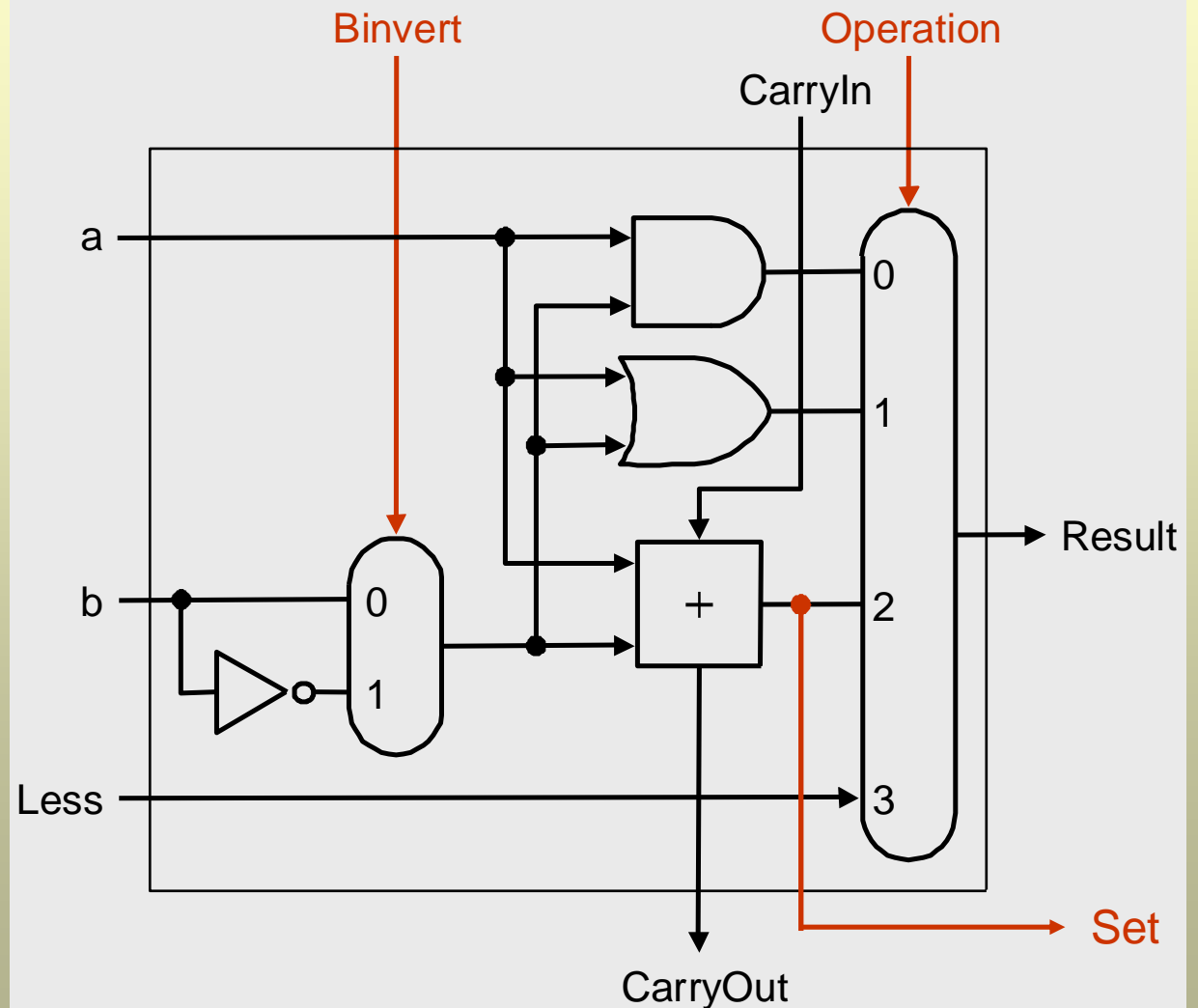- Use the sign bit obtained from the 1-bit ALU at the MSB position to indicate the result of SLT.




1-bit ALU of MSB (bit 31) with AND, OR, Add, Sub, and SLT capability

1-bit ALU with AND, OR, Add, Sub, and SLT (3)



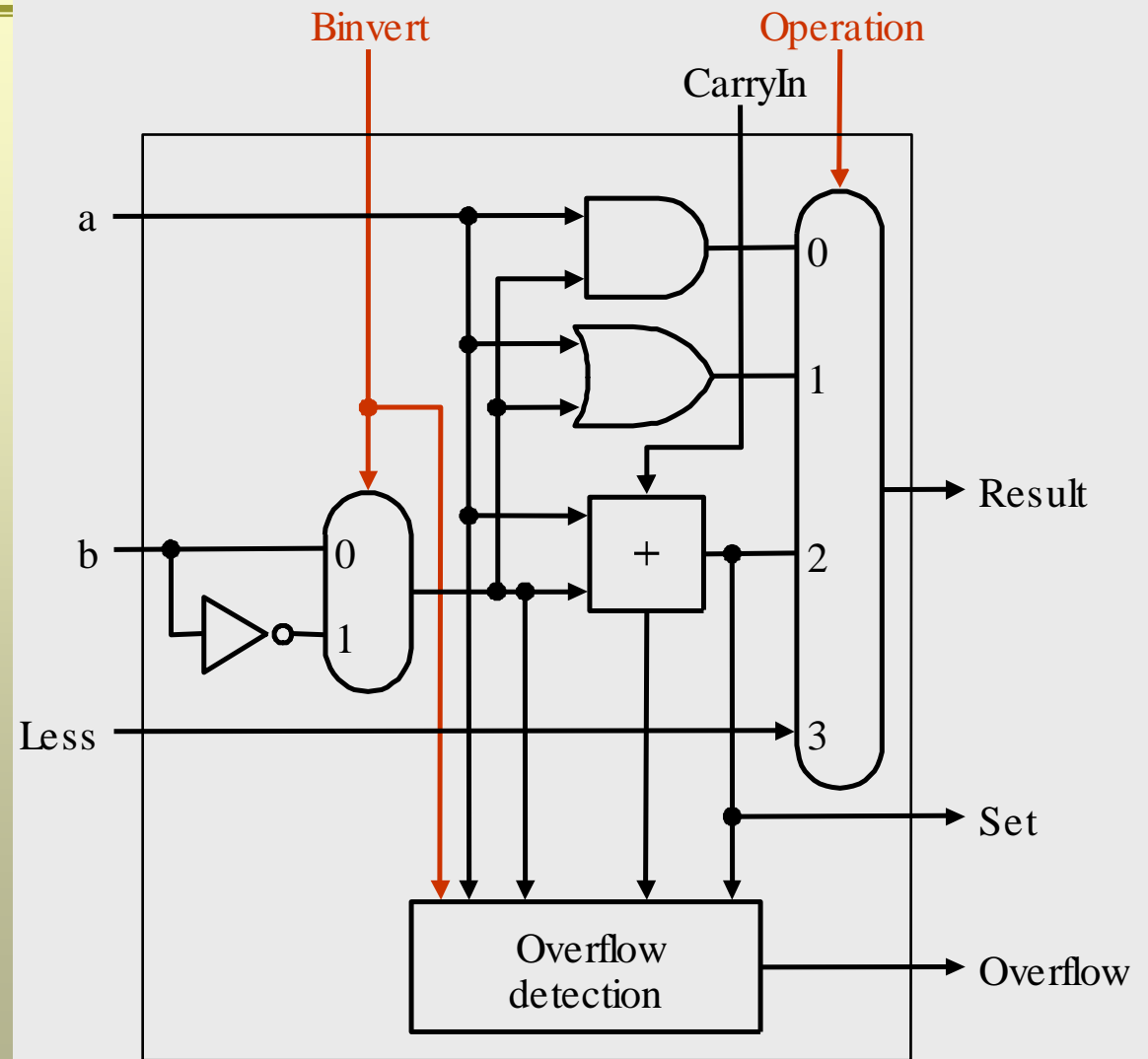- In fact we also include the overflow circuit within the 1-bit ALU at the MSB





1-bit ALU of MSB (bit 31) with AND, OR, Add, Sub, SLT, and overflow



1-bit ALU (4)



1-bit ALU for bits (0 – 30)

 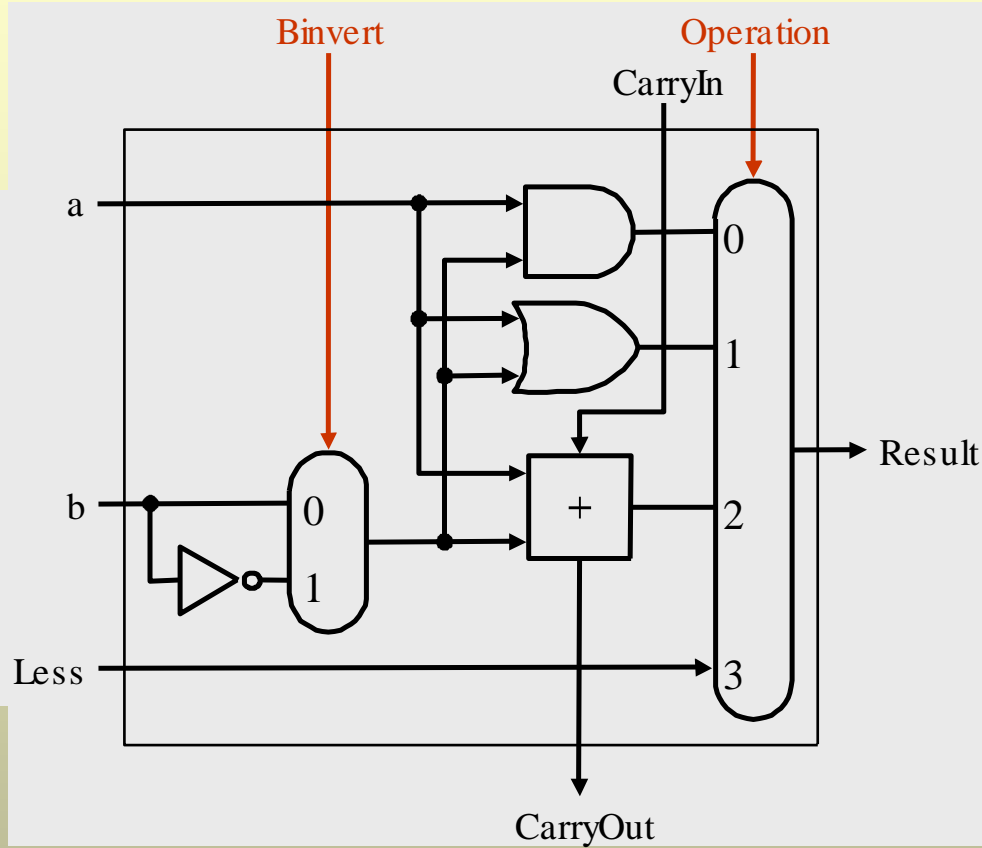

1-bit ALU for MSB (bit 31)

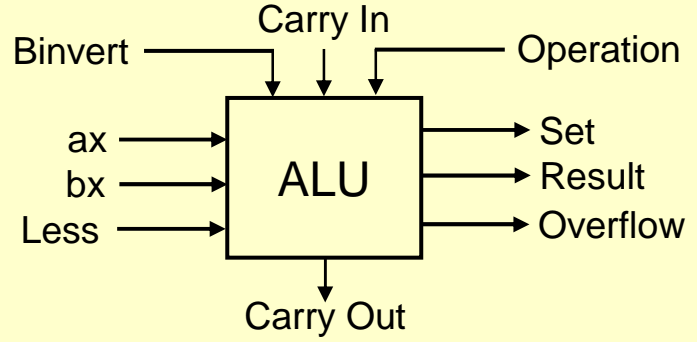 

W5-W

32-bit ALU


w/ And, OR, Add, Subtract, and SLT

- The 1-bit ALU's can be cascaded together to form a 32 bit ALU
- Operations are controlled by the Operation bus

ALU Control Lines			Result
Binvert	Carry In	Operation	
0	0	0 = (00) _{two}	AND (a·b)
0	0	1 = (01) _{two}	OR (a+b)
0	0	2 = (10) _{two}	Add sum(a,b)
1	1	2 = (11) _{two}	Subtract (a - b)
1	1	3 = (11) _{two}	SLT Set Result0 if (a < b)


- Note that Binvert is always the same as Carry In
- To test equality between a and b , subtract b from a and check if the result is 0.

W5-W

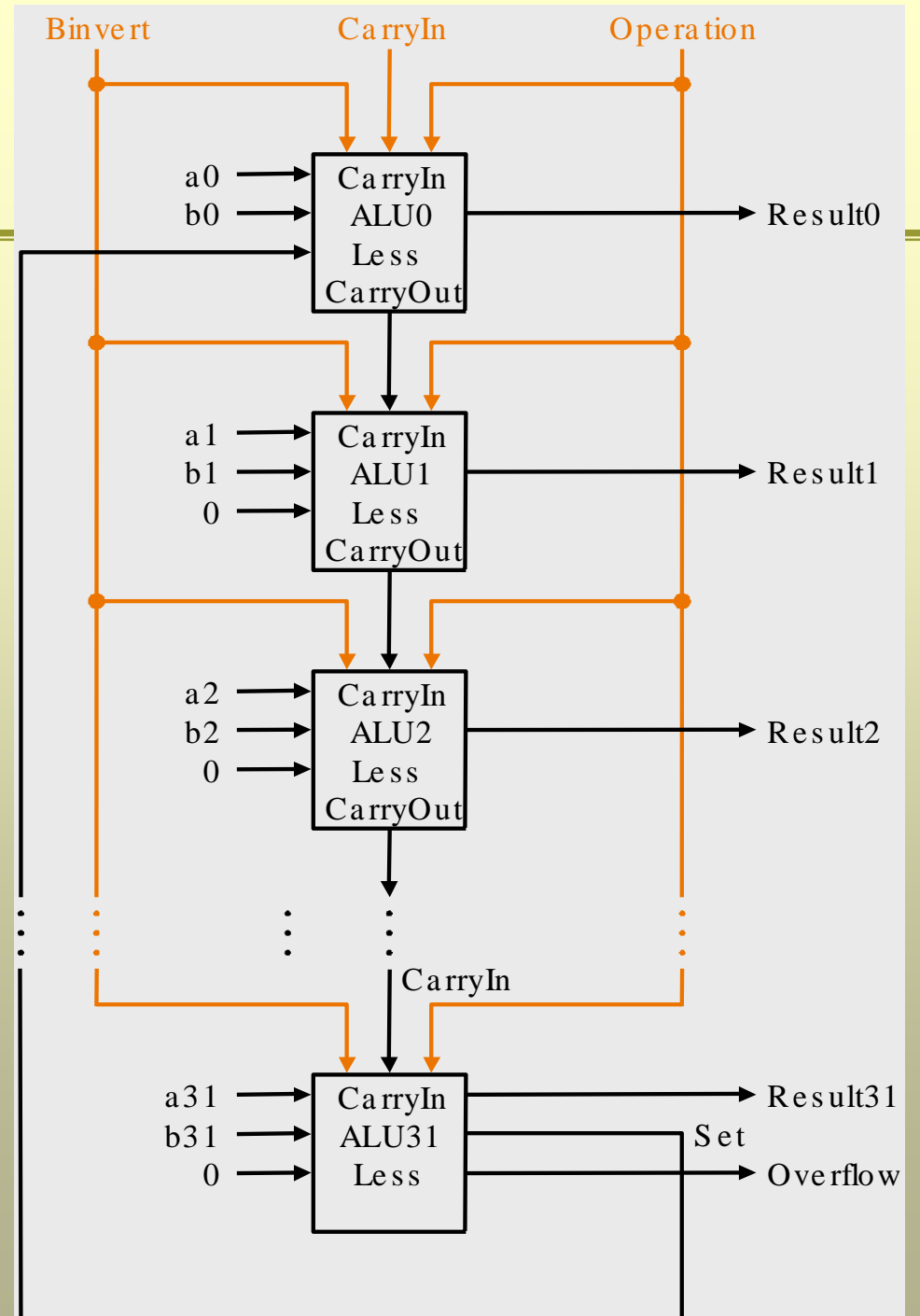

32-bit ALU w/ And, OR, Add, Subtract, SLT, and Equality Test

ALU Control Lines			Result
Binvert	Carry In	Operation	
0	0	$0 = (00)_{two}$	AND ($a \cdot b$)
0	0	$1 = (01)_{two}$	OR ($a + b$)
0	0	$2 = (10)_{two}$	Add $sum(a,b)$
1	1	$2 = (10)_{two}$	Subtract ($a - b$)
1	1	$3 = (11)_{two}$	SLT if ($a < b$) Result0 = 1
1	1	$2 = (10)_{two}$	Test Equality Zero = 1 if ($a < b$)

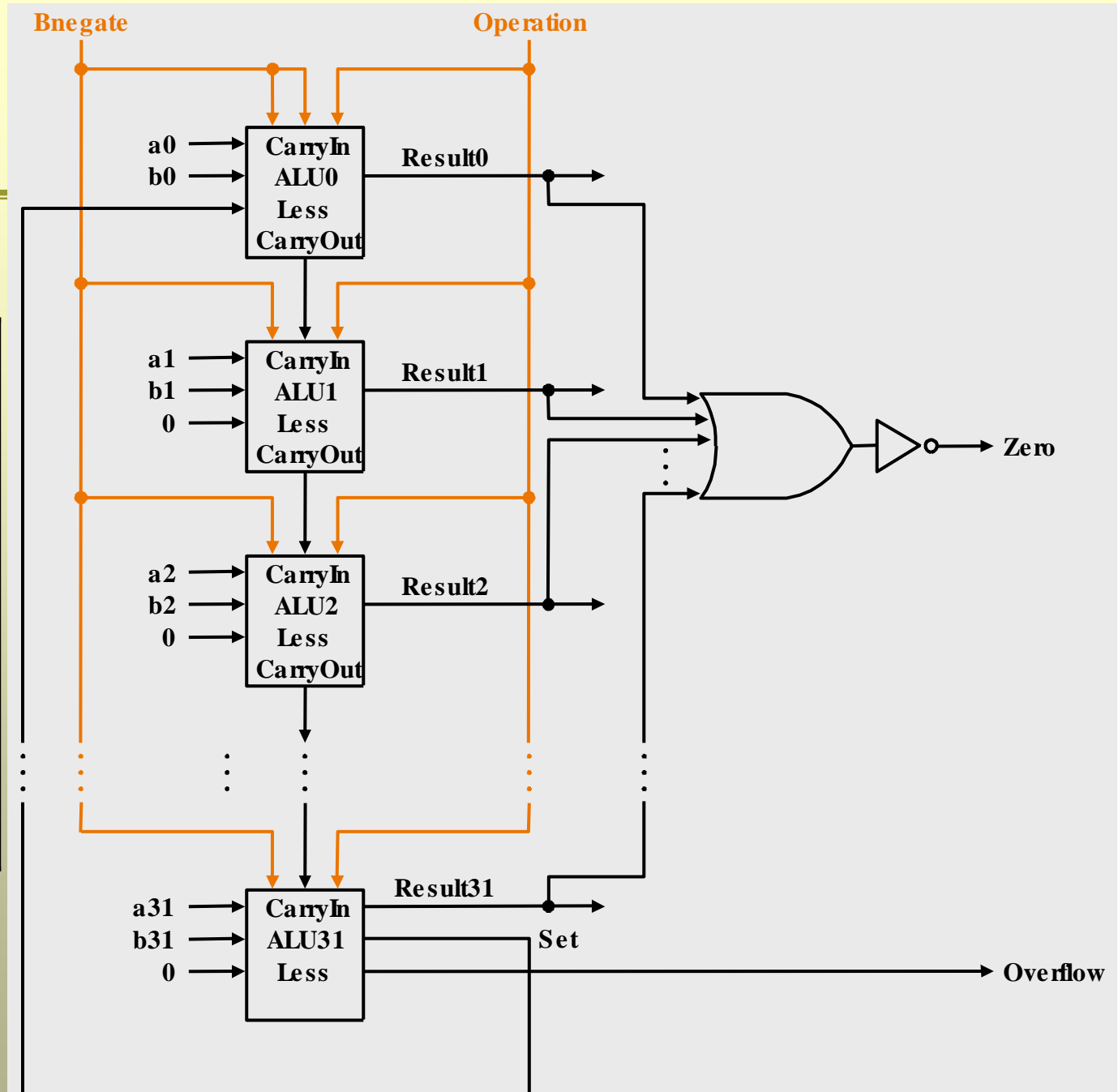

32-bit ALU w/ And, OR, Add, Subtract, SLT, and Equality Test

