

CSTE 2021 COMPUTER ORGANIZATION

HUGH CHESSER,
CSTE B 1012U





Agenda

Topics:

1. Basics: Clock, Latches and Flip Flops
2. Sequential and Combinational Circuits

Patterson: Appendix C, Section 4.1, 4.2, 4.3

Schedule, Reminders



*Allowed aids
for the
midterm:*

- Green Sheet
- 8.5 x 11 Cheat Sheet

WEEK OF	Mon	Wed	Lab	Topic
Sep 07	-	□	-	Overview of the course
Sep 14	□	□	-	Performance and Data Translation
Sep 21	□	□	A	Code Translation
Sep 28	□	Quiz #1	B	Translating Utility Classes
Oct 05	□	□	C	Translating Objects
Oct 12	-	-	-	READING WEEK - No Classes
Oct 19	□	Mid-term in TEL 0014	D	Introduction to Hardware
Oct 26	□	□	Make-up Labs	Machine Language + Floating-Point
Nov 02	□	□	K	The CPU Datapath
Nov 09	□	Quiz #2	L	The Single-Cycle Control
Nov 16	□	□	M	Pipelining
Nov 23	□	□	N	Caches
Nov 30	□	Quiz #3	Make-up Labs	
Dec 07	□	-	-	No lecture on Wednesday

Requirements for Cheat, Instruction Sheets (Midterm and Final Exam)



Cheat Sheets MUST:

- Be no larger than 8.5" x 11" in size
- Information MUST be original handwriting – NO printed or copied cheat sheets are permitted
- A single sheet, writing permitted on both sides


Green (MIPS Instruction) Sheets:

- MUST be extracted from textbook
- OR you may use a print out of the pdf version from the course web site

From Last Time...



32-bit ALU w/ And, OR, Add, Subtract, SLT, and Equality Test

ALU Control Lines			Result
Binvert	Carry In	Operation	
0	0	$0 = (00)_{two}$	AND ($a \cdot b$)
0	0	$1 = (01)_{two}$	OR ($a + b$)
0	0	$2 = (10)_{two}$	Add $sum(a,b)$
1	1	$2 = (10)_{two}$	Subtract ($a - b$)
1	1	$3 = (11)_{two}$	SLT if ($a < b$) Result0 = 1
1	1	$2 = (10)_{two}$	Test Equality Zero = 1 if ($a = b$)

 

From Last Time...

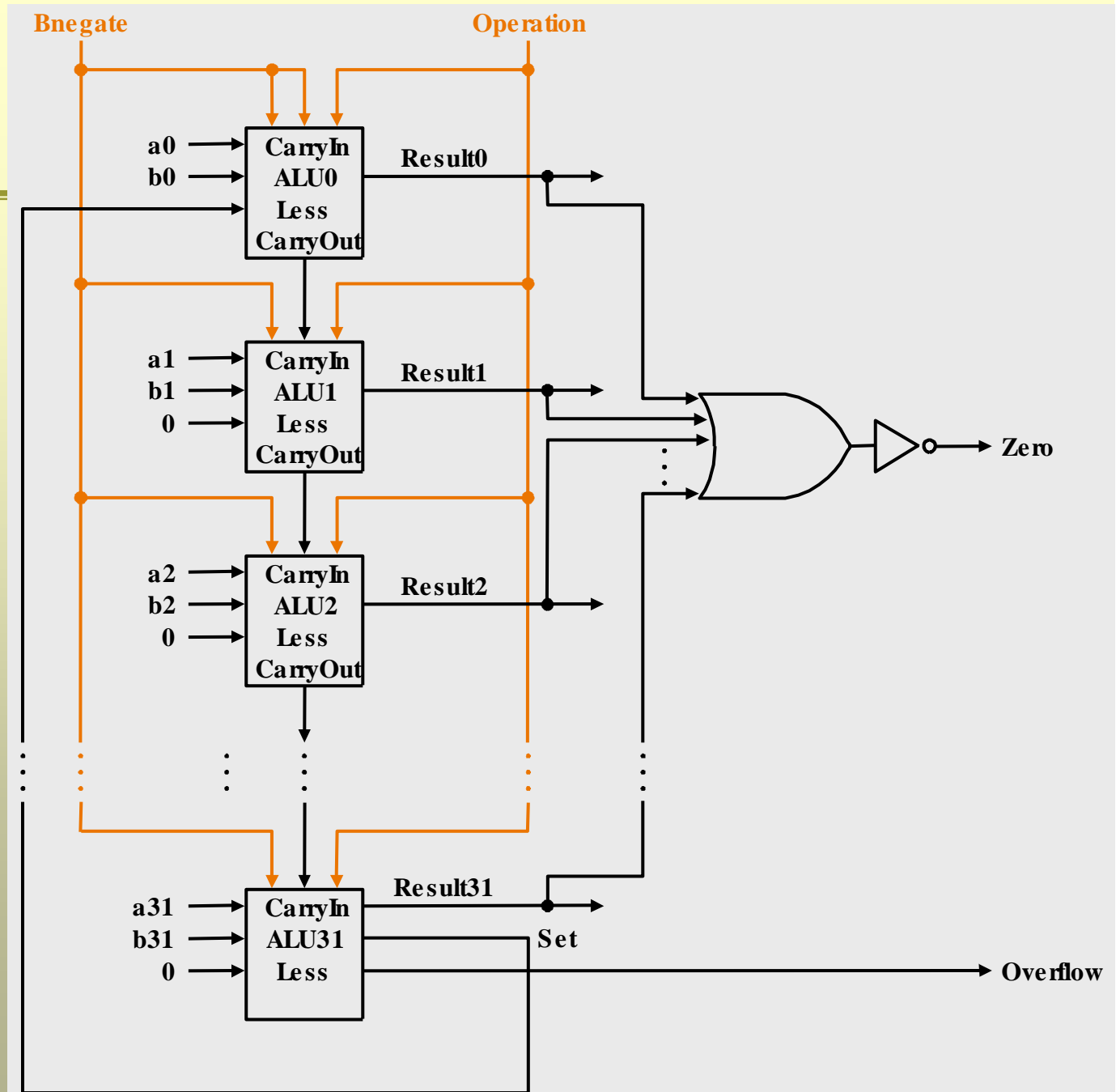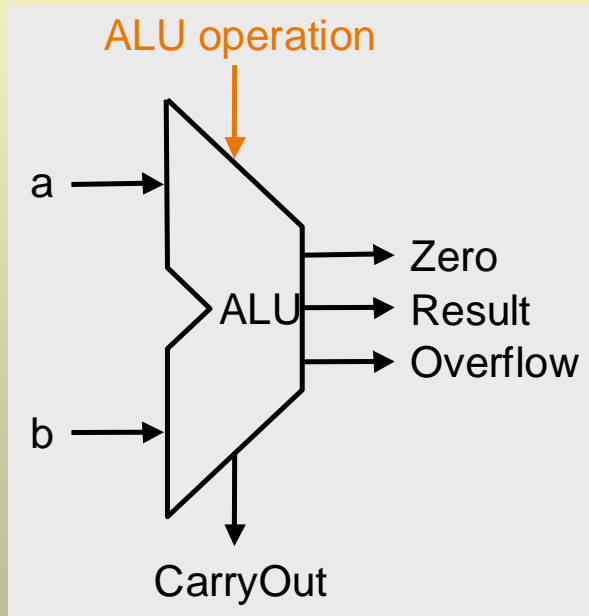32-bit ALU w/ And, OR, Add, Subtract, SLT, and Equality Test



Overview (1)



Goal: Implement a subset of core instructions from the MIPS instruction set, given below

Category	Instruction	Example	Meaning	Comments
Arithmetic and Logical	add	<code>add \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 + \$s3$	
	subtract	<code>sub \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 - \$s3$	
	and	<code>and \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 \& \$s3$	& => and
	or	<code>or \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 \$s3$	 => or
	slt	<code>slt \$s1,\$s2,\$s3</code>	If $\$s1 < \$s3$, $\$s1 \leftarrow 1$ else $\$s1 \leftarrow 0$	
Data Transfer	load word	<code>lw \$s1,100(\$s2)</code>	$\$s1 \leftarrow \text{Mem}[\$s2 + 100]$	
	store word	<code>sw \$s1,100(\$s2)</code>	$\text{Mem}[\$s2 + 100] \leftarrow \$s1$	
Branch	branch on equal	<code>beq \$s1,\$s2,L</code>	<code>if(\$s1==\$s2) go to L</code>	
	unconditional jump	<code>j 2500</code>	<code>go to 10000</code>	

Overview (2)



For each instruction, the first two steps are the same

Step 1: Based on the address in the program counter (PC), fetch instruction from memory

Step 2: Read 1 or 2 registers specified in the instruction

Steps 3 and 4 vary from one instruction to another

Step 3: Perform the arithmetic operation specified by the instruction

load/store word (sw/lw): add offset to \$s2

(add/sub/and/or): appropriate operation is performed on \$s2, \$s3

(beq/slt): compare \$s2 and \$s3 (requires \$s2 - \$s3)

jump (j): calculate address

Step 4: Complete the instruction

sw: write data into memory

lw: read data from memory


add/sub/and/or: store result in \$s1

beq/j: jump to the appropriate instruction

We will now focus on the hardware implementation of each of these instructions



Abstract view of the Implementation

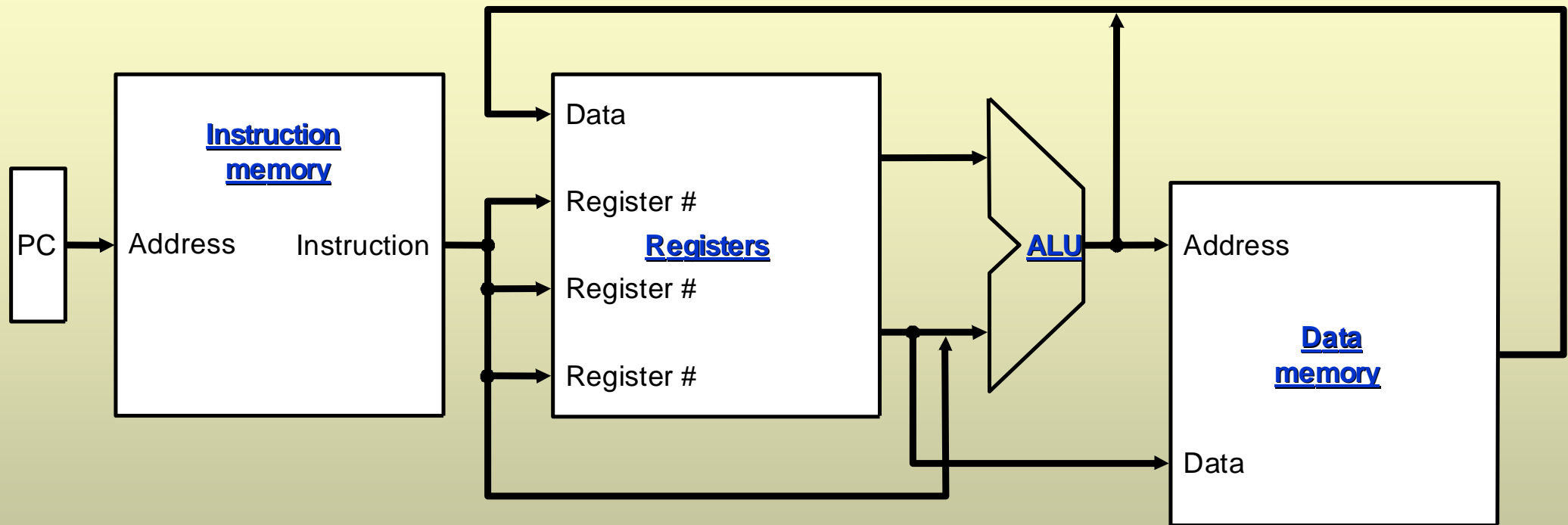

1. Program counter provides the instruction address
2. Instruction is fetched from instruction memory based on address in the PC
3. Register numbers are specified by the instruction
4. ALU computes an arithmetic result or address of memory
 - Arithmetic operation: Result is saved in a register
 - Data transfer: Data is extracted from data memory & transferred to a register or vice versa



Basics: Sequential vs. Combinational Circuits (1)

Digital circuits can be classified into two categories

1. Combinational Circuits:

- Output depends only on the current input
- Same set of inputs will always produce the same output
- Consist of AND, OR, NOR, NAND, and NOT gates
- Common examples are adder circuits and ALU

2. Sequential Circuits:


- Output depends on the current input and **state of the circuit**
- Same set of inputs can produce completely different outputs
- Consist of memory elements such as **flip-flops and registers** in addition to combinational circuits
- Examples are traffic signals and street lights

Datapath and control circuits of an ALU use sequential circuits.




Basics: Clocks (2)

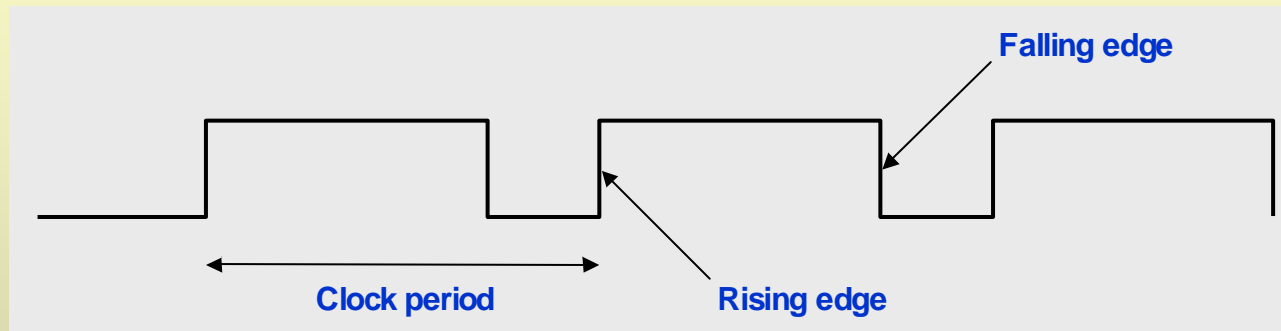1. Clock is a periodic signal oscillating between low and high states with fixed cycle time.
2. Clock frequency is inverse of clock cycle time. What is the cycle time for 1GHz clock?



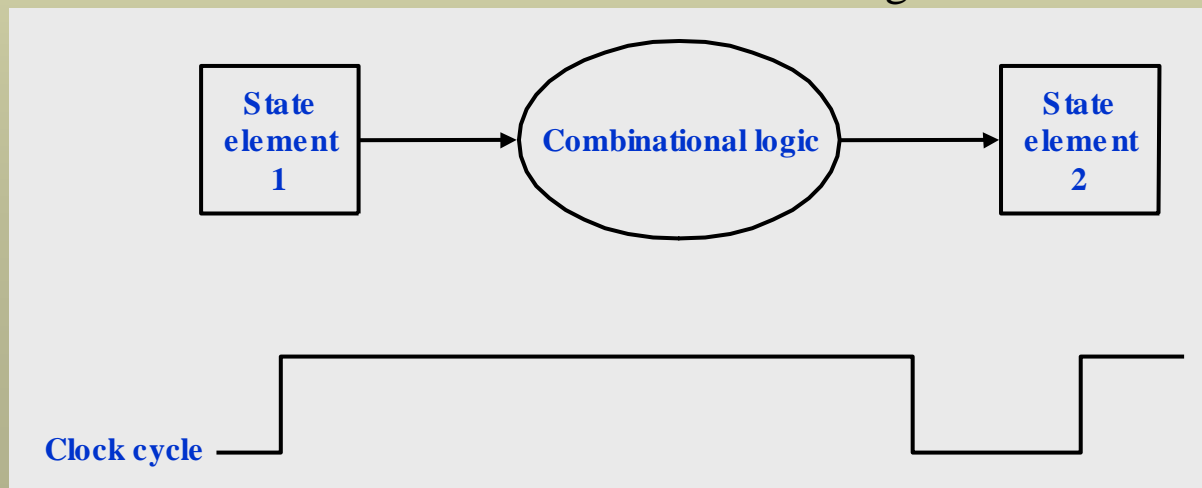3. Clock controls when the state of a memory element changes.
4. We assume falling edge-triggered clocking implying that the state changes only at the falling edge. When is the state element 2 modified in the following circuit?




Basics: RS Latch (3)



Simplest memory elements are Flip-flops and Latches

 - In clocked latches, state changes whenever input changes and the clock is **asserted**.
- In flip-flops, state changes only at the trailing edge of the clock



Logic Diagram

Inputs		Outputs		Comments
S	R	Q	\bar{Q}	
		0	1	Initial Condition
1	0	1	0	
0	0	1	0	After S = 1, R = 0
0	1	0	1	
0	0	0	1	After S = 0, R = 1
1	1	0	0	Undefined

Function Table


RS Unclocked Latch

- For a RS-latch: output $Q = 1$ when $S = 1, R = 0$ (set condition)
output $Q = 0$ when $S = 0, R = 1$ (reset condition)



Basics: Clocked D Latch (4)

 - For a D-latch: output $Q = 1$ when $D = 1$ (set condition)
output $Q = 0$ when $D = 0$ (reset condition)




Logic Diagram

Inputs		Outputs		Comments
C	D	Q	\bar{Q}	
0	X	Unchanged		
1	0	0	1	Reset
1	1	1	0	Set


Function Table

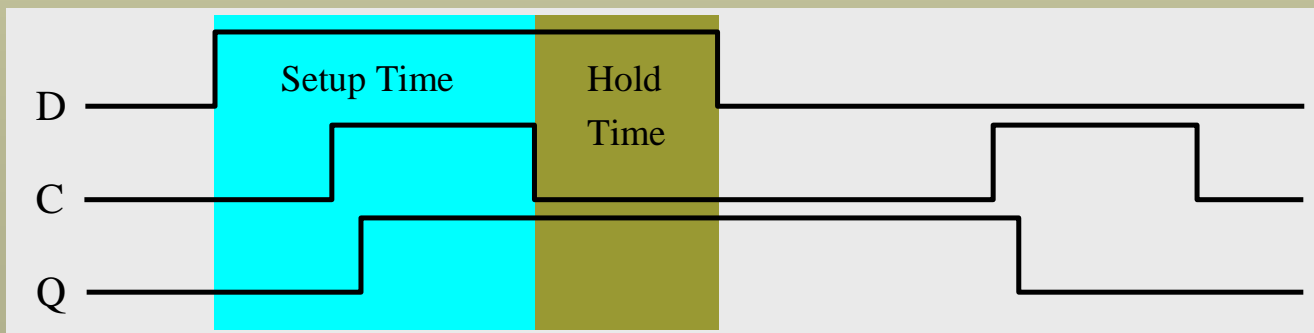- D Latch requires clock to be asserted for output to change






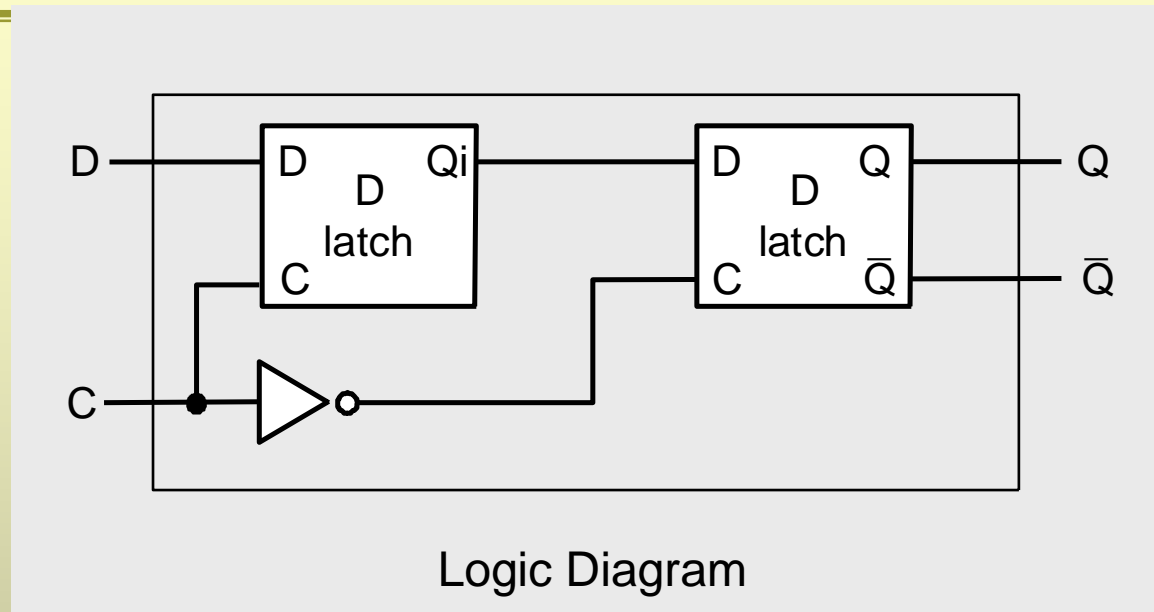Basics: Falling Edge Triggered D flip-flop (5)



 Output Q follows D but changes only at the falling edge



Basics: 32-bit Registers (6)



Falling edge triggered D flip-flops can be combined to form a register

