

CSE 2021 COMPUTER ORGANIZATION

HUGH CHESSER
CSE B 1012U

Agenda



Topics:

1. Basics: Clock, Latches and Flip Flops
2. Sequential and Combinational Circuits

Today and Wednesday: Patterson: Appendix C,
Section 4.1, 4.2, 4.3

What is the difference between these two ALUs?

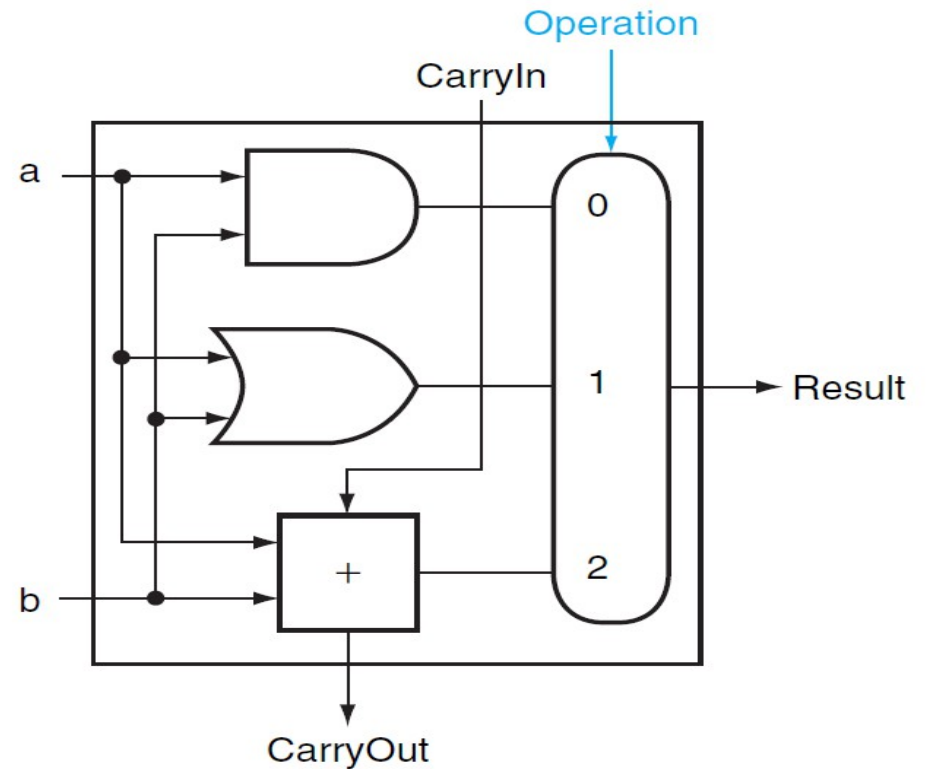
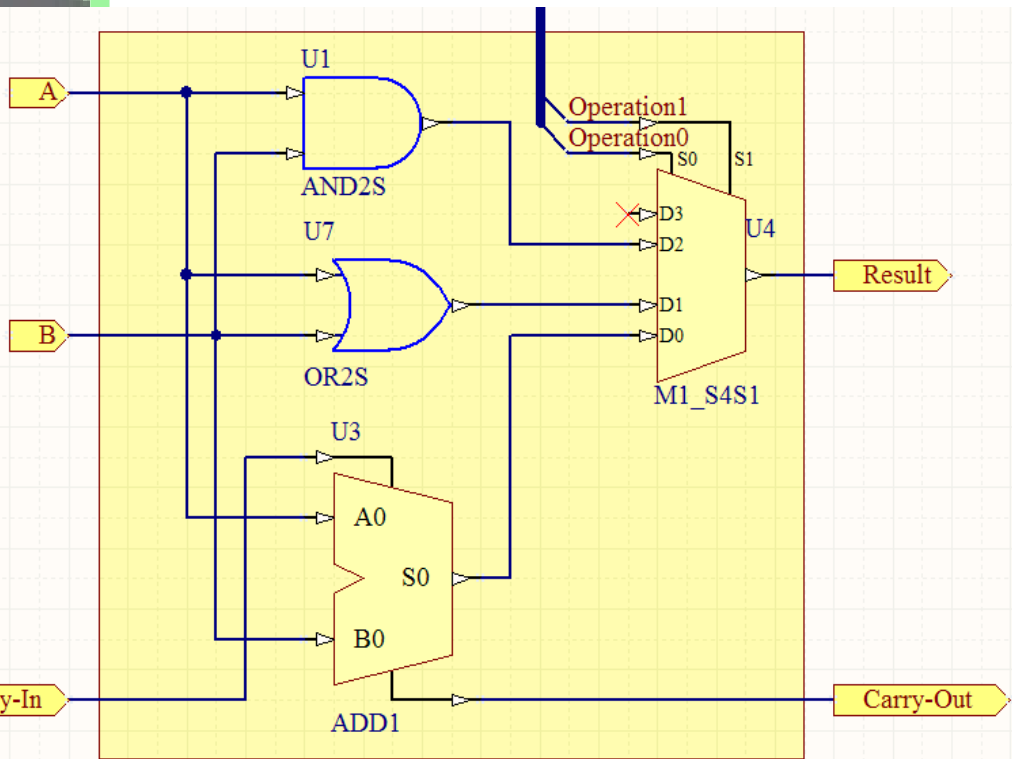
- The 1-bit adder is supplemented with AND and OR gates
- A multiplexer controls which output is selected





1-bit ALU with AND, OR, and Addition capability

SLT (and Nor) Logic Added

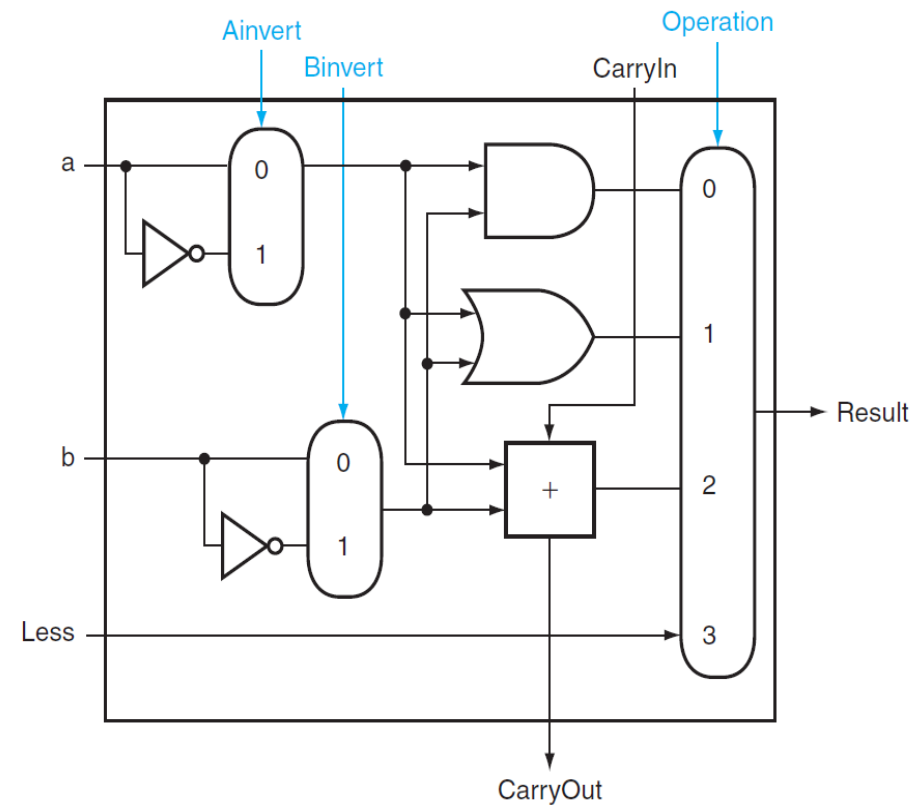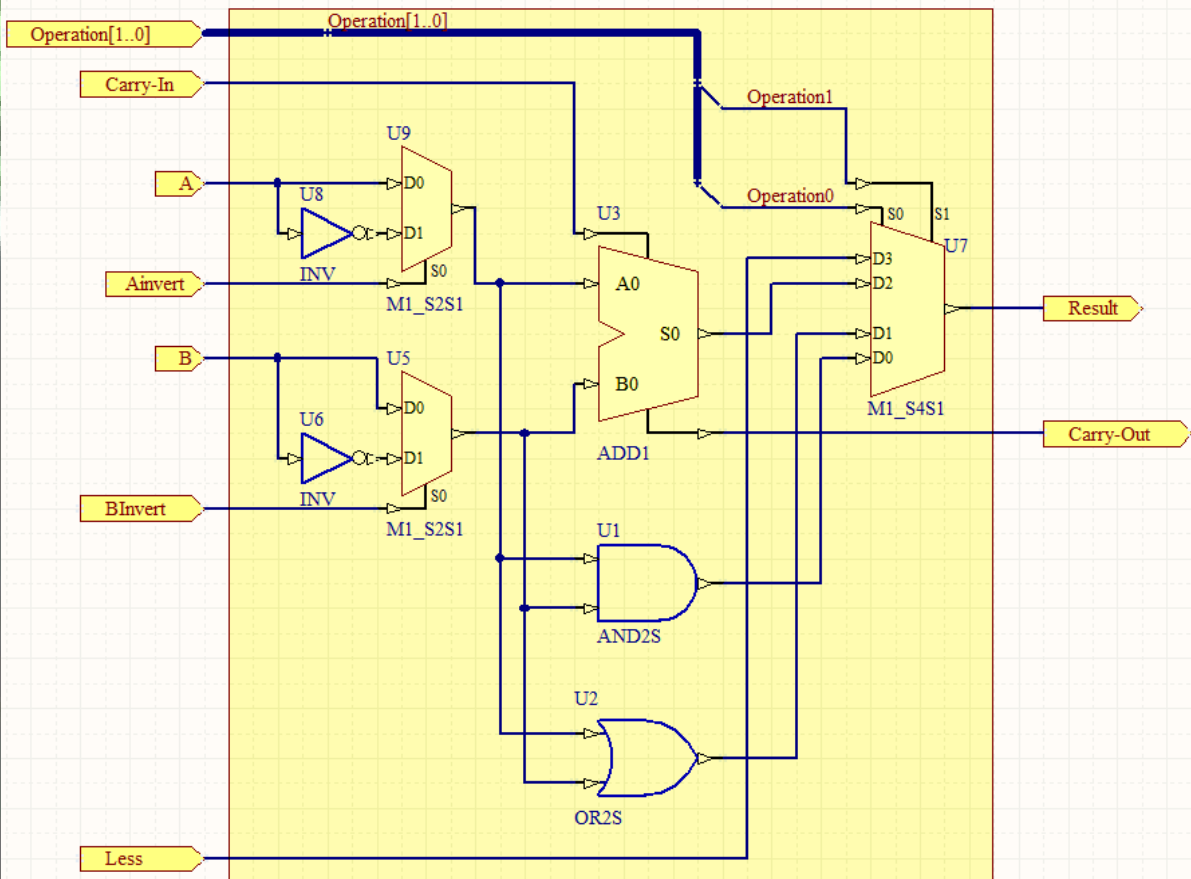- The 1-bit adder is supplemented with AND and OR gates
- A multiplexer controls which gate is connected to the output





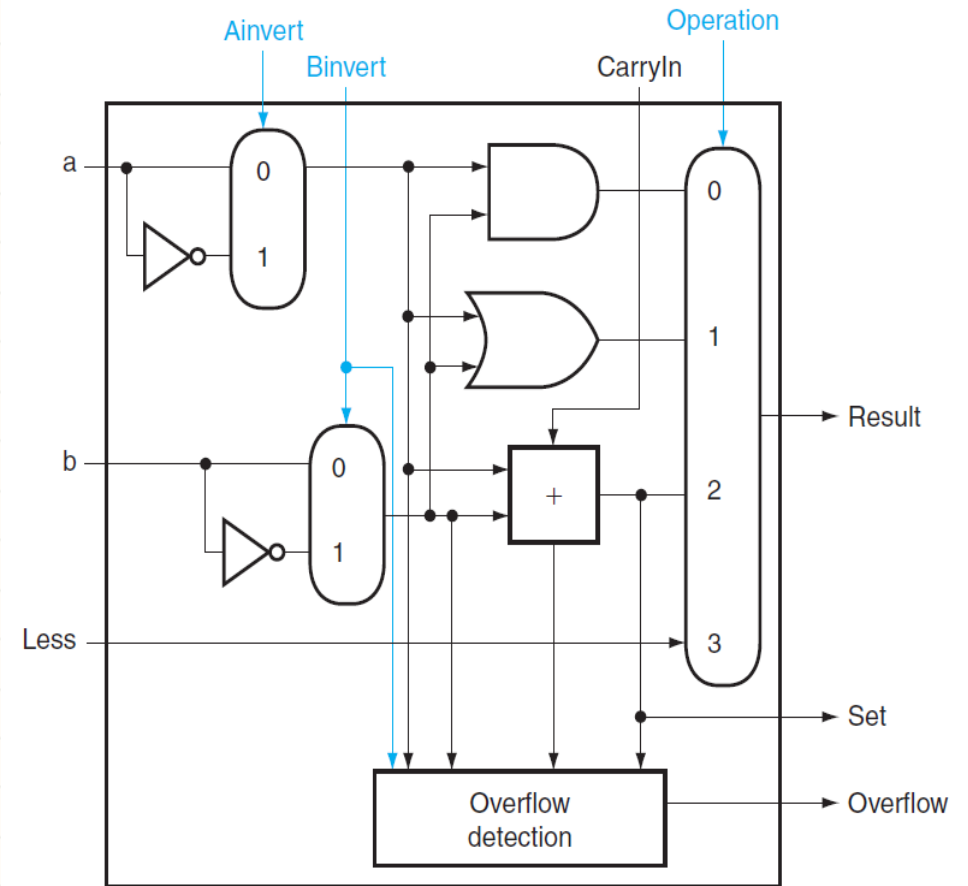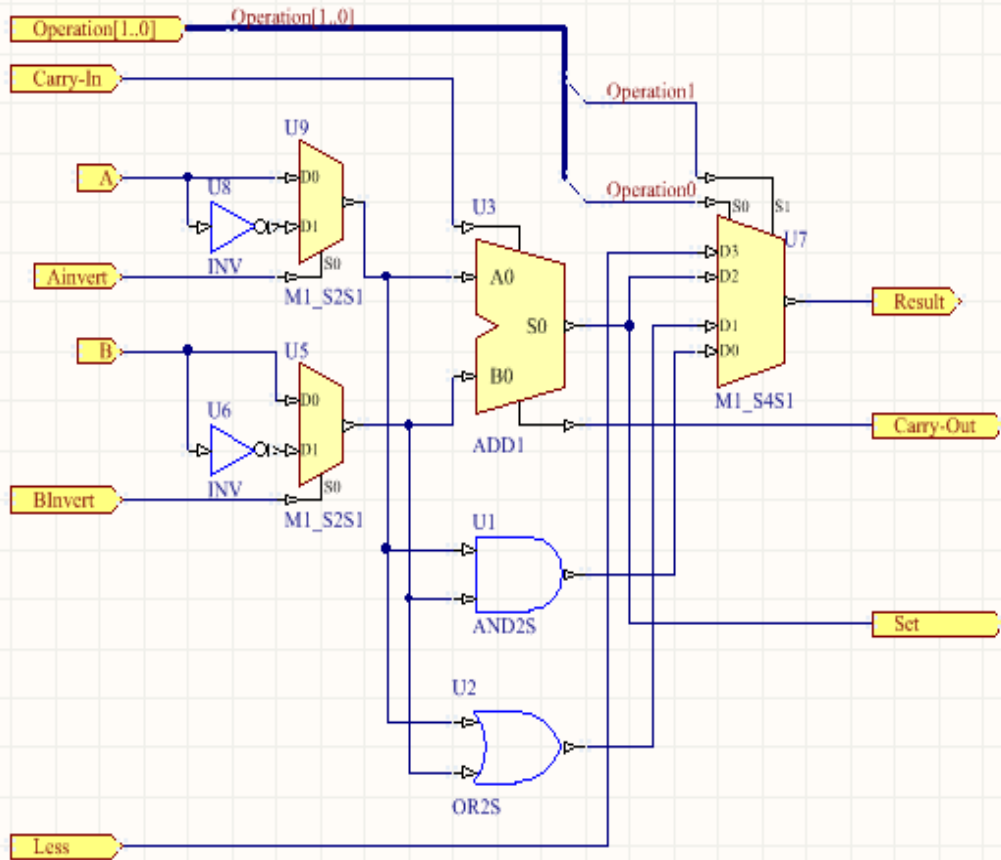Most Significant Bit (Could Actually Be Every Bit)



SLT (and Nor) Logic Added

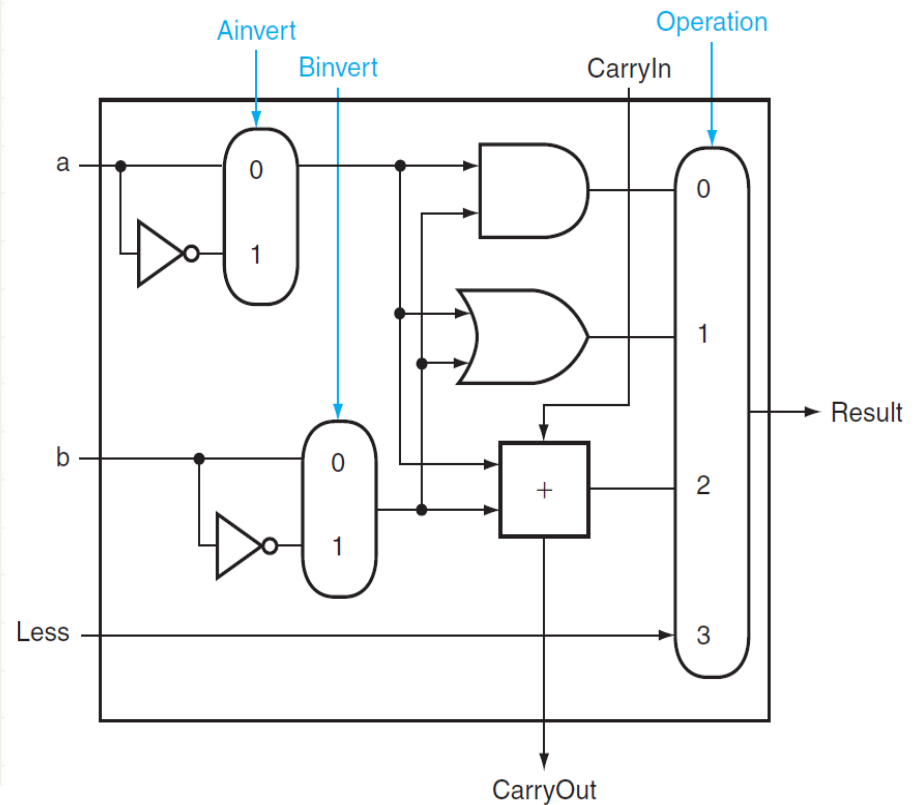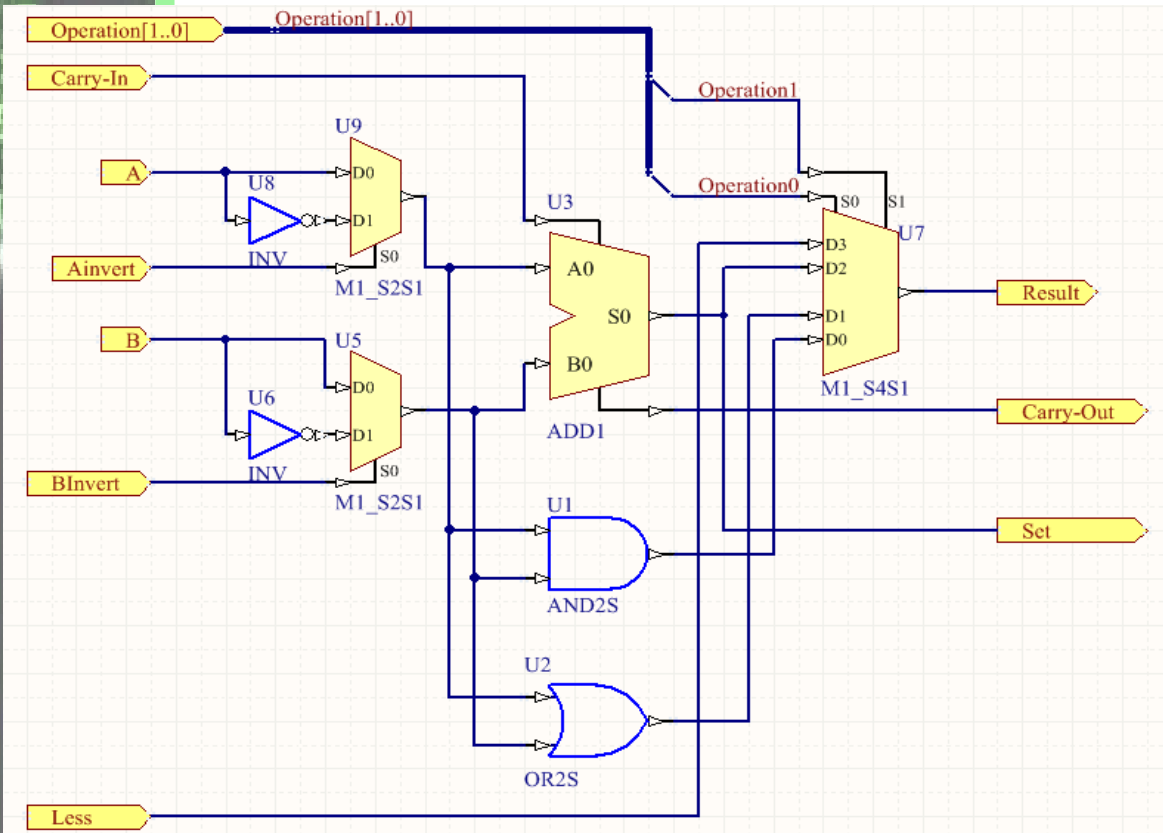- The 1-bit adder is supplemented with AND and OR gates
- A multiplexer controls which gate is connected to the output




1-bit ALU with AND, OR, NOR and Addition capability

From Last time...


32-bit ALU w/ And, OR, Nor, Add, Subtract, SLT, and Equality Test

Carry In	ALU Control Lines (ALUOp[3..0])			Result
	Binvert	Ainvert	Operation	
0	0	0	$0 = (00)_{\text{two}}$	AND ($a \cdot b$)
0	0	0	$1 = (01)_{\text{two}}$	OR ($a + b$)
0	1	1	$0 = (00)_{\text{two}}$	NOR ($\bar{a} \cdot \bar{b}$)
0	0	0	$2 = (10)_{\text{two}}$	Add $\text{sum}(a, b)$
1	1	0	$2 = (10)_{\text{two}}$	Subtract ($a - b$)
1	1	0	$3 = (11)_{\text{two}}$	SLT if ($a < b$) Result0 = 1
1	1	0	$2 = (10)_{\text{two}}$	Test Equality Zero = 1 if ($a < b$)

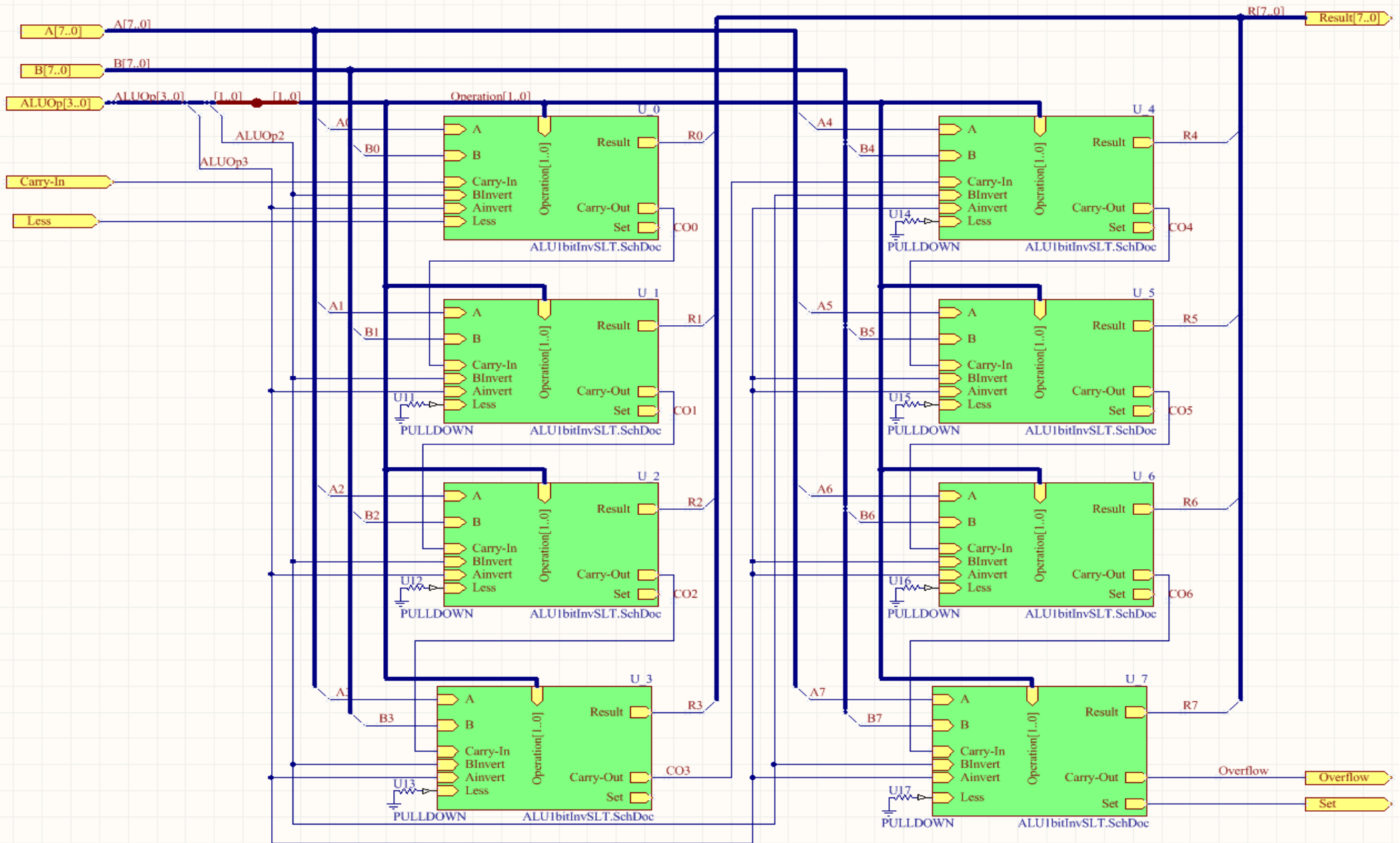8-bit ALU w/ And, OR, Nor, Add, Subtract, SLT, and Equality Test



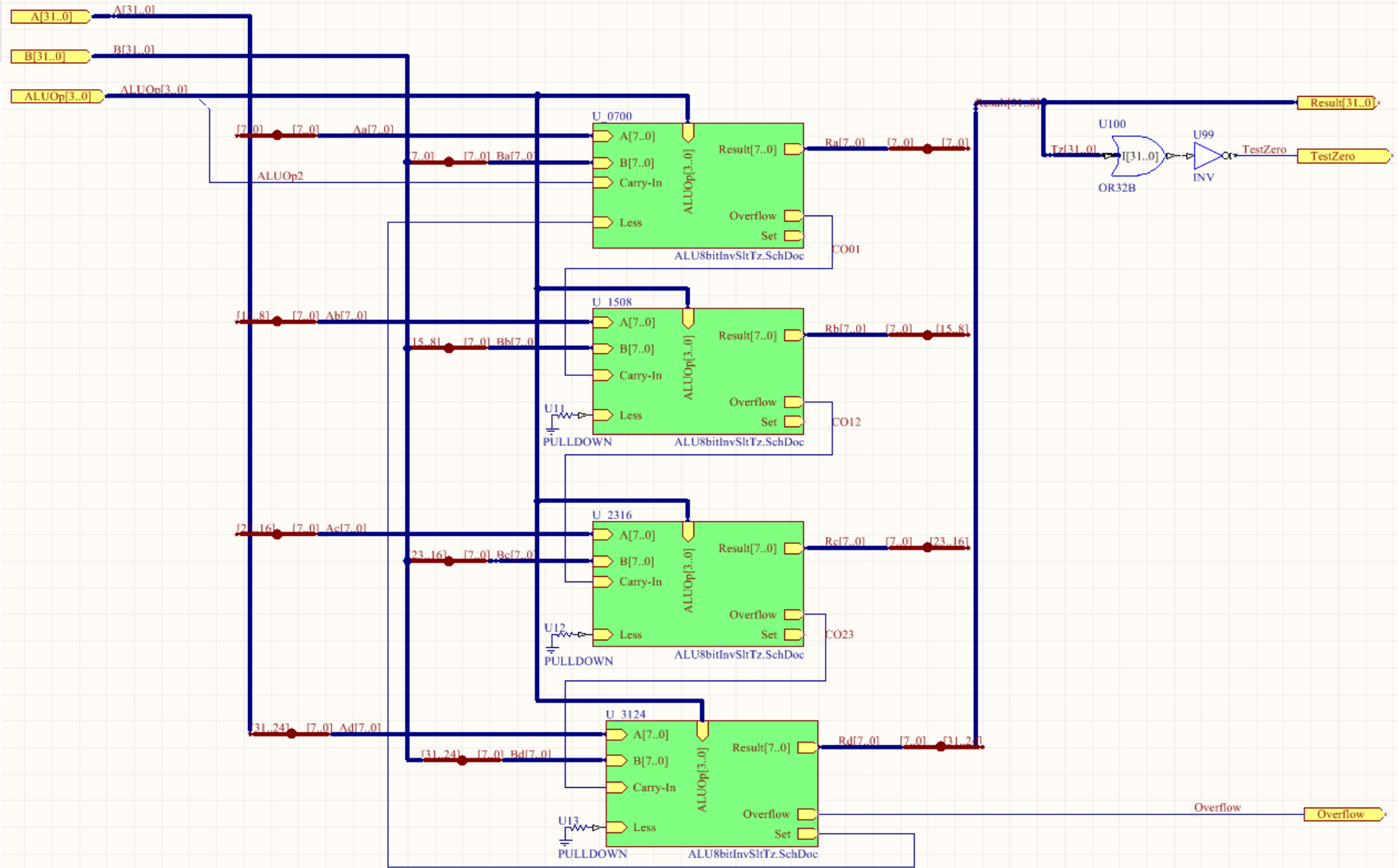32-bit ALU w/ And, OR, Nor, Add, Subtract, SLT, and Equality Test



Overview (1)

Goal: Implement a subset of core instructions from the MIPS instruction set, given below

Category	Instruction	Example	Meaning	Comments
Arithmetic and Logical	add	<code>add \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 + \$s3$	
	subtract	<code>sub \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 - \$s3$	
	and	<code>and \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 \& \$s3$	& => and
	or	<code>or \$s1,\$s2,\$s3</code>	$\$s1 \leftarrow \$s2 \$s3$	 => or
	slt	<code>slt \$s1,\$s2,\$s3</code>	If $\$s1 < \$s3$, $\$s1 \leftarrow 1$ else $\$s1 \leftarrow 0$	
Data Transfer	load word	<code>lw \$s1,100(\$s2)</code>	$\$s1 \leftarrow \text{Mem}[\$s2 + 100]$	
	store word	<code>sw \$s1,100(\$s2)</code>	$\text{Mem}[\$s2 + 100] \leftarrow \$s1$	
Branch	branch on equal	<code>beq \$s1,\$s2,L</code>	if $(\$s1 == \$s2)$ go to L	
	unconditional jump	<code>j 2500</code>	go to 10000	

Overview (2)

For each instruction, the first two steps are the same

Step 1: Based on the address in the program counter (PC), fetch instruction from memory

Step 2: Read 1 or 2 registers specified in the instruction

Steps 3 and 4 vary from one instruction to another

Step 3: Perform the arithmetic operation specified by the instruction

load/store word (sw/lw): add offset to \$s2

(add/sub/and/or): appropriate operation is performed on \$s2, \$s3

(beq/slt): compare \$s2 and \$s3 (requires \$s2 - \$s3)

jump (j): calculate address

Step 4: Complete the instruction

sw: write data into memory


lw: read data from memory

add/sub/and/or: store result in \$s1

beq/j: jump to the appropriate instruction

We will now focus on the hardware implementation of each of these instructions

Abstract view of the Implementation

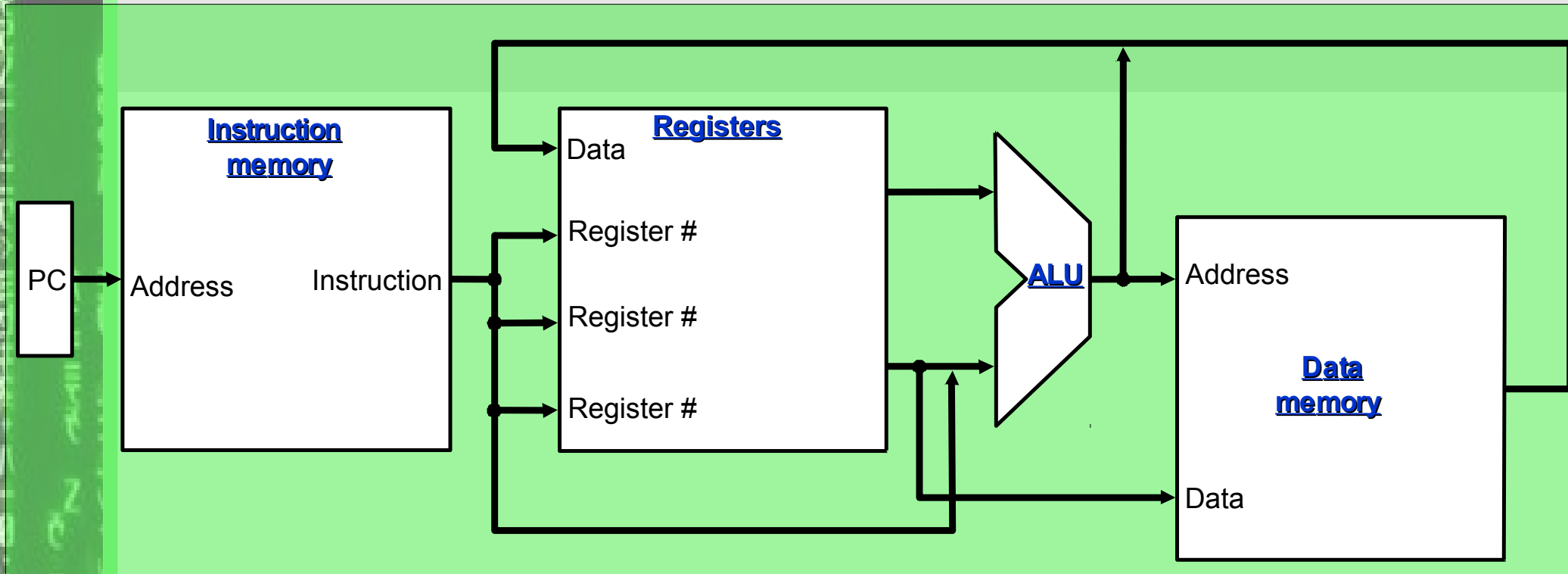

1. Program counter provides the instruction address
2. Instruction is fetched from instruction memory based on address in the PC
3. Register numbers are specified by the instruction
4. ALU computes an arithmetic result or address of memory
 - Arithmetic operation: Result is saved in a register
 - Data transfer: Data is extracted from data memory & transferred to a register or vice versa

Basics: Sequential vs. Combinational Circuits (1)

Digital circuits can be classified into two categories

1. Combinational Circuits:

- Output depends only on the current input
- Same set of inputs will always produce the same output
- Consist of AND, OR, NOR, NAND, and NOT gates
- Common examples are adder circuits and ALU


2. Sequential Circuits:

- Output depends on the current input and **state of the circuit**
- Same set of inputs can produce completely different outputs
- Consist of memory elements such as **flip-flops and registers** in addition to combinational circuits
- Examples are traffic signals and street lights


Datapath and control circuits of an ALU use sequential circuits.

Basics: Clocks (2)

 1. Clock provides a periodic signal oscillating between low and high states with fixed cycle time.
2. Clock frequency is inverse of clock cycle time. What is the cycle time for 1GHz clock?



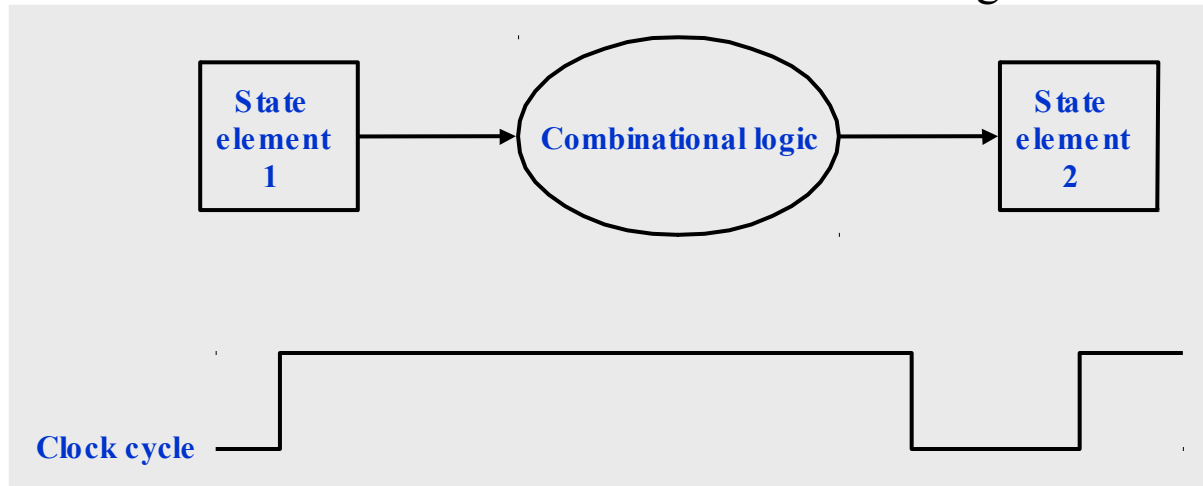
3. Clock controls when the state of a memory element changes.
4. We assume falling edge-triggered clocking implying that the state changes only at the falling edge. When is the state element 2 modified in the following circuit?



Basics: RS Latch (3)

Simplest memory elements are Flip-flops and Latches

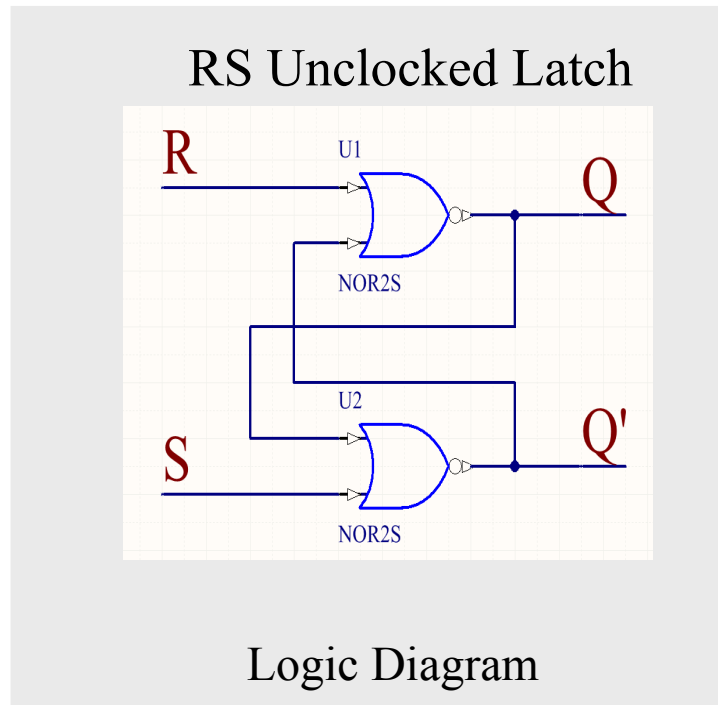- In clocked latches, state changes whenever input changes and the clock is **asserted**.
- In flip-flops, state changes only at the trailing edge of the clock




Inputs		Outputs		Comments
S	R	Q	$Q' = \bar{Q}$	
		0	1	Initial Condition
1	0	1	0	
0	0	1	0	After S = 1, R = 0
0	1	0	1	
0	0	0	1	After S = 0, R = 1
1	1	0	0	Undefined

Function Table

- For a RS-latch: output $Q = 1$ when $S = 1, R = 0$ (set condition)
output $Q = 0$ when $S = 0, R = 1$ (reset condition)

Basics: Clocked D Latch (4)

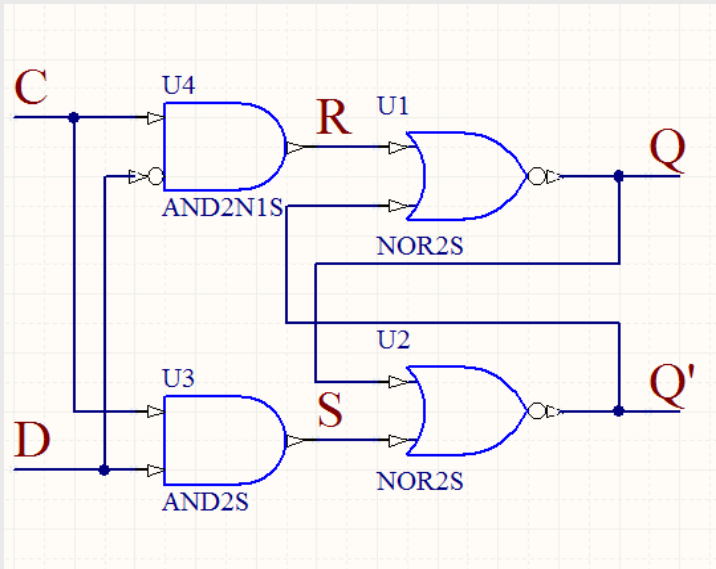- For a D-latch:
 - output $Q = 1$ when $D = 1$ (set condition)
 - output $Q = 0$ when $D = 0$ (reset condition)




Logic Diagram


Inputs		Outputs		Comments
C	D	Q	$Q' = \bar{Q}$	
0	X	Unchanged		
1	0	0	1	Reset
1	1	1	0	Set

Function Table

 - D Latch requires clock to be asserted for output to change – characteristic of the flip-flop being used:



Flip Flop Metastability

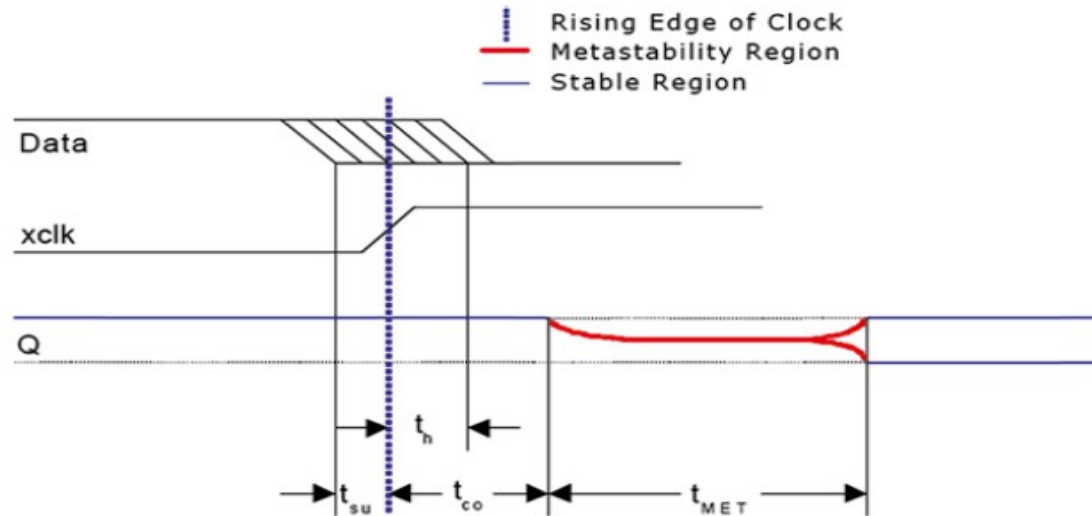


- If data signal changes state during set-up and hold phase – flip-flop can be left in an indeterminate state (metastable).
- Takes some clock cycles to recover to a determinate state

Source: Arora, M., “The Art of Hardware Architecture Design Methods and Techniques for Digital Circuits”, library e-book


<http://theta.library.yorku.ca/uhtbin/cgiisirs/x/0/0/5?searchdata1=a2962292{CKEY}>

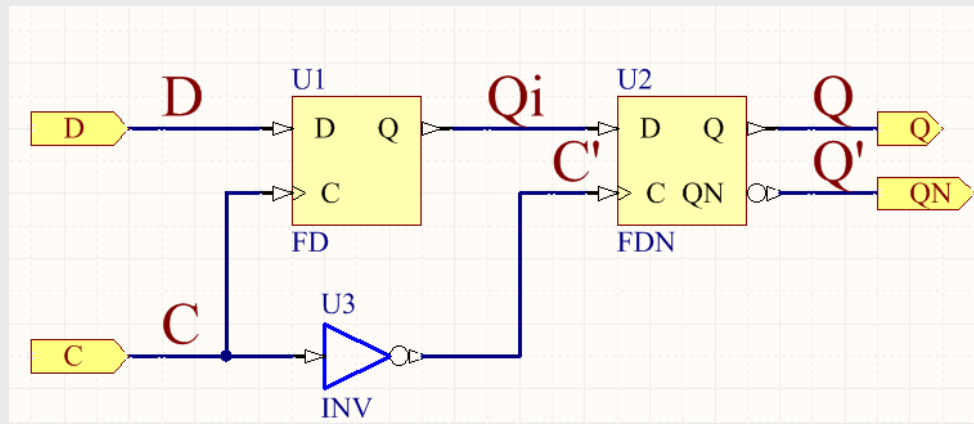Basics: Falling Edge Triggered D flip-flop (5)



Logic Diagram

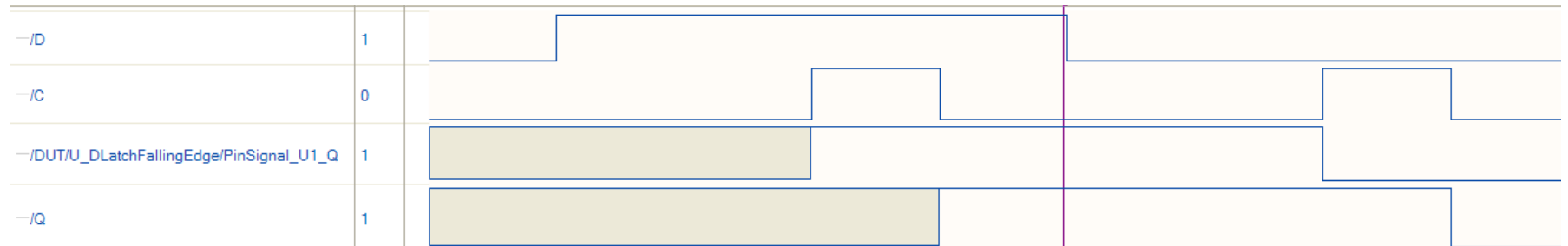Output Q follows D but changes only at the falling edge



Basics: 32-bit Registers (6)

Falling edge triggered D flip-flops can be combined to form a register

