

# ENG2200

## Electric Circuits

### Chapter 2


#### Circuit Elements

### **Chapter 2 Circuits Elements**

- Voltage and current sources
- Resistance (Ohm's law)
- Kirchhoff's laws
- Dependent sources

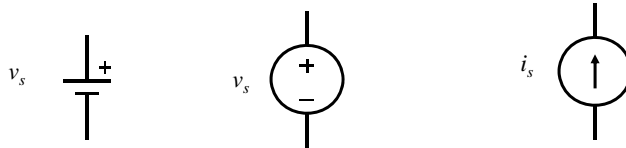
## Voltage and Current Sources (Independent)

- Ideal voltage source: Constant voltage across its terminals regardless of the current flowing in these terminals
- Ideal current source: Constant current through its terminals regardless of the voltage across these terminals



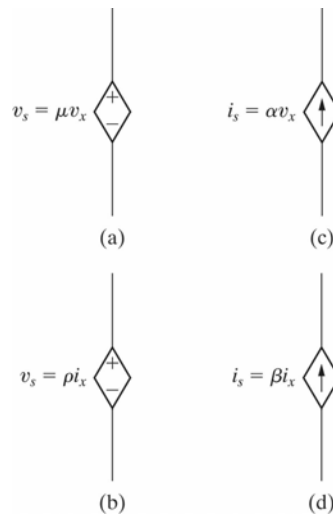
## Dependent Sources

- Some times referred to as *controlled sources*
- The value depends on the current or voltage in another part of the circuit.








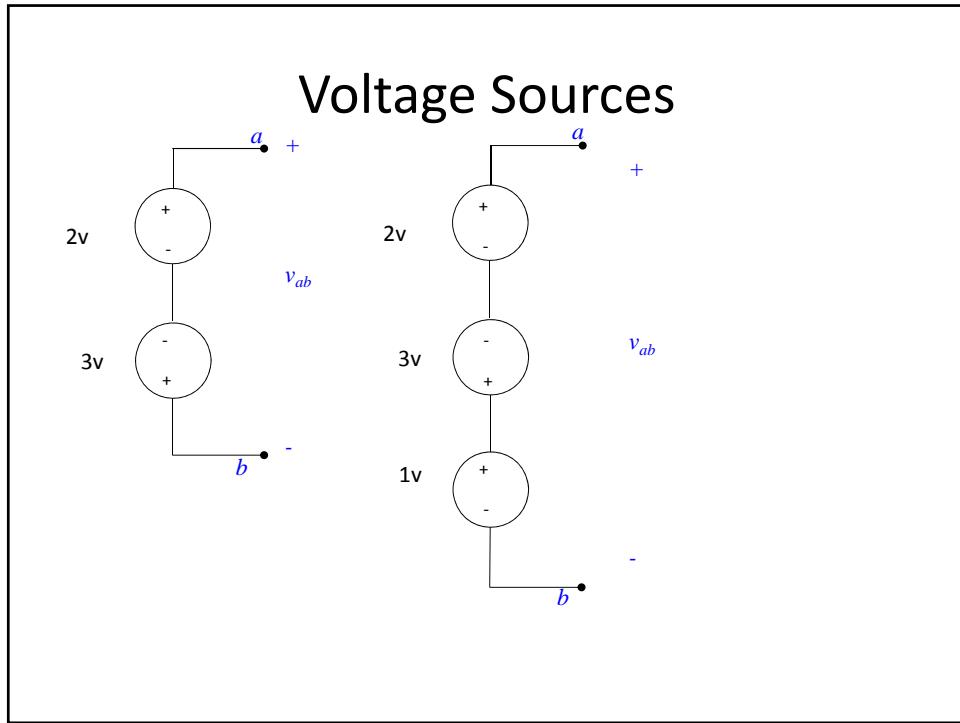Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


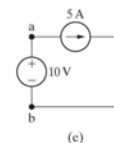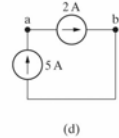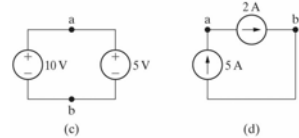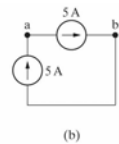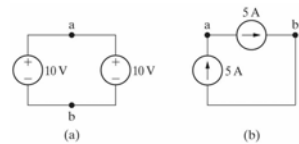
### Example





- Which of the circuits to the right is valid?



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


**Example**

- Which of these circuits are valid?

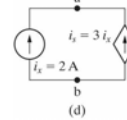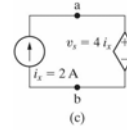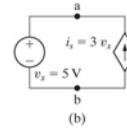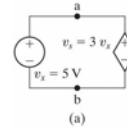

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


**Example**

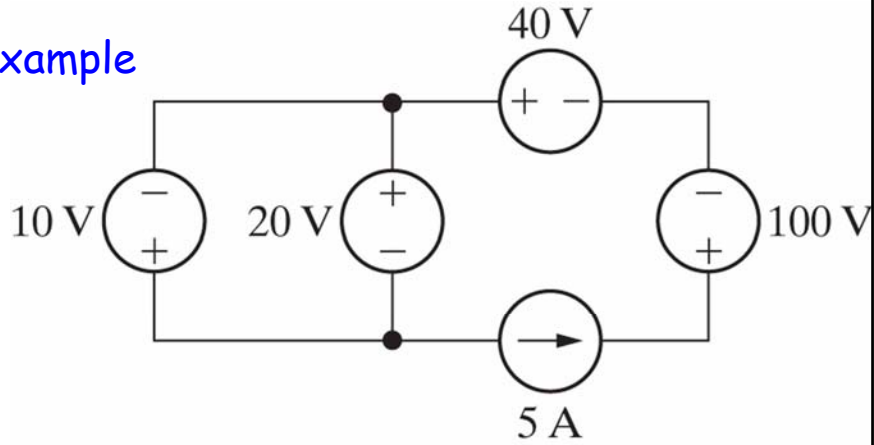

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

- If the interconnection is valid, find the total power developed by the voltage sources. If not explain why.

### Example

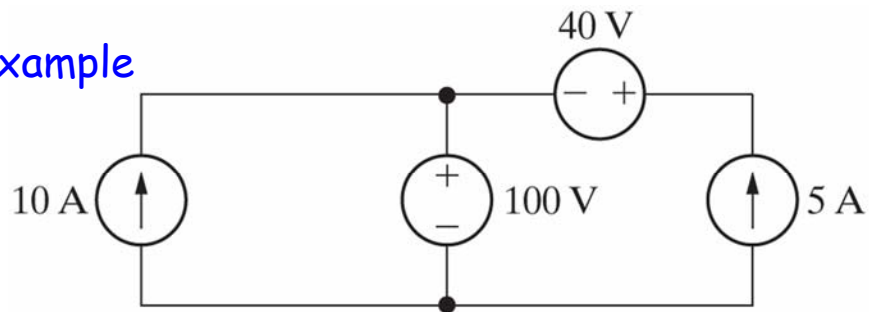

- If the interconnection is valid, find the total developed by the voltage sources. If not explain why.


### Resistance

- Resistance is the capacity of the material to impede the flow of current (charges)  $R$  and is measured in ohm  $\Omega$ .
- The inverse of the capacitance is **conductance**,  $G$  measured in siemens (S)
- The resistance of a wire is 
$$R = \rho \frac{l}{A}$$
- $R$  is the resistance,  $l$  is the length in meters,  $A$  is the cross-sectional area in square meters,  $\rho$  is the resistivity of the material in ohm meter

## Resistance

- Typical values for resistivity in  $\Omega\cdot\text{m}$
- Silver  $1.59 \times 10^{-8} \Omega\cdot\text{m}$  at 20 C
- Copper  $1.68 \times 10^{-8} \Omega\cdot\text{m}$
- Germanium  $4.6 \times 10^{-1} \Omega\cdot\text{m}$
- Sea water  $2 \times 10^{-1} \Omega\cdot\text{m}$
- Hard rubber  $1 \times 10^{+13} \Omega\cdot\text{m}$

## Ohm's Law

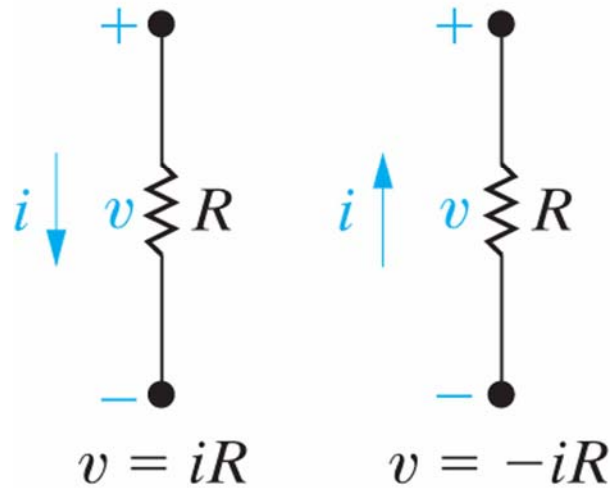


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

## Power in a resistor

$$p = vi$$


$$p = i^2 R$$

$$p = \frac{v^2}{R}$$

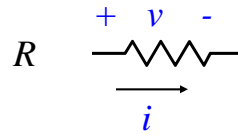


### Example


find  $v$  or  $i$  in every circuit

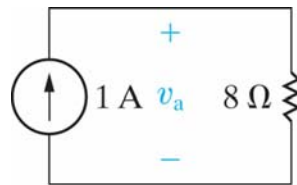


(a)

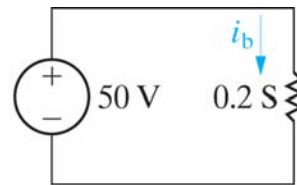

(b)

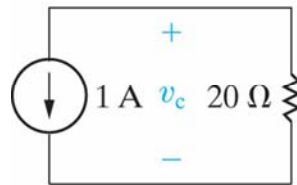

(c)

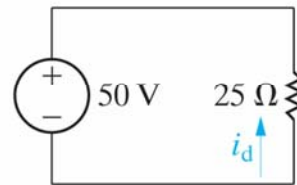

(d)

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

## Short Circuit and Open Circuit

- Short Circuit
  - Wire
  - $R = 0$
  - No resistance
  - No voltage
- Open Circuit
  - Air (or insulator)
  - $R = \infty$
  - No current flowing



(a)



(b)



(c)

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


## I-V Characteristics of a Device

- I-V characteristic of a resistor
- Ideal voltage source
- ideal current source


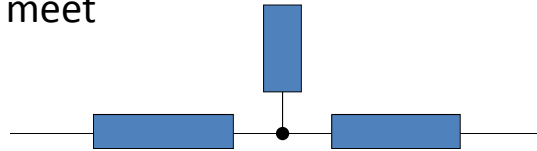
## Kirchoff's Laws

- A node is a point where two or more circuit elements meet



- **KCL: The algebraic sum of all currents at any node in a circuit equals zero**

## Kirchoff's Laws

- **Closed Path** or a **loop**: Starting from any node, trace a closed path going through some of the basic circuit elements and returning to the starting node without passing through an element twice;
- **KVL: The algebraic sum of all voltages around any closed path in a circuit equals zero.**

leaving = positive


a:  $-i_2 - i_5 + i_1 + i_4 = 0$   
 b:  $i_2 + i_3 - i_1 - i_a - i_b = 0$   
 c:  $i_b - i_3 - i_c - i_4 = 0$   
 d:  $i_5 + i_a + i_c = 0$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


a:  $-v_1 + v_2 + v_4 - v_b - v_3 = 0$   
 b:  $v_3 + v_5 - v_a = 0$   
 c:  $v_b - v_4 - v_c - v_6 - v_5 = 0$   
 d:  $-v_a - v_1 + v_2 - v_c + v_7 - v_d = 0$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

### Example -- Find $i_o$

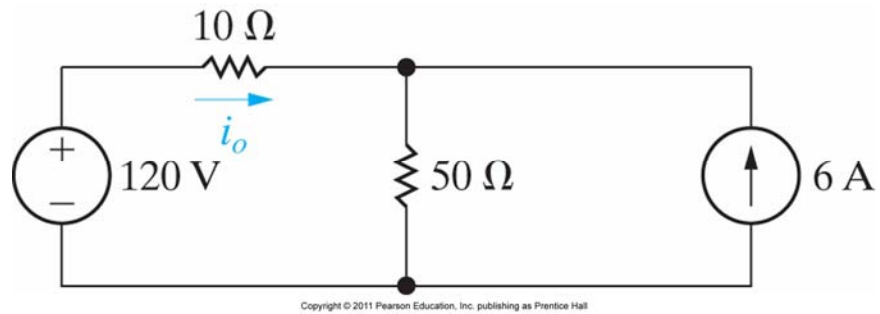


### Example

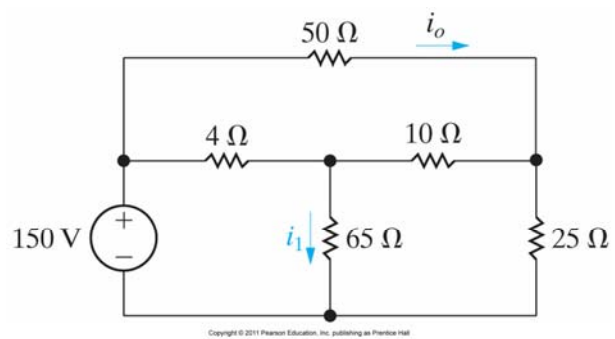


- If  $i_o=1\text{A}$ , find  $i_1$
- Find the power dissipated in every register

More difficult

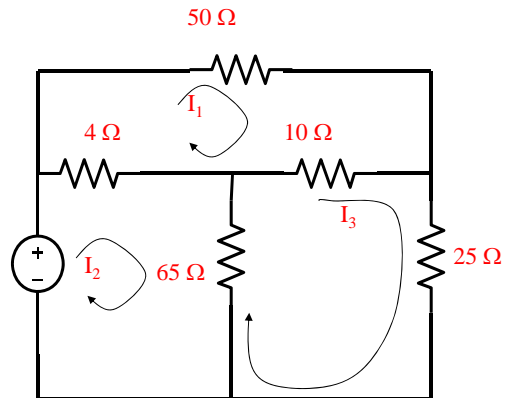


Find  $i_o$

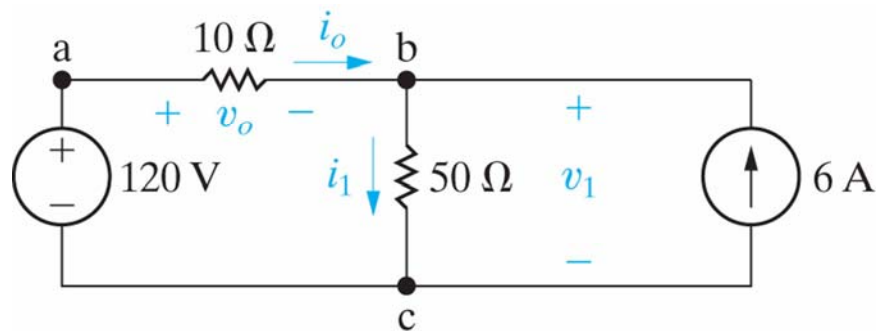

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

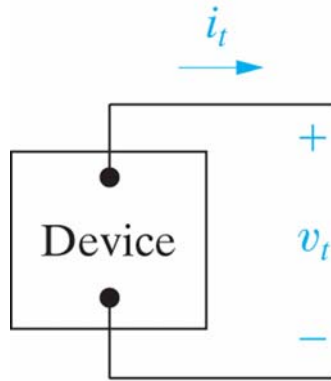**Construct a circuit model for the device**




(a)

$v_t$ (V)	$i_t$ (A)
30	0
15	3
0	6


(b)

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

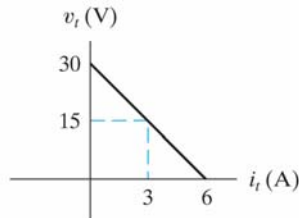**Find the power delivered to a  $10 \Omega$  R**




(a)

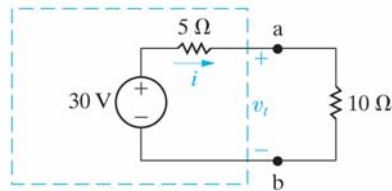


(b)

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


**Figure 2.22** A circuit with a dependent source.

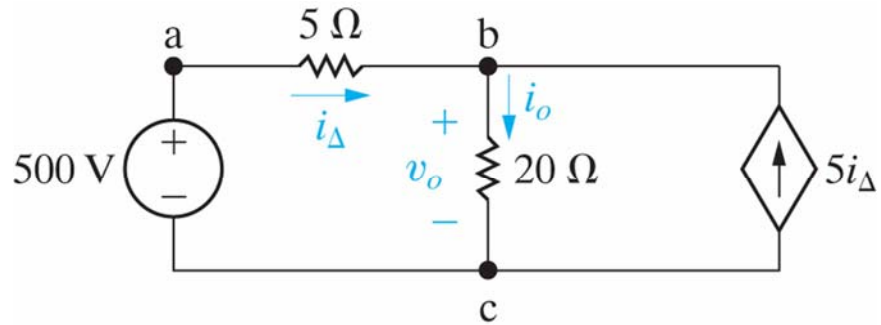

**Example**

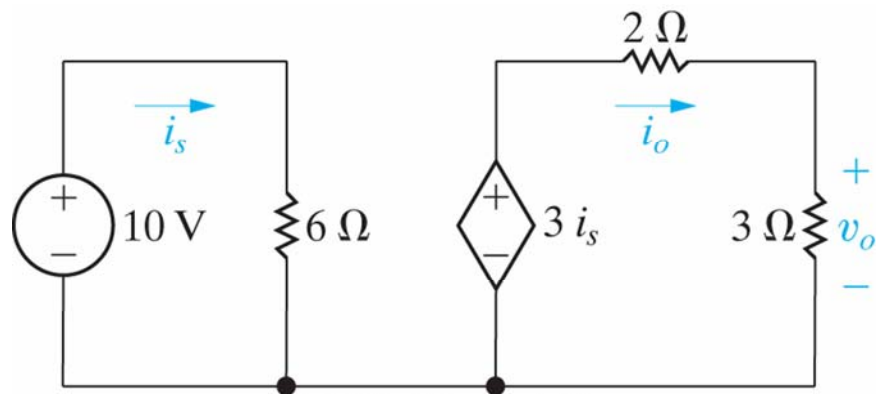

### Example

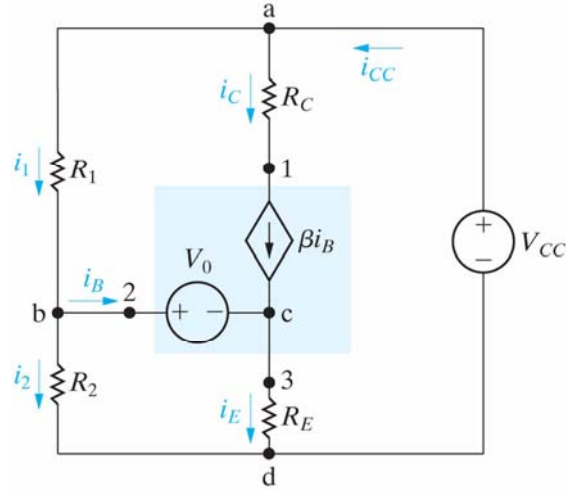


**TABLE 2.1 Physiological Reactions to Current Levels in Humans**

Physiological Reaction	Current
Barely perceptible	3–5 mA
Extreme pain	35–50 mA
Muscle paralysis	50–70 mA
Heart stoppage	500 mA


*Note:* Data taken from W. F. Cooper, *Electrical Safety Engineering*, 2d ed. (London: Butterworth, 1986); and C. D. Winburn, *Practical Electrical Safety* (Monticello, N.Y.: Marcel Dekker, 1988).

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

### Example 2.9

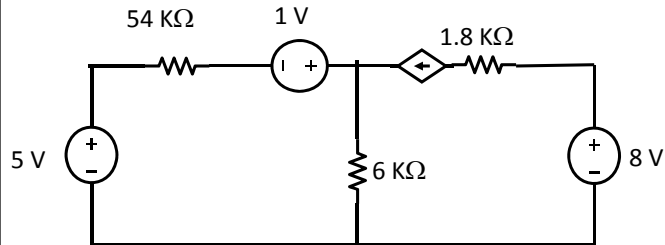




### Figure P2.9

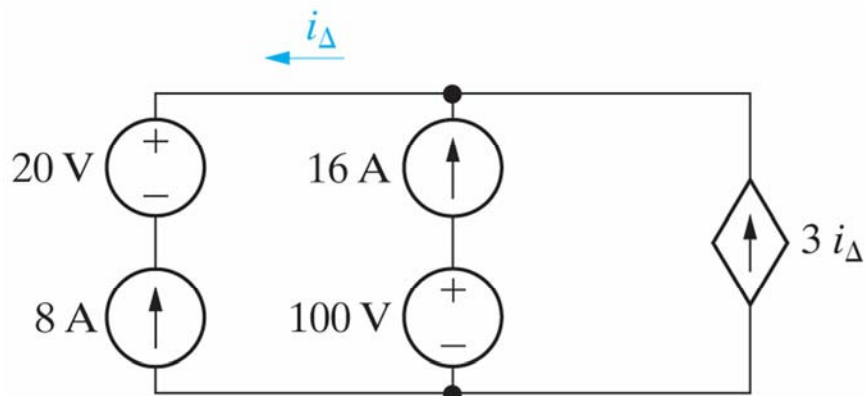

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall



Figure P2.33

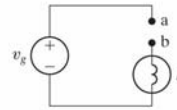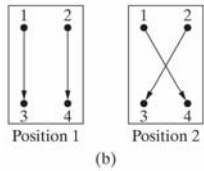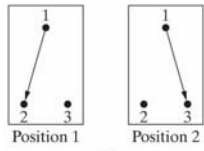

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall