

# ENG2210

## Electronic Circuits


Mokhtar A. Aboelaze  
York University

### Chapter 3 Diodes


- **Objectives**
- Learn the characteristics of ideal diode and how to analyze and design circuits containing multiple diodes
- Learn the  $i$ - $v$  characteristic of the junction diode
- Learn a simple model of the diode
- Learn the use of diodes operating in the forward and reverse bias region to provide constant dc voltage.
- Learn application of the diode in the design of rectifier circuits.


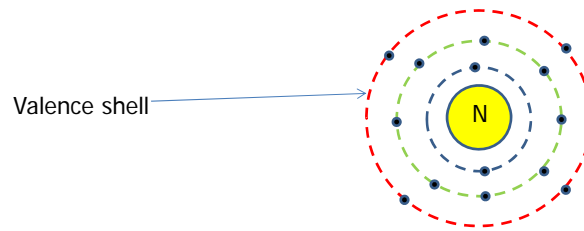
# Atoms



- Atoms consists of a positively charged nucleus and a number of negatively charged electrons rotating around the nucleus.
- Electrons are arranged in shells
- The electrons in the outer shell (<8) are called *valence electrons*.



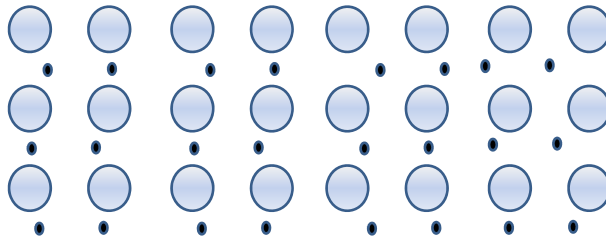- Conductors: The valence electrons are free to move around.
- When applying an electric field, these electrons starts to move in the opposite direction of the filed (current).



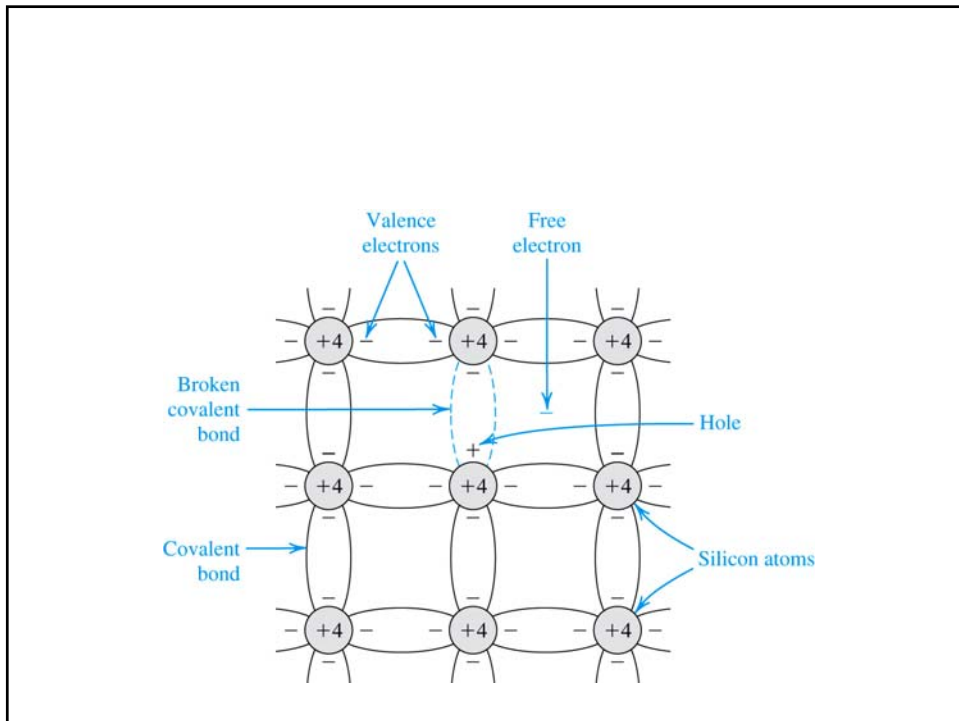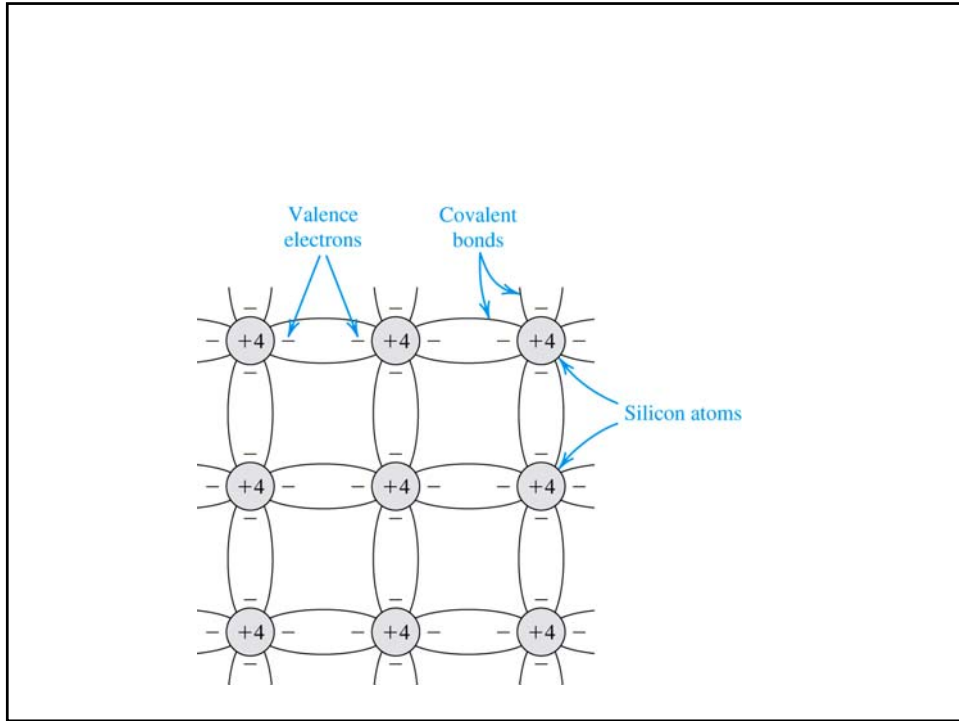

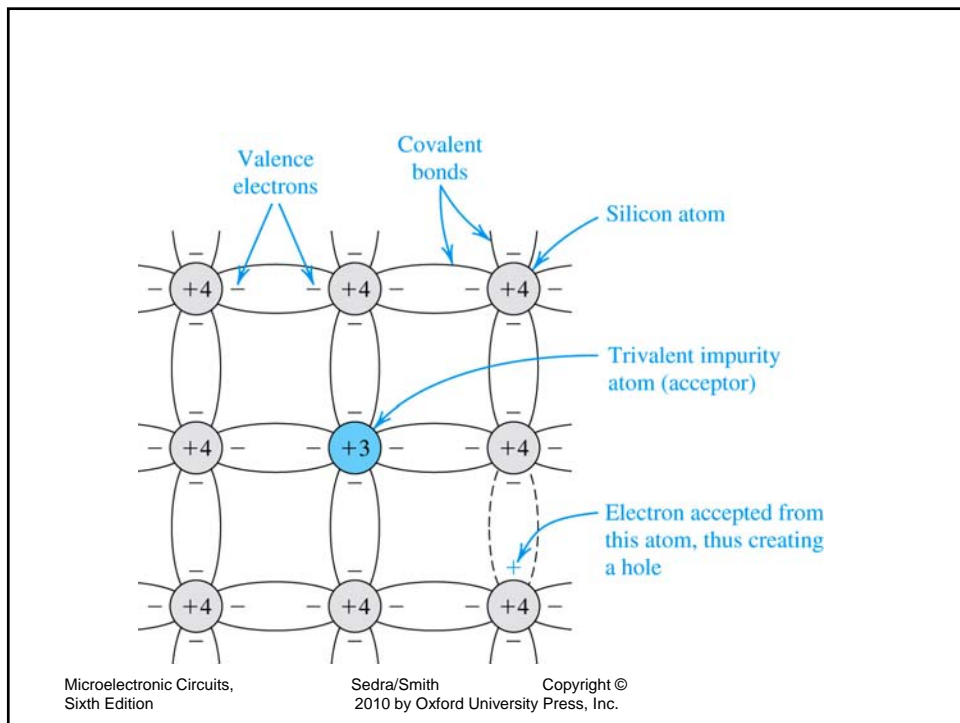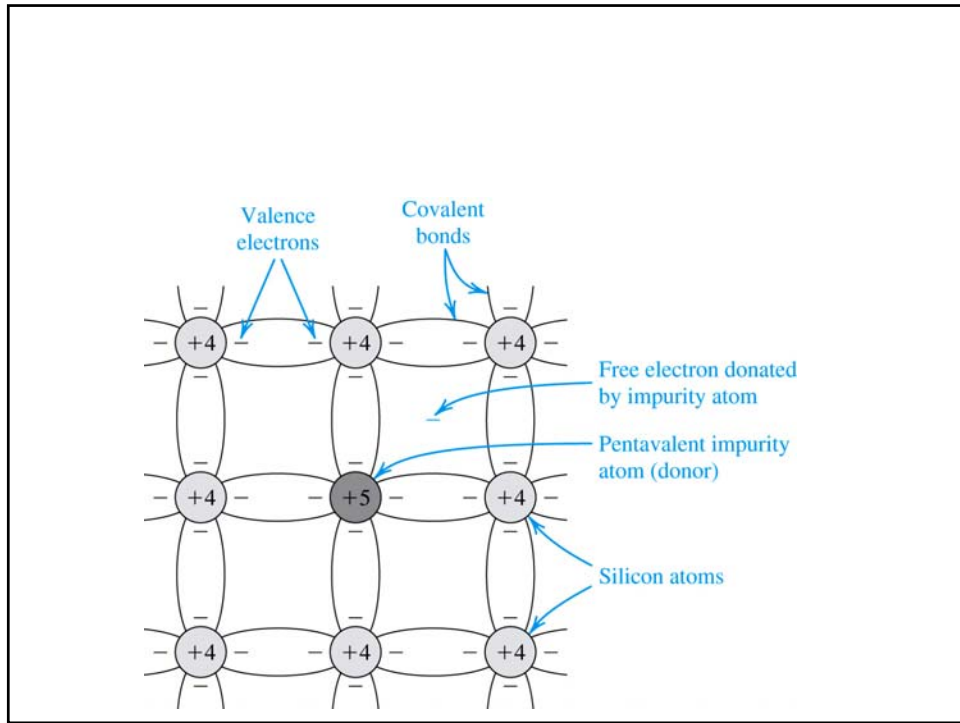

Microelectronic Circuits,  
Sixth Edition

Sedra/Smith  
2010 by Oxford University Press, Inc.

Copyright ©



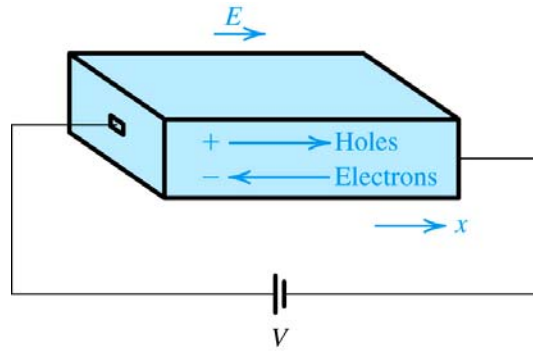



Figure 3.5 An electric field  $E$  established in a bar of silicon causes the holes to drift in the direction of  $E$  and the free electrons to drift in the opposite direction. Both the hole and electron drift currents are in the direction of  $E$ .

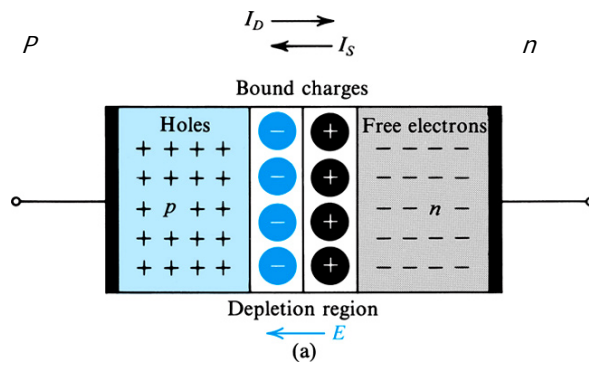

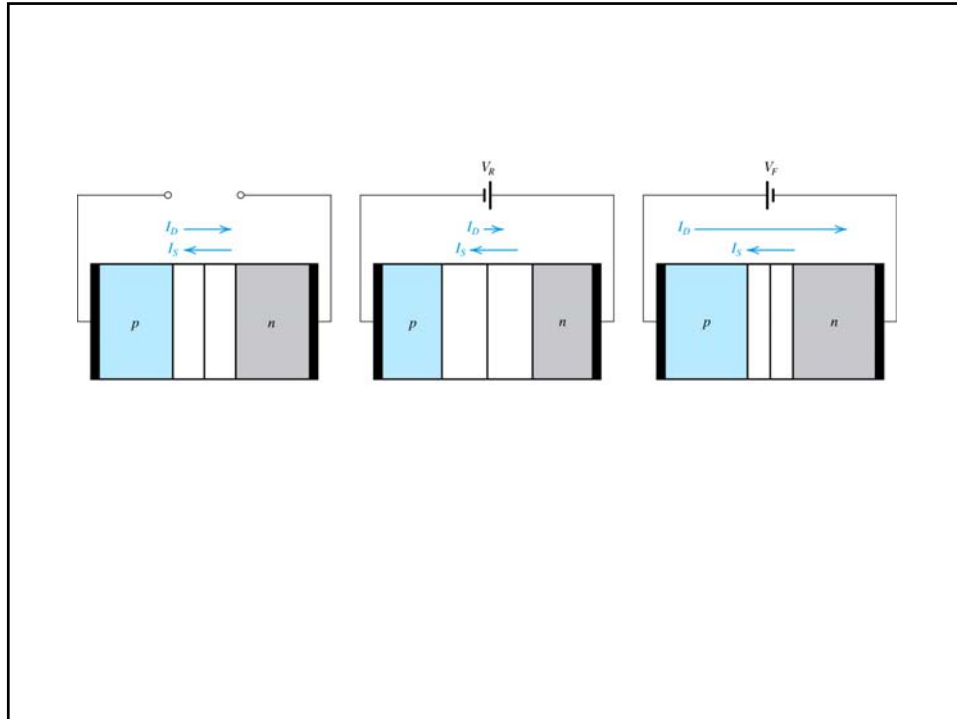

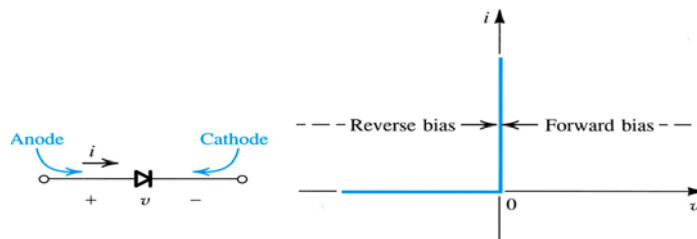
## The Ideal Diode

- So far, we are dealing with linear elements.
- An ideal diode allows current to flow in only one direction, it has a resistance of  $\infty$  in the other direction.
- Short circuit in one direction, and open circuit in the other direction




## Ideal Diode

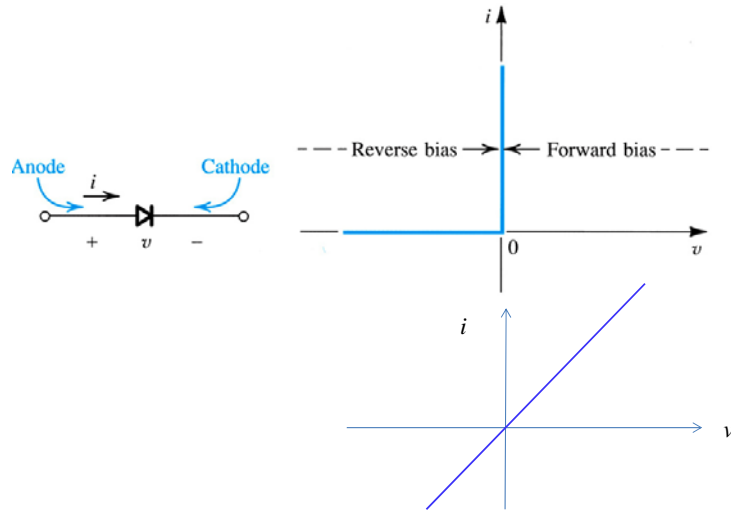


## Diodes

- Conducts or not (ON or OFF) based on the relative polarity. Voltage drop across diode not voltage values.

Reverse biased

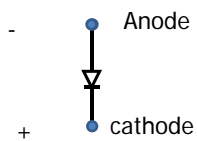


Forward biased

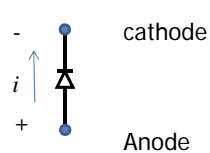

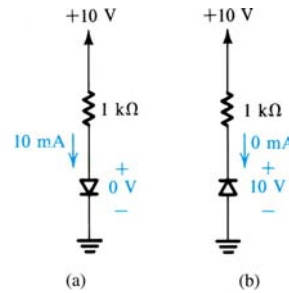
# The Ideal Diode

- Forward biased  $R=0$
- Reverse biased  $R=\infty$


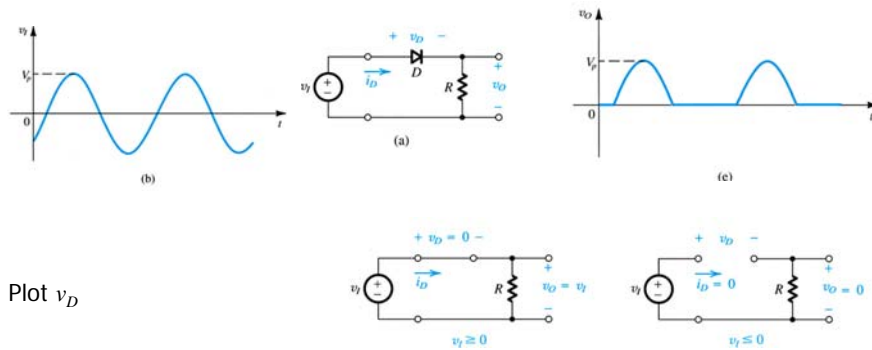
# Rectifier


- A fundamental application of the diode is the rectifier.





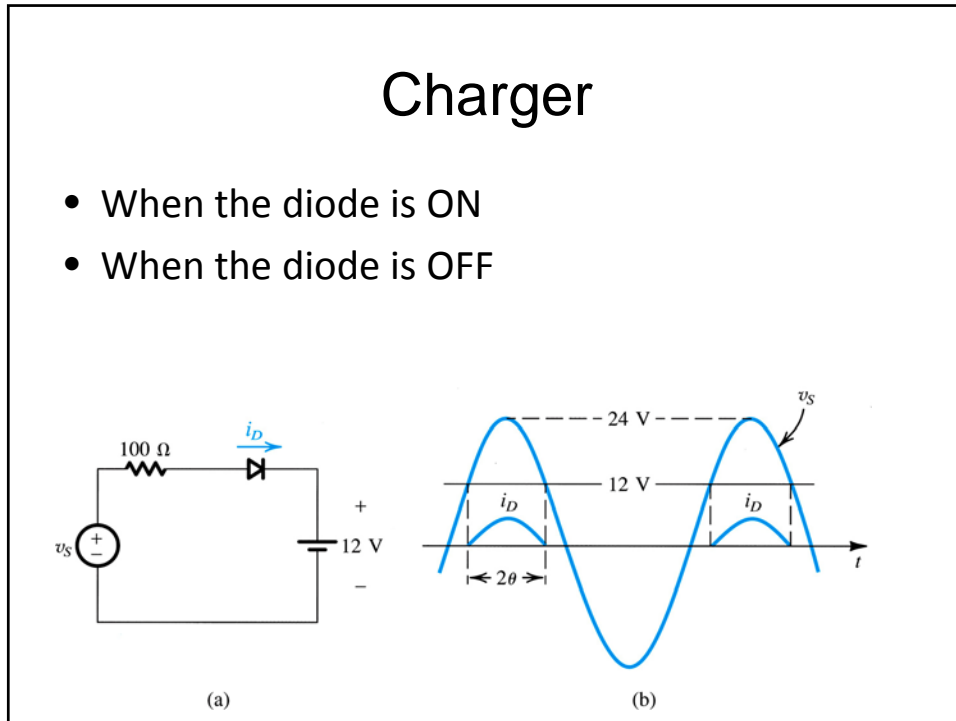
## Charger

- When the diode is ON
- When the diode is OFF



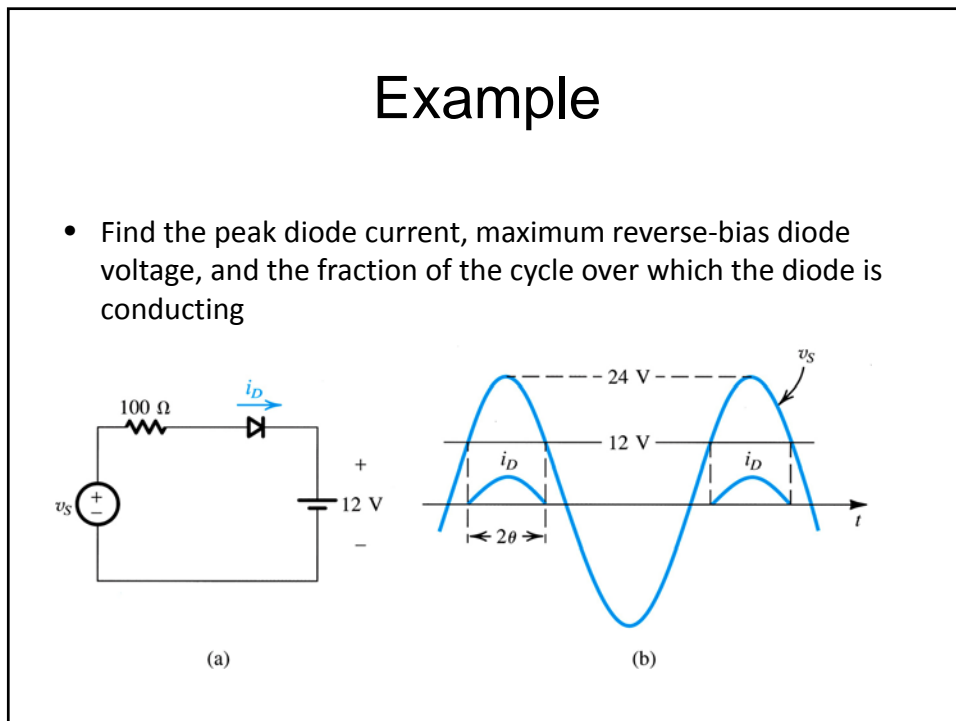
## Example

- Find the peak diode current, maximum reverse-bias diode voltage, and the fraction of the cycle over which the diode is conducting




## Logic Gates

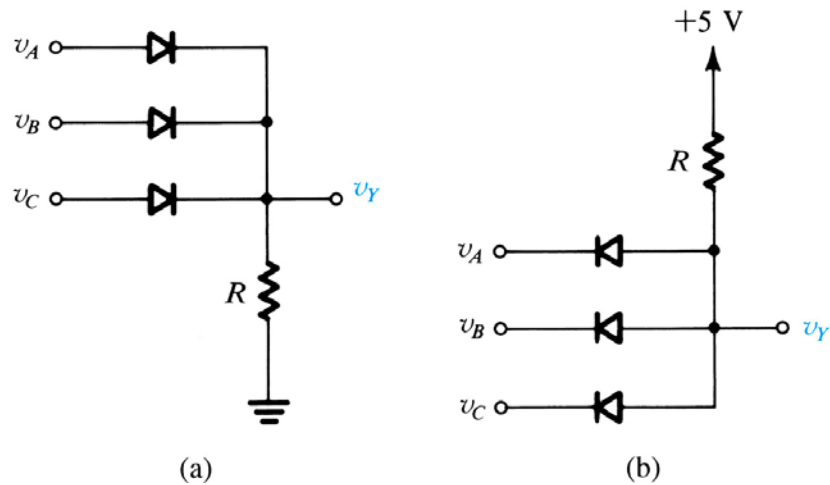

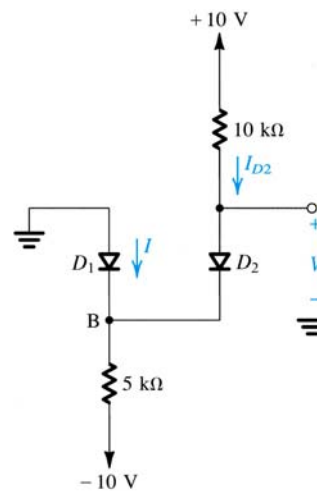
## Example

- Make an assumption, then validate your assumption
- Both are ON
- $V_B = 0 = V$
- $I_{D2} = (10 - 0) / 10\text{K} = 1\text{mA}$
- $1\text{mA} + I = (0 - (-10)) / 5\text{k}$
- $I = 1\text{mA}$
- Assumption is O.K.


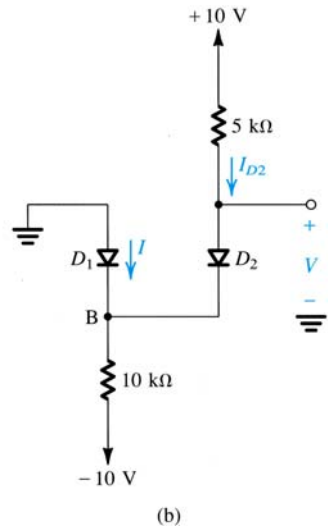
# Example

- Assume both ON
- $V_B = 0 = V$
- $I_{D2} = (10 - 0) / 5k = 2mA$
- $I_{D2} + I = (0 - -10) / 5 = 2 mA$
- $2 + I = 10 / 10K = 1mA$
- $I = -1 mA$
- D1 is not ON, invalid assumption
- Try it for D1 OFF



# Terminal Characteristics

Changes with temp

Sometimes  $v/nV_T$

$$i = I_s (e^{v/V_T} - 1)$$


$I_s$  Saturation current

$$V_T = \frac{KT}{q}$$

Thermal voltage

if  $v \gg V_T, i = I_s e^{v/V_T}$

$$v = V_T \ln \frac{i}{I_s}$$

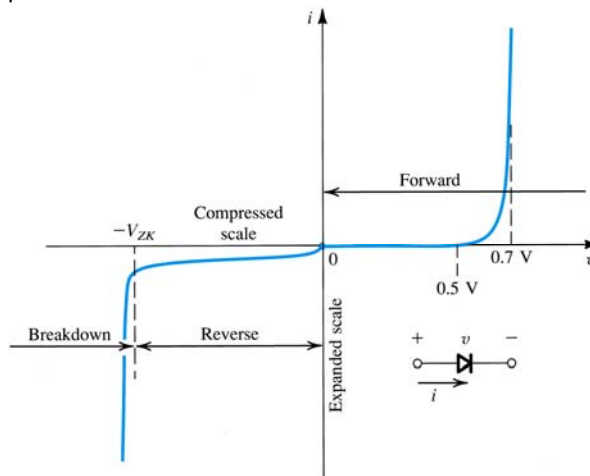

Compare this to an ideal diode

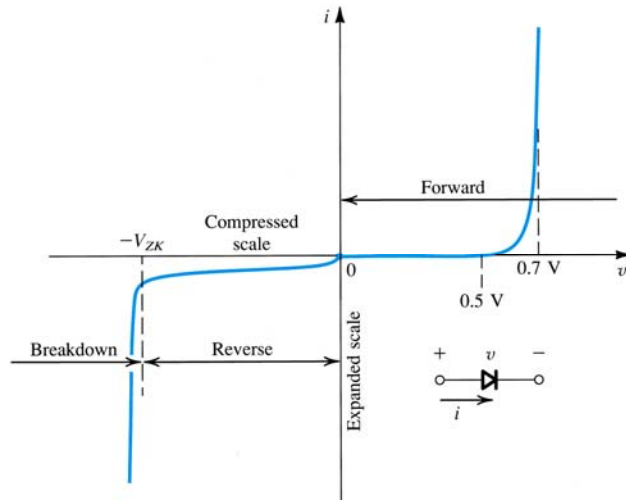


Figure 4.8 The diode  $i-v$  relationship with some scales expanded and others compressed in order to reveal details.

Microelectronic Circuits,  
Sixth Edition

Sedra/Smith Copyright ©  
2010 by Oxford University Press, Inc.


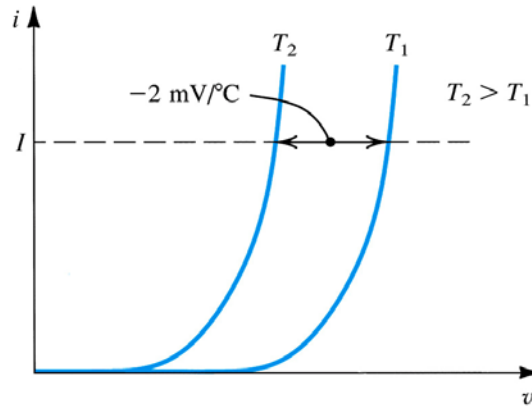
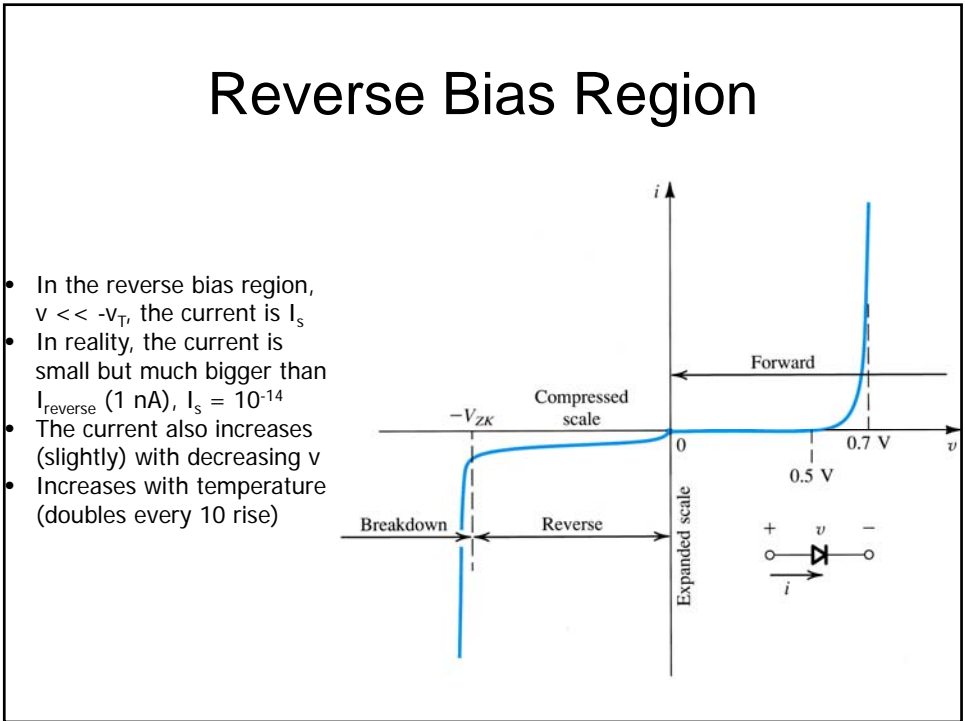


Figure 4.9 Temperature dependence of the diode forward characteristic. At a constant current, the voltage drop decreases by approximately 2 mV for every 1°C increase in temperature.


Microelectronic Circuits,  
Sixth Edition

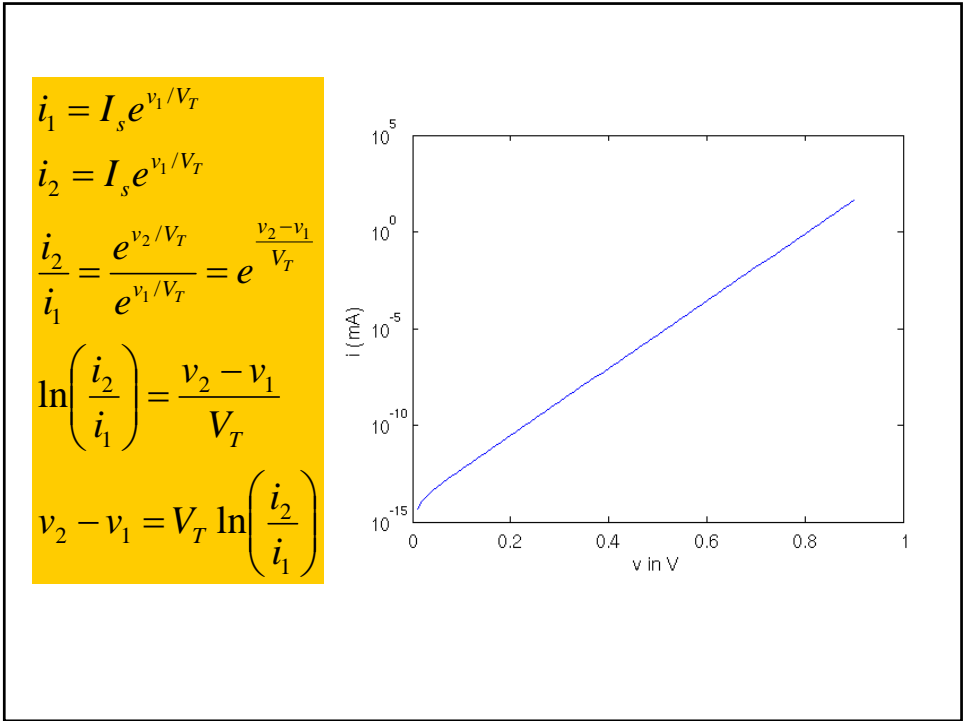Sedra/Smith Copyright ©  
2010 by Oxford University Press, Inc.



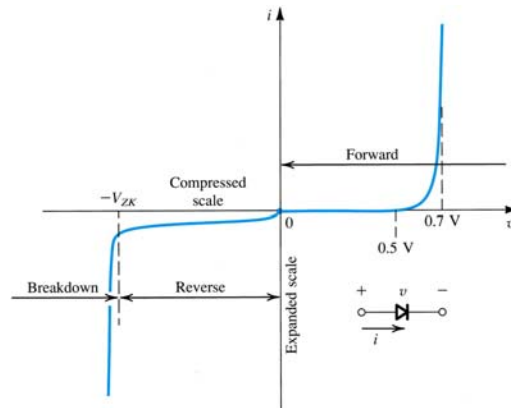
## The Breakdown Region

- The current  $I$  increases rapidly with almost no change in voltage drop
- It is normally not destructive if the power dissipation is limited
- This is useful for voltage regulation



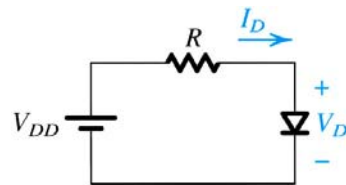
## Diode Models

- Diode can be modeled in different ways depends on the application (and the required accuracy).
  - Exponential model
  - Constant voltage drop model
  - Ideal diode model
  - Piecewise Linear Model
  - Small signal model


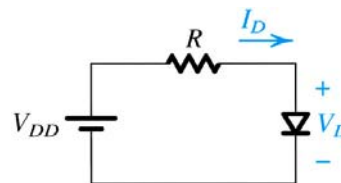
## The exponential Model

- Most accurate, but highly nonlinear
- Assume diode voltage greater than 0.5V
- The diode current is  $I_D = I_S e^{V_D/V_T}$
- Also, the diode current is  $I_D = \frac{V_{DD} - V_D}{R}$
- Solve these 2 equations



Microelectronic Circuits,  
Sixth Edition

Sedra/Smith  
2010 by Oxford University Press, Inc.

Copyright ©

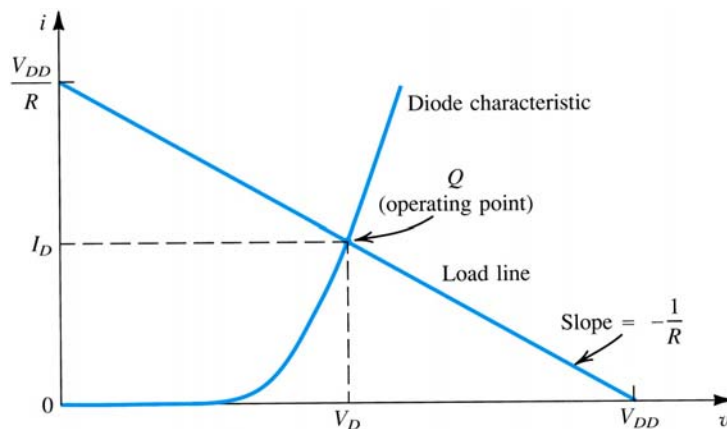


Figure 4.11 Graphical analysis of the circuit in Fig. 4.10 using the exponential diode model.

Microelectronic Circuits,  
Sixth Edition

Sedra/Smith  
2010 by Oxford University Press, Inc.

Copyright ©