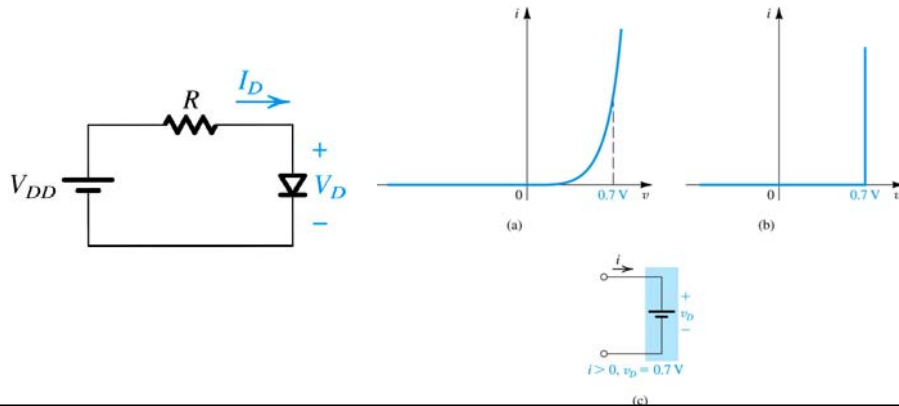



## Constant Voltage Drop Model

- Assume that if the diode is ON, it has a constant voltage drop (0.7V)




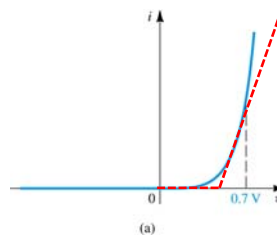
## Piecewise Linear Model

- Constant voltage up to  $\sim 0.5\text{V}$  then resistor


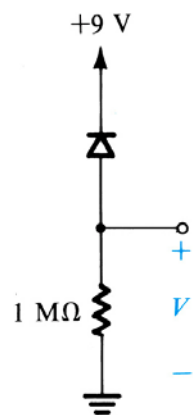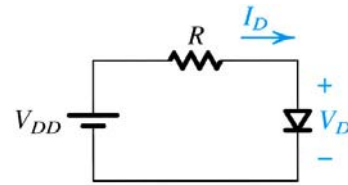
## Ideal Diode Model

- Similar to constant voltage drop, but the voltage drop is 0 V



Find  $I_D$  and  $V_D$  for  $V_{DD} = 5V$ ,  $R=10K\Omega$   
Assume 0.7 V at 1-mA Use iteration

Design a circuit to provide output voltage of 2.4V  
(0.7 V at 1 mA)


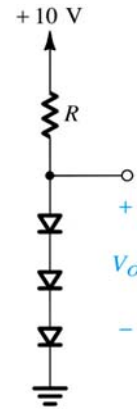


Figure E4.11


Microelectronic Circuits,  
Sixth Edition

Sedra/Smith Copyright ©  
2010 by Oxford University Press, Inc.

## Small Signal Model

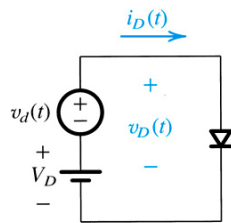

(a)

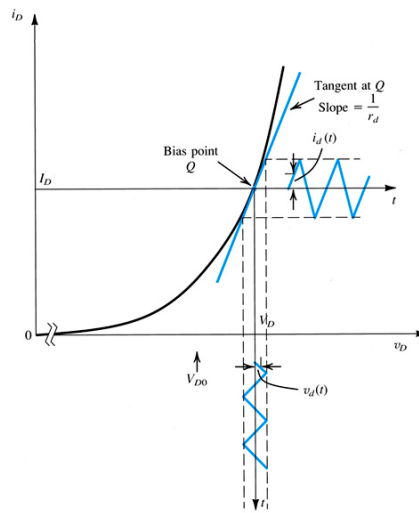

(b)

Microelectronic Circuits,  
Sixth Edition

Sedra/Smith Copyright ©  
2010 by Oxford University Press, Inc.

Solve

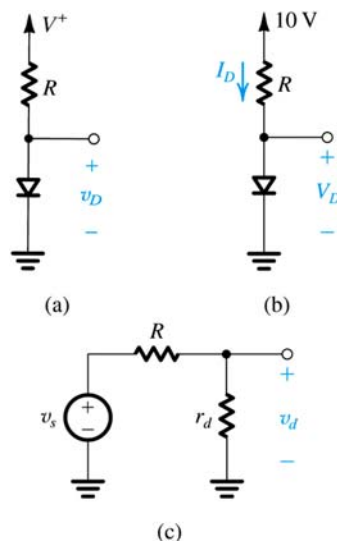


Figure 4.14 (a) Circuit for Example 4.5. (b) Circuit for calculating the dc operating point. (c) Small-signal equivalent circuit.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

## Voltage Regulator (forward bias)

- A voltage regulator is a circuit that provides a constant DC voltage even with the changes of the load resistance or the source resistance.
- Since the diode in the forward bias region have a constant voltage with relatively large changes in current, it could be used as a voltage regulator

Solve

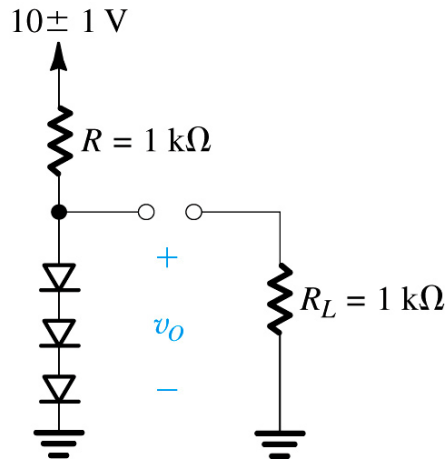


Figure 4.15 Circuit for Example 4.6.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Solve

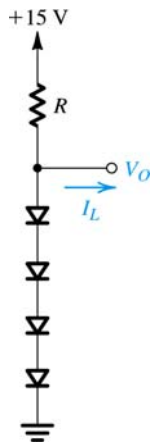


Figure E4.15


Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

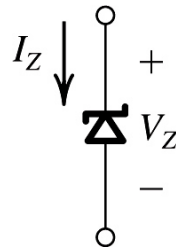
## Zener Diode

- Diodes that are designed to operate in the reverse breakdown region.
- Used for low current regulators (although regulators chips are widely used now).



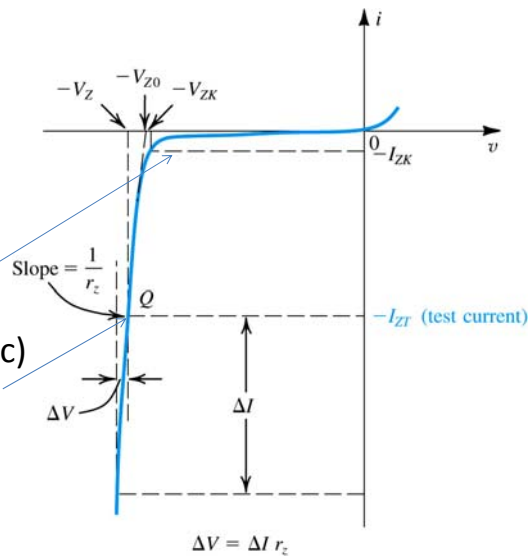
## Zener diodes

- Characterized by
  - $V_Z$  at a specified test current  $I_{ZT}$
  - Maximum power
  - Knee current  $I_{KZ}$
  - Incremental (dynamic) resistance  $r_z = \Delta V / \Delta I$


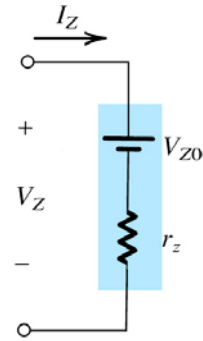
# Zener Diodes

- Equivalent circuit
- $V_{Z0}$  in practice is the same as the knee voltage




Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Assume a 6.8-V Zener diode with  $V_Z = 6.8$  at  $I_Z = 5\text{mA}$ ,  $r_z = 20\ \Omega$ ,  $I_{ZK} = 0.2\ \text{mA}$ ,  $V^+ = 10\text{V} \pm 1\text{V}$

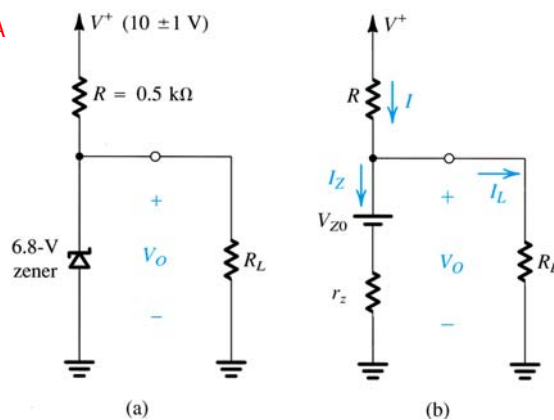- Find  $V_O$  and the line regulation at no load
- Find the load regulation when the load current is  $1\text{mA}$
- Find  $V_O$  for  $R = 2\ \text{k}\Omega$ ,  $0.5\ \text{k}\Omega$
- Find the minimum load for the diode to operate in the breakdown region



Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Changing amplitude and **Electrical isolation**

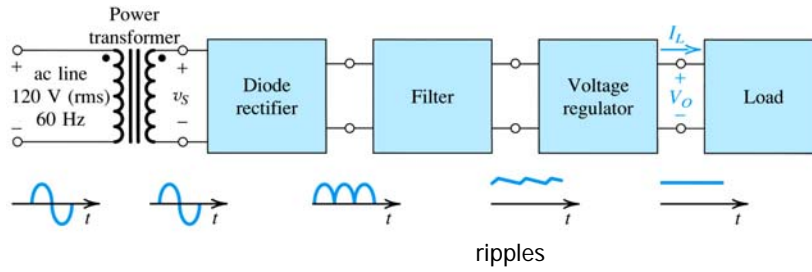


Figure 4.20 Block diagram of a dc power supply.


Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.
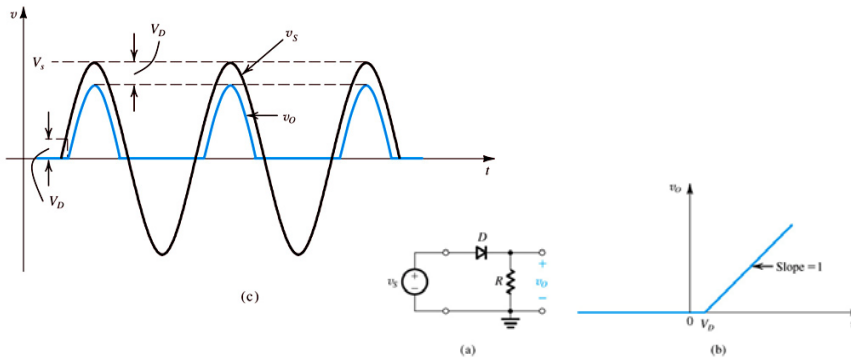
# Half-Wave Rectifier

- Removes the negative voltage half cycle
- Peak inverse voltage < breakdown voltage





Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.



# Full-Wave Rectifier

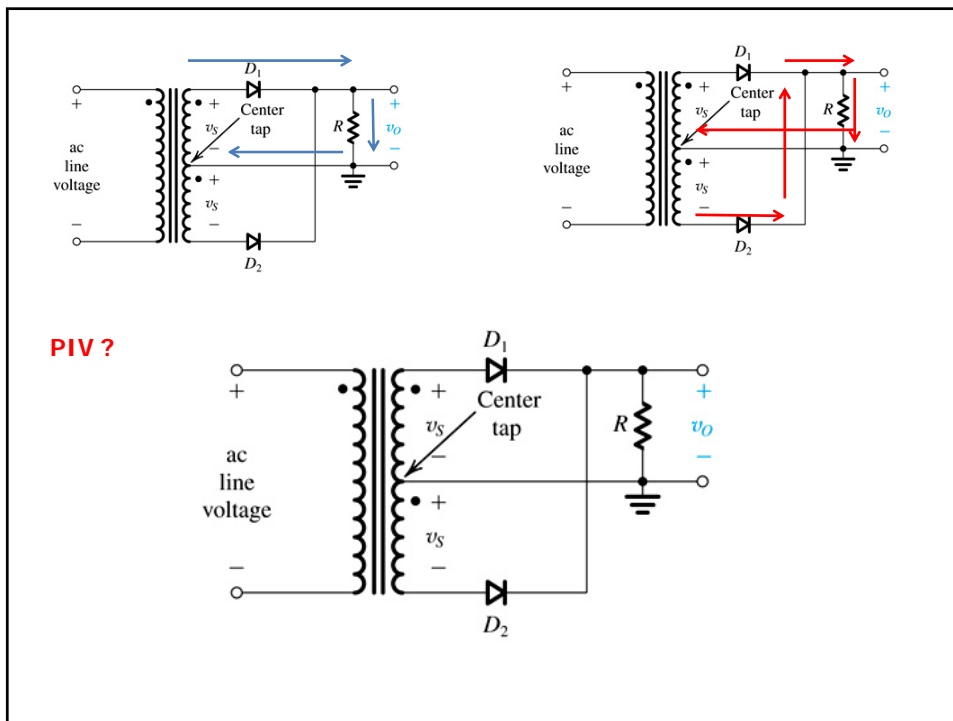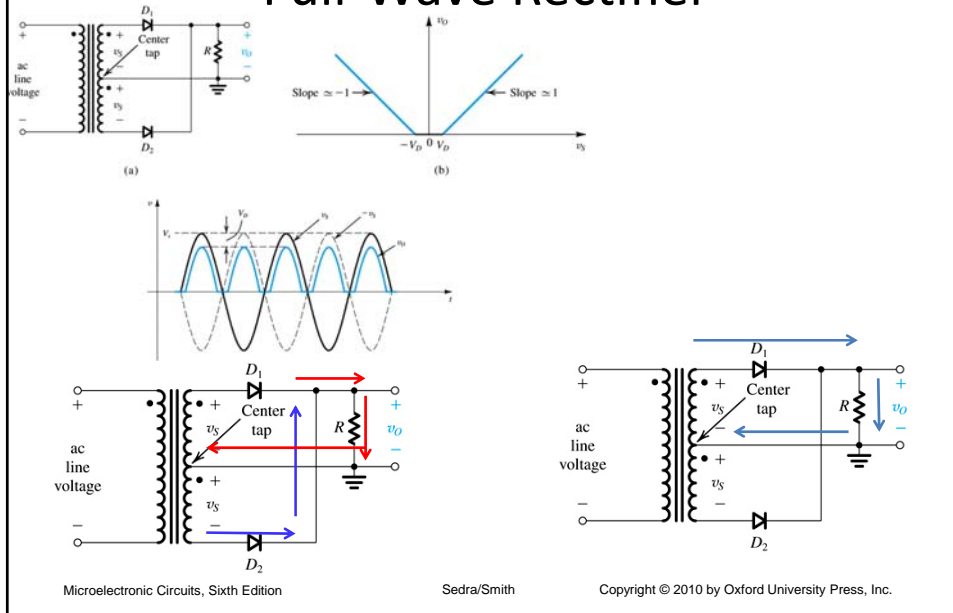

# Bridge Rectifier

PIV ?

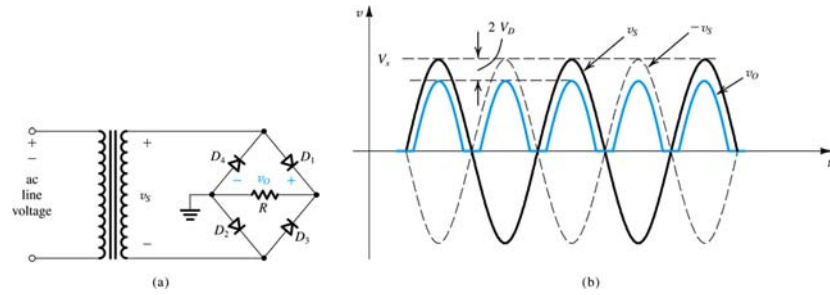


Figure 4.23 The bridge rectifier: (a) circuit; (b) input and output waveforms.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.


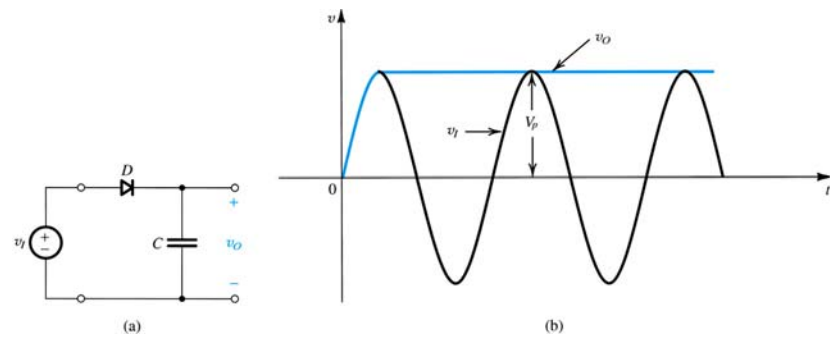
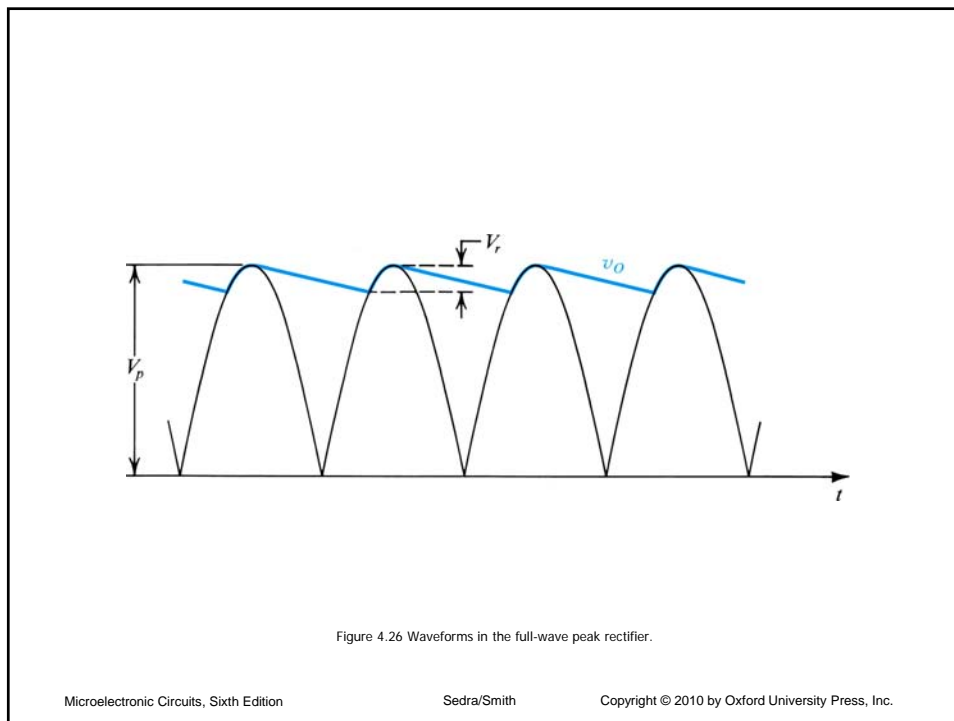


Figure 4.24 (a) A simple circuit used to illustrate the effect of a filter capacitor. (b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a *peak rectifier* or a *peak detector*.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

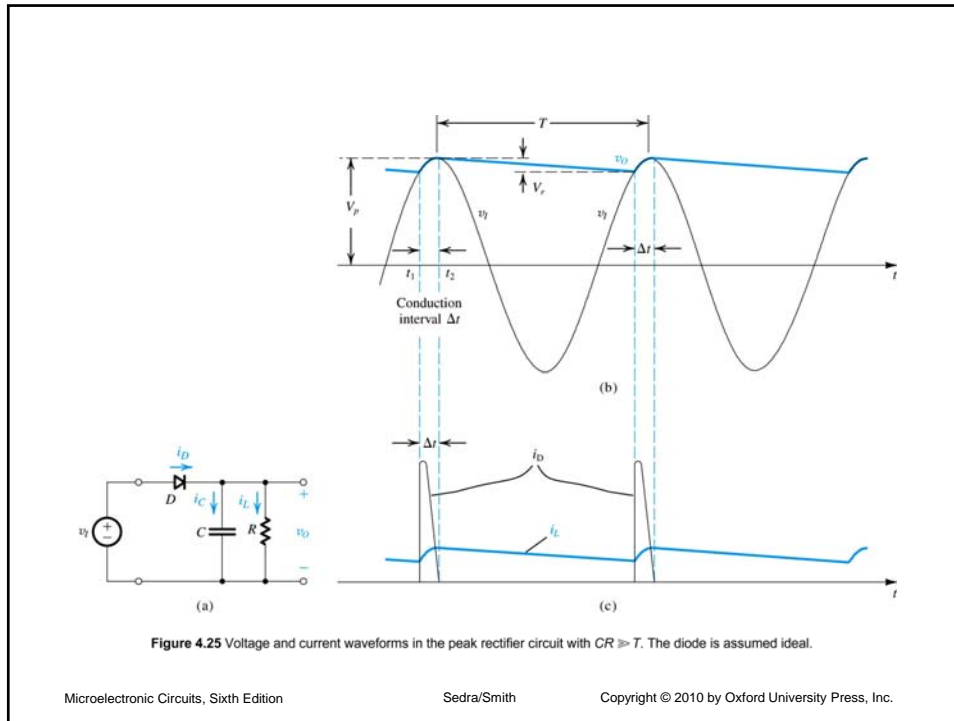Copyright © 2010 by Oxford University Press, Inc.




## Superdiode

- There is one or 2 diode voltage drops in the rectifier circuits we studied.
- That is O.K. when we are designing a DC power supply.
- Can not be used to rectify a small voltage signal (100 mV).
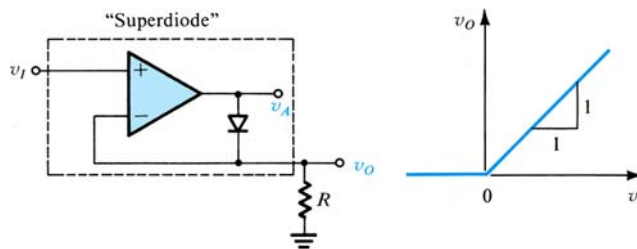
## Superdiode

- When  $v_I$  is positive,  $v_A$  is positive, the diode conducts providing the  $-ve$  feed back and  $v_O = v_I$
- When  $v_I$  is  $-ve$   $v_A$  is negative diode is reverse biased, no current in R, no drop on R,  $v_O = 0$



Microele

(a)

(b)


ord University Press, Inc.

## Diode Circuits


- Limiter circuits
- Clamped capacitor or DC restorer
- Voltage doubler
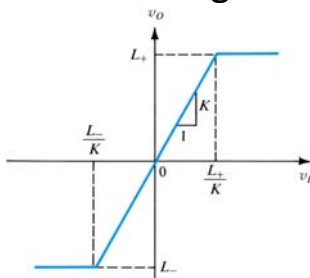
## Limiter Circuits

- $K$  could be  $> 1$ , but we concentrate on  $k \leq 1$  (passive limiter)
- Also known as clippers
- Soft limiting vs. hard limiting





Microelectronic Circuits, Sixth Edition

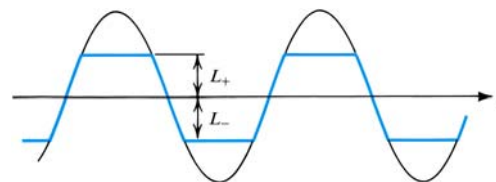


Sedra/Smith

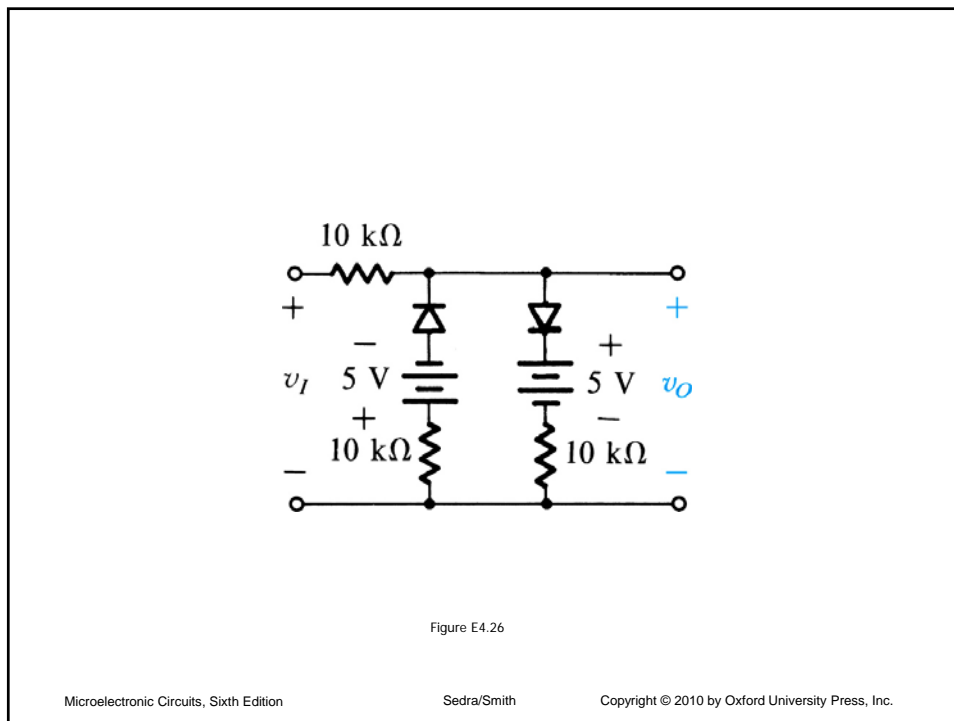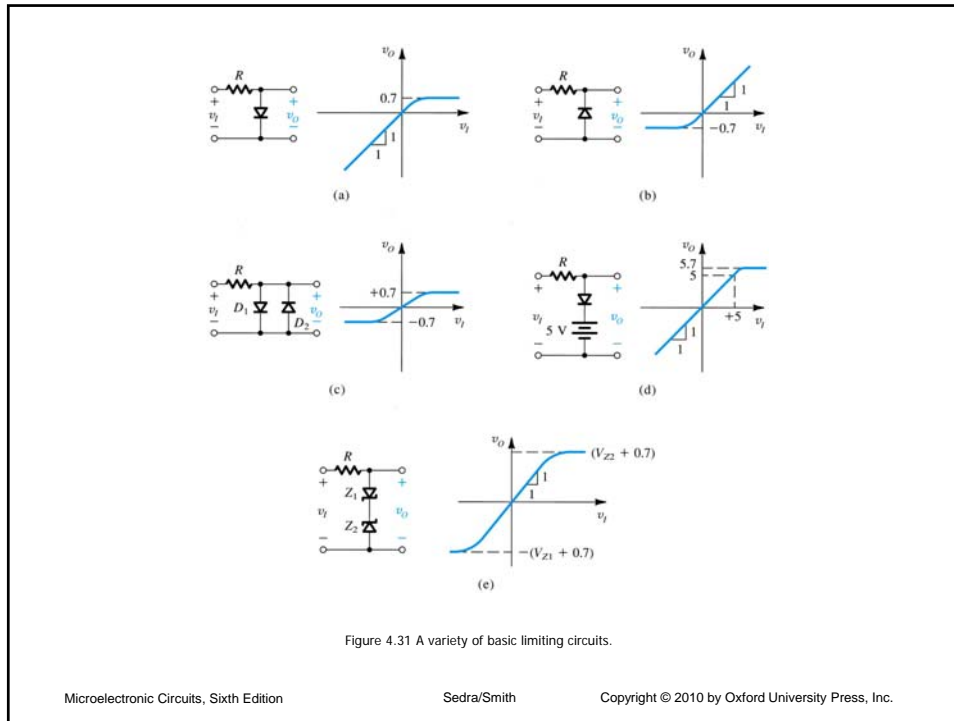Copyright © 2010 by Oxford University Press, Inc.


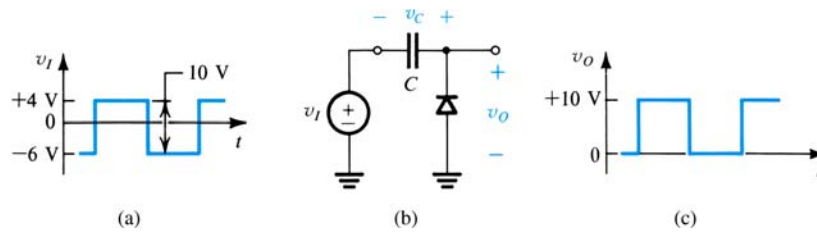
## Clamped Capacitor (DC restorer)

- Shifts the input signal by a specific amount
- When  $v_I$  is  $-6$ ,  $v_C = 6$  V as shown
- When  $v_I$  is  $+4$ , diode is off and capacitor does not discharge
- $v_O = v_I + v_C$




Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

## Clamped Capacitor with a Load

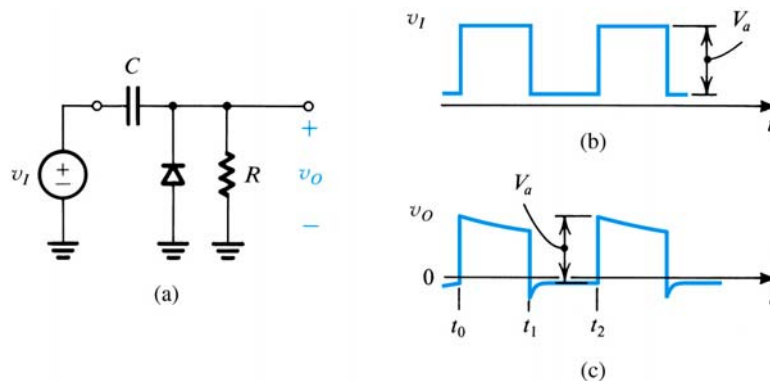Figure 4.33 The clamped capacitor with a load resistance  $R$ .

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

# Voltage Doubler

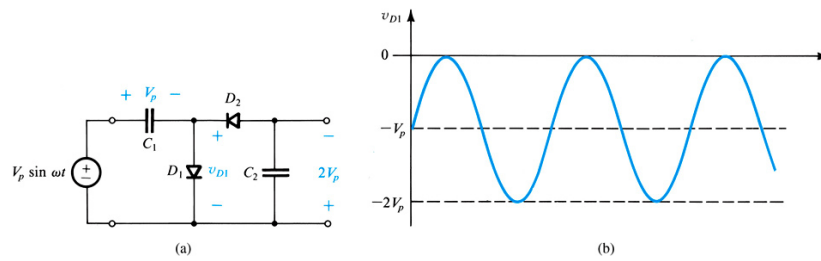


Figure 4.34 Voltage doubler: (a) circuit; (b) waveform of the voltage across  $D_1$ .

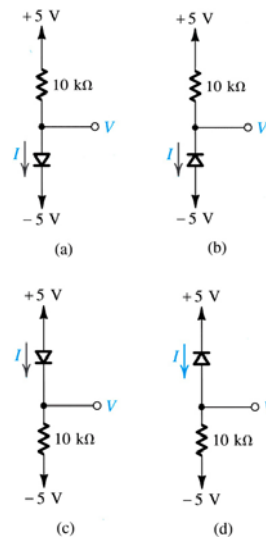


Figure P4.2



