

MOSFETs as Amplifiers

- In saturation, the MOSFET acts as a voltage controlled current source


$$i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{ov}^2 (1 + \lambda v_{DS})$$



- Non-linear V_{ov}^2
- If the current (i_D) flows in a resistive load, output voltage is proportional to i_D .



MOSFET as an amplifier

$$v_o = v_{DS} = V_{DD} - i_D R_D$$

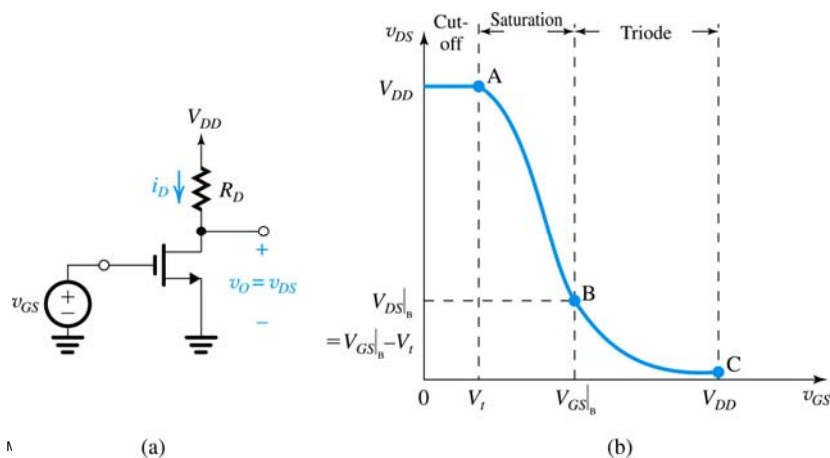Later, we will discuss small signal equivalent circuit




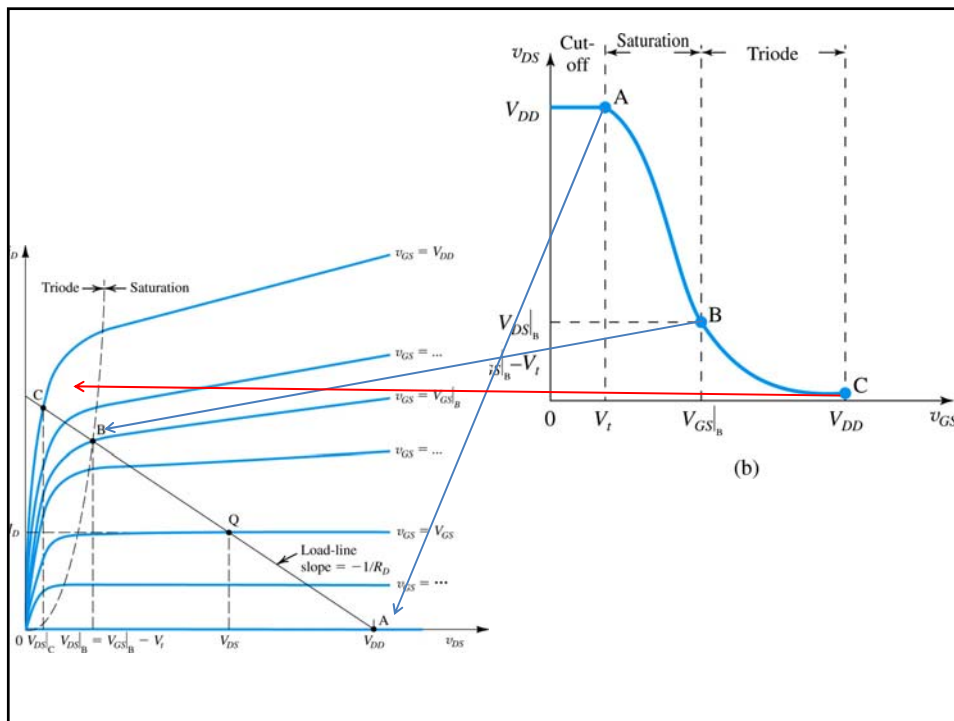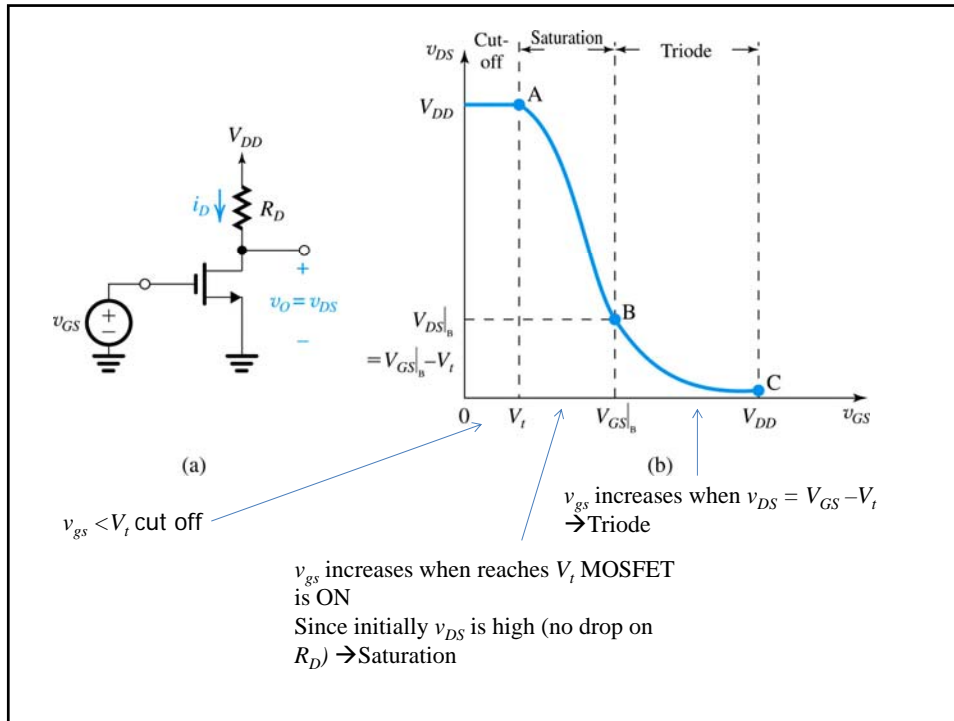

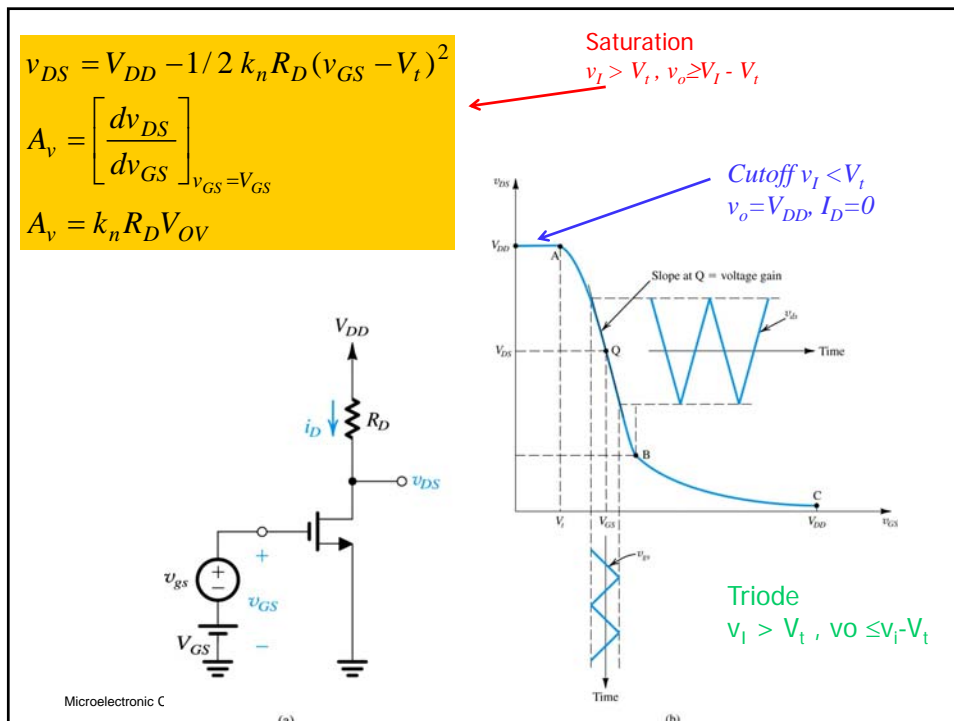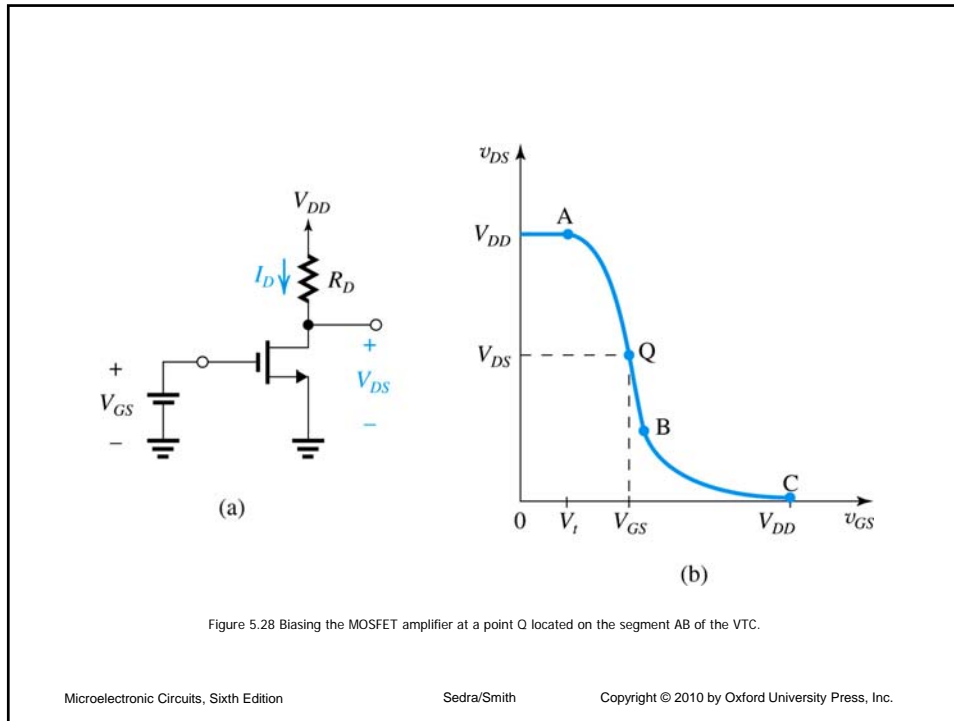

$$V_{DS} = V_{DD} - 1/2 k_n R_D (v_{GS} - V_t)^2$$

$$v_{GS}(t) = V_{GS} + v_{gs}(t)$$

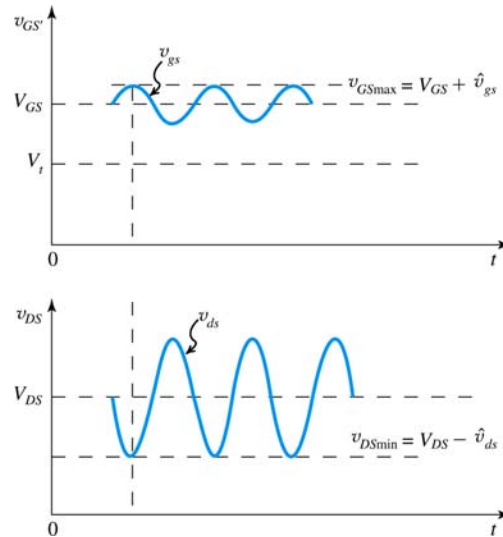



Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.


VTC by Graphical Analysis

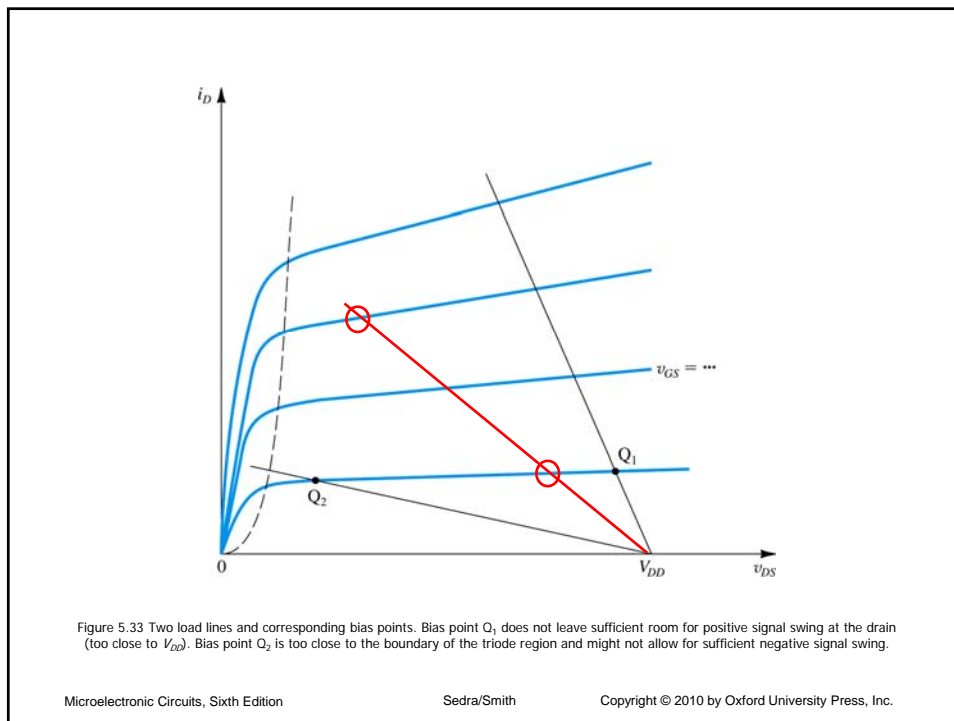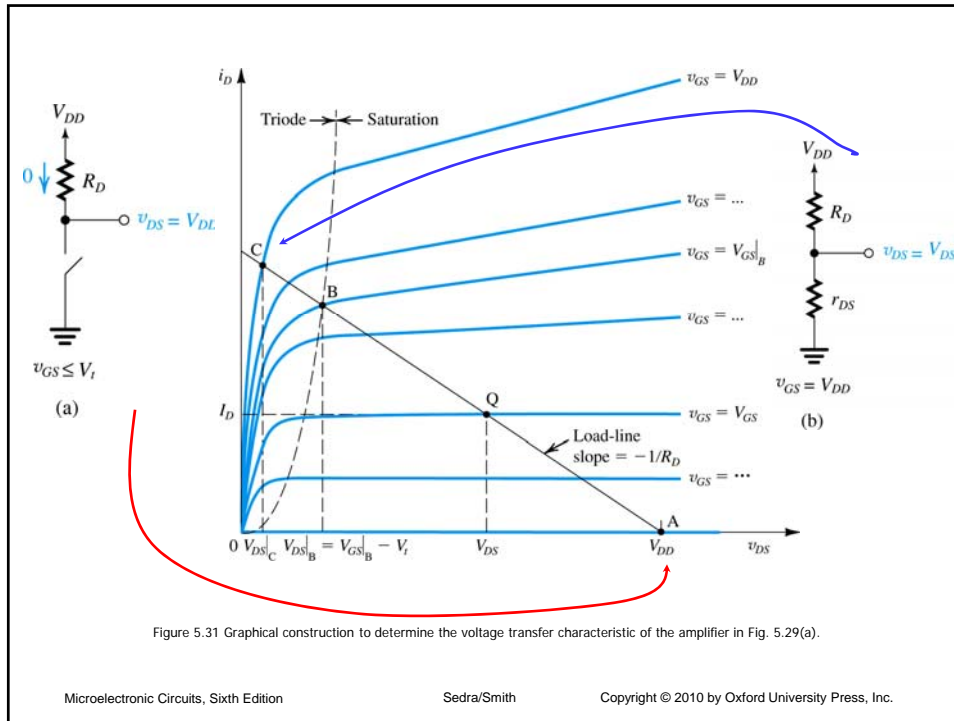- From elementary circuit theory we have
- $V_{DD} = i_D R_D + v_{DS}$
- That represents a line with a slope of $-1/R_D$
- The transistor operates on a point along that line.



Small Signal Operations

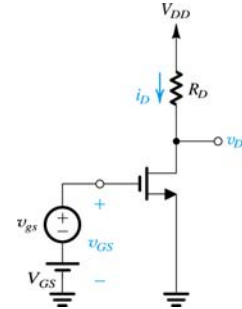- The signal v_{gs} is superimposed on V_{GS}
- $v_{GS} = V_{GS} + v_{gs}$
- $I_D = \frac{1}{2} k_n V_{OV}^2$
- $i_D = \frac{1}{2} k_n (V_{OV} + v_{gs})^2$



$$i_D = \underbrace{\frac{1}{2} k_n V_{OV}^2}_{I_D} + \underbrace{k_n V_{OV} v_{gs}}_{i_d} + \underbrace{\frac{1}{2} k_n v_{gs}^2}_{\text{nonlinear}}$$

Small Signal Operation

- To minimize the nonlinear part

$$\frac{1}{2} k_n v_{gs}^2 \ll k_n V_{OV} v_{gs}$$

$$v_{gs} \ll 2V_{OV}$$

- $i_D \approx I_D + i_d$

$$v_{DS} = V_{DD} - i_D R_D$$

$$v_{DS} = V_{DD} - (I_D + i_d) R_D$$

$$v_{DS} = V_{DS} - i_d R_D$$

Small Signal Operation

$$i_D = \frac{1}{2}k_n V_{OV}^2 + k_n V_{OV} v_{gs} + \frac{1}{2}k_n v_{gs}^2$$

Assuming small

$$i_d = k_n V_{OV} v_{gs}$$


$$g_m = \frac{i_d}{v_{gs}} = k_n V_{OV}$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}}$$


- Transconductance: relates i_d and v_{ds}

Transconductance

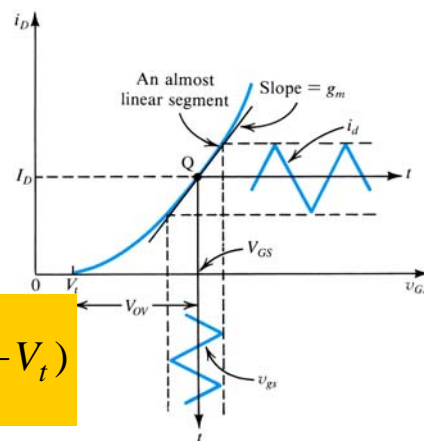- The slope of the i_{DS} - v_{DS} characteristics at the Q point (DC bias point)
- As shown, almost linear.


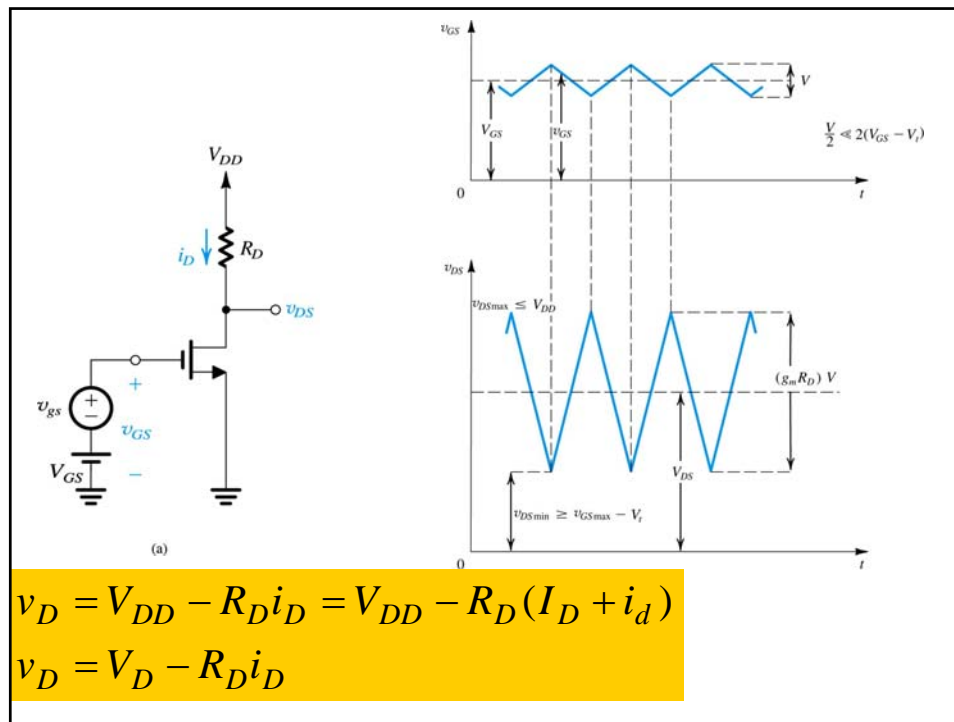
$$g_m = \frac{i_D}{v_{GS}} = k_n' \left(\frac{W}{L} \right) (V_{GS} - V_t)$$




Separating DC Analysis and Signal Analysis

- Signal quantities are superimposed on DC quantities.
- We can separate DC and AC Analysis.
- The DC Analysis determine the Q Point
- (Bypass) Capacitors are added to prevent disturbing the DC bias (Q point). **WHY?**
- Draw the circuit from the signal point of view
 - DC voltages (current) are short (open)
 - Capacitors are short
 - MOSFET replaced by **small signal equivalent Circuit**


Why Capacitors

- Adding the load

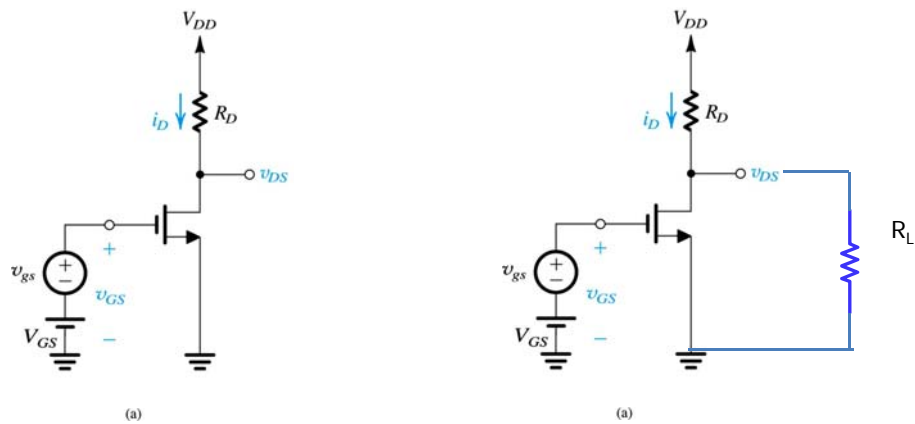


Small Signal Equivalent Circuit

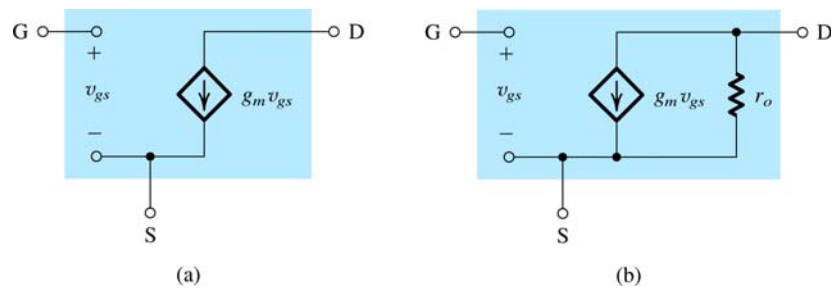- Represents only time varying component (DC only determine the bias point)
- What is the difference between (a) and (b).




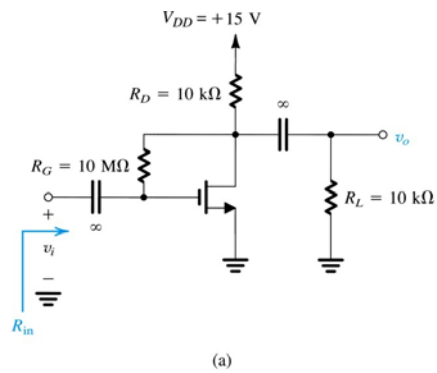Example


- Find the small signal voltage gain, input resistance, and the largest allowable input signal. $V_t=1.5\text{V}$, $k'_n=0.25\text{mA/V}^2$, $V_A=50\text{V}$.




Example cont.

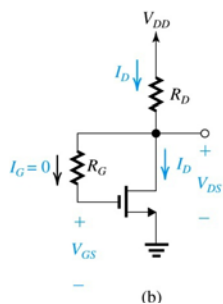

Example cont.

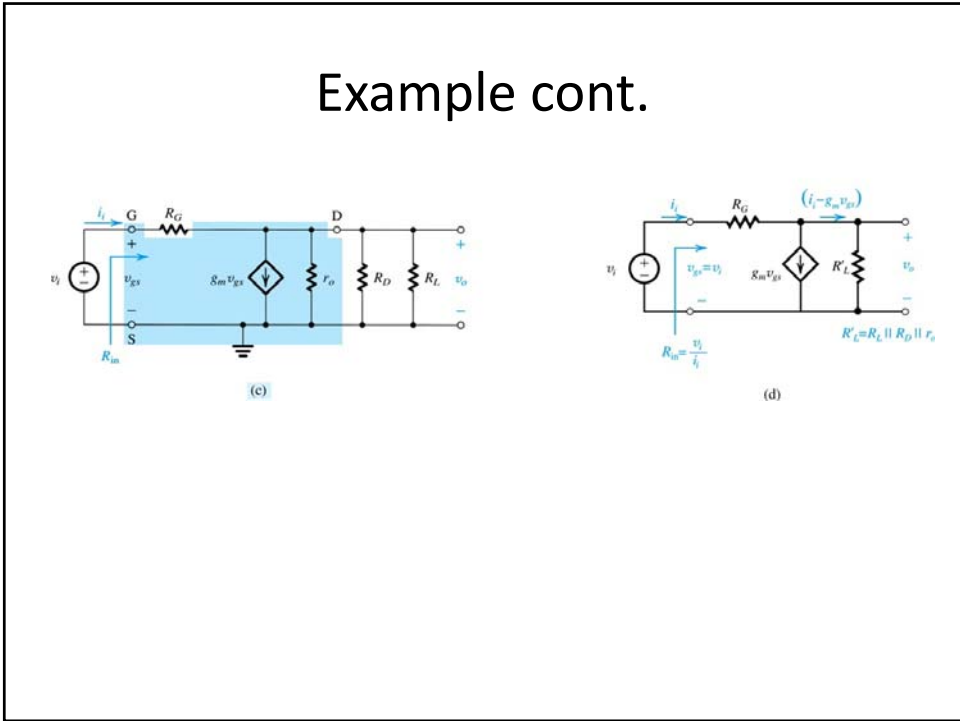


T-Equivalent-Circuit Model

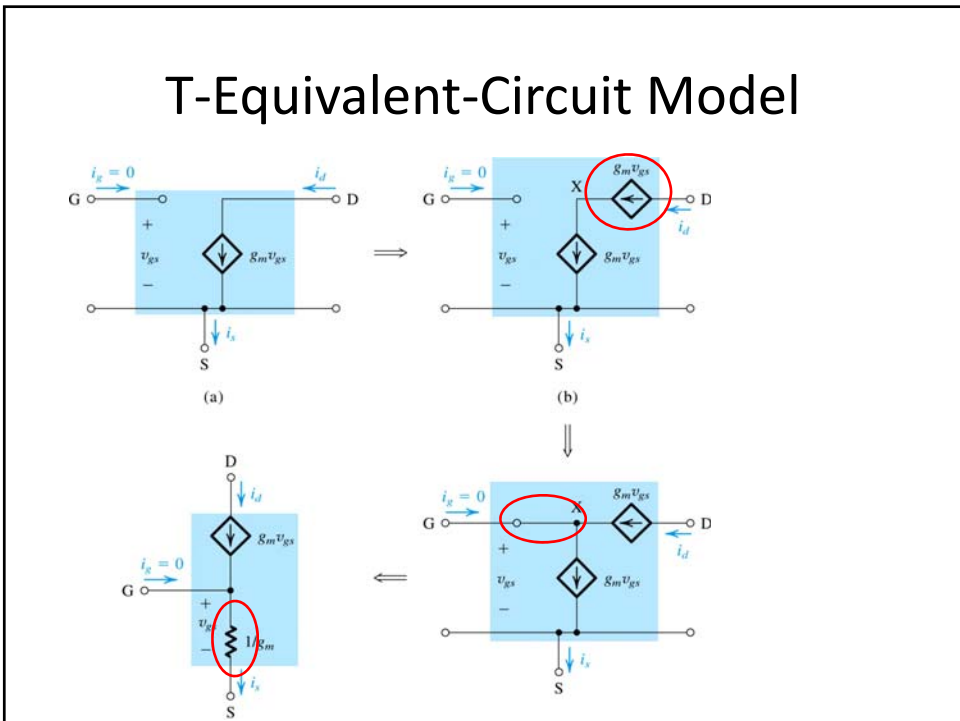


Example

- Assume saturation, find gain and input

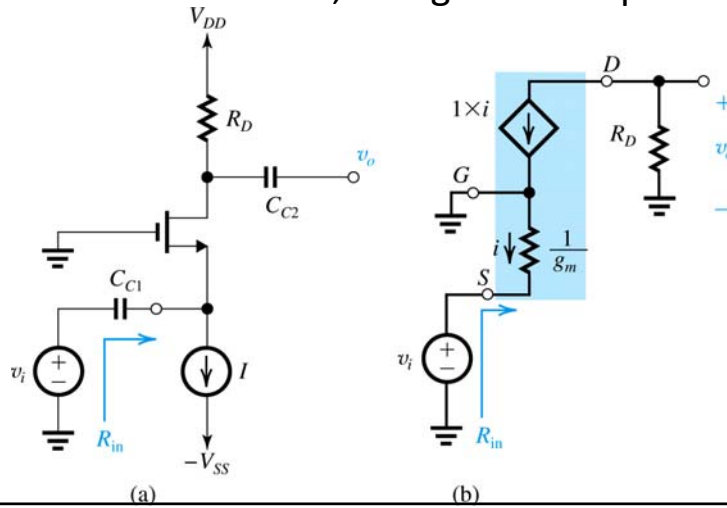

Incorporating r_o

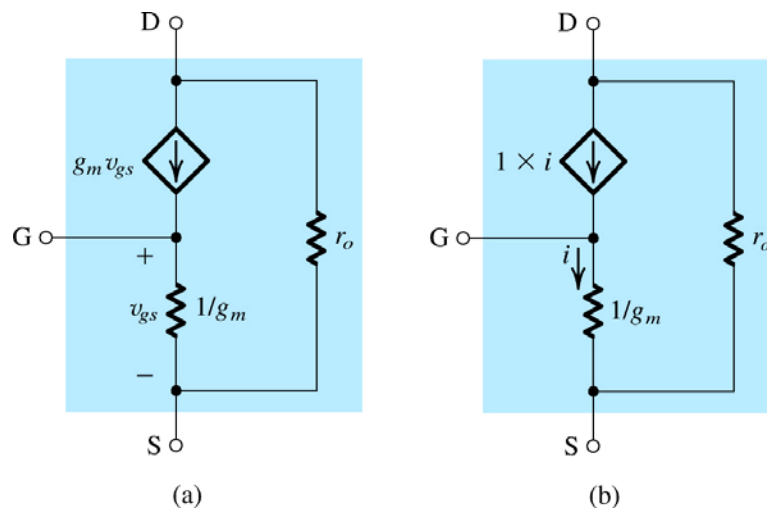


MOSFET Amplifier Configuration

- Single stage
- The signal is fed to the amplifier represented as v_{sig} with an internal resistance R_{sig} .
- MOSFET is represented by its small signal model.
- Generally interested of gain, input and output resistance (overall amplifier circuit not only the small signal model).


MOSFET Amplifier Configuration

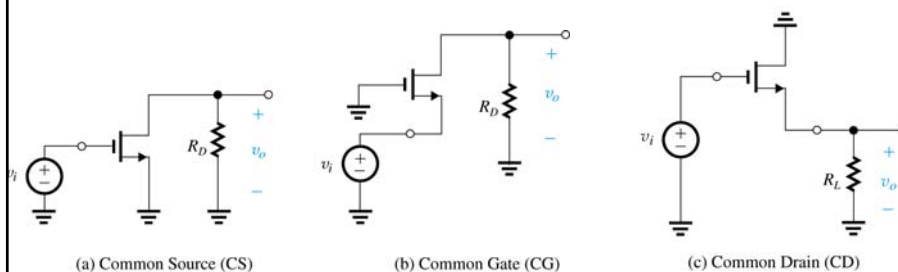- Considering only the small signal not the bias



Characterizing Amplifiers

- Find gain, input and output resistance

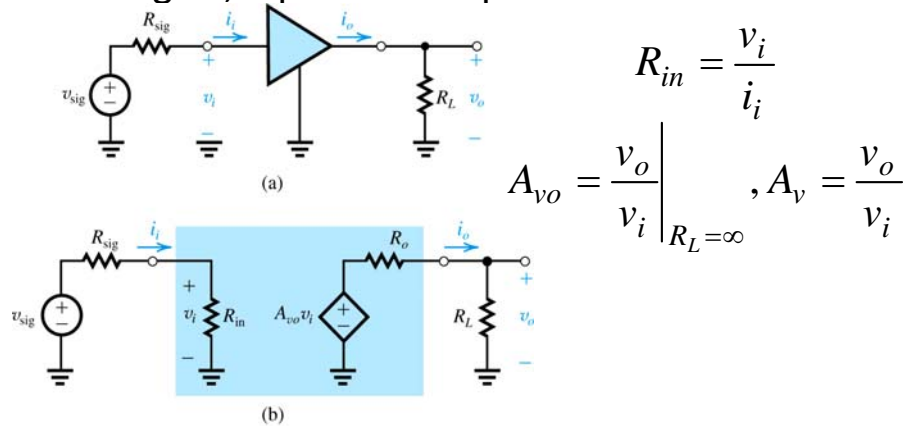

Amplifier Configuration

- Common Source
- Common Source with a source resistance
- Common gate
- Common drain or voltage follower


Amplifiers

$$v_o = A_{vo} v_i \frac{R_L}{R_L + R_o}$$

$$v_i = v_{sig} \frac{R_{in}}{R_{in} + R_{sig}}$$

$$A_v = A_{vo} \frac{R_L}{R_L + R_o}$$

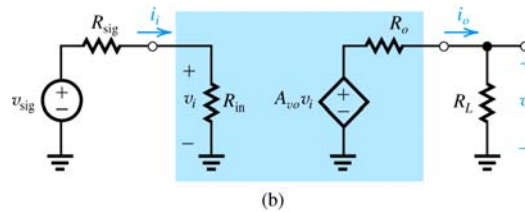
$$G_v = \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_o}$$



Common Source

- Most widely used configuration
- In multistage amplifiers, the bulk of the gain is from common source.
- The source is grounded, making it common between input and output.
- We can use hybrid π model.



Common Source

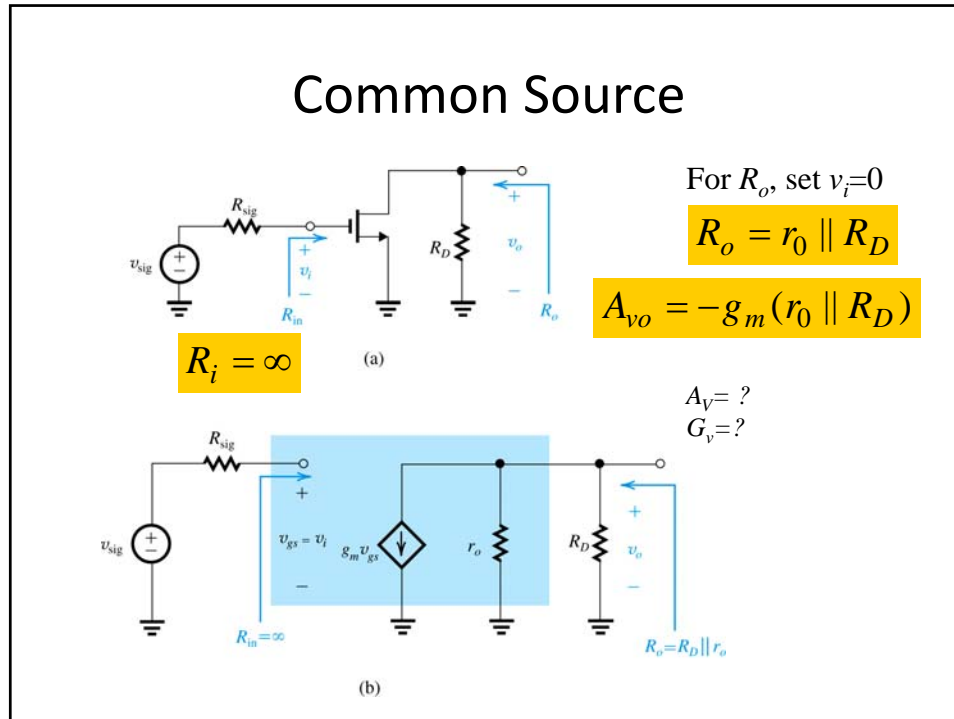

Common Source with Source R

- For simplicity, r_o is not included.
- No effect on discrete implementation, not so for IC's
- R_s provides a negative feedback to control the magnitude of the signal to prevent nonlinear distortion.
- Also reduces the voltage gain and extends the useful bandwidth.



Common Source with Source R

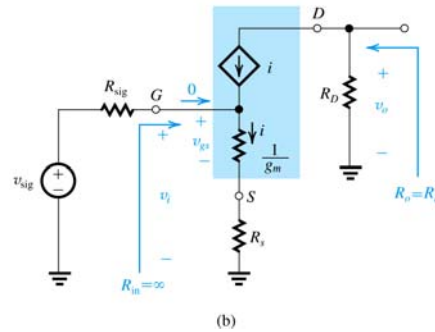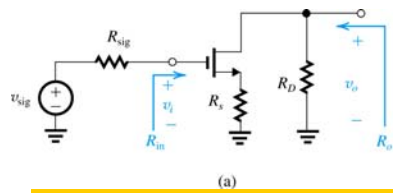


$$v_{gs} = -g_m v_i \frac{1/g_m}{1/g_m + R_S}$$

$$v_{gs} = \frac{v_i}{1 + g_m R_S}$$

Common Gate Amplifier

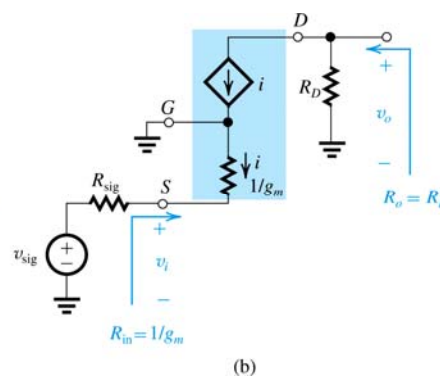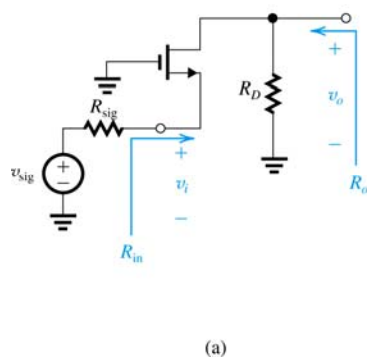


Common Drain Amplifier – Source Follower

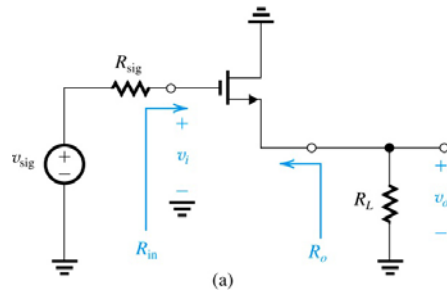

Since there is a resistance R_L connected to the source, it is easier to use the T-model

Common Source – Voltage Follower

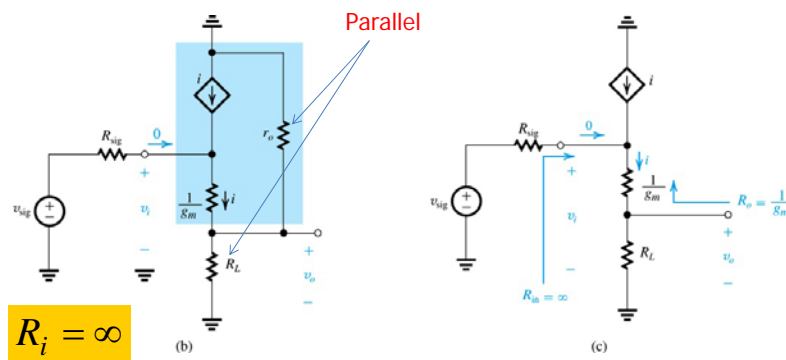


Comparison

	CS	CS+RS	CG	CD
Rin	∞	∞	$\frac{1}{g_m}$	∞
Rout	$R_D \parallel r_o$	R_D	R_D	$1/g_m$
G	$-g_m(R_D \parallel R_L \parallel r_o)$	$A_v = \frac{g_m(R_D \parallel R_L)}{1 + g_m R_S}$	$G_v = \frac{(R_D \parallel R_L)}{1/g_m + R_{sis}}$	$G_v = \frac{A_v R_L}{1/g_m + R_L}$


Discrete CMOS Amplifiers



- MOS are mostly used in IC's
- However, we present practical circuits for discrete implementation.
- Good if you are building a circuit on a breadboard (in the lab).

Common Source

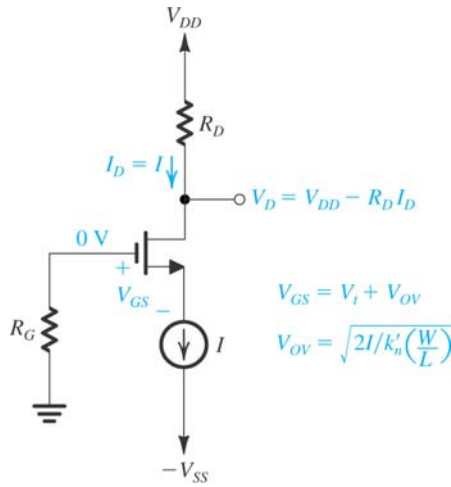


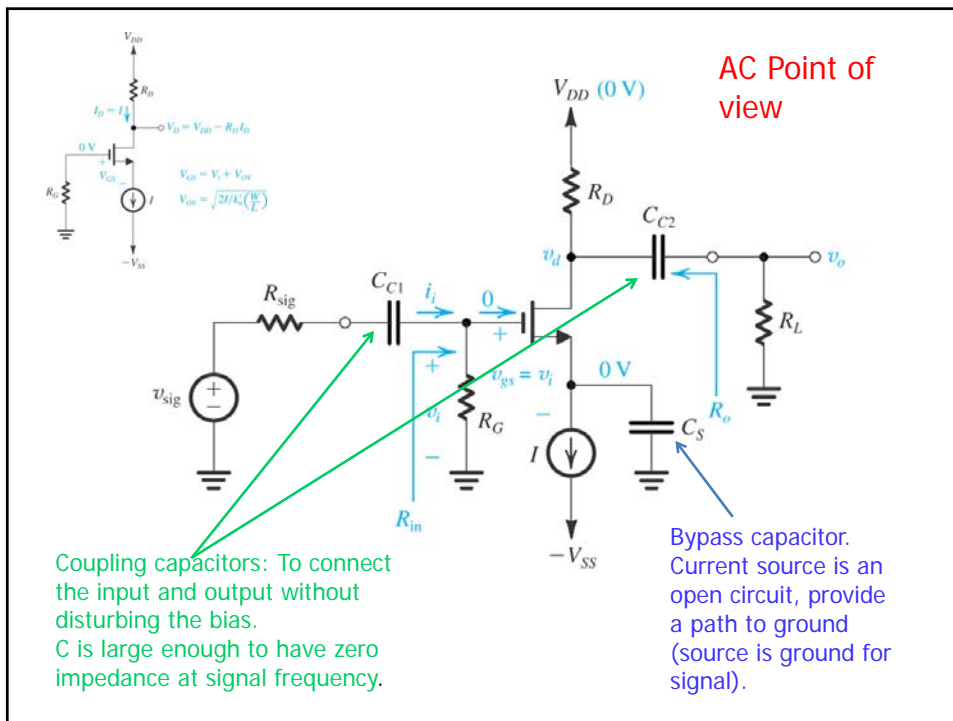- DC Analysis
- Can use any biasing technique we studied
- Calculate the bias (Q) point



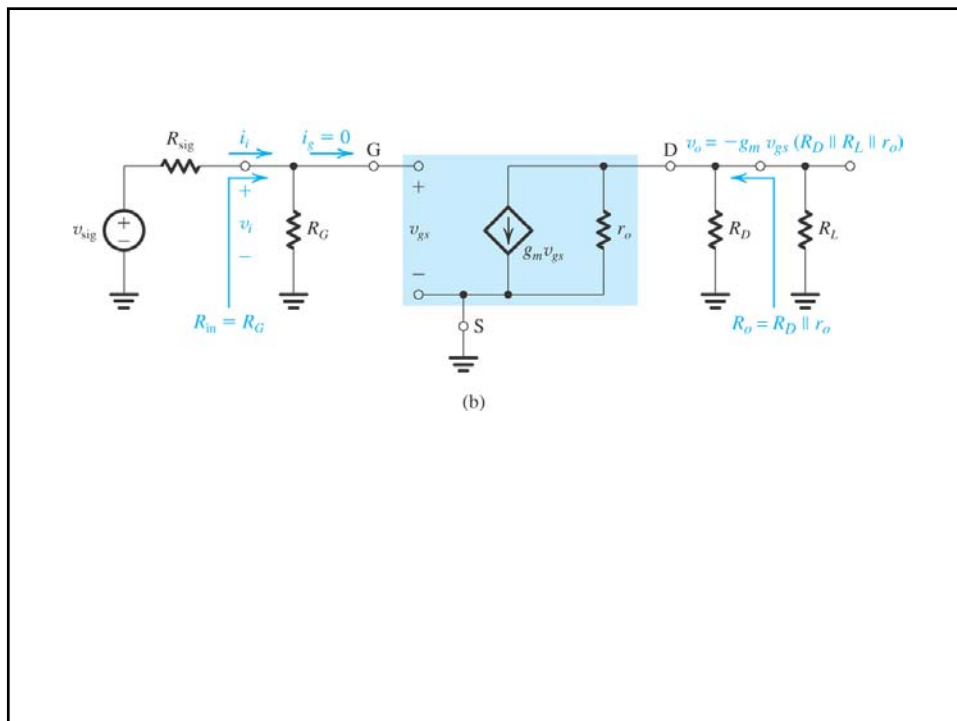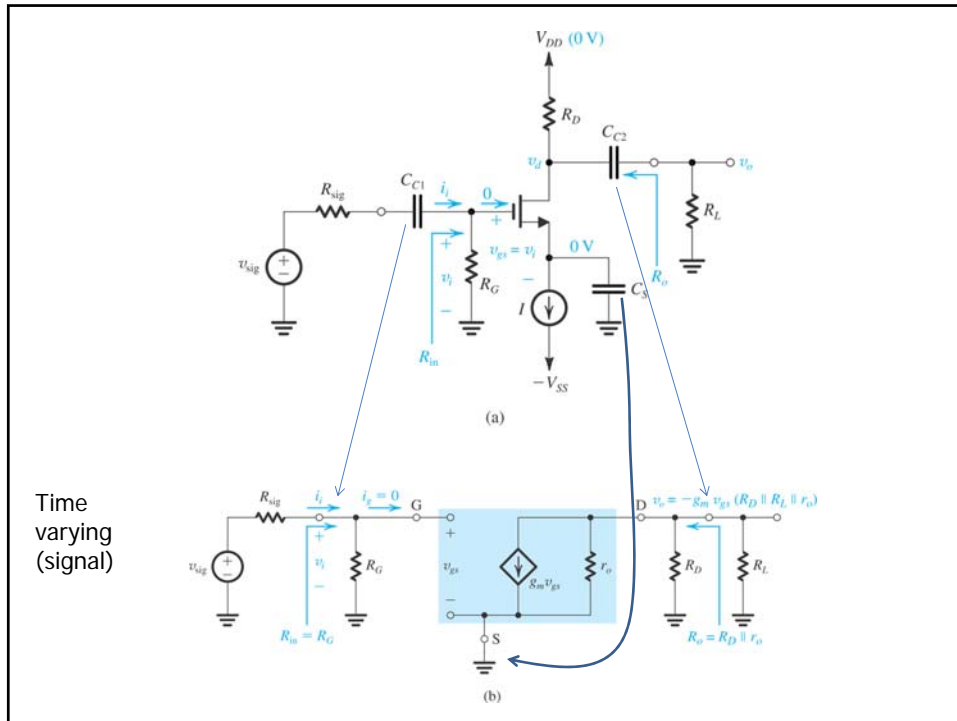

Common Gate

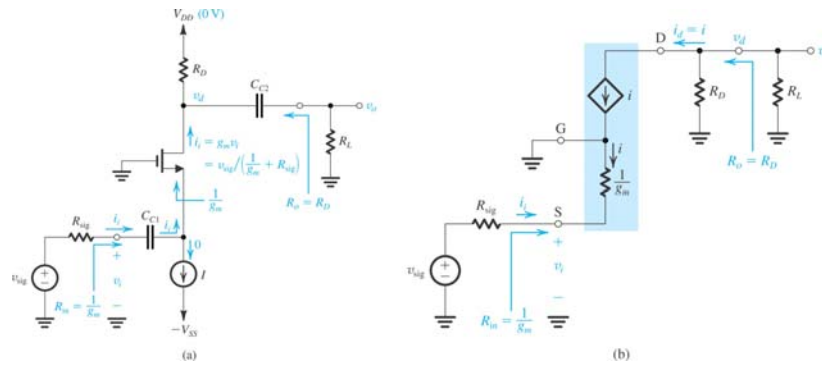

Voltage Follower

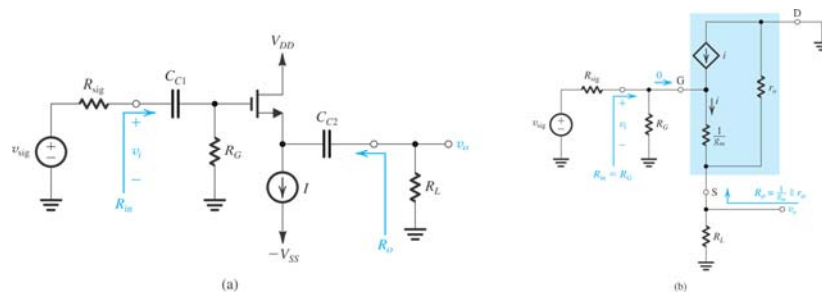


Figure 5.60 (a) A source-follower amplifier. (b) Small-signal, equivalent-circuit model.