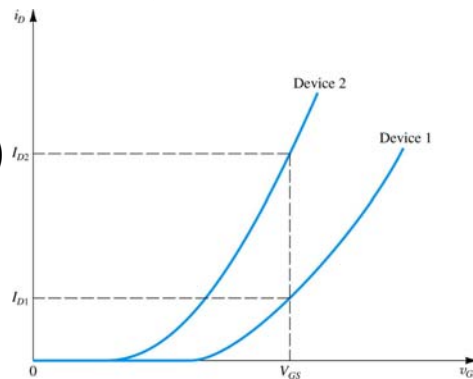


Biassing in MOS Amplifiers

- How to choose the operating point?
- Want a stable Q-point (known I_D and V_{DS}) to ensure operation in the saturation region.


Biassing -- Fixing V_{GS}

- I_D depends on μ , C_{ox} , W/L and V_p and V_{GS}
- C_{ox} , V_{GS} (even W/L) can vary across devices of the same type.
- Not a good idea to.
- Many parameters(t)




Biassing – Fixing V_G and R_S

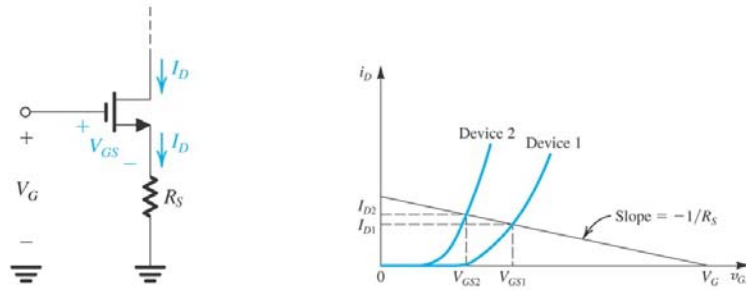
- R_S provides a negative feedback to stabilize I_D



Biassing – Fixing V_G and R_S

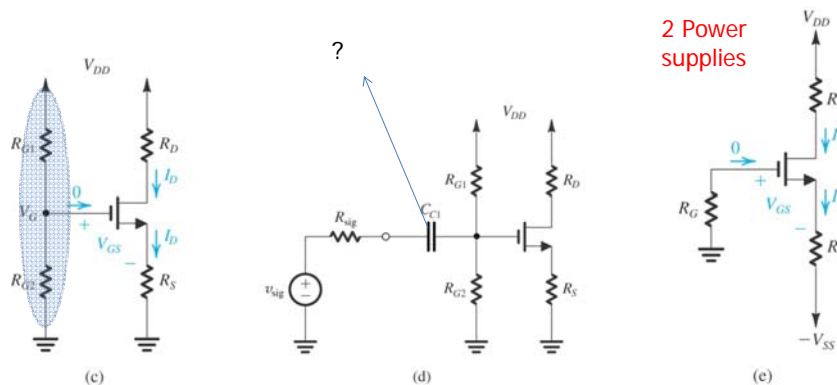
- Uses one power supply
- What is the effect on input resistance when you add v_{gs} signal



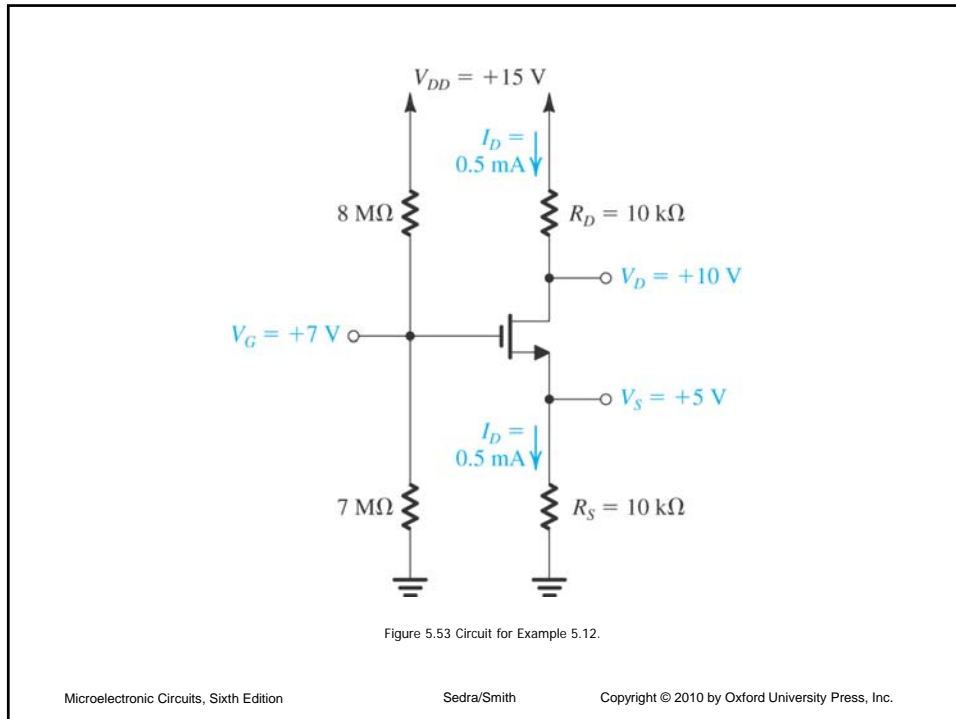

Biasing – D-to-G Resistor

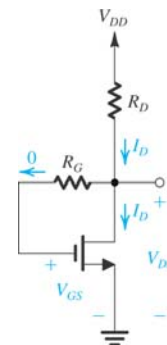- $V_{GS} = V_{DS} = V_{DD} - I_D R_D$
- $V_{DD} = V_{GS} + I_D R_D$
- Provides a feedback resistor to stabilize I_D



Biassing – Constant Current Source

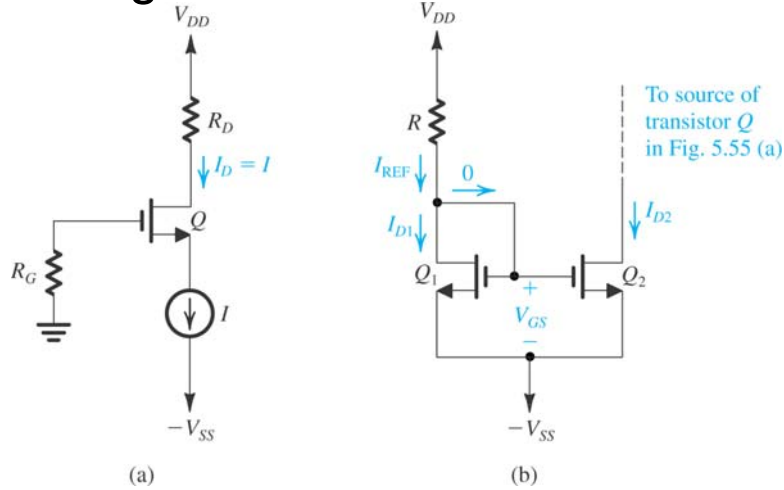


Figure 5.55 (a) Biasing the MOSFET using a constant-current source I . (b) Implementation of the constant-current source I using a current mirror.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Frequency Response

