

Solutions to CSE3201 Assignment 1

1.

Solution in book.

2.

Solution in book.

3.

Solution in book.

4.



$$\begin{aligned}(x+y) \bullet (x+z) &= xx + xz + xy + yz \\&= x + xz + xy + yz \\&= x(1 + z + y) + yz \\&= x \cdot 1 + yz \\&= x + yz\end{aligned}$$

5.

Solution in book

6.

7.

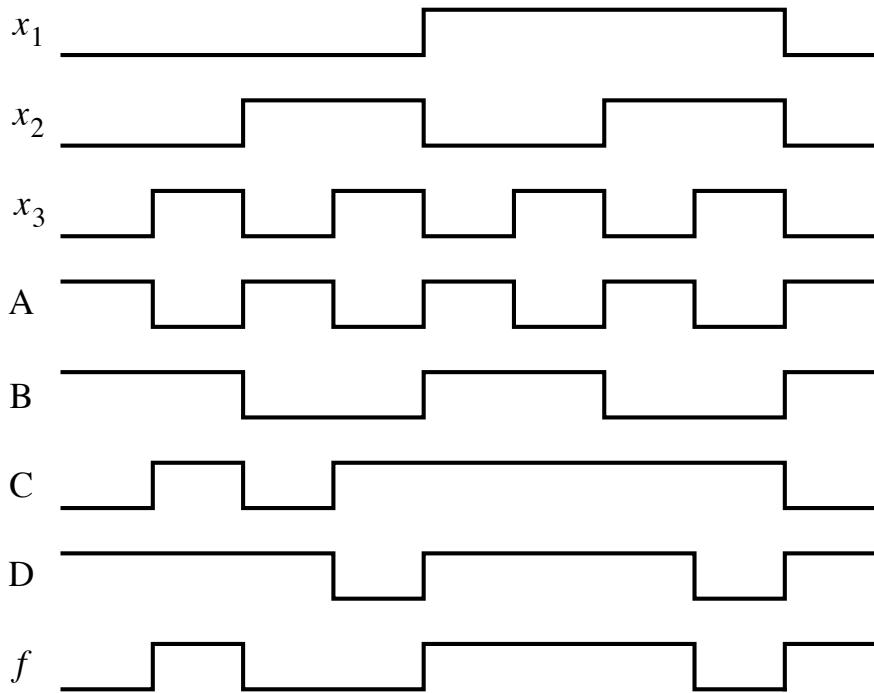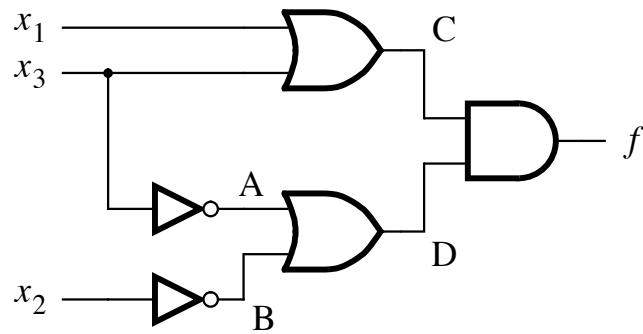

8.

$$\begin{aligned}
 f &= x_1 x_3 + x_1 \bar{x}_2 + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3 \\
 &= x_1 (\bar{x}_2 + x_2) x_3 + x_1 \bar{x}_2 (\bar{x}_3 + x_3) + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3 \\
 &= x_1 \bar{x}_2 x_3 + x_1 x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3 \\
 &= x_1 x_3 + (x_1 + \bar{x}_1) x_2 x_3 + (x_1 + \bar{x}_1) \bar{x}_2 \bar{x}_3 \\
 &= x_1 x_3 + x_2 x_3 + \bar{x}_2 \bar{x}_3
 \end{aligned}$$

9. A CMOS inverter is composed of an NMOS transistor with an equivalent ON resistance of 1 kOhms and a PMOS transistor with an

ON resistance of 1.5 kOhms. The equivalent capacitance of the NMOS transistor at the output of the inverter is 2 fF and for the PMOS transistor it is 2.5 fF. On top of this, the capacitive load being driven by the inverter is 5 fF. What is the rise time delay of the inverter? What is its fall time delay?

10.

$$\begin{aligned}
 f(x_1, x_2, x_3) &= \sum_{m(3,4,6,7)} \\
 &= \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 \bar{x}_3 + x_1 x_2 x_3 \\
 &= (\bar{x}_1 + x_1) x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 \bar{x}_3 \\
 &= x_2 x_3 + x_1 \bar{x}_3 (\bar{x}_2 + x_2) \\
 &\leftarrow x_2 x_3 + x_1 \bar{x}_3
 \end{aligned}$$

11.

12.

$$\begin{aligned}
 f(x_1, x_2, x_3) &= \text{PI M}(0,1,5,7) \\
 &= (x_1 + x_2 + x_3)(x_1 + x_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3) \\
 &= (x_1 + x_2)(x_3 + \bar{x}_3)(x_1 + \bar{x}_3)(x_2 + \bar{x}_2) \\
 &= (x_1 + x_2)(x_1 + \bar{x}_3)
 \end{aligned}$$

13.

14.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$\begin{matrix} 00 & 01 & 11 & 10 \\ \hline 0 & 1 & 1 & 1 \\ 1 & 0 & 1 & 0 \end{matrix}$

$$f = (x_1 + x_2 + x_3)(\bar{x}_1 + x_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + x_3)$$

15.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$\begin{matrix} 00 & 01 & 11 & 10 \\ \hline 0 & 1 & 1 & 1 \\ 1 & 0 & 1 & 0 \end{matrix}$

$x_1 x_2$

$$x_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_3 + \bar{x}_1 \bar{x}_2 + x_2 x_3 = f$$

$$f = \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 x_3$$

- identify which minterms share at least two literals
- and make duplicates of the one linked that shares the most links
(remember) $a = a + a$

$$= \bar{x}_1 x_2 x_3 + x_1 x_2 x_3 + \\ \bar{x}_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 x_3 + \\ \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 x_3 + \\ x_1 \bar{x}_2 \bar{x}_3$$

$$f = x_2 x_3 + \\ \bar{x}_1 x_2 + \\ \bar{x}_1 x_3 + x_1 \bar{x}_2 \bar{x}_3$$

16.

$$f(x_1, x_2, x_3) = \sum_m (1, 4, 7) + D(2, 5)$$

x_1	x_2	x_3	00	01	11	10
0	0	1	0	d		
1	1	d	1	0		

$$\text{SOP: } f = x_1 \bar{x}_2 + x_1 x_3 + \bar{x}_2 x_3$$

$$\text{POS: } f = (x_1 + x_3)(x_1 + \bar{x}_2)(\bar{x}_2 + x_3)$$

17.

x_1x_2	x_3x_4	00	01	11	10
00		0	0	0	0
01		0	0	1	0
11		0	1	1	1
10		0	0	1	0

$$f = x_1x_2x_4' + x_1x_2x_3 + x_2x_3x_4 + x_1x_3x_4$$

18.

19.

```
module prob2_46 (x1, x2, x3, f);
    input x1, x2, x3;
    output f;

    not (notx1, x1);
    not (notx2, x2);
    not (notx3, x3);
    and (a, notx1, notx2, x3);
    and (b, notx1, x2, notx3);
    and (c, x1, notx2, notx3);
    and (d, x1, x2, x3);
    or (f, a, b, c, d);

endmodule
```

20.