

ENG2210

Electronic Circuits

Mokhtar A. Aboelaze
York University



Chapter 2 Operational Amplifiers

- Objectives
- Learn the terminal characteristics of the op amp
- Learn how to analyze circuits containing op amps
- Learn how to design amplifiers having precise characteristics
- How to design circuits (summing, integrator, differentiator, ..)
- Nonideal characteristics of the op amps and how these limits affect performance



Introduction

- Very cheap
- Versatile, could be used to design many circuits
- Actual op amps have characteristics that are very close to the ideal one.
- Consists of many transistors, but we will not into the details of how it is made.
- Direct Coupled Amplifiers ?

Introduction

  


  - 2 inputs one output
- Amplify difference of inputs
- V_{CC} and V_{EE} are typically 12 V




The inverting Configuration

 - Input signal is connected to the inverted input
- Feedback resistor from output to inverted input
- Non-inverted input grounded




The Inverting Configuration

 

The Effect of Finite Open-Loop Gain

 
- What if A is finite
- Redo the last example assuming that A is finite




Input Resistance

- The input resistance of the inverting configuration is R_1
- R_1 must be very large (the input signals divided by R_1 and output resistance of the source)
- If R_1 is high, and we want a high gain, then R_2 may be impractically high

Example

 


Weighted Summer

 


$$v_O = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$

Weighted Summer

 

The Noninverting Configuration

 


Exercise: Repeat if the gain is not infinite


Input and Output Resistance

- No current flows into the +ve input of the op amp, input resistance is infinite
- Output resistance is zero

Voltage Follower

 - Unity gain – Buffer Amplifier
- Infinite input R, and zero output R



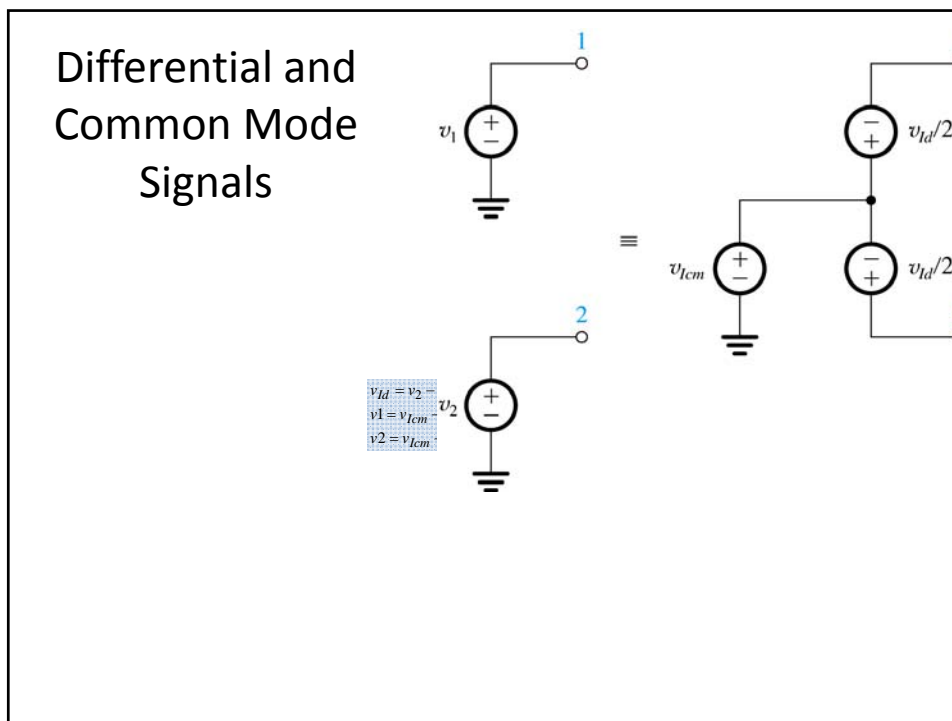

Difference Amplifiers


- Amplify the difference between the 2 signals and rejects signals that are common to both inputs. Ideally,
- $v_o = A_d v_{Id} + A_{cm} v_{Icm}$
- A_d is the differential gain, A_{cm} is the common gain
- Because of the very high gain, we can not use the opamp as a difference amplifier
- Common mode rejection ration CMRR

$$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|}$$

Difference Amplifiers

- The gain for the inverting mode is $-R_2/R_1$
- For the noninverting $1+R_2/R_1$
- We can combine these together, but we have to attenuate the noninverting input for the to make it equal in magnitude to the inverting input.


Difference Amplifier

 

Attenuated by $R_3 || R_4$


Difference Amplifiers

- Using Superposition

 


Input Resistance

 - $R_{id} = 2R_1$
- For large gain (R_2/R_1) R_1 is small (relatively)
- Instrumentation Amplifier solves this




Instrumentation Amplifier

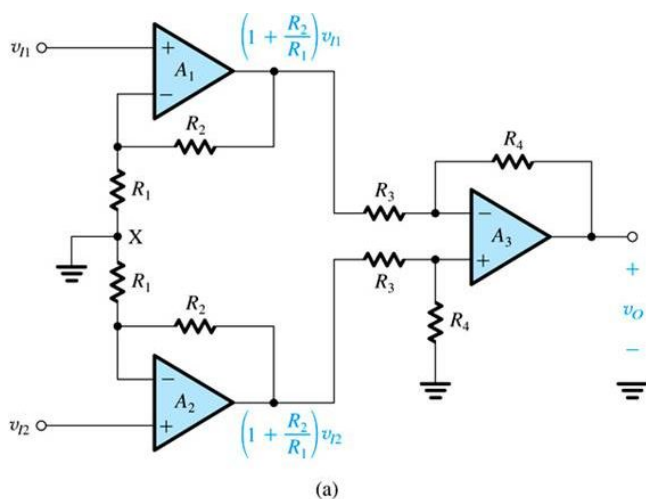- The problem with the difference amplifier is low input resistance.
- We can use a voltage follower to buffer the 2 inputs thus solving this problem.
- We can also get some voltage gain from these 2 extra op amps.





What is a mismatch between the 2 R_2 's or R_1 's

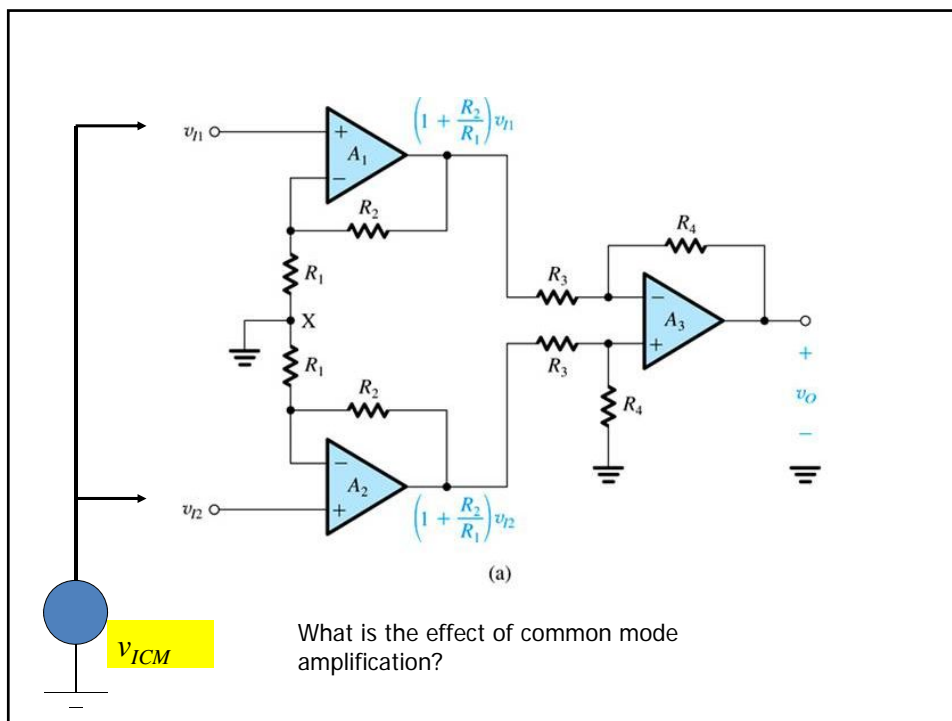
$$A_d = \left(\frac{R_4}{R_3} \right) \left(1 + \frac{R_2}{R_1} \right)$$



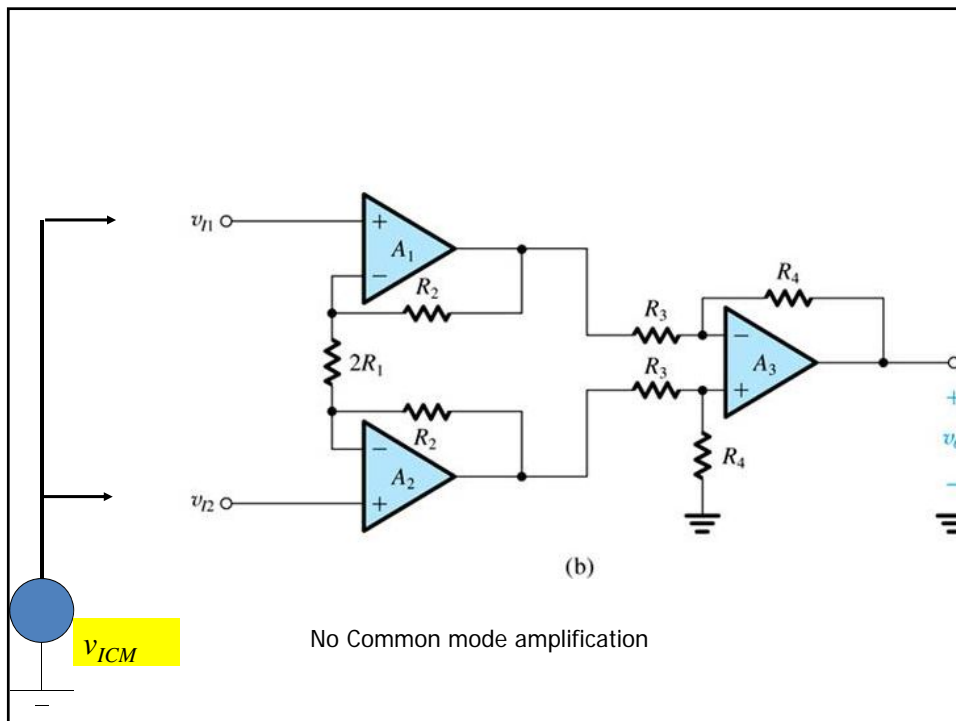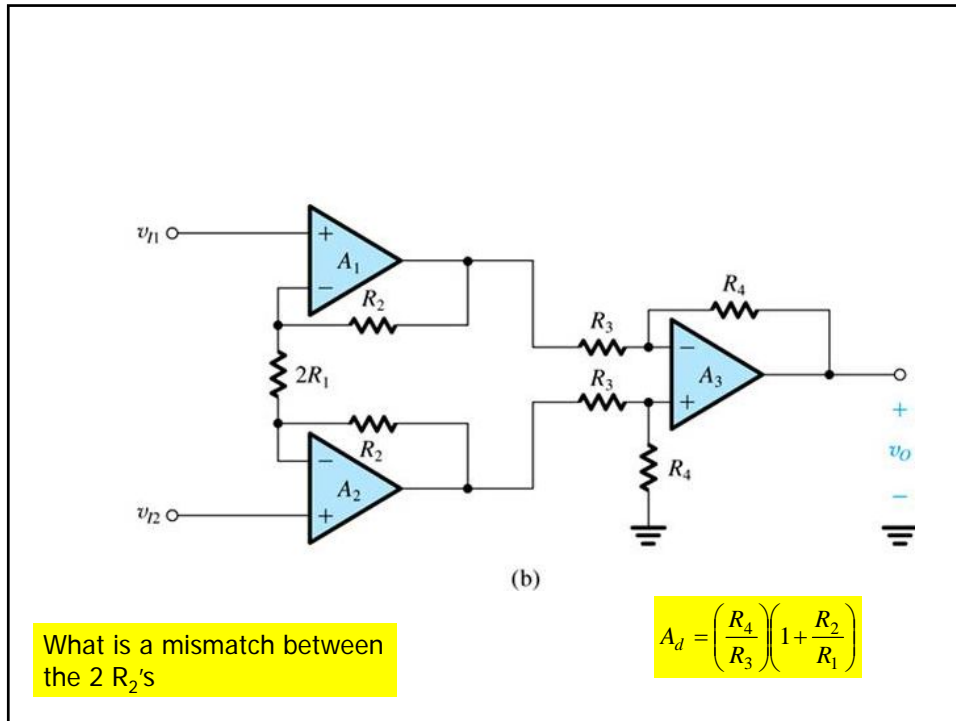Problems

- The input common mode is amplified by the first stage, and need to be dealt with in the second (higher CMRR).
- The two amplifiers channels in the first stage have to be perfectly matched.
- To vary the differential gain, 2 resistors must be varied simultaneously.



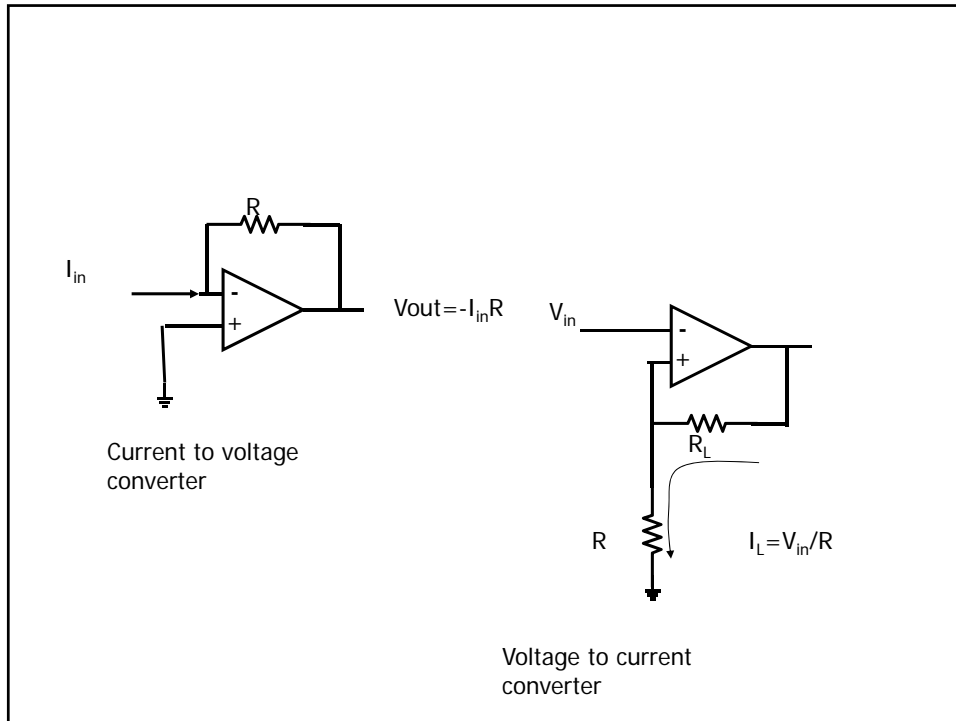


Integrator

- Consider the following circuit.

$$v_o = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau - V_0$$

$$\frac{V_o}{V_i} = -\frac{1}{sCR}$$
 
$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega CR}$$




Integrator

$$v_o = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau - V_0$$

$$\frac{V_o}{V_i} = -\frac{1}{sCR}$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega CR}$$


Some problems,
what is the gain at
DC?


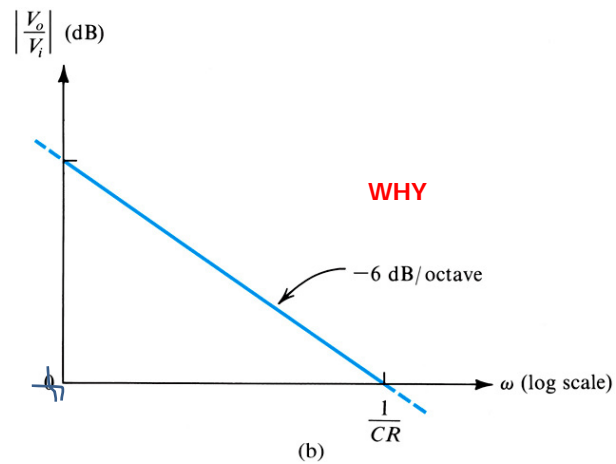


Integrator

$$\frac{V_o}{V_i} = -\frac{R_F/R}{1 + sCR_2}$$
 
$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_F}{R} \frac{1}{1 + j\omega CR_F}$$



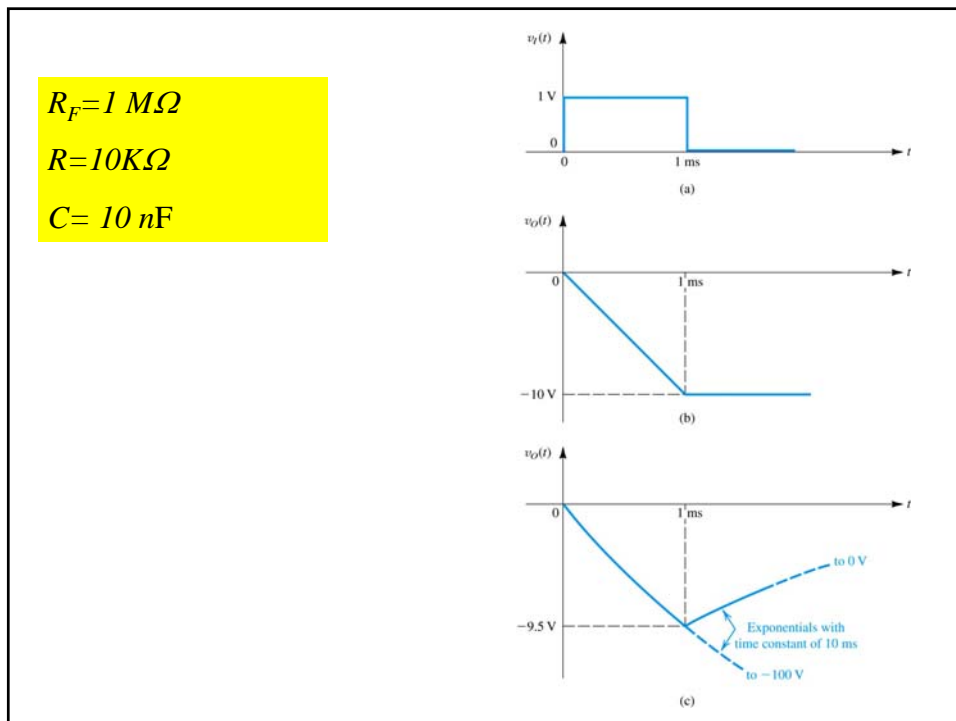 



Differentiator

- An ideal differentiator

$$i(t) = C \frac{dv_i(t)}{dt}$$

$$v_o(t) = -CR \frac{dv_i(t)}{dt}$$

$$\frac{V_o}{V_i} = -sCR$$

  

$$v_o = -CR \frac{dv_i(t)}{dt}$$

$$\frac{V_o}{V_i} = -sCR$$



$$\frac{V_o(j\omega)}{V_i(j\omega)} = -j\omega RC$$

DC Imperfections

- Thus far, we considered the opamp to be ideal (except for finite A).
- In reality, we have to consider the effect of these *non-ideal* behavior of the opamp
- We will discuss FEW of these imperfections



Offset Voltage

  - If the 2 terminals are connected to ground, the output should be 0.
- Can be represented as the shown circuit.
- Due to mismatches in the input differential stage
- Data sheet specify V_{OS} but not its polarity
- Also, changes with temperature ($\mu\text{V}/^\circ\text{C}$)





Offset Voltage

  - V_o is not zero.
- The actual signal is superimposed in V_o .
- Limits the voltage swing.
- If amplifying DC even worse.
- Some opamps have 2 terminals for compensation.
- Still the problem of temp variation




Offset Voltage

  - We can use capacitive coupling.
- O.K. if we are not dealing with DC or low frequency.
- At DC gain is 1 (not $1 + R_2/R_1$).
- At high frequency (high pass filter)




Input Bias and Offset Currents

 - The opamp needs an input current to operate.
- Datasheet usually specify average value (input bias current) and the difference (input offset current).
- What is V_o ?




Input Bias and Offset Currents

 - We can reduce the output DC voltage due to input bias current.
- R_3 has a negligible effect from the signal point of view.




Input Bias and Offset Currents

 - Always provide a dc path from each of the inputs to the ground




Effect of V_{OS} and I_{OS}

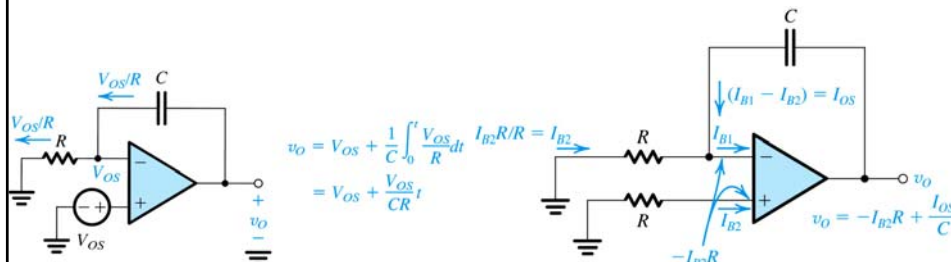- The effect of V_{OS} and I_{OS} result in charging the capacitor and saturating the output
- Consider a shunt R with the C
- Although R is used to keep I_B from flowing into C , but not I_{OS}



Finite Open Loop gain and B.W.

 - The differential open loop gain is finite and decreases with frequency.
- If internally compensated, it behaves like a single time constant LPF



$$A(S) = \frac{A_0}{1 + \frac{s}{\omega_b}}$$

Finite Open Loop Gain

$$A(S) = \frac{A_0}{1 + s / \omega_b}$$

$$A(j\omega) = \frac{A_0}{1 + j\omega / \omega_b}$$

$$A(j\omega) = \frac{A_0 \omega_b}{j\omega} \quad \omega \gg \omega_b$$

$$|A(j\omega)| = \frac{A_0 \omega_b}{\omega}$$

$$\omega_t = A_0 \omega_b$$

Unity-gain BW or Gain BW product

Closed Loop Gain

$$\frac{V_0(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + (1 + R_2/R_1)/A}$$

$$\frac{V_0(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + (1 + R_2/R_1)/(A_0/(1 + s/w_b))}$$

$$A \gg R_2/R_1$$

$$\frac{V_0(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + \frac{s}{\omega_t/(1 + R_2/R_1)}}$$


STC LPF with gain R_2/R_1
 $\omega_{3dB} = \omega_t/(1 + R_2/R_1)$

Closed Loop Gain non-inverting

This is equivalent to an STC LPF with a DC gain of $(1 + R_2/R_1)$ and a 3dB frequency of

$$\frac{V_0(s)}{V_i(s)} = \frac{1 + R_2/R_1}{1 + \frac{s}{\omega_t/(1 + R_2/R_1)}}$$
 
$$\omega_{3dB} = \omega_t / \left(1 + \frac{R_2}{R_1}\right)$$



Large Signal Operation

- The output of the opamp saturates at **rated output voltage** (+- 13)
- Also, there is a limit on the output current (datasheet). The opamp can not supply more than the output current limit. If this is the case, the voltage saturates at the limit.

Slew Rate

- The output can not change with a rate greater than the slew rate.
- The slew rate is specified in the datasheet in $V/\mu s$

