

ENG2210

Electronic Circuits


Mokhtar A. Aboelaze
York University

Chapter 3 Diodes


- **Objectives**
- Learn the characteristics of ideal diode and how to analyze and design circuits containing multiple diodes
- Learn the i - v characteristic of the junction diode
- Learn a simple model of the diode
- Learn the use of diodes operating in the forward and reverse bias region to provide constant dc voltage.
- Learn application of the diode in the design of rectifier circuits.



Atoms


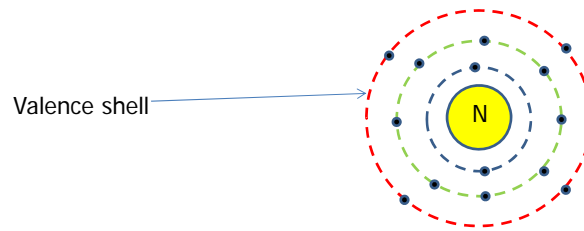
- Atoms consists of a positively charged nucleus and a number of negatively charged electrons rotating around the nucleus.
- Electrons are arranged in shells
- The electrons in the outer shell (<8) are called *valence electrons*.



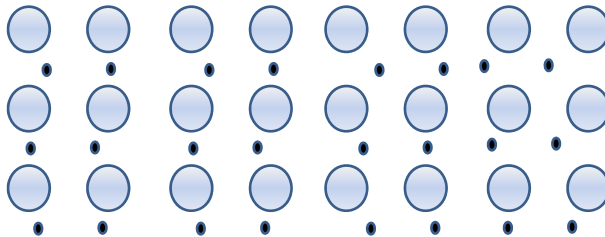- Conductors: The valence electrons are free to move around.
- When applying an electric field, these electrons starts to move in the opposite direction of the filed (current).



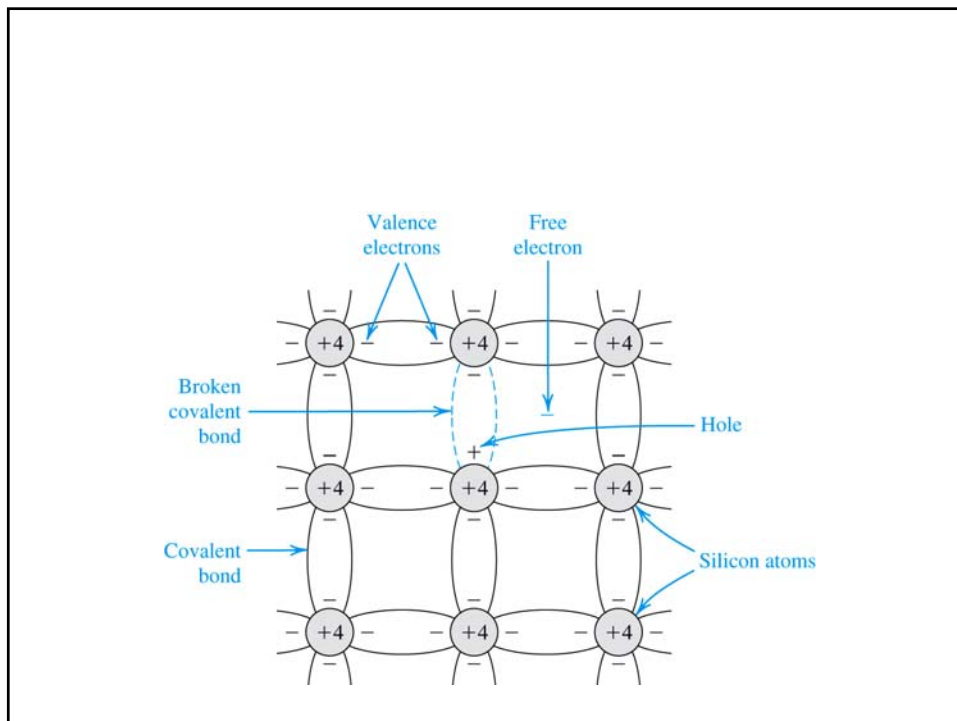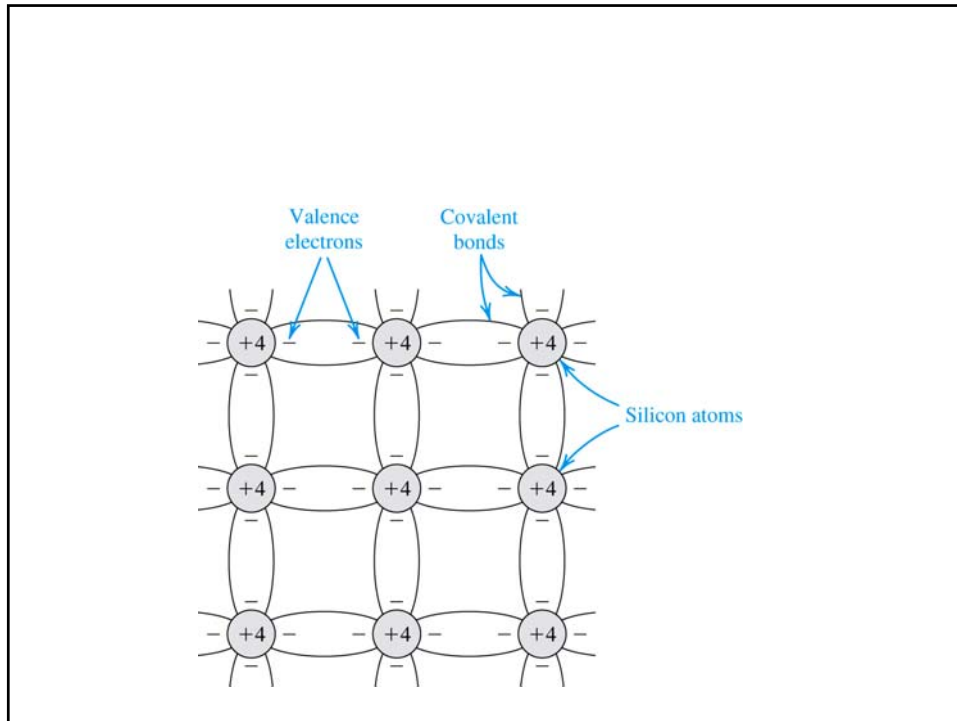

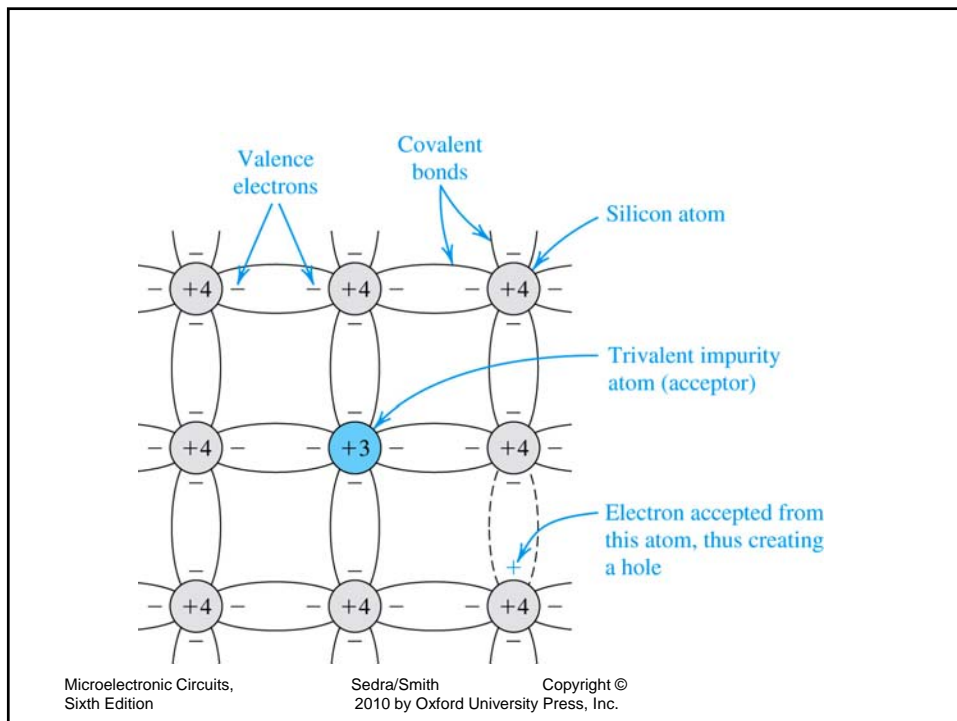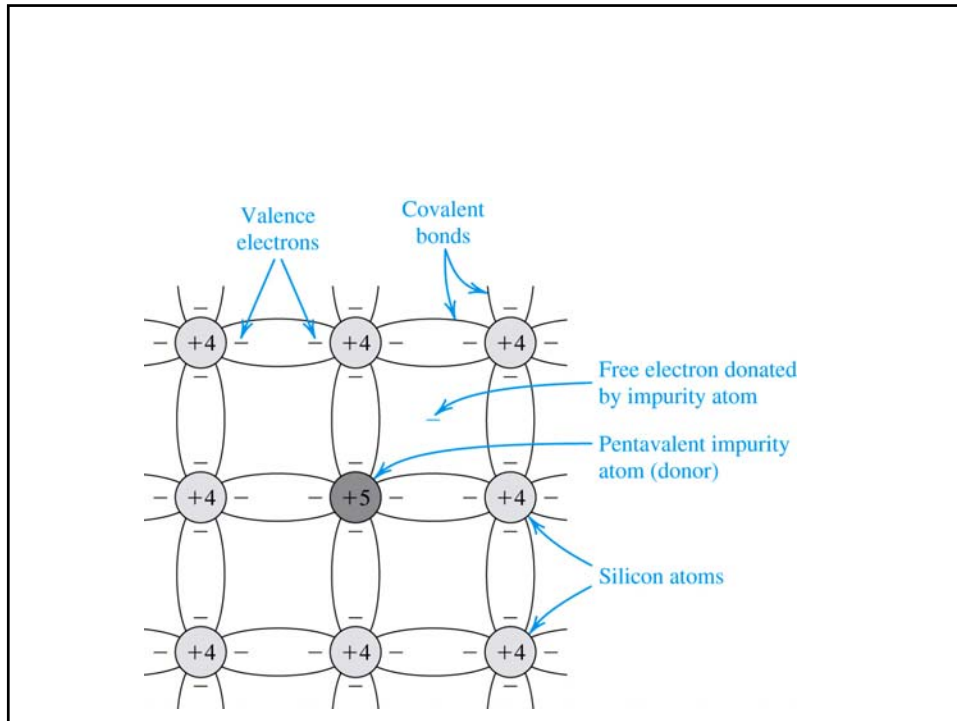

Microelectronic Circuits,
Sixth Edition

Sedra/Smith
2010 by Oxford University Press, Inc.

Copyright ©



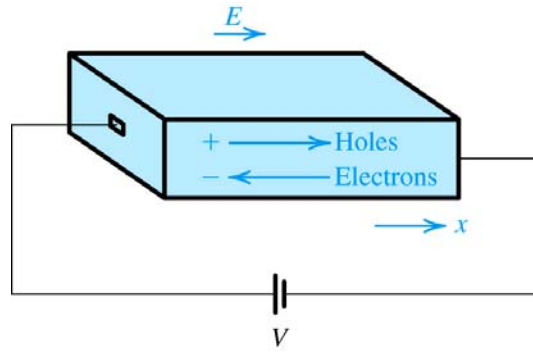



Figure 3.5 An electric field E established in a bar of silicon causes the holes to drift in the direction of E and the free electrons to drift in the opposite direction. Both the hole and electron drift currents are in the direction of E .

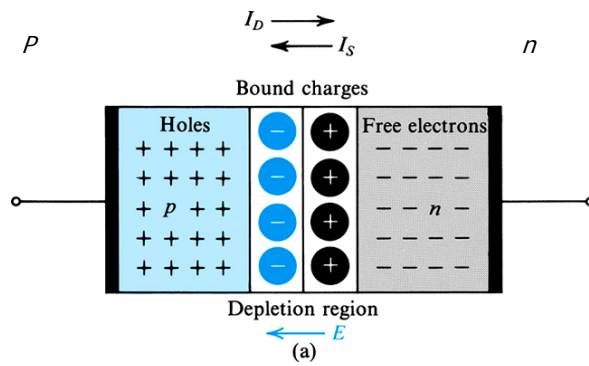

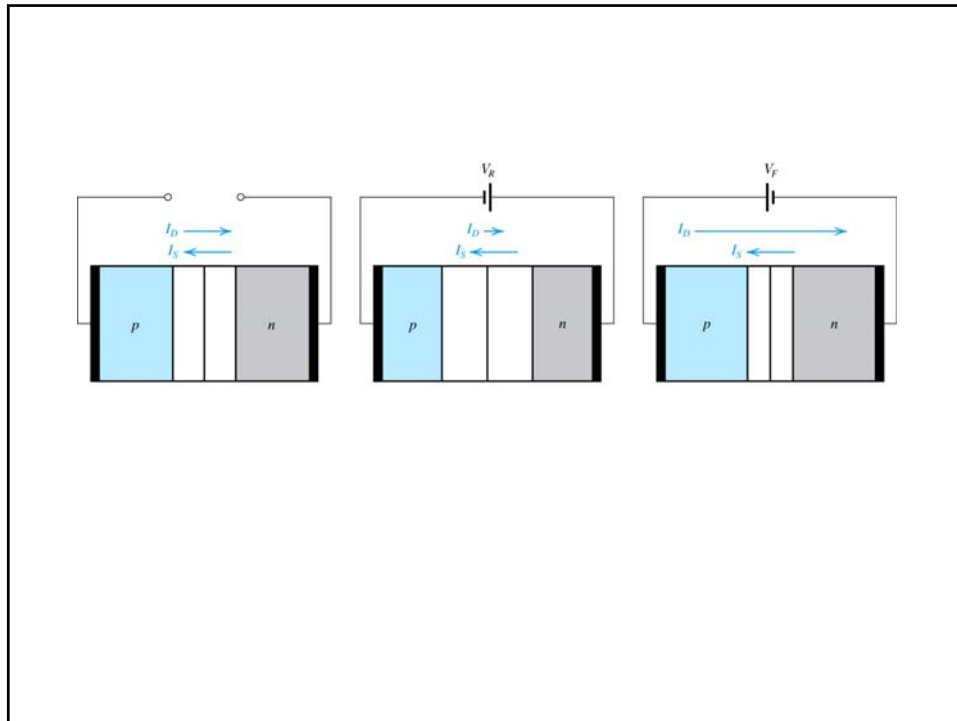


The Ideal Diode

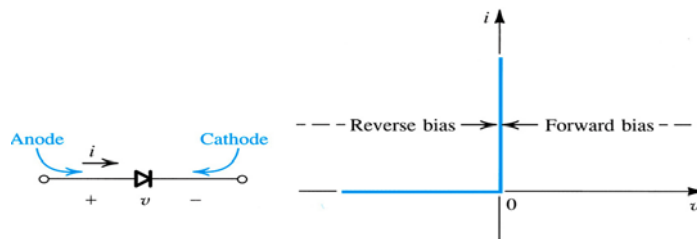- So far, we are dealing with linear elements.
- An ideal diode allows current to flow in only one direction, it has a resistance of ∞ in the other direction.
- Short circuit in one direction, and open circuit in the other direction




Ideal Diode

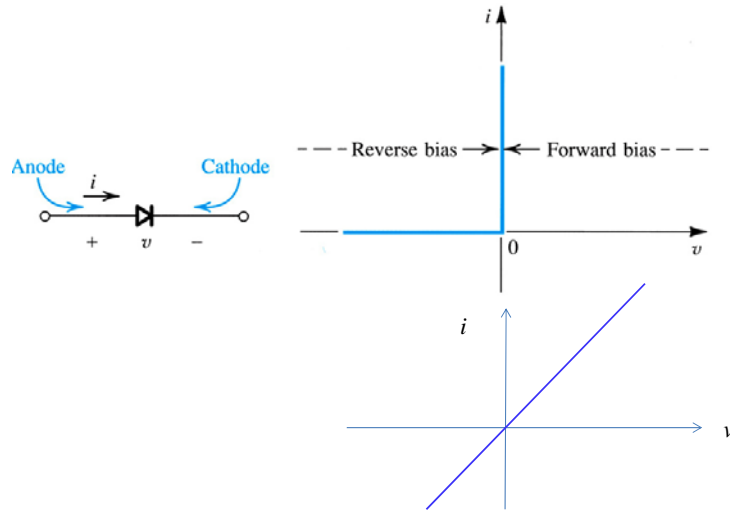


Diodes

- Conducts or not (ON or OFF) based on the relative polarity. Voltage drop across diode not voltage values.

Reverse biased

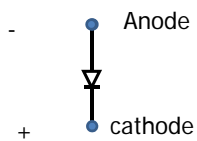


Forward biased

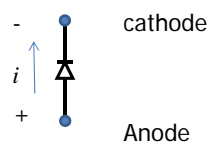


The Ideal Diode

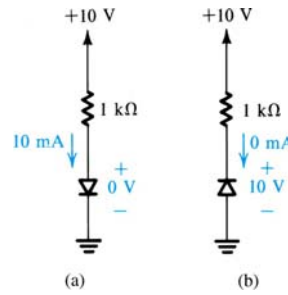- Forward biased $R=0$
- Reverse biased $R=\infty$




Rectifier

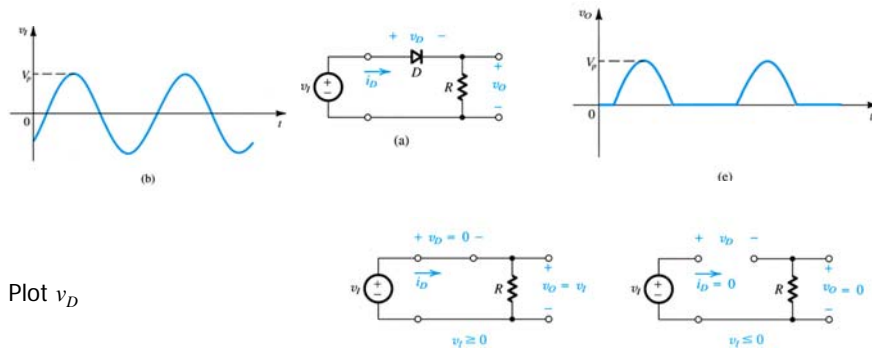- A fundamental application of the diode is the rectifier.




Charger

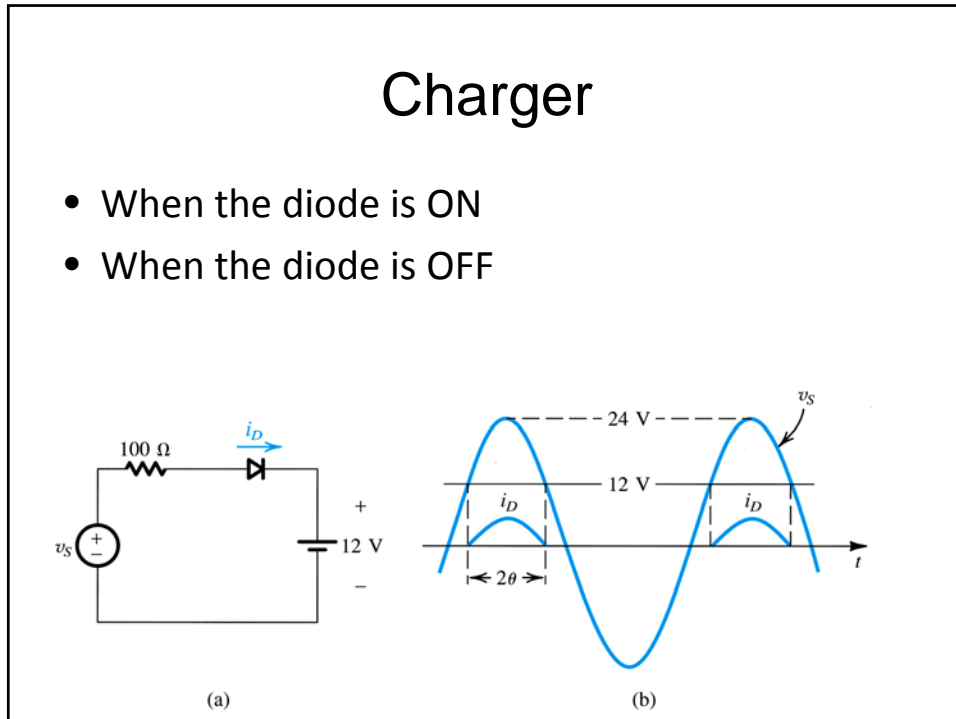- When the diode is ON
- When the diode is OFF




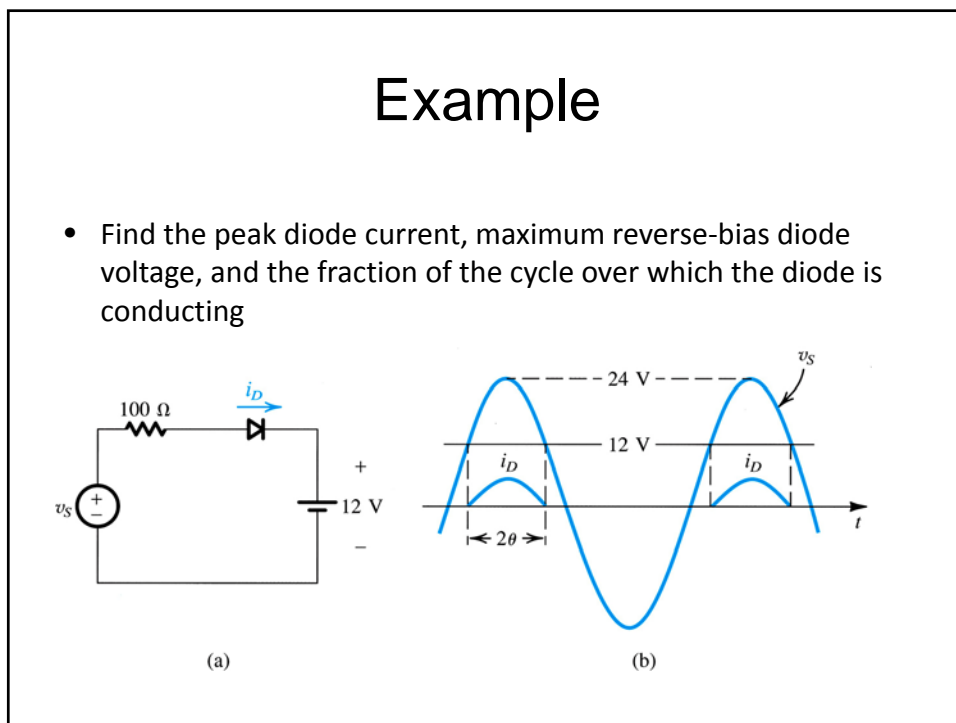Example

- Find the peak diode current, maximum reverse-bias diode voltage, and the fraction of the cycle over which the diode is conducting




Logic Gates

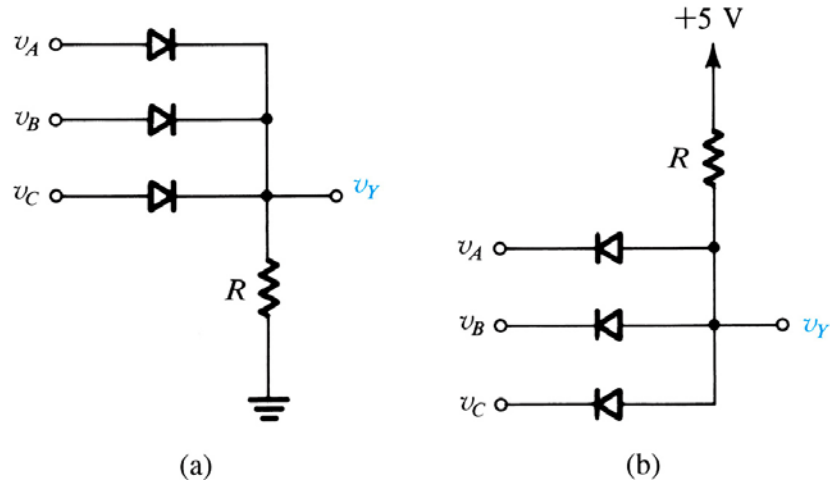

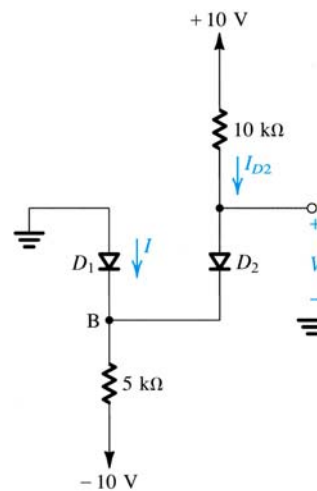
Example

- Make an assumption, then validate your assumption
- Both are ON
- $V_B = 0 = V$
- $I_{D2} = (10 - 0) / 10\text{K} = 1\text{mA}$
- $1\text{mA} + I = (0 - (-10)) / 5\text{k}$
- $I = 1\text{mA}$
- Assumption is O.K.



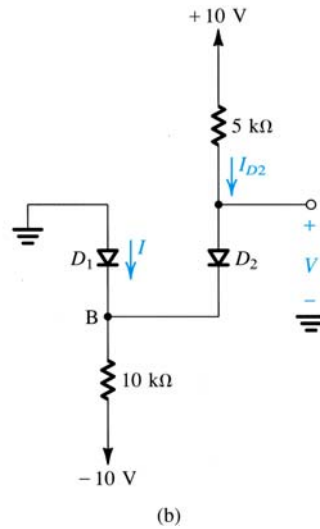Example

- Assume both ON
- $V_B = 0 = V$
- $I_{D2} = (10 - 0) / 5k = 2\text{mA}$
- $I_{D2} + I = (0 - -10) / 5 = 2\text{ mA}$
- $2 + I = 10 / 10K = 1\text{mA}$
- $I = -1\text{ mA}$
- D1 is not ON, invalid assumption
- Try it for D1 OFF



Terminal Characteristics

Changes with temp

Sometimes v/nV_T


$$i = I_s (e^{v/V_T} - 1)$$

I_s Saturation current

$$V_T = \frac{KT}{q} \text{ Thermal voltage}$$

if $v \gg V_T$, $i = I_s e^{v/V_T}$

$$v = V_T \ln \frac{i}{I_s}$$

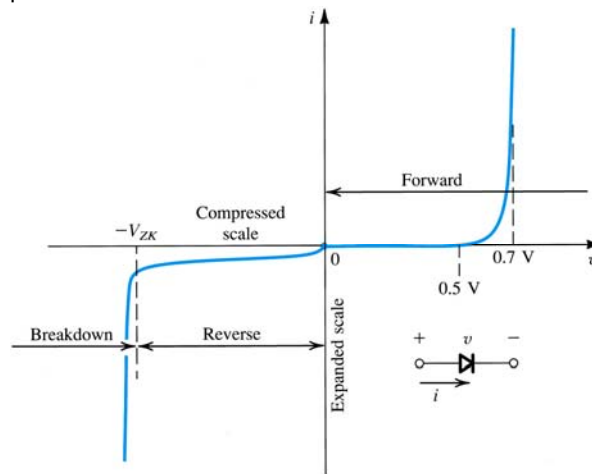

At room temperature, $V_T = 25.3\text{ mV}$

Compare this to an ideal diode

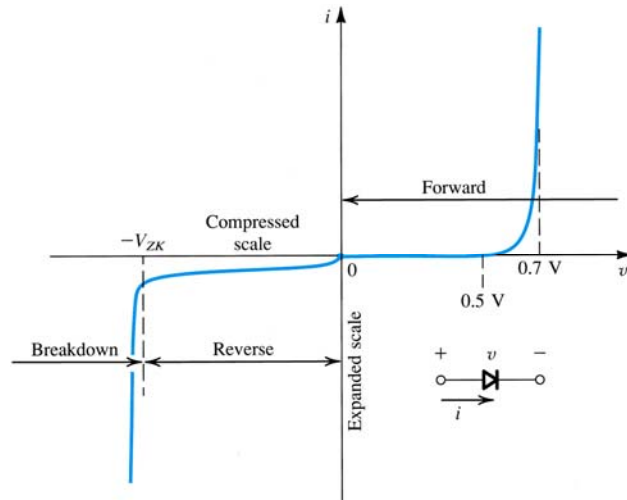


Figure 4.8 The diode $i-v$ relationship with some scales expanded and others compressed in order to reveal details.

Microelectronic Circuits,
Sixth Edition

Sedra/Smith Copyright ©
2010 by Oxford University Press, Inc.


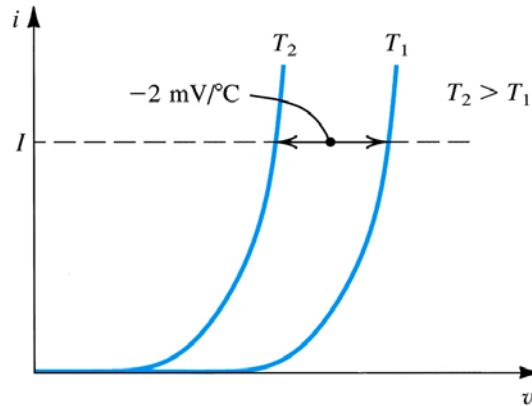
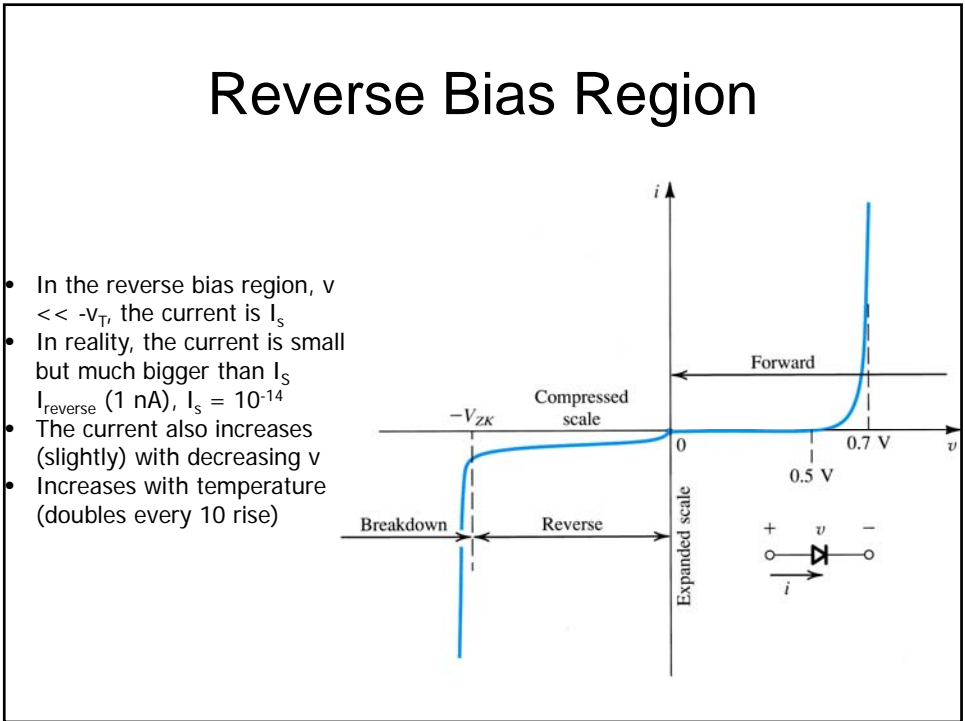


Figure 4.9 Temperature dependence of the diode forward characteristic. At a constant current, the voltage drop decreases by approximately 2 mV for every 1°C increase in temperature.


Microelectronic Circuits,
Sixth Edition

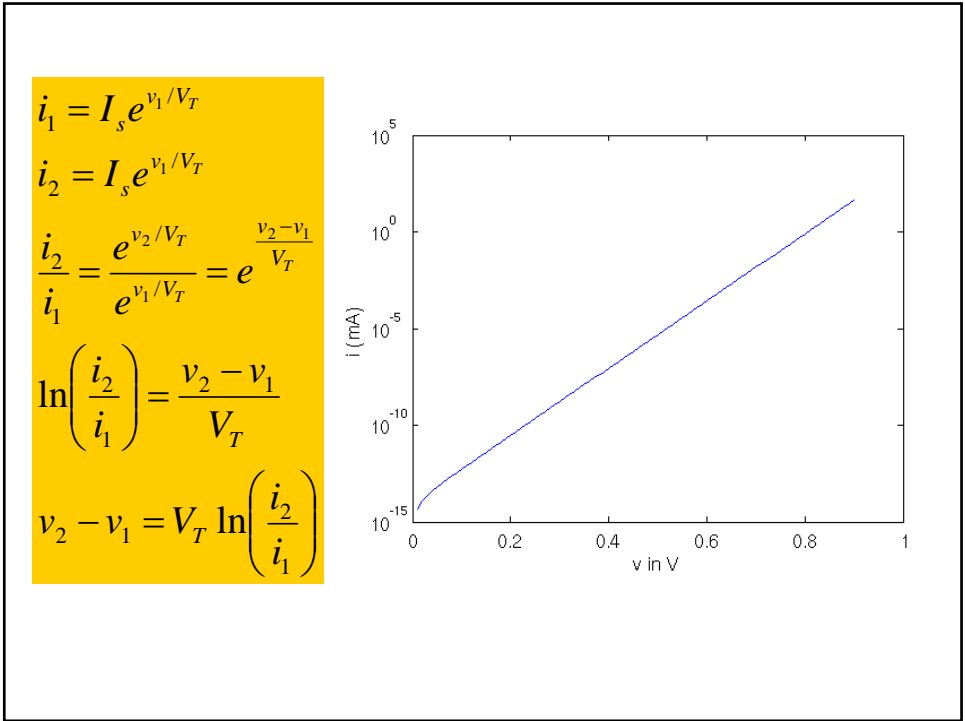Sedra/Smith Copyright ©
2010 by Oxford University Press, Inc.




The Breakdown Region

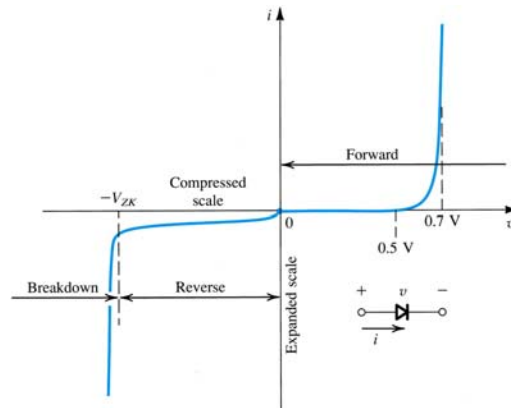- The current I increases rapidly with almost no change in voltage drop
- It is normally not destructive if the power dissipation is limited
- This is useful for voltage regulation




Diode Models

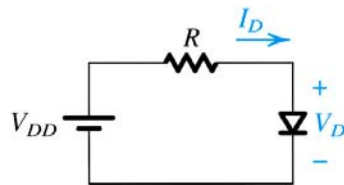- Diode can be modeled in different ways depends on the application (and the required accuracy).
 - Exponential model
 - Constant voltage drop model
 - Ideal diode model
 - Piecewise Linear Model
 - Small signal model



The exponential Model

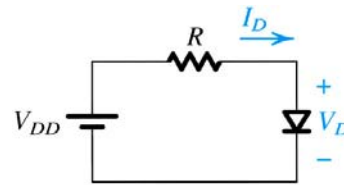- Most accurate, but highly nonlinear
- Assume diode voltage greater than 0.5V
- The diode current is $I_D = I_S e^{V_D/V_T}$
- Also, the diode current is $I_D = \frac{V_{DD} - V_D}{R}$
- Solve these 2 equations



Microelectronic Circuits,
Sixth Edition

Sedra/Smith
2010 by Oxford University Press, Inc.

Copyright ©

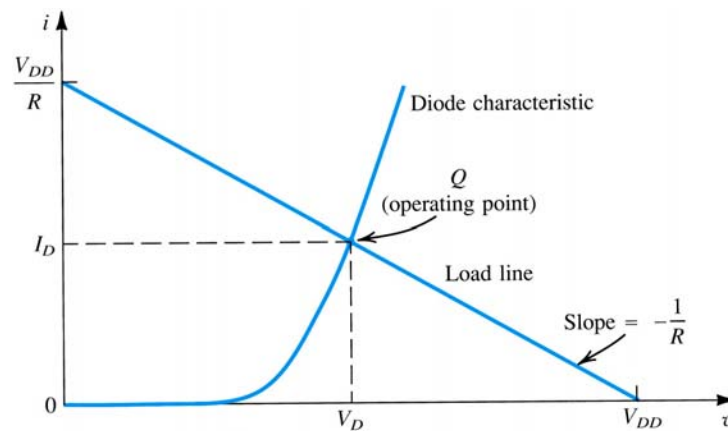


Figure 4.11 Graphical analysis of the circuit in Fig. 4.10 using the exponential diode model.


Microelectronic Circuits,
Sixth Edition

Sedra/Smith
2010 by Oxford University Press, Inc.

Copyright ©


Constant Voltage Drop Model

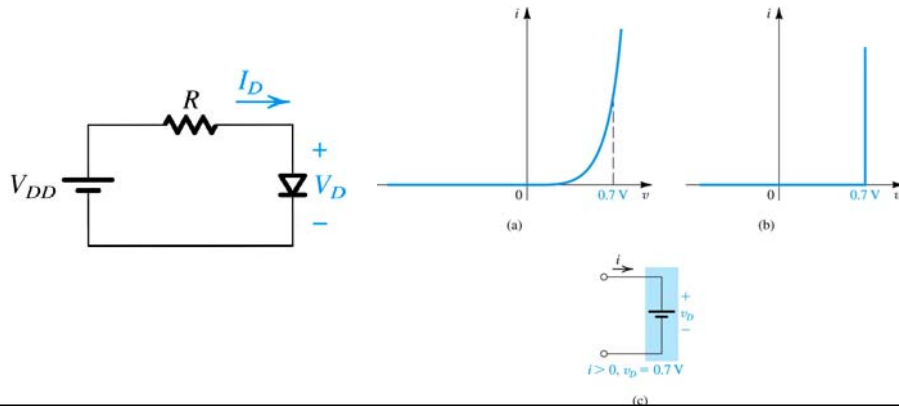- Assume that if the diode is ON, it has a constant voltage drop (0.7V)




Piecewise Linear Model

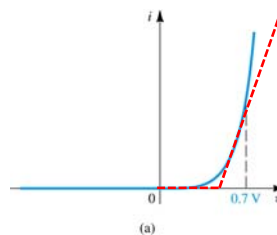- Constant voltage up to $\sim 0.5\text{V}$ then resistor




Ideal Diode Model

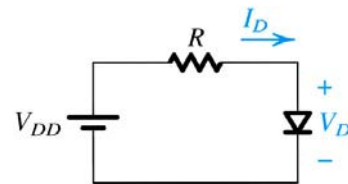- Similar to constant voltage drop, but the voltage drop is 0 V



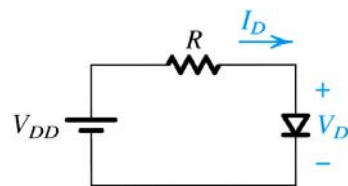Find I_D and V_D for $V_{DD} = 5V$, $R=1K\Omega$
Assume 0.7 V at 1-mA Use iteration



Design a circuit to provide output voltage of 2.4V
(0.7 V at 1 mA)


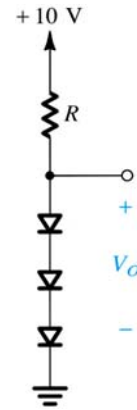


Figure E4.11


Microelectronic Circuits,
Sixth Edition

Sedra/Smith Copyright ©
2010 by Oxford University Press, Inc.

Small Signal Model

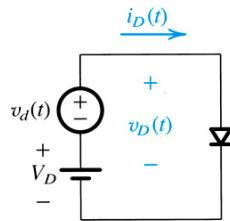

(a)

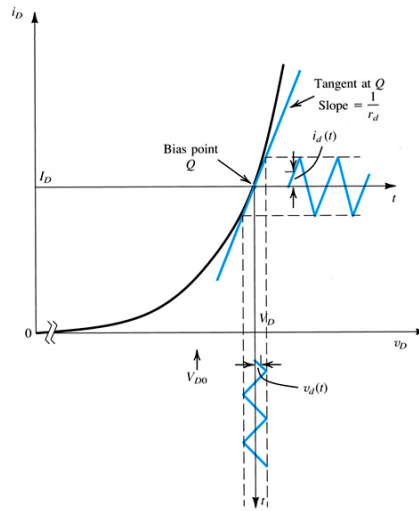

(b)

Microelectronic Circuits,
Sixth Edition

Sedra/Smith Copyright ©
2010 by Oxford University Press, Inc.

Solve

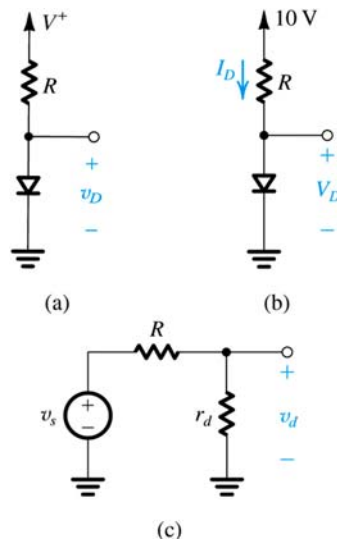


Figure 4.14 (a) Circuit for Example 4.5. (b) Circuit for calculating the dc operating point. (c) Small-signal equivalent circuit.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Voltage Regulator (forward bias)

- A voltage regulator is a circuit that provides a constant DC voltage even with the changes of the load resistance or the source resistance.
- Since the diode in the forward bias region have a constant voltage with relatively large changes in current, it could be used as a voltage regulator

Solve

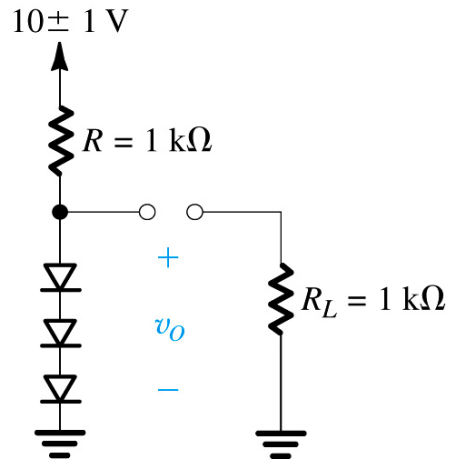


Figure 4.15 Circuit for Example 4.6.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Solve

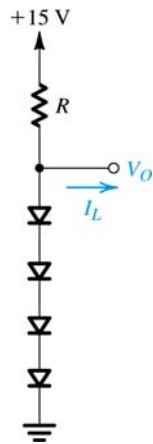


Figure E4.15


Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.


Zener Diode

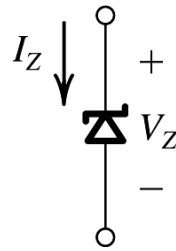- Diodes that are designed to operate in the reverse breakdown region.
- Used for low current regulators (although regulators chips are widely used now).




Zener diodes

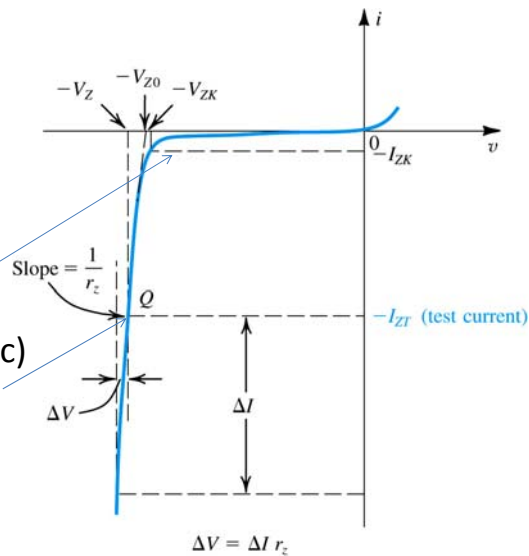- Characterized by
 - V_Z at a specified test current I_{ZT}
 - Maximum power
 - Knee current I_{KZ}
 - Incremental (dynamic) resistance $r_z = \Delta V / \Delta I$



Zener Diodes

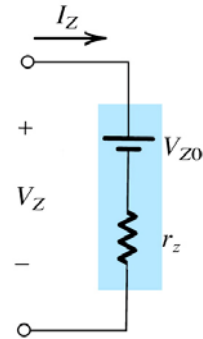- Equivalent circuit
- V_{Z0} in practice is the same as the knee voltage




Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Assume a 6.8-V Zener diode with $V_Z = 6.8$ at $I_Z = 5\text{mA}$, $r_z = 20\ \Omega$, $I_{ZK} = 0.2\ \text{mA}$, $V^+ = 10\text{V} \pm 1\text{V}$

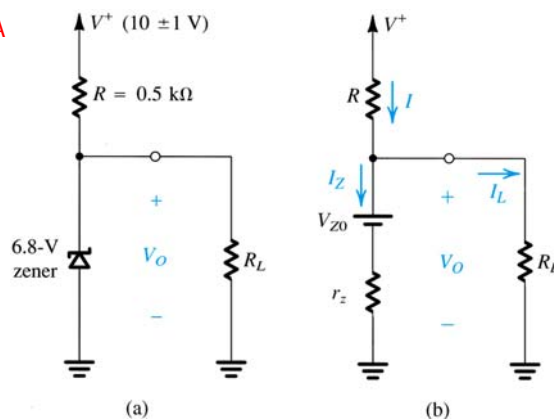- Find V_O and the line regulation at no load
- Find the load regulation when the load current is 1mA
- Find V_O for $R = 2\ \text{k}\Omega$, $0.5\ \text{k}\Omega$
- Find the minimum load for the diode to operate in the breakdown region



Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Changing amplitude and **Electrical isolation**

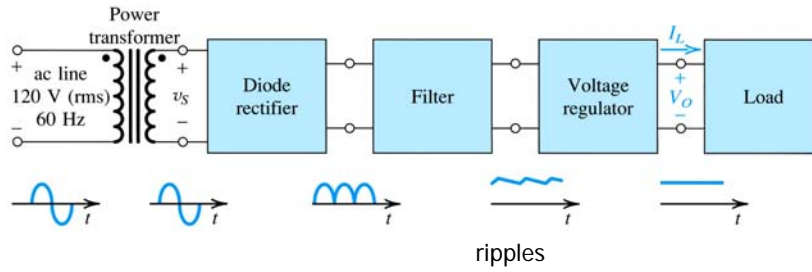


Figure 4.20 Block diagram of a dc power supply.


Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Half-Wave Rectifier

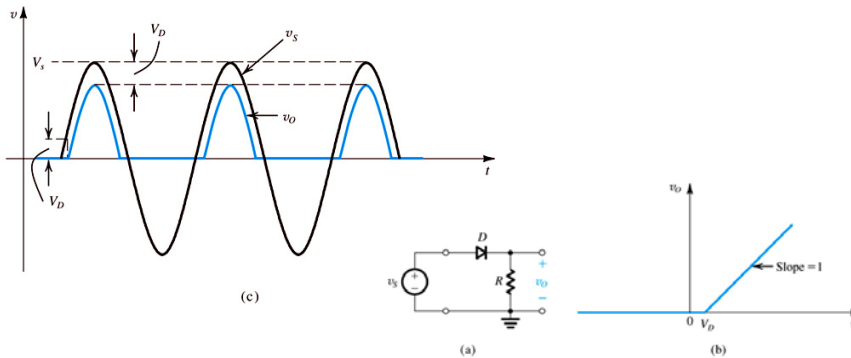- Removes the negative voltage half cycle
- Peak inverse voltage < breakdown voltage





Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Full-Wave Rectifier

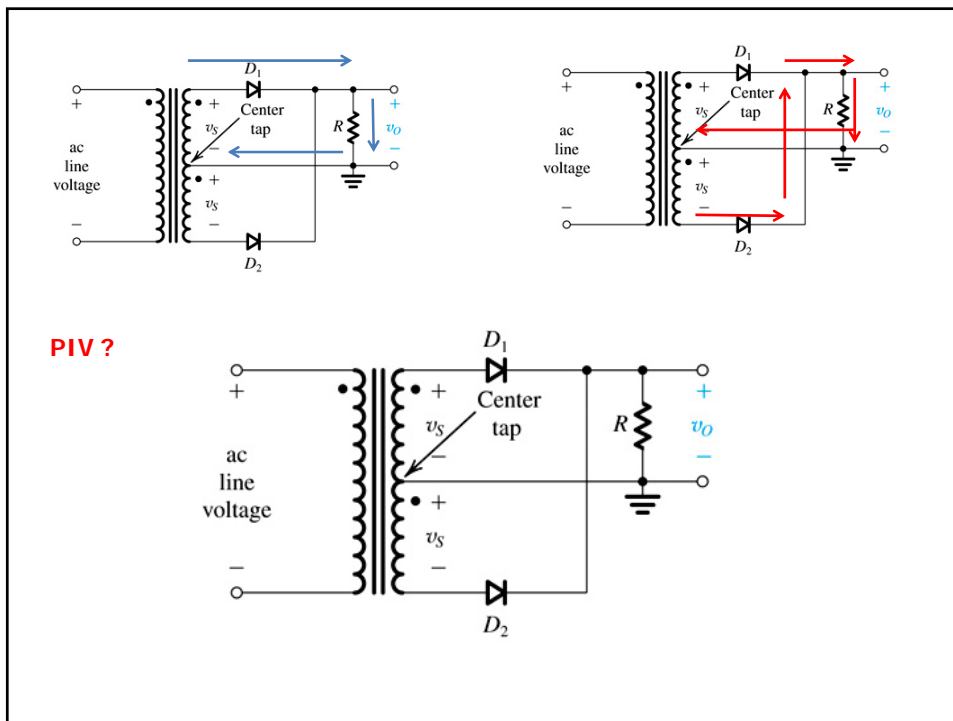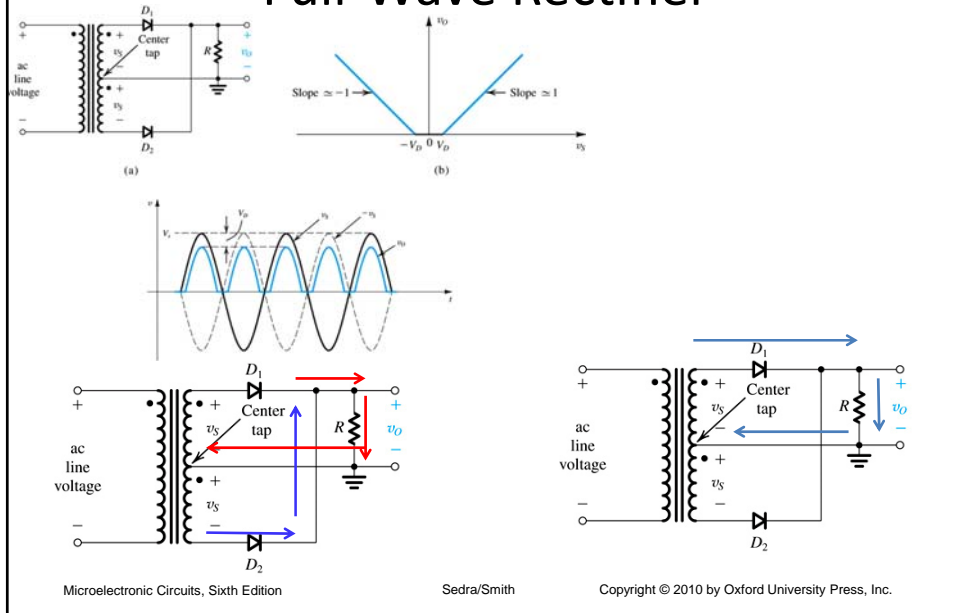

Bridge Rectifier

PIV ?

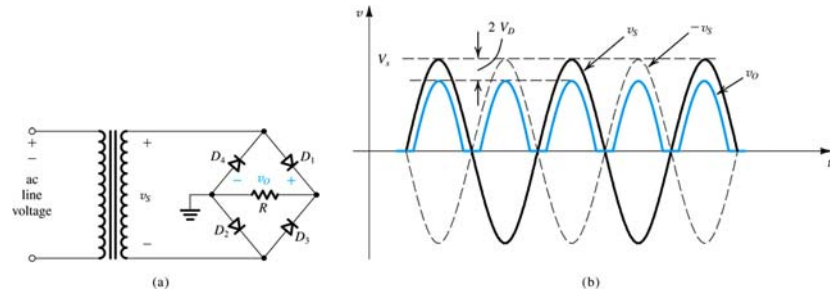


Figure 4.23 The bridge rectifier: (a) circuit; (b) input and output waveforms.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.


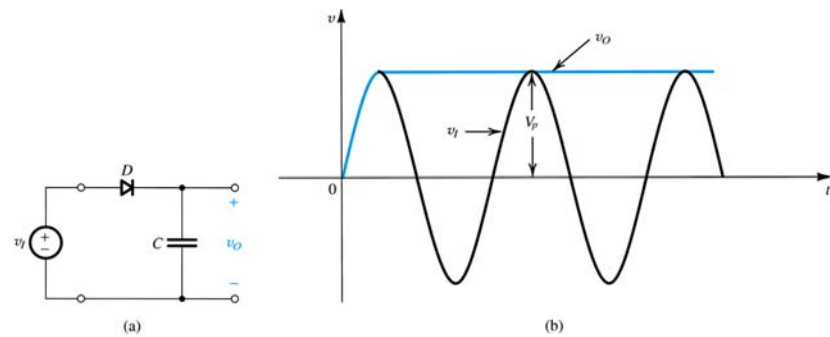
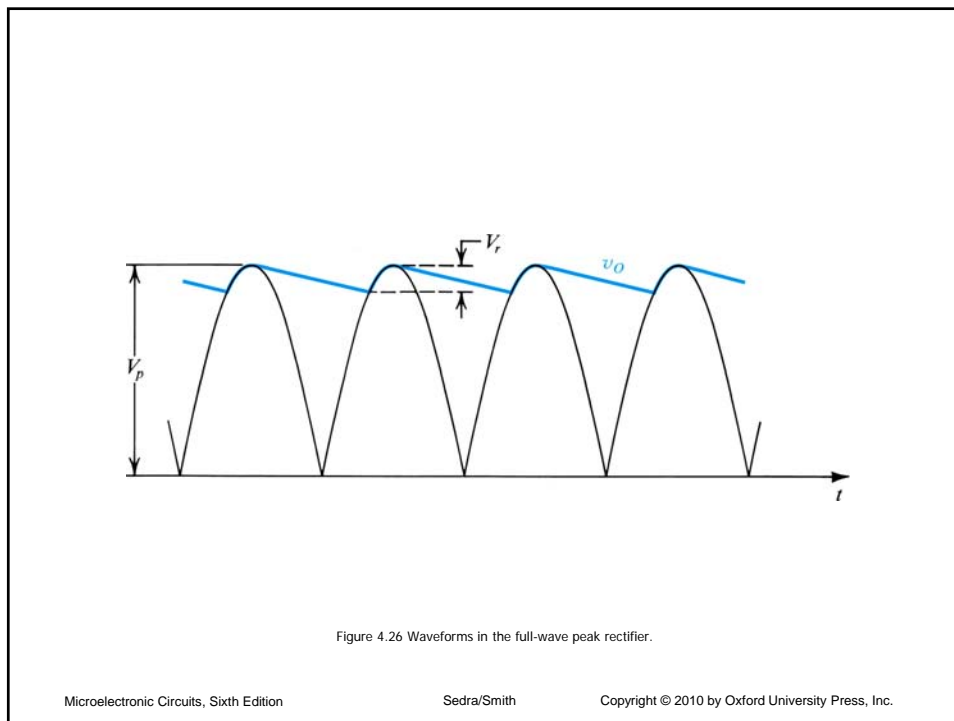


Figure 4.24 (a) A simple circuit used to illustrate the effect of a filter capacitor. (b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a *peak rectifier* or a *peak detector*.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

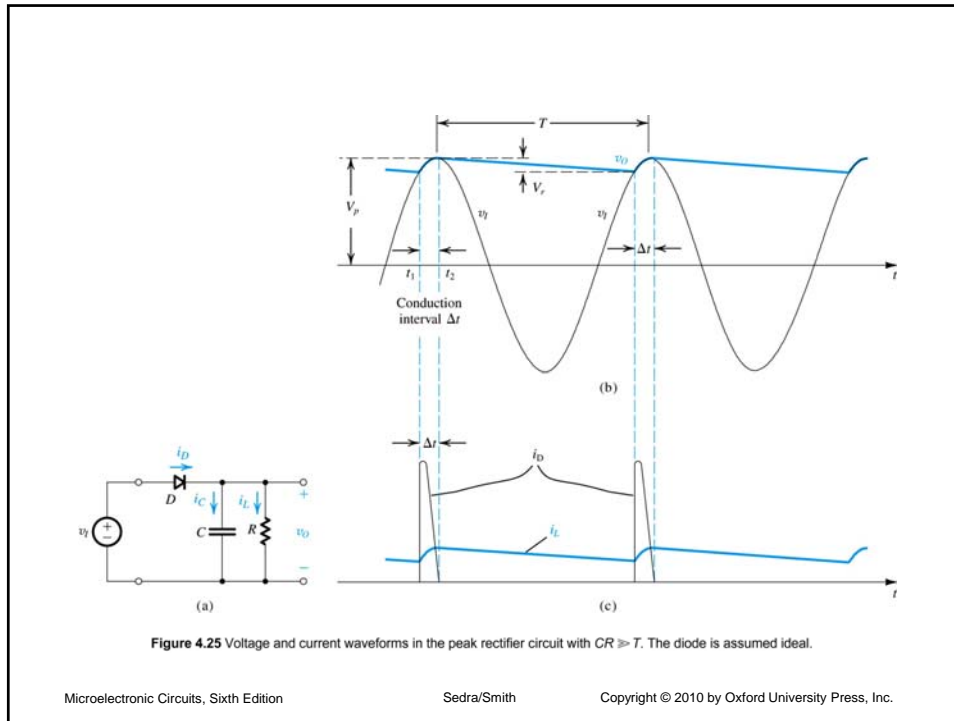Copyright © 2010 by Oxford University Press, Inc.




Superdiode

- There is one or 2 diode voltage drops in the rectifier circuits we studied.
- That is O.K. when we are designing a DC power supply.
- Can not be used to rectify a small voltage signal (100 mV).

Superdiode

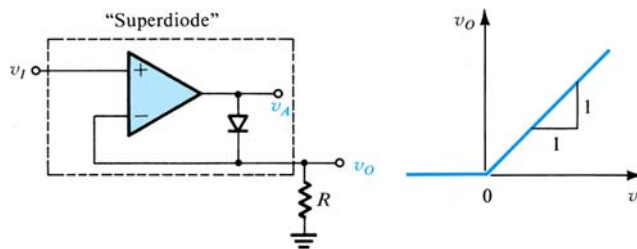- When v_I is positive, v_A is positive, the diode conducts providing the $-ve$ feed back and $v_O = v_I$
- When v_I is $-ve$ v_A is negative diode is reverse biased, no current in R, no drop on R, $v_O = 0$



Microele

(a)

(b)


rd University Press, Inc.

Diode Circuits


- Limiter circuits
- Clamped capacitor or DC restorer
- Voltage doubler

Limiter Circuits

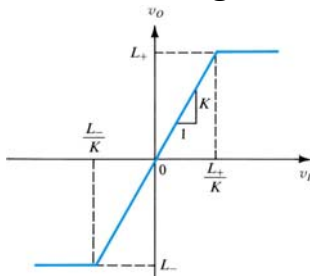- K could be > 1 , but we concentrate of $k \leq 1$ (passive limiter)
- Also known as clippers
- Soft limiting vs. hard limiting





Microelectronic Circuits, Sixth Edition

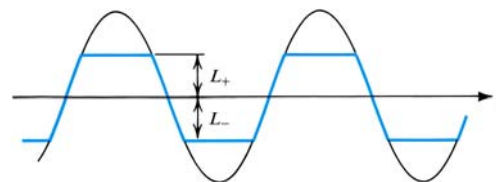


Sedra/Smith

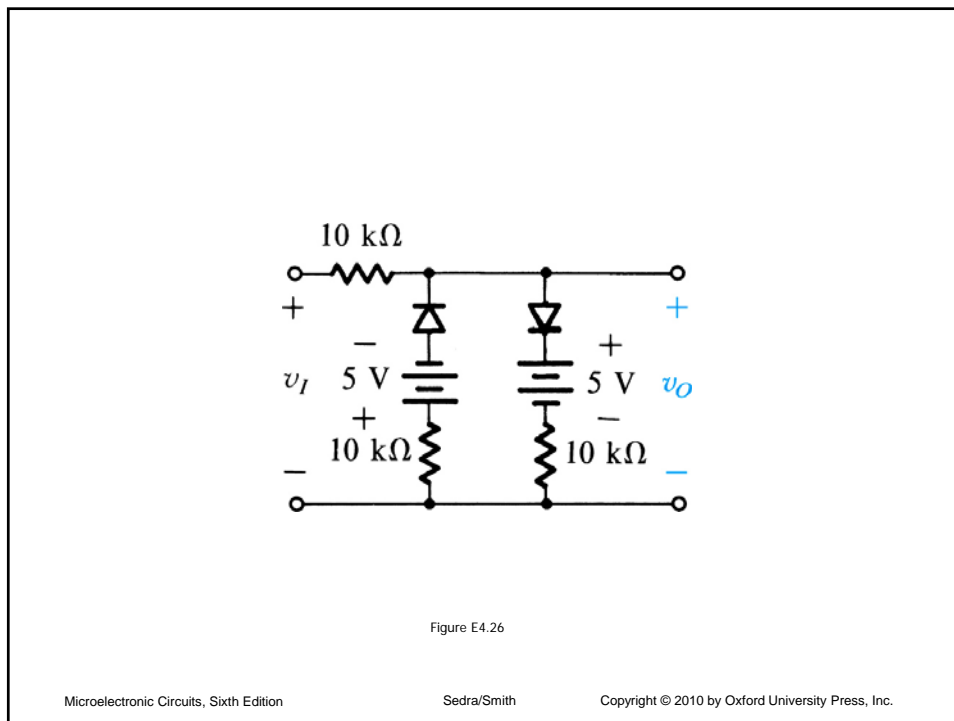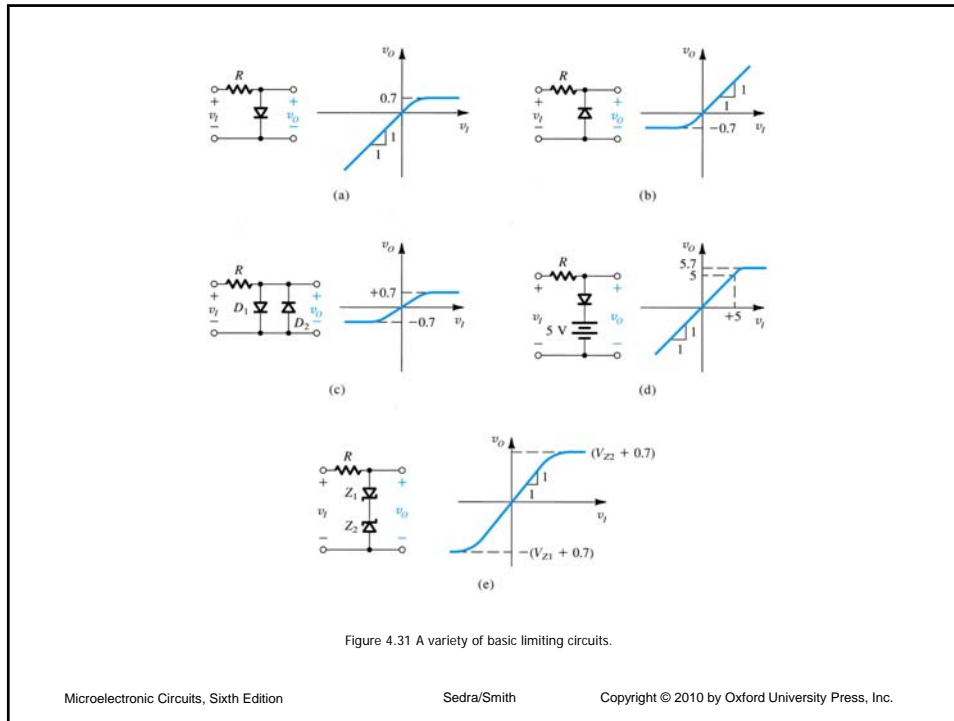Copyright © 2010 by Oxford University Press, Inc.



Clamped Capacitor (DC restorer)

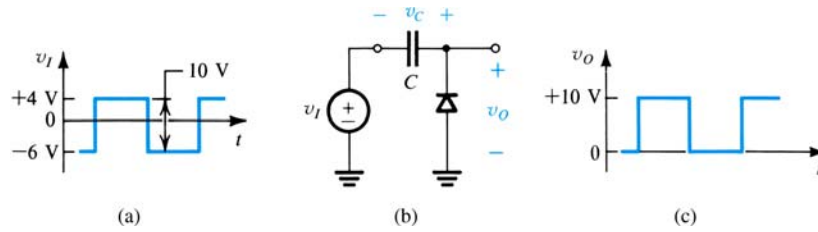- Shifts the input signal by a specific amount
- When v_I is -6 , $v_C = 6$ V as shown
- When v_I is $+4$, diode is off and capacitor does not discharge
- $v_O = v_I + v_C$



Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Clamped Capacitor with a Load

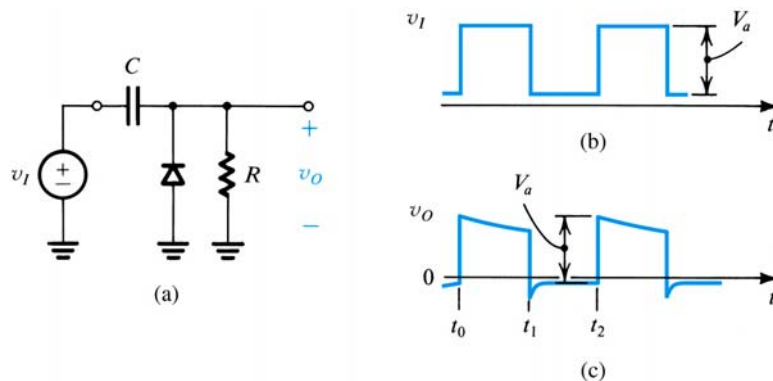


Figure 4.33 The clamped capacitor with a load resistance R .

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Voltage Doubler

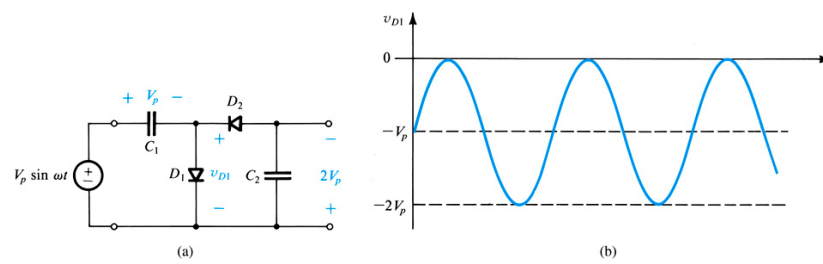


Figure 4.34 Voltage doubler: (a) circuit; (b) waveform of the voltage across D_1 .