

ENG2210  
Electronic Circuits  
Chapter 4 MOSFET

Mokhtar A. Aboelaze  
York University

**Disclaimer:** Most of the slides are skeletons that will be filled/modified in the lecture. Please do not assume that you can know the material just by reading the slides.

## Chapter Objectives

- Learn the physical structure of the MOSFET and how it works.
- How to analyze circuits that contains MOSFET.
- How to obtain linear amplification from a nonlinear MOSFET.
- The three basic ways for connecting a MOSFET to construct amplifiers.
- Practical circuits for MOSFET.

## MOSFET– Metal Oxide Semiconductor Field Effect Transistor


- Transistors (3 terminal devices) diodes are 2 terminal devices – more complicated.
- One terminal usually control the current between the other two terminals.
- Used in digital and analog circuits
- Mainly MOSFET and BJT (vast majority of IC's are MOSFET)
  - Smaller
  - Loss power than BJT – very important –

## MOSFET


- This is not a course on semiconductor (nor this is a physics course). However, understanding how the device work is very important.
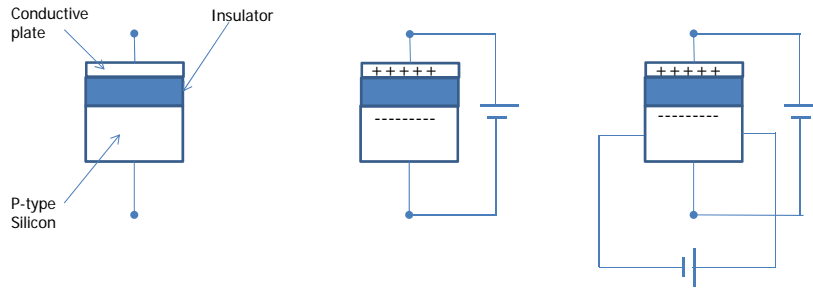
# MOSFET


Not a real device, just to explain the idea



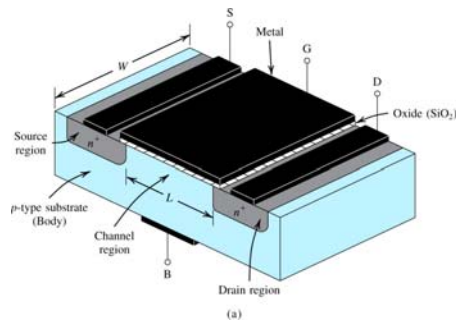
Gate is isolated (SiO<sub>2</sub>) no current from gate



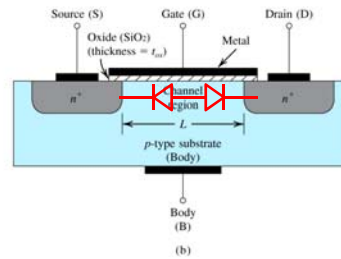No current can flow between source and drain



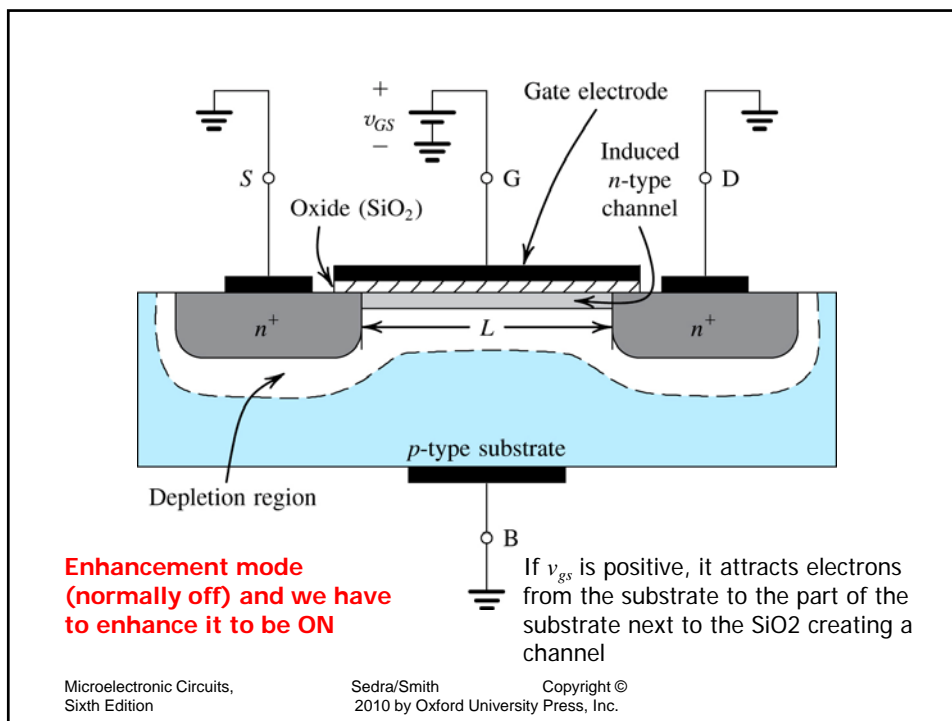Usually body contact is connected to the source



## MOSFET Operation

- We start by explaining how things work, then we use mathematics to derive equations.
- Start with n-MOS

$V_G=0$ , because of the back-to-back diodes, no current flows from source to destination

$V_G>0$ , Holes are repelled by the positive gate voltage and leaving behind negative ions forming a depletion region

As  $V_G$  increases (Threshold voltage), Electrons are attracted to the surface forming a channel where current **might** flow

From Fundamentals of microelectronics – Behzad Razavi

### IEEE Standard MOS Transistor Circuit Symbols

(a) NMOS enhancement-mode device

(b) PMOS enhancement-mode device

(c) NMOS depletion-mode device

(d) PMOS depletion-mode device


(e) Three-terminal NMOS transistor

(f) Three-terminal PMOS transistor

Transistors11

Source: <http://people.seas.harvard.edu/~jones/es154/>


# NMOS Characteristics

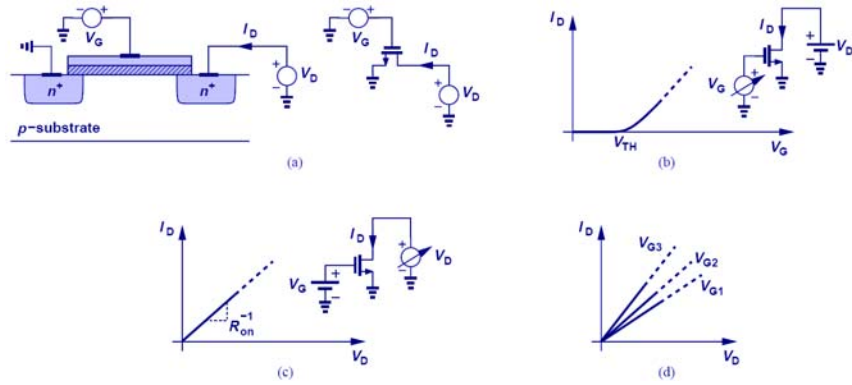

- We can vary  $V_G$  and keeping  $V_D$  constant
- Or vary  $V_D$  and keeping  $V_G$  constant





From Fundamentals of microelectronics – Behzad Razavi

# Effect of $L$ and $t_{ox}$

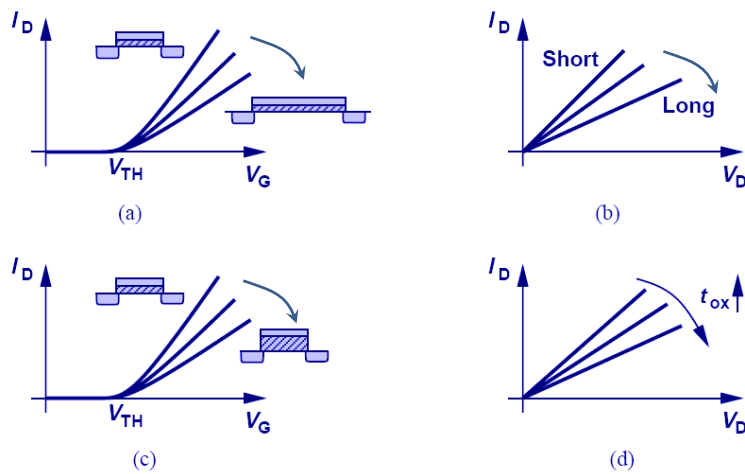

From Fundamentals of microelectronics – Behzad Razavi


# Effect of $W$

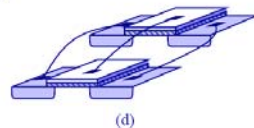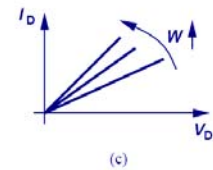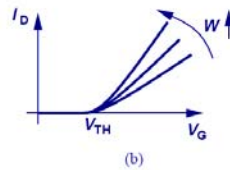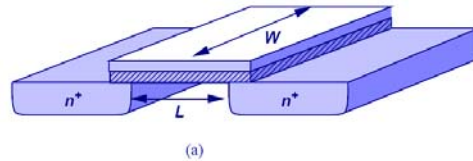



From Fundamentals of microelectronics – Behzad Razavi

# Channel Pinch-off

$V_G > V_{TH}$

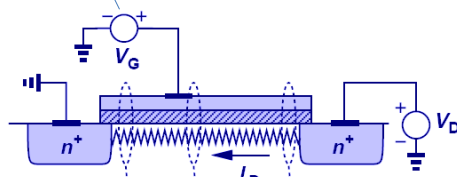

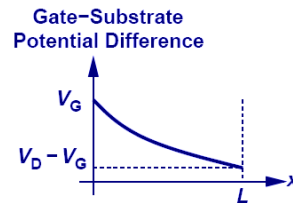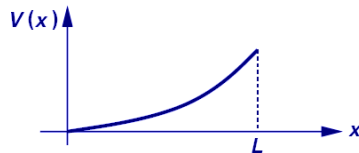
Potential Difference =  $V_G$  <  $V_G$  =  $V_G - V_D$




The channel acts as a resistance, voltage increases from S ( $V=0$ ) to D ( $V=V_D$ )

From Fundamentals of microelectronics – Behzad Razavi

# Channel Pinch-Off

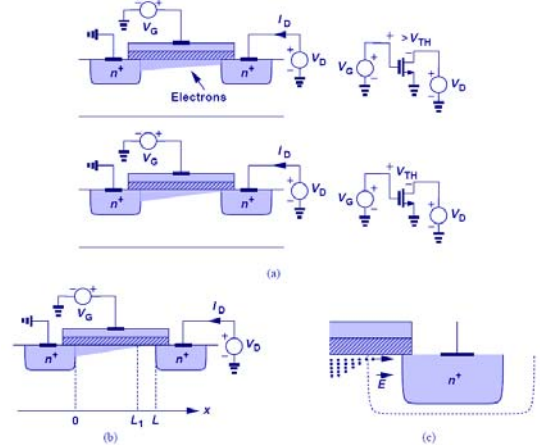


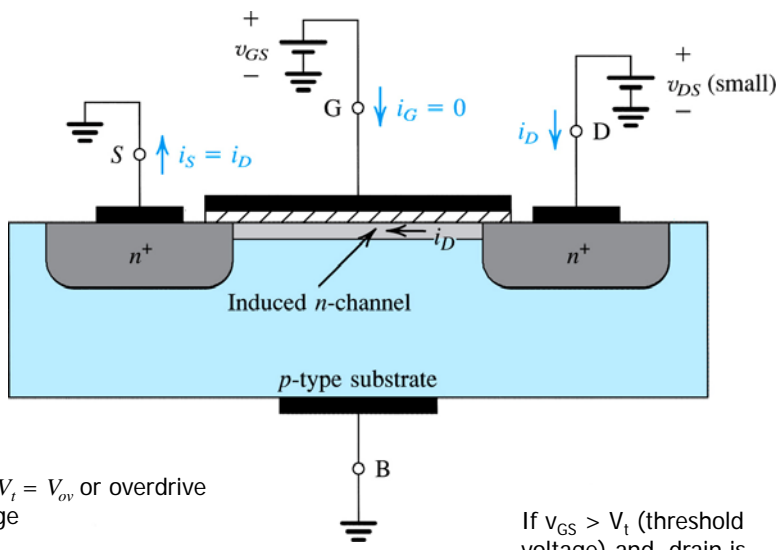- As  $V_D$  increases, at some distance  $x$ ,  $V_G - V_D < V_{TH}$  and the channel does not exist anymore.
- Does that mean No current? No, The high electric field in the depletion region carry them through, but  $V_D$  does not control the current anymore (constant current source)





### Small $v_{DS}$

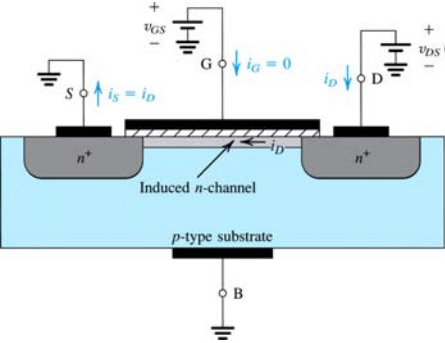

$$\frac{Q}{\text{Unit length}} = \frac{CV}{L} = \frac{(\epsilon_{ox}A/t_{ox})V}{L}$$

$$\frac{Q}{\text{Unit length}} = C_{ox}Wv_{ov}, \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$|E| = \frac{v_{DS}}{L}$$

Electron drift velocity =  $\mu_n |E| = \mu_n \frac{v_{DS}}{L}$

$$i_D = \frac{Q}{\text{Unit length}} \times \text{speed}$$

$$i_D = C_{ox} W V_{ov} \times \mu_n \frac{v_{DS}}{L}$$

$$i_D = \left[ (\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov} \right] v_{DS}$$

### Small $v_{DS}$


$$i_D = \left[ (\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov} \right] v_{DS}$$

Conductance

$$g_{DS} = (\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov}$$



Linear resistance

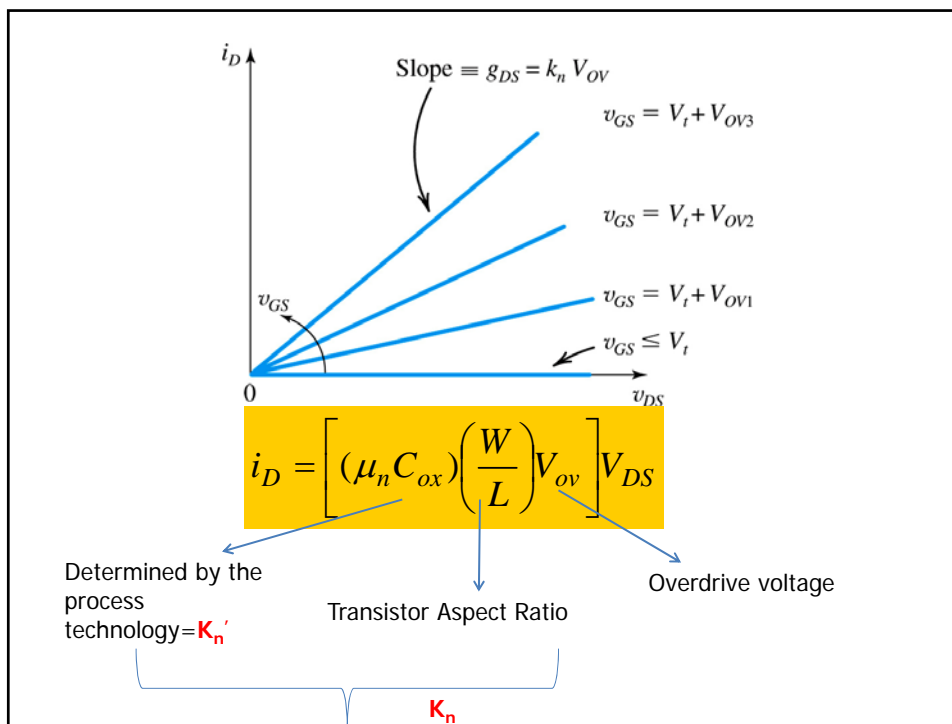
$$r_{DS} = \frac{1}{(\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov}}$$


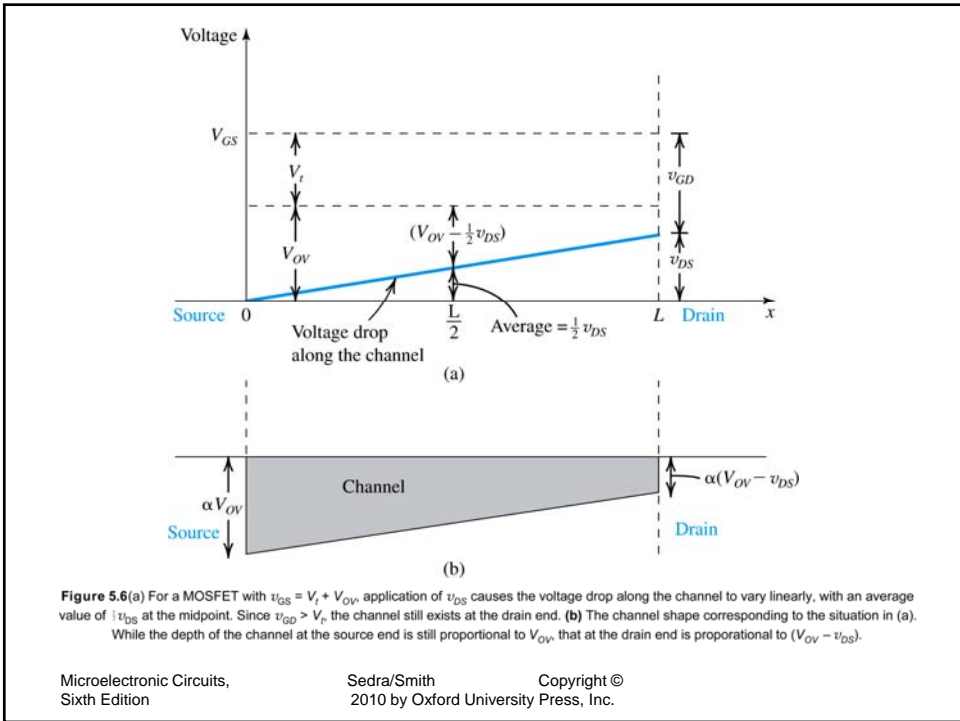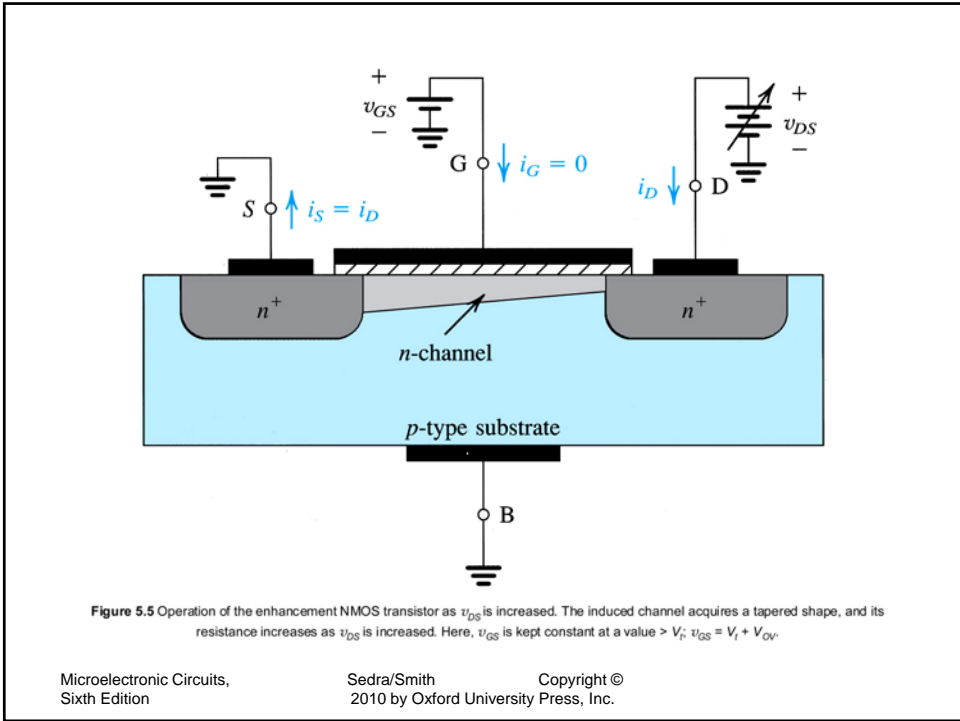
## Not Small $v_{DS}$

- As  $v_{DS}$  increases we can not assume a constant voltage between the gate and any point along the channel.
- The voltage at one end of the channel is 0, while at the other end is  $v_{DS}$



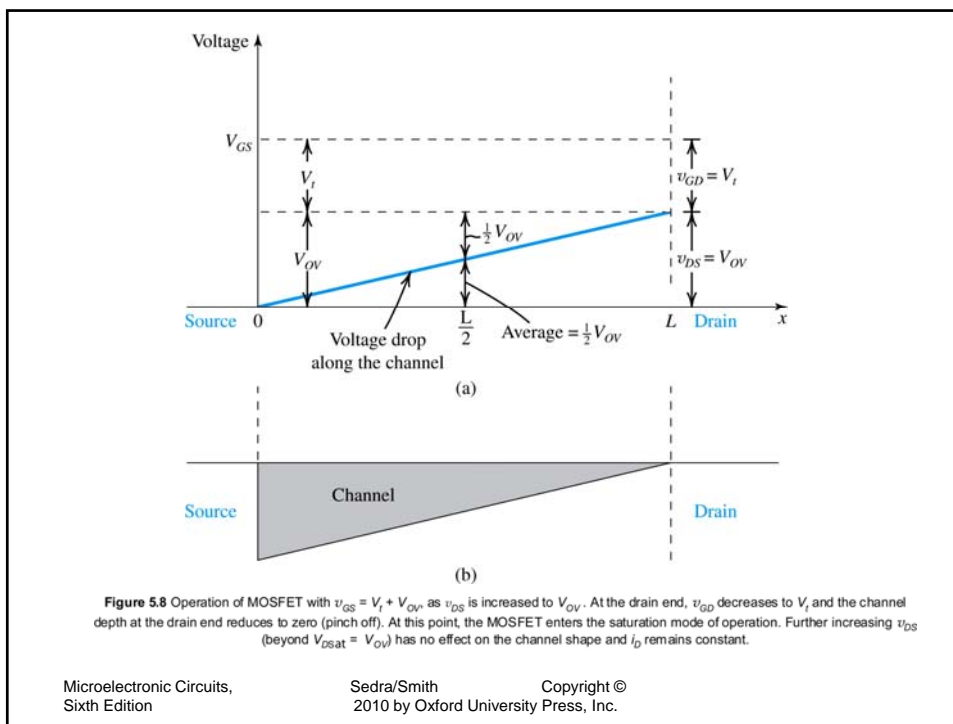

(b)

$$i_D = \left[ (\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov} \right] v_{DS}$$

$$i_D = \left[ (\mu_n C_{ox}) \left( \frac{W}{L} \right) \left( V_{ov} - \frac{1}{2} v_{DS} \right) \right] v_{DS}$$


$$i_D = \left[ k'_n \left( \frac{W}{L} \right) \left( V_{ov} - \frac{1}{2} v_{DS} \right) \right] v_{DS}$$



As  $v_{DS}$  increases the resistance increases and the current does not continue to grow with the same rate



$$v_{DS} \geq V_{ov}$$



- As  $V_{DS}$  grows, the channel pinches off.
- When  $v_{DS} = V_{ov}$  the channel depth is zero
- Increasing  $v_{DS}$  beyond that has no effect.
- The drain current saturates (saturation region)
- Electrons can still go through the depletion region
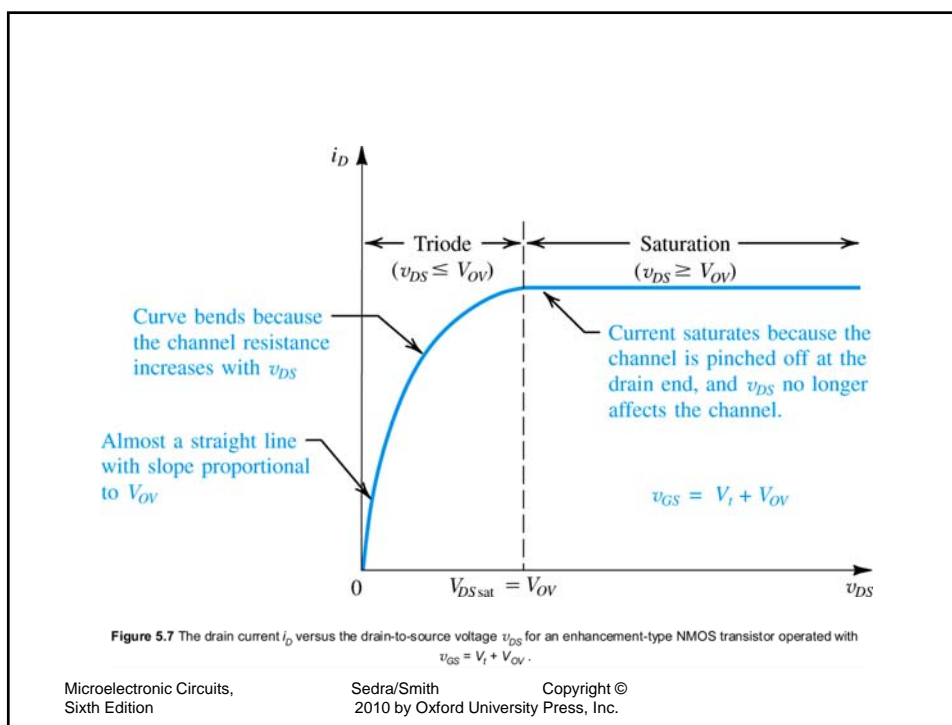
$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) V_{ov}^2$$



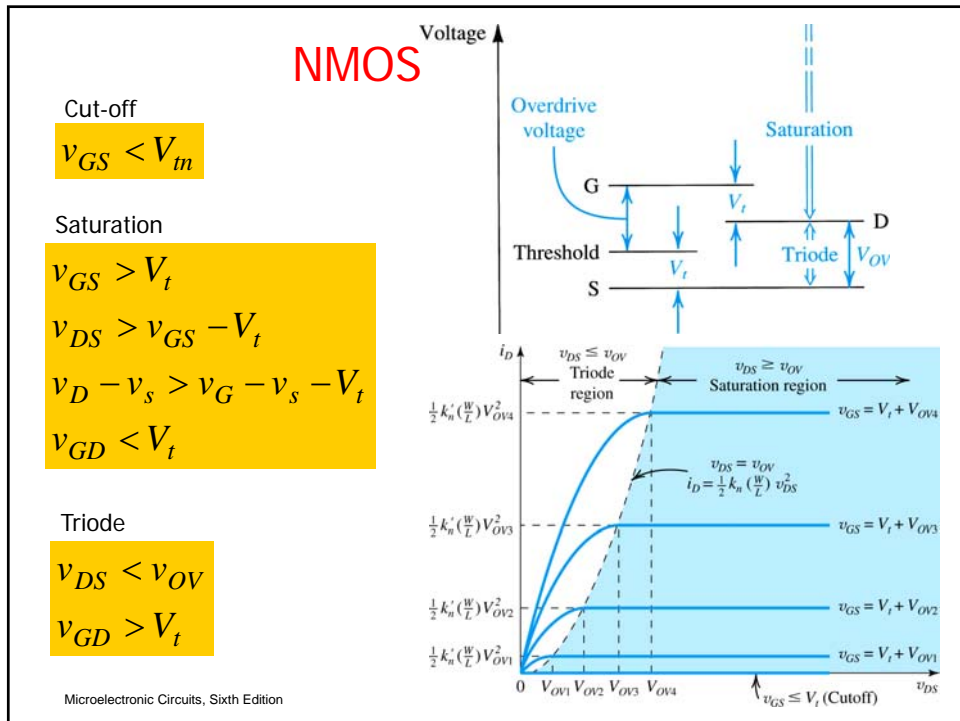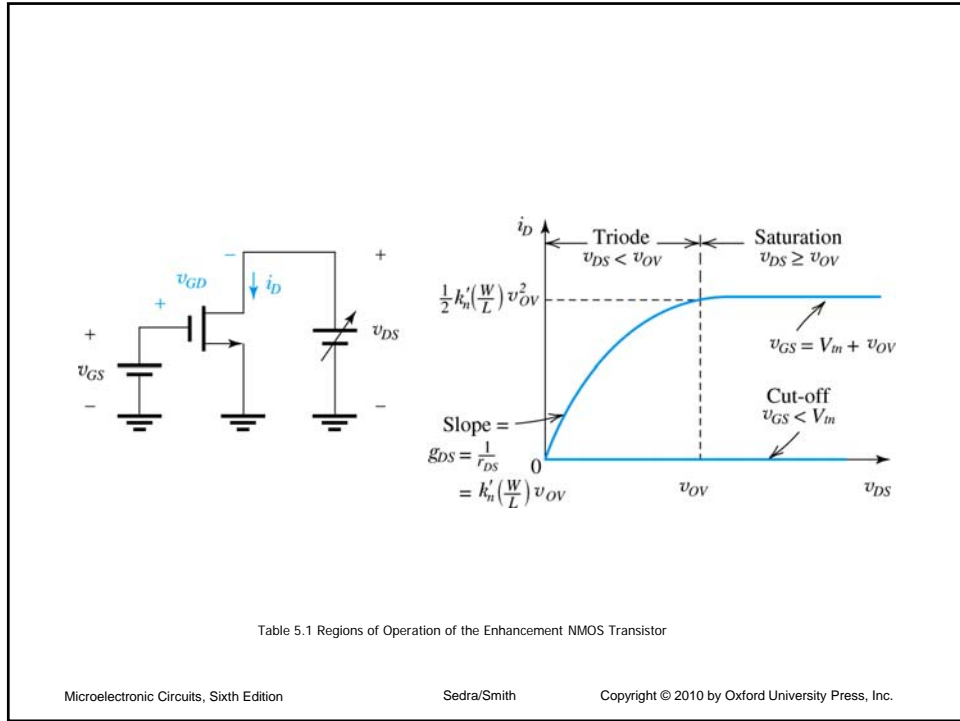


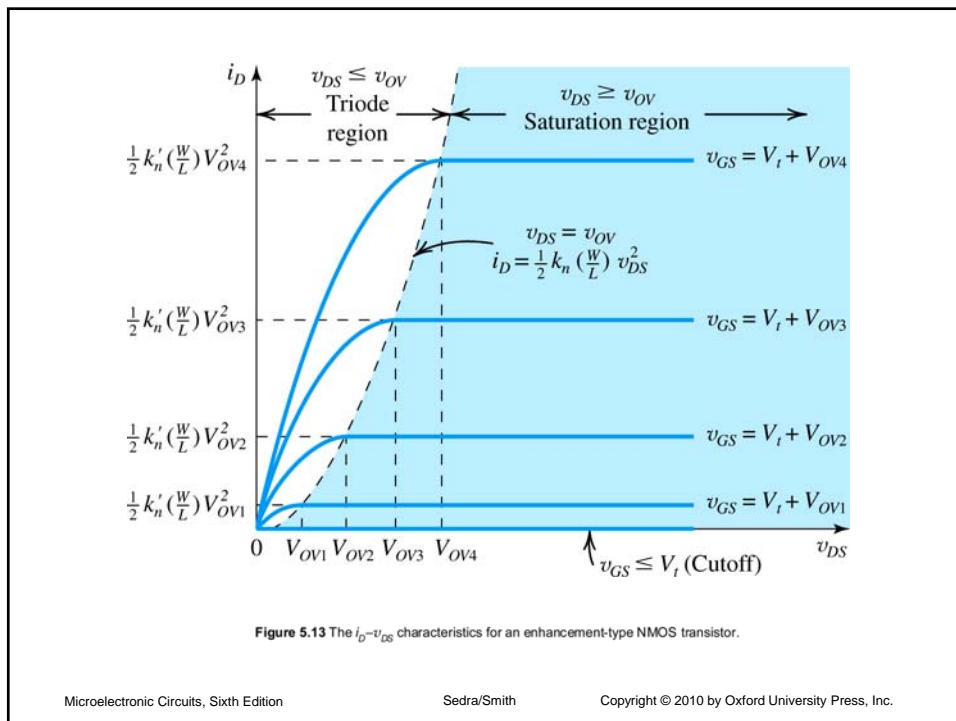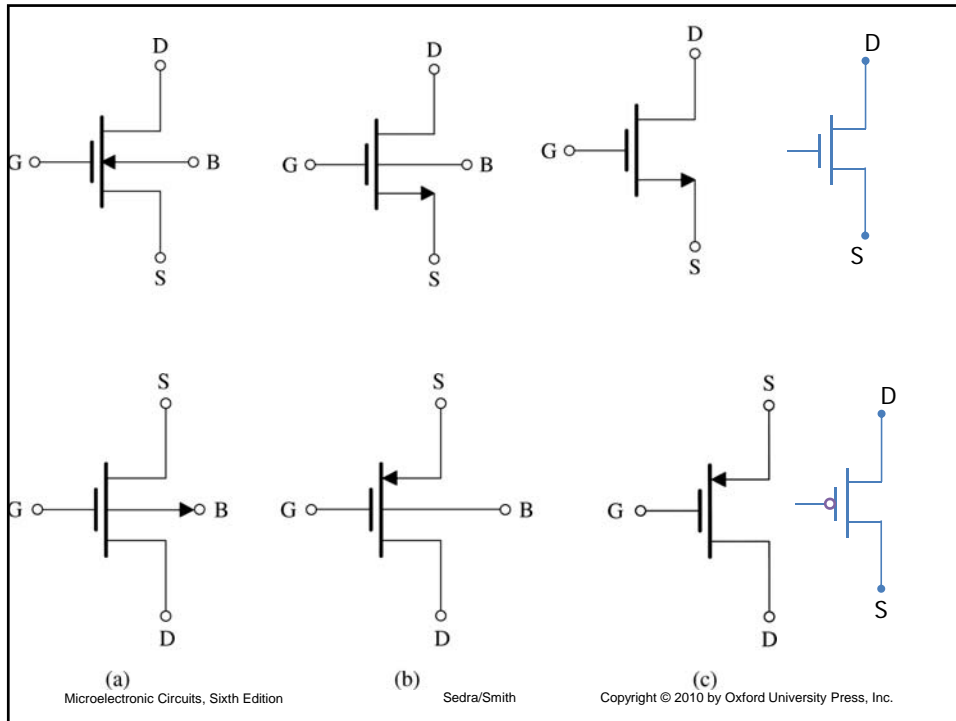

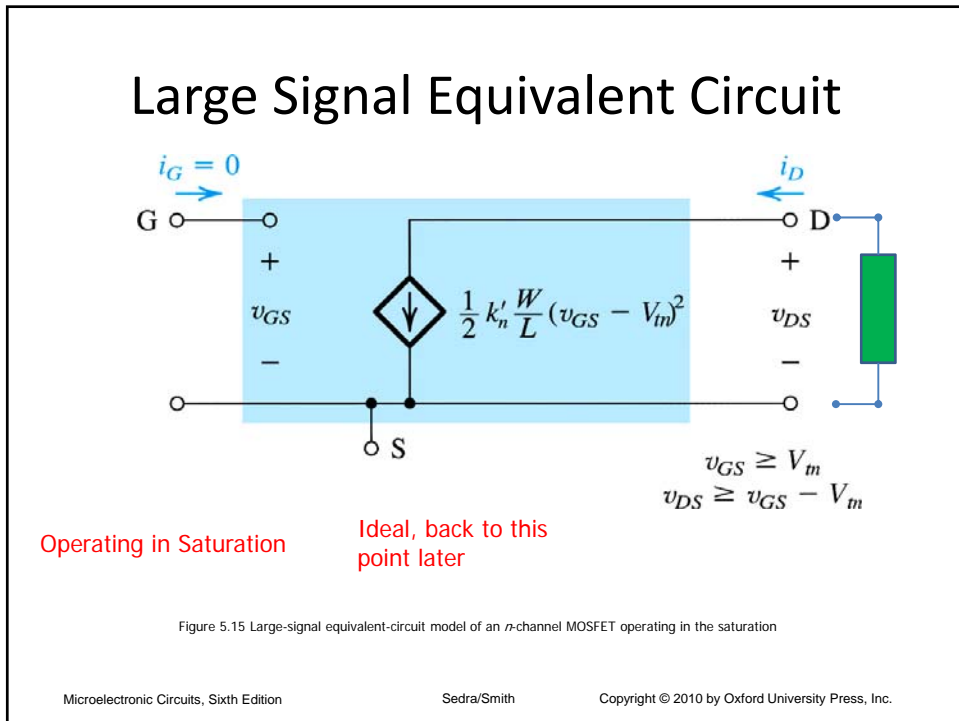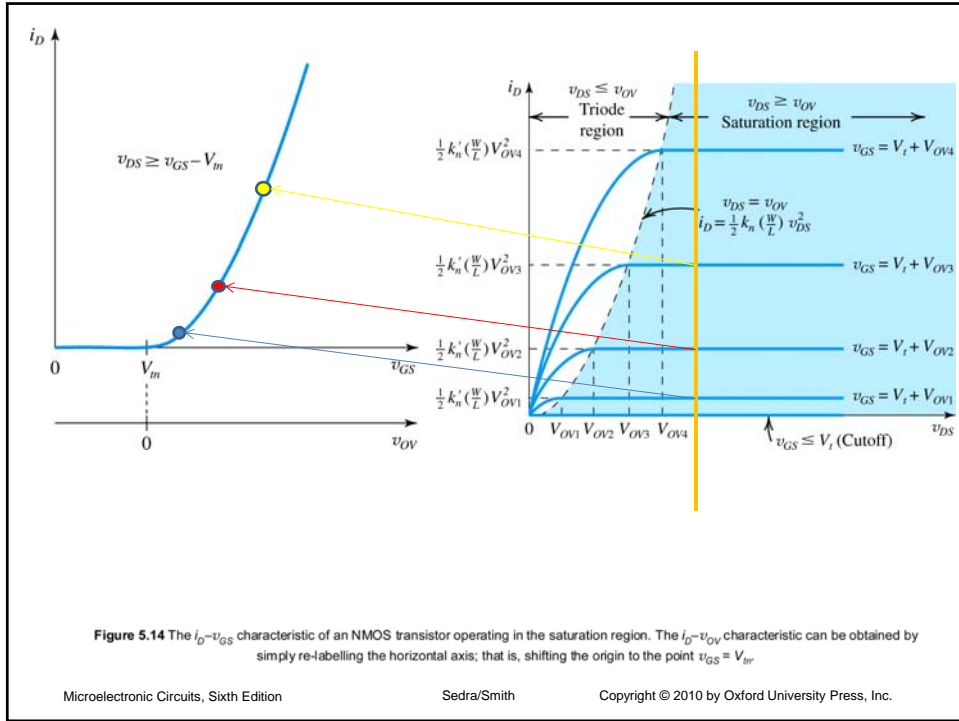



# Finite Output Resistance

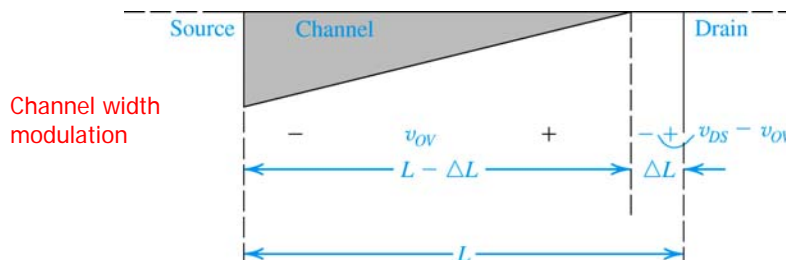

- As  $v_{DS}$  increases, the channel *pinch off* moves away from the drain ( $L$  gets smaller).
- Voltage across the channel remains  $v_{ov}$ .
- A voltage drop of  $v_{DS} - v_{ov}$  appears across the small depletion region
- This voltage accelerates the electrons that reach the drain (increases current)

$$i_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) V_{ov}^2$$

$$i_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) V_{ov}^2 (1 + \lambda v_{DS})$$

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

$$r_o = \left[ \frac{\partial i_D}{\partial v_{DS}} \right]_{v_{GS} \text{ constant}}^{-1}$$

$$r_o = \left[ \lambda \frac{k_n' W}{2 L} (V_{GS} - V_t)^2 \right]^{-1}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

$$i_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) V_{ov}^2 (1 + \lambda v_{DS})$$

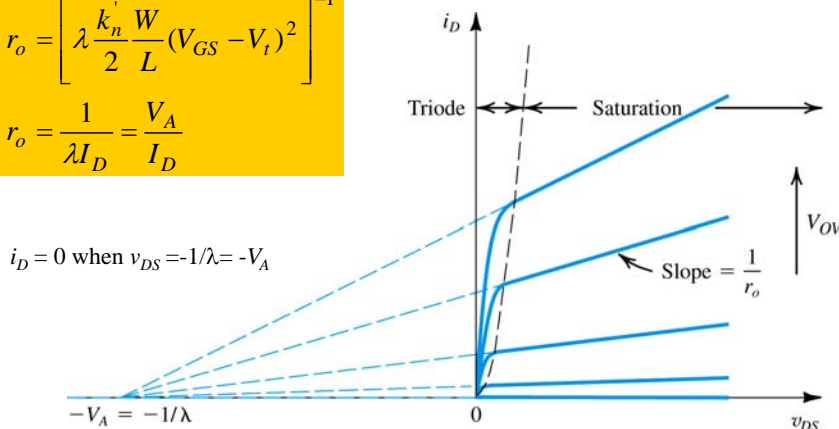


Figure 5.17 Effect of  $v_{DS}$  on  $i_D$  in the saturation region. The MOSFET parameter  $V_A$  depends on the process technology and, for a given process, is proportional to the channel length  $L$ .

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

## Example

- Find  $R_S$  and  $R_D$  such that
- $I_D = 0.4 \text{ mA}$ ,  $V_D = +0.5 \text{ V}$
- $V_t = 0.7 \text{ V}$ ,  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$
- $L = 1 \mu\text{m}$ ,  $W = 32 \mu\text{m}$ .

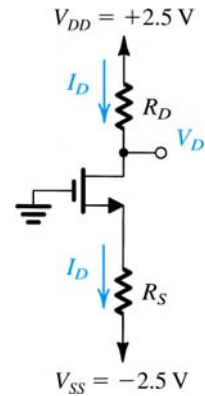


Figure 5.21 Circuit for Example 5.3.

## Large Signal Equivalent Circuit



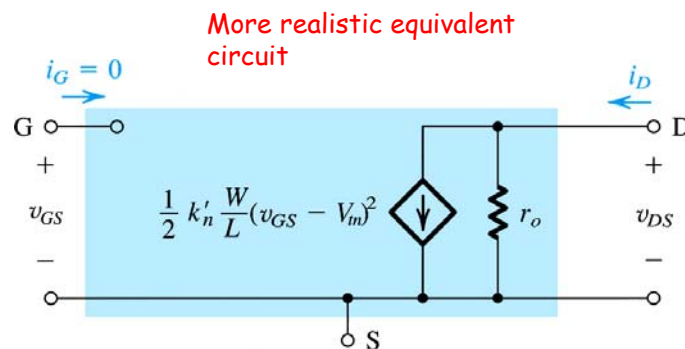




Figure 5.18 Large-signal equivalent circuit model of the  $n$ -channel MOSFET in saturation, incorporating the output resistance  $r_o$ . The output resistance models the linear dependence of  $i_D$  on  $v_{DS}$  and is given by Eq. (5.23).



# PMOS

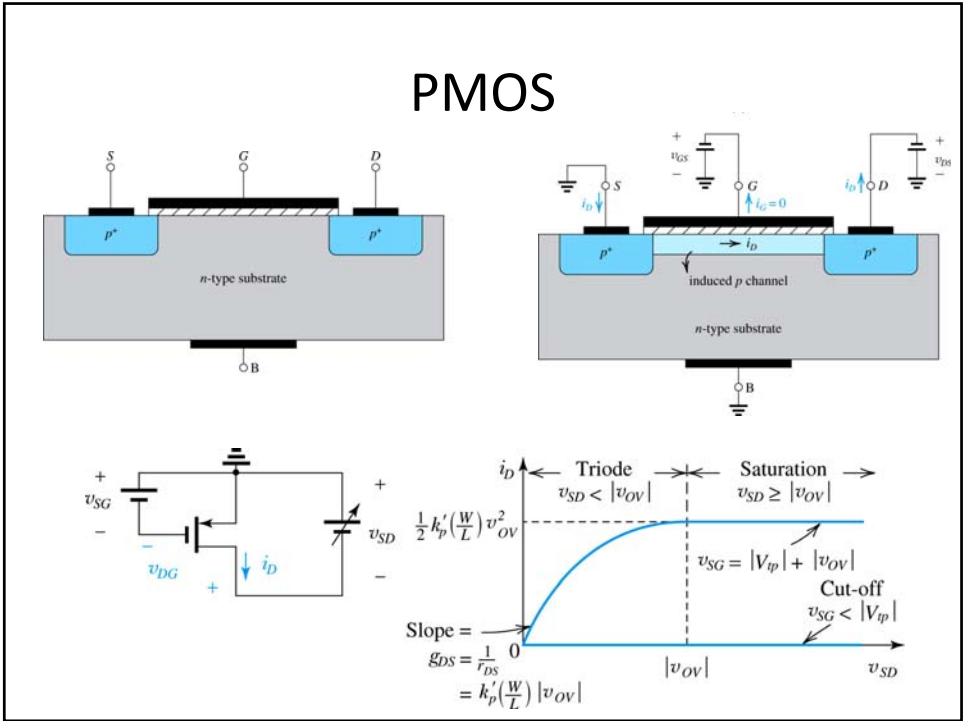

# PMOS vs. NMOS

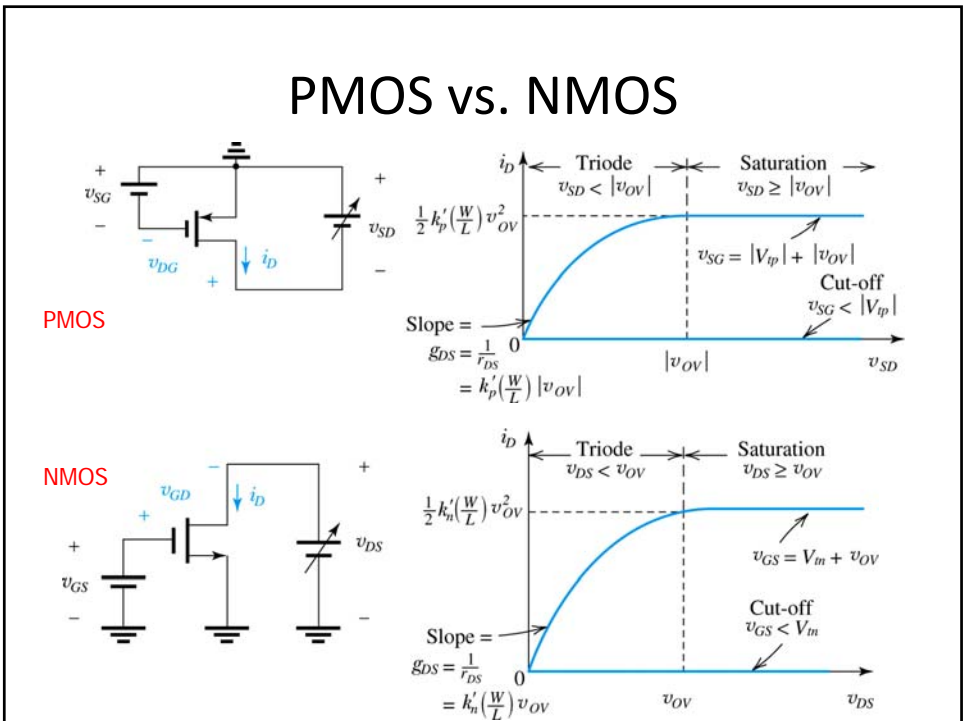

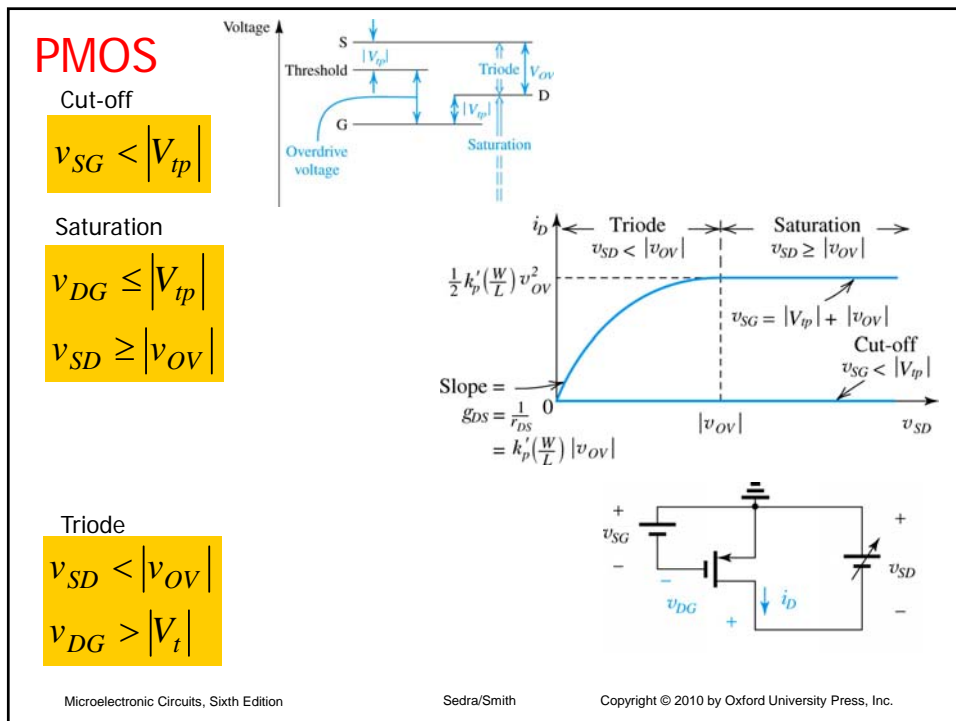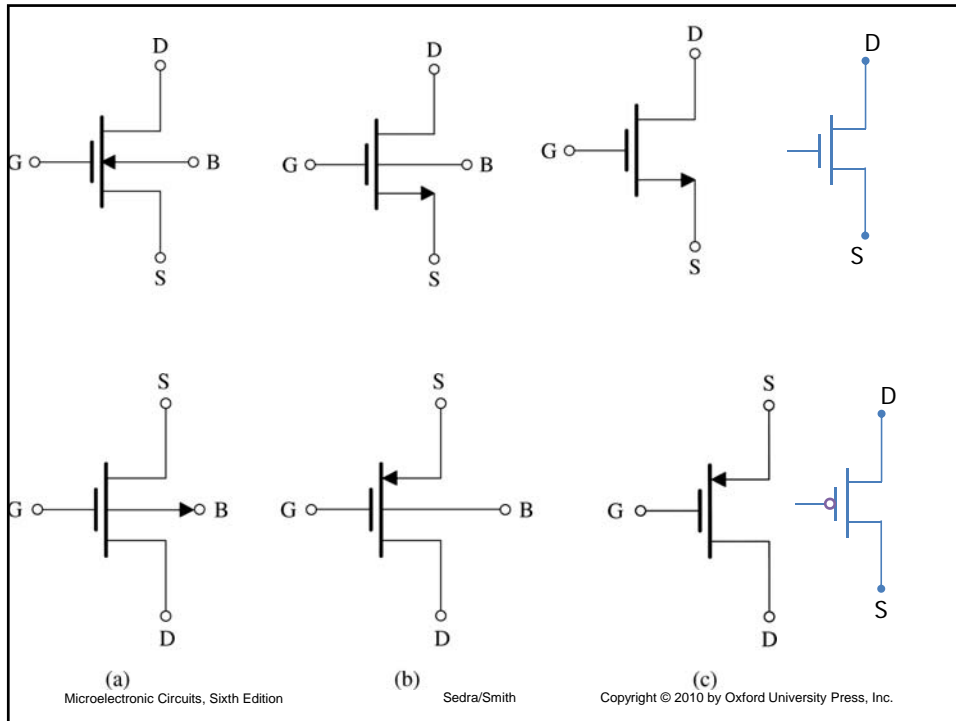

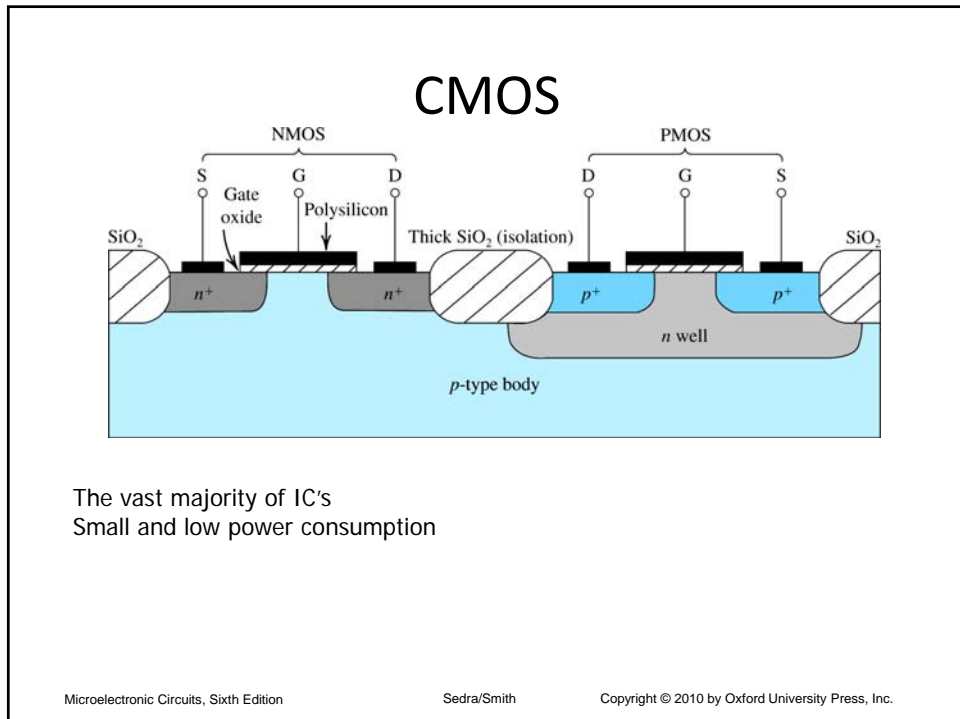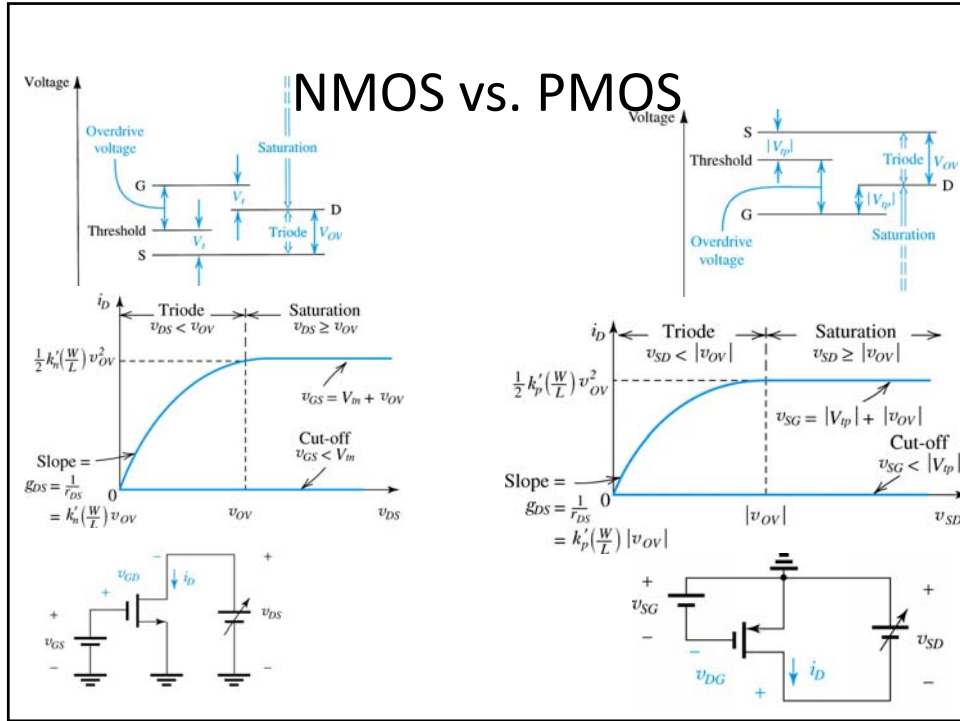

# EXAMPLE


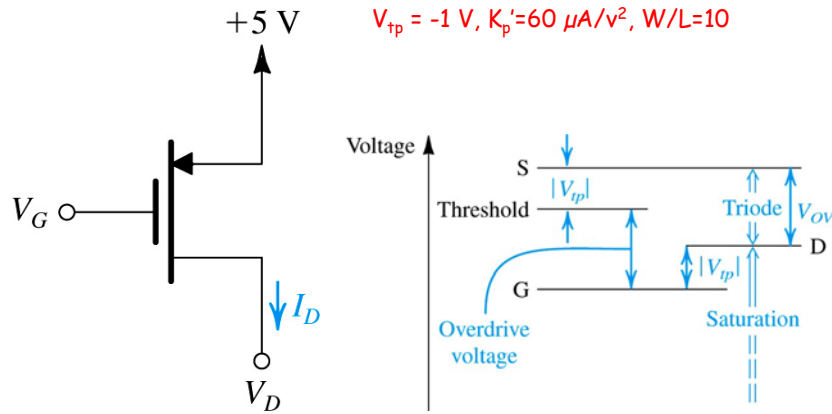


Figure E5.7

Microelectronic Circuits, Sixth Edition

Sedra/Smith

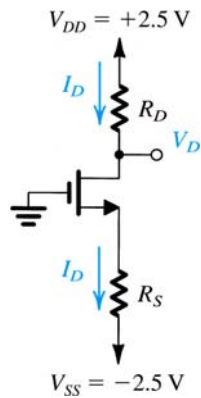Copyright © 2010 by Oxford University Press, Inc.



Find  $R_S$  and  $R_D$  such that  $I_D = 0.4\text{ mA}$  and  $V_D = +0.5\text{ V}$   
 Given  $V_t = 0.7\text{ V}, \mu_n C_{ox} = 100\ \mu\text{A}/\text{V}^2$  and  $W/L = 32$