




# EECS 3201: Digital Logic Design Lecture 10

Ihab Amer, PhD, SMIEEE, P.Eng.


# Blocking Vs Non-Blocking Assignment

- Example: If initially,  $A = 4$  and  $B = 13$

- Non-Blocking Assignment

$B \leq A$   
 $C \leq B + 1$    $C = 14$

- Blocking Assignment

$B = A$   
 $C = B + 1$    $C = 5$

# Wakerly Rules for an **always** block

- Always use blocking assignment (=) in **always** blocks intended to create **combinational** logic
- Always use non-blocking assignment (<=) in **always** blocks intended to create **sequential** logic
- Do not mix blocking and non-blocking assignments in the same **always** block
- Do not make assignments to the same variable in two different **always** blocks


# Important Book Chapters

- Related sections of chapter 5 in the textbook

# Finite State Machines

- Sequential circuits are sometimes called finite state machines
- The name comes from the fact that such circuits have a finite number of possible states ( $\leq 2^n$ ), where  $n$  is the number of storage elements (e.g. FF's) in the circuit

# State Machine Structure

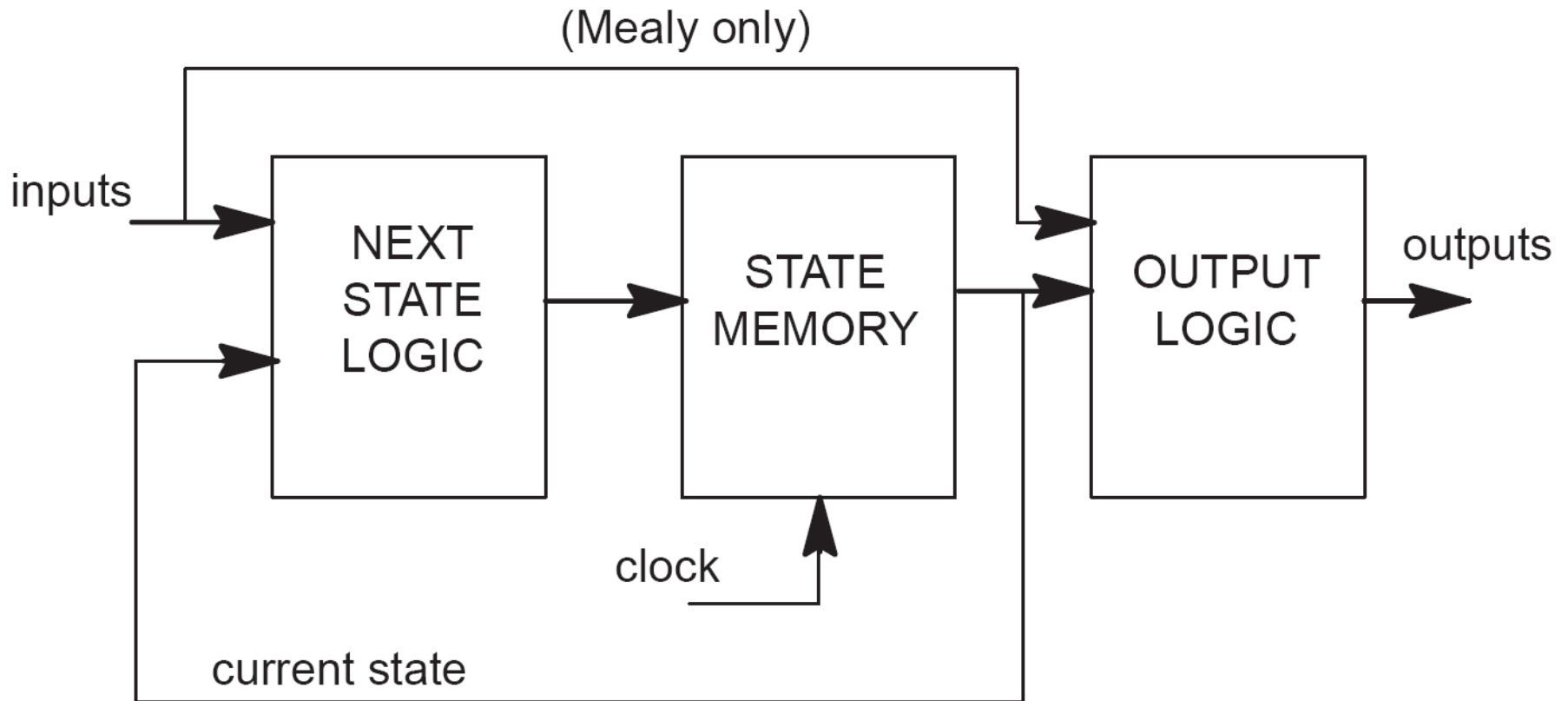

# I. Analysis of Sequential Circuits

- Given a sequential circuit, obtain the state table, state diagram, and/or the timing diagram

# Example 1

Analyze the following sequential circuit:


FF Input Equation(s)

$$D_A = Ax + Bx$$

$$D_B = A'x$$

Output Equation(s)

$$y = (A + B) x'$$

 



# State Table

*By using the FF ch's table*

*By substitution in the o/p eq.*

Present State		Input	Next State		Output	FF Inputs	
A	B	x	A	B	y	D <sub>A</sub>	D <sub>B</sub>
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	0

FF Input Equation(s)

$$D_A = Ax + Bx$$

$$D_B = A'x$$

Output Equation(s)


$$y = (A + B) x'$$

*By substitution in the FF i/p eq.*

D-FF Ch's Table

D	Q(t+1)
0	0
1	1

# State Diagram

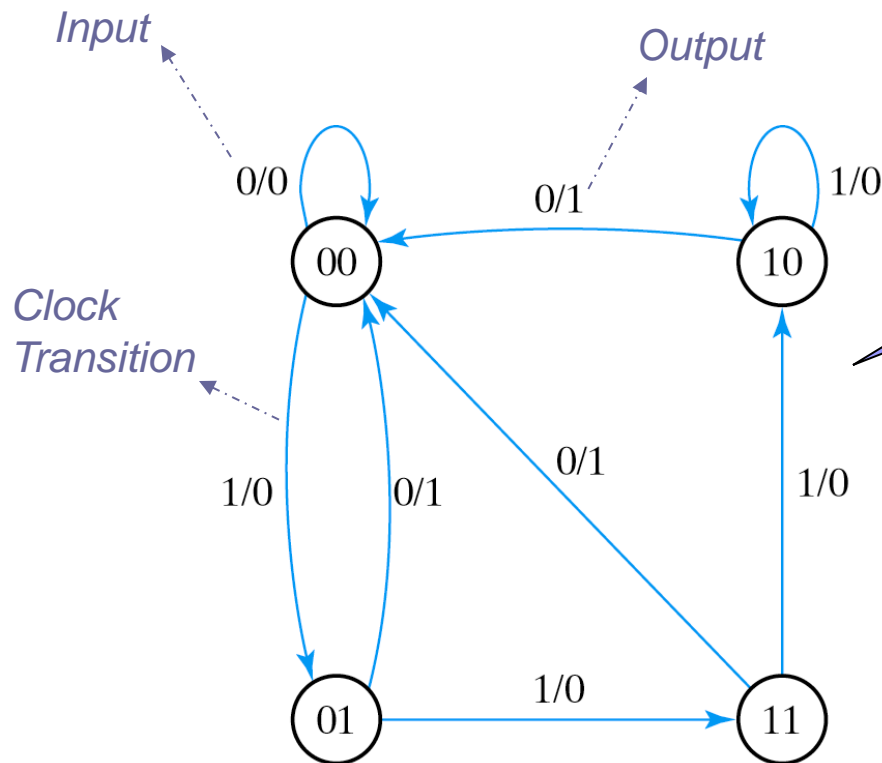

**Mealy Machine**

Output depends on current state and INPUT

# HDL for Mealy FSM

```

module Mealy_mdl (x,y,CLK,RST);
  input x,CLK,RST;
  output y;
  reg y;
  reg [1:0] Prstate, Nxtstate;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge CLK or negedge RST)
    if (~RST) Prstate = S0; //Initialize to state S0
    else Prstate = Nxtstate; //Clock operations
  always @ (Prstate or x) //Determine next state
    case (Prstate)
      S0: if (x) Nxtstate = S1;
      S1: if (x) Nxtstate = S3;
           else Nxtstate = S0;
      S2: if (~x)Nxtstate = S0;
      S3: if (x) Nxtstate = S2;
           else Nxtstate = S0;
    endcase

```


*There are other consistent and non-consistent styles to code a Mealy FSM*

```

  always @ (Prstate or x) //Evaluate output
    case (Prstate)
      S0: y = 0;
      S1: if (x) y = 1'b0; else y = 1'b1;
      S2: if (x) y = 1'b0; else y = 1'b1;
      S3: if (x) y = 1'b0; else y = 1'b1;
    endcase
endmodule

```

# Example 2

 


(a) Circuit diagram

FF Input Equation

$$D_A = A \oplus x \oplus y$$

Present state	Inputs		Next state
<i>A</i>	<i>x</i>	<i>y</i>	<i>A</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

 


Moore Machine

(c) State diagram
 
# Example 3

Analyze the following sequential circuit:



FF Input Equation(s)

$$J_A = B$$

$$K_A = Bx'$$

$$J_B = x'$$

$$K_B = A \oplus x$$

# State Table

Present State		Input	Next State		FF Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

## FF Input Equation(s)


$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A \oplus x$$

## JK-FF Ch's Table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

# State Diagram

 

Moore Machine

# HDL for Moore FSM

```

module Moore_mdl (x,AB,CLK,RST);
  input x,CLK,RST;
  output [1:0]AB;
  reg [1:0] state;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge CLK or negedge RST)
    if (~RST) state = S0; //Initialize to state S0
  else
    case (state)
      S0: if (~x) state = S1;           // else state = S0;
      S1: if (x) state = S2; else state = S3;
      S2: if (~x) state = S3;           // else state = S2;
      S3: if (~x) state = S0;           // else state = S3;
    endcase
  assign AB = state;           //Output of flip-flops
endmodule


```

*There are other consistent and non-consistent styles to code a Moore FSM*


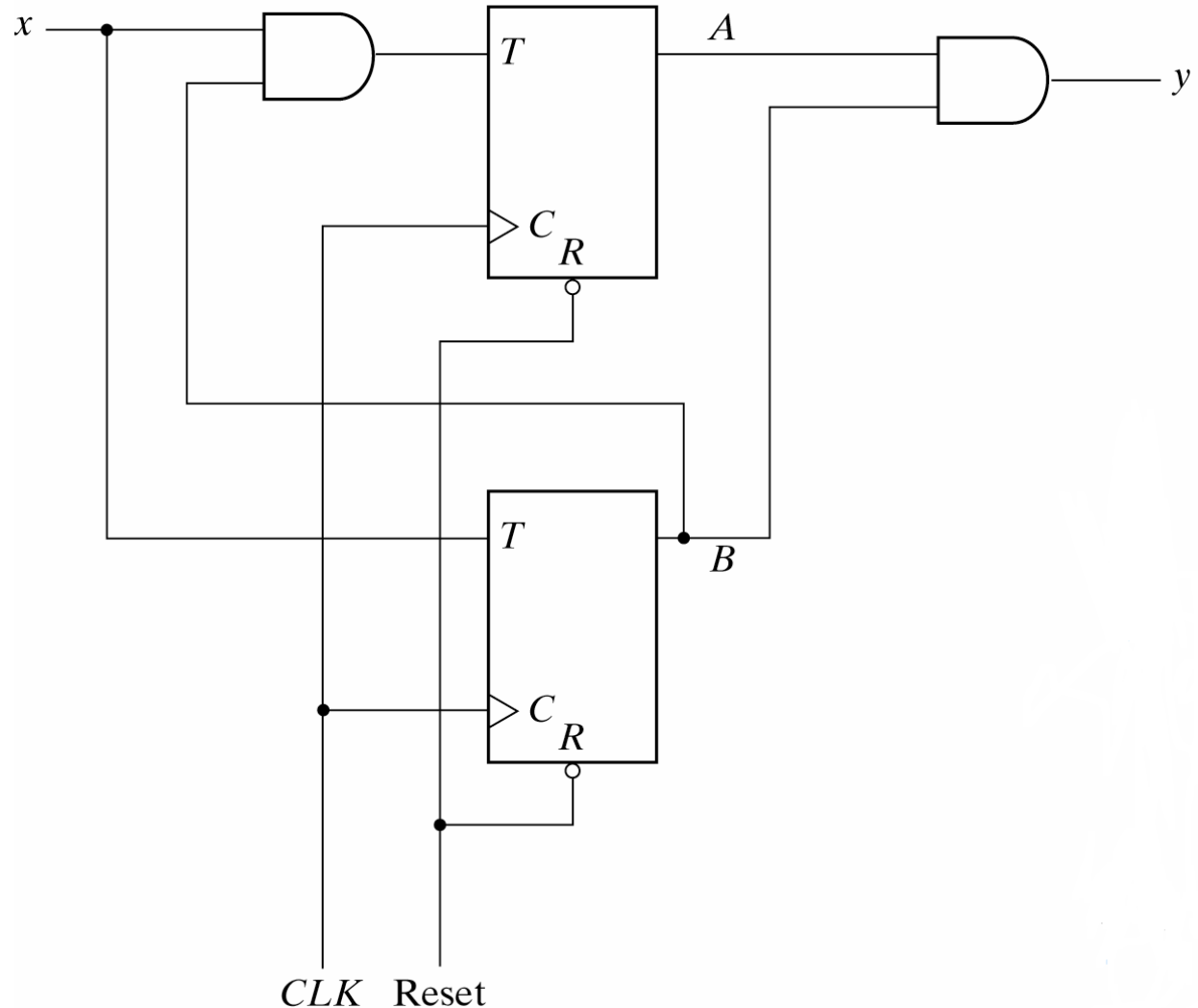
# Example 4

Analyze the following sequential circuit:



FF Input Equation(s)

$$T_A = Bx$$

$$T_B = x$$

Output Equation(s)

$$y = AB$$

# State Table

Present State		Input	Next State		Output	FF Inputs	
A	B	x	A	B	y	T <sub>A</sub>	T <sub>B</sub>
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	1	0	0	0
0	1	1	1	0	0	1	1
1	0	0	1	0	0	0	0
1	0	1	1	1	0	0	1
1	1	0	1	1	1	0	0
1	1	1	0	0	1	1	1

FF Input Equation(s)

$$T_A = Bx$$

$$T_B = x$$


Output Equation(s)

$$y = AB$$

T-FF Ch's Table

T	Q(t+1)
0	Q(t)
1	Q'(t)

# State Diagram

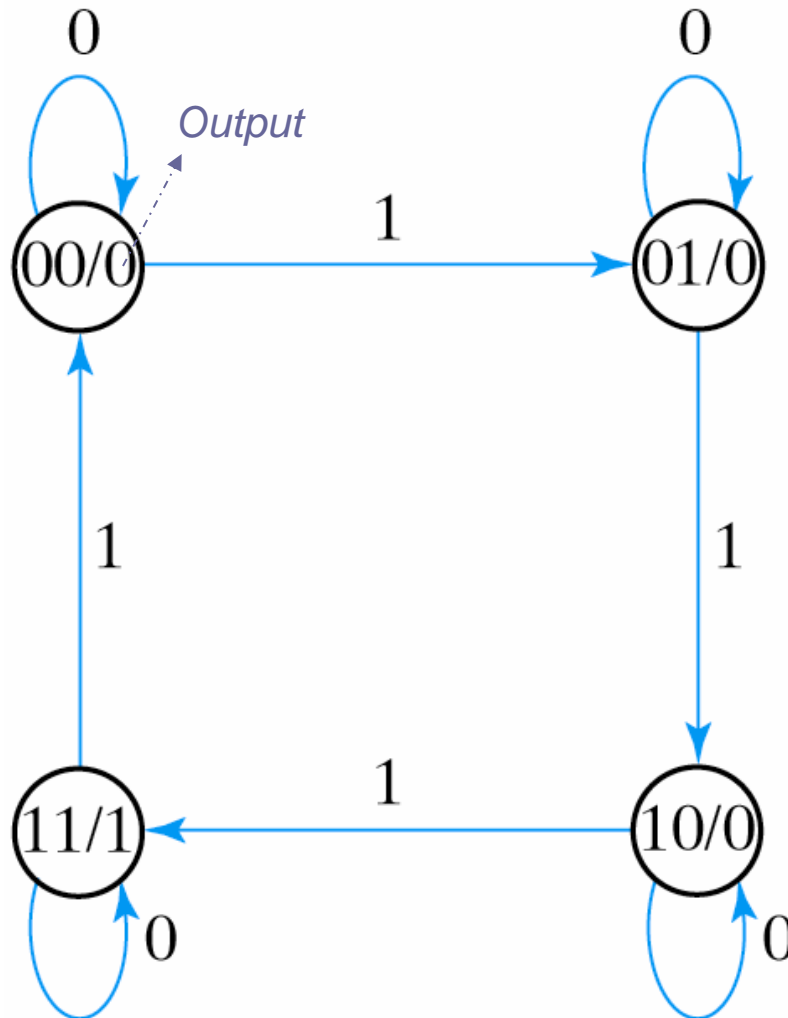

**Moore Machine**

Output depends on current state ONLY

# Structural Description of FSM

```

module Tcircuit (x,y,A,B,CLK,RST);
  input x,CLK,RST;
  output y,A,B;
  wire TA,TB;
  //Flip-flip input equations
  assign TB = x,
          TA = x & B;
  //Output equation
  assign y = A & B;
  //Instantiate T flip-flops
  T_FF BF (B,TB,CLK,RST);
  T_FF AF (A,TA,CLK,RST);
endmodule
  /*****/
  //T flip-flop
  module T_FF (Q,T,CLK,RST);
    output Q;
    input T,CLK,RST;
    reg Q;
    always @ (posedge CLK or negedge RST)
      if (~RST) Q = 1'b0;
      else Q = Q ^ T;
  endmodule


```

```

//Stimulus for testing sequential circuit
module testTcircuit;
  reg x,CLK,RST; //inputs for circuit
  wire y,A,B; //output from circuit
  // instantiate circuit
  Tcircuit TC (x,y,A,B,CLK,RST);
  initial
    begin
      RST = 0;
      CLK = 0;
      #5 RST = 1;
      repeat (16)
        #5 CLK = ~CLK;
    end
  initial
    begin
      x = 0;
      #15 x = 1;
      repeat (8)
        #10 x = ~x;
    end
endmodule


```

# Timing Diagram of FSM

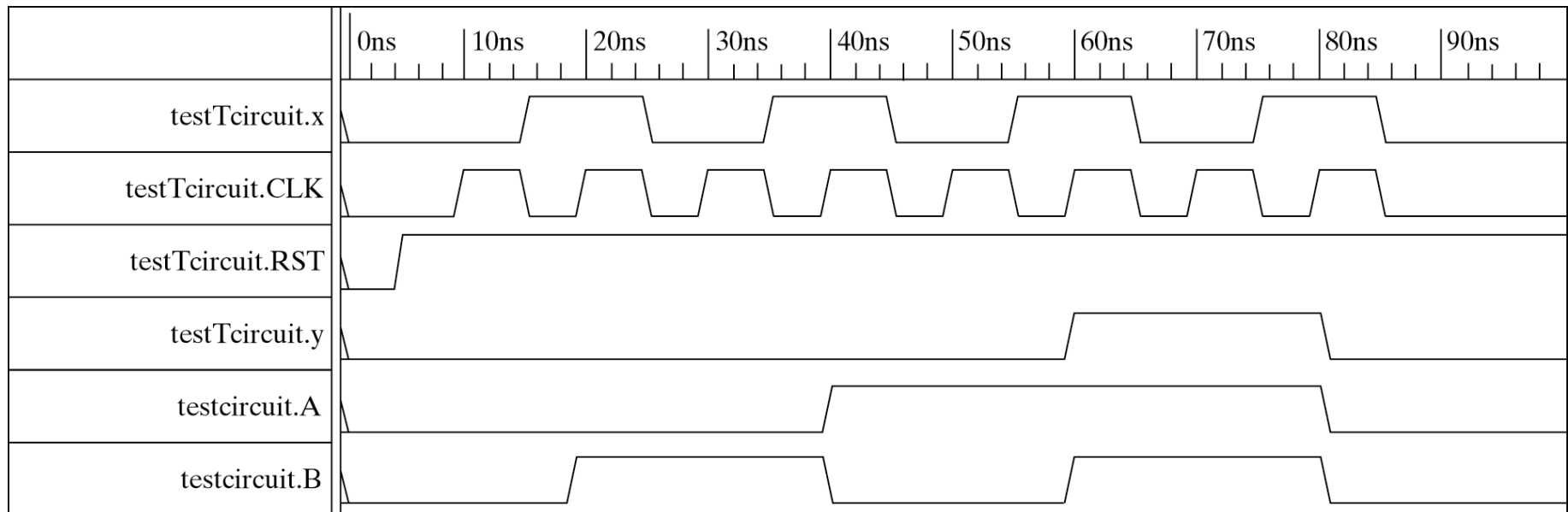

*What if Mealy FSM?*

# Example of a Mealy Glitch

 

# Important Book Chapter

- Chapter 5 in textbook

# References

- Lecture Notes of Dr. Sebastian Magierowski – Fall 2013
- “Digital Design”, Morris Mano , Prentice Hall
- “Digital Fundamentals (10<sup>th</sup> Edition)”, Thomas L. Floyd, Prentice Hall, 2010
- [http://ece.gmu.edu/coursewebpages/ECE/ECE448/S10/cpk.auc.dk/education/SSU-2007/mm10/ssu\\_mm10.pdf](http://ece.gmu.edu/coursewebpages/ECE/ECE448/S10/cpk.auc.dk/education/SSU-2007/mm10/ssu_mm10.pdf)
- [www.ece.cmu.edu/~thomas/VSLIDES.pdf](http://www.ece.cmu.edu/~thomas/VSLIDES.pdf)
- [http://ece.gmu.edu/courses/ECE448/index\\_S06.htm](http://ece.gmu.edu/courses/ECE448/index_S06.htm)
- MIT Lecture Notes on:  
<http://www.ece.concordia.ca/~asim>