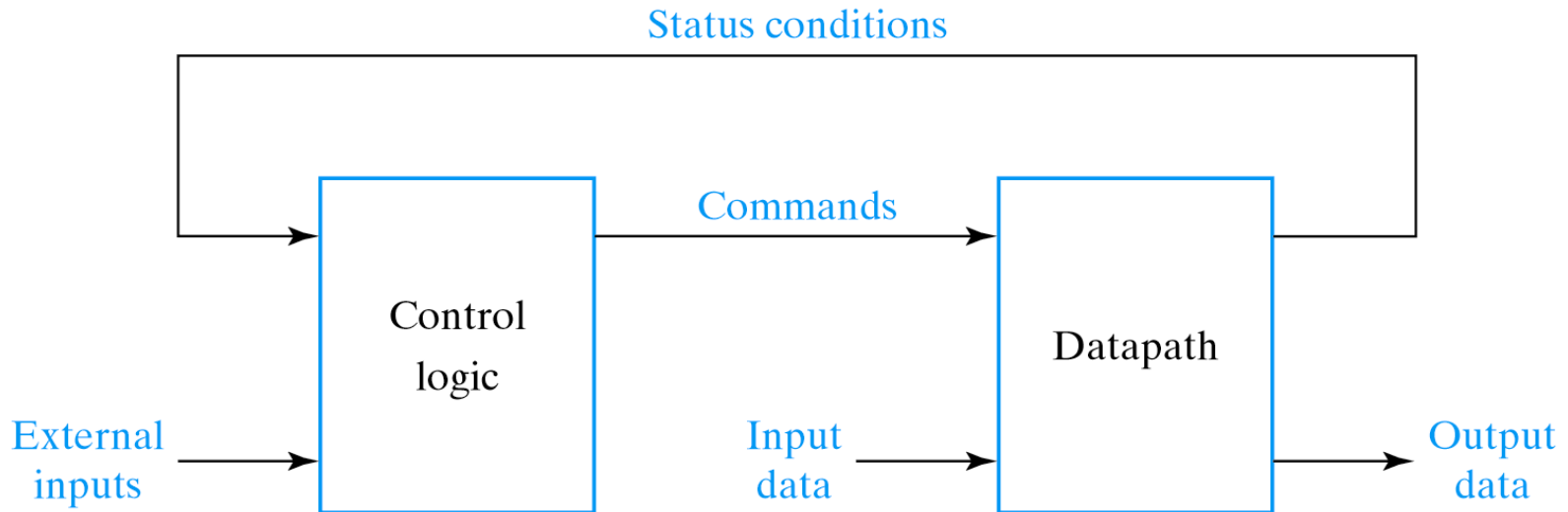


EECS 3201: Digital Logic Design Lecture 15

Ihab Amer, PhD, SMIEEE, P.Eng.


Structure of a Typical Digital System




Control and Datapath Interaction

Elements Used in ASM Charts

(1/2)

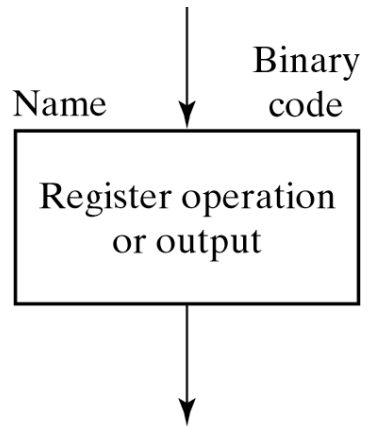


(a) General description

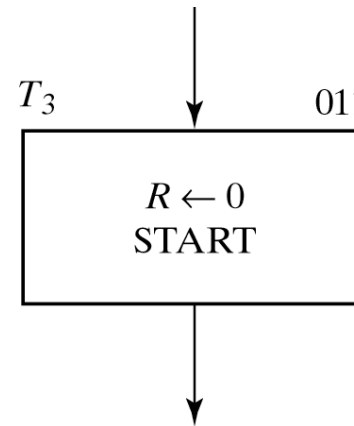


(b) Specific example

State Box

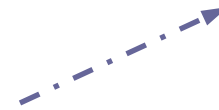

Decision Box

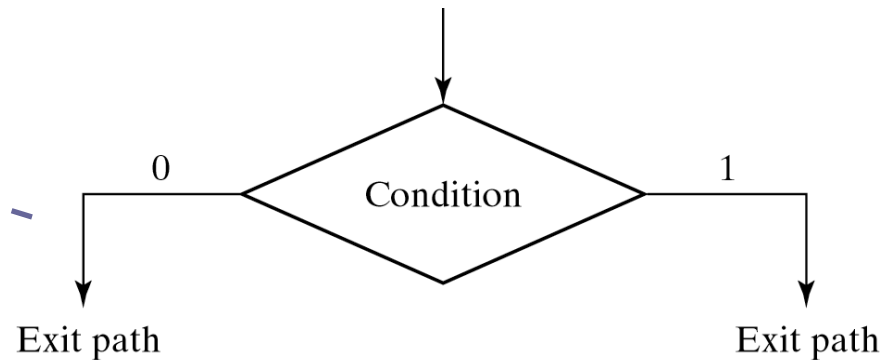


Elements Used in ASM Charts


(2/2)

Conditional Box

From exit path of decision box

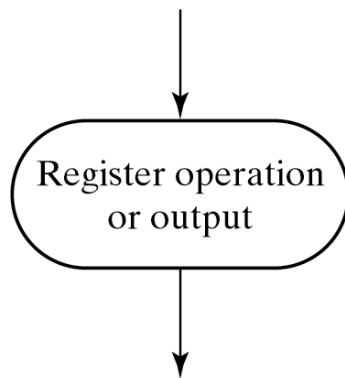

(a) General description

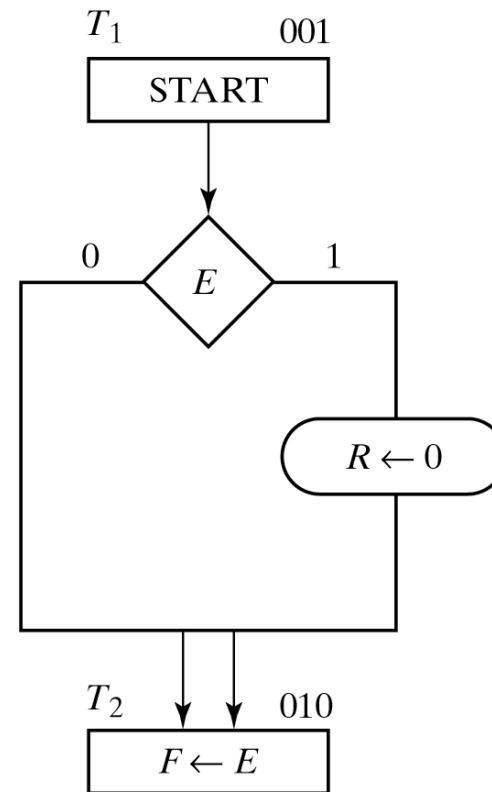


(b) Example with conditional box

Design with MUXs

- When binary assignment is used, the sequential circuit of a control unit typically consist of: flip-flops, decoder, and logic gates.
- Replacing the gates with MUXs results in a regular pattern of 3 levels of components:
 - MUXs that determine the next state
 - Flip-flops that hold the present binary state
 - Decoder that provide a separate o/p for each state
- These 3 types of components are pre-defined standard cells in many ICs


Example (1/4)

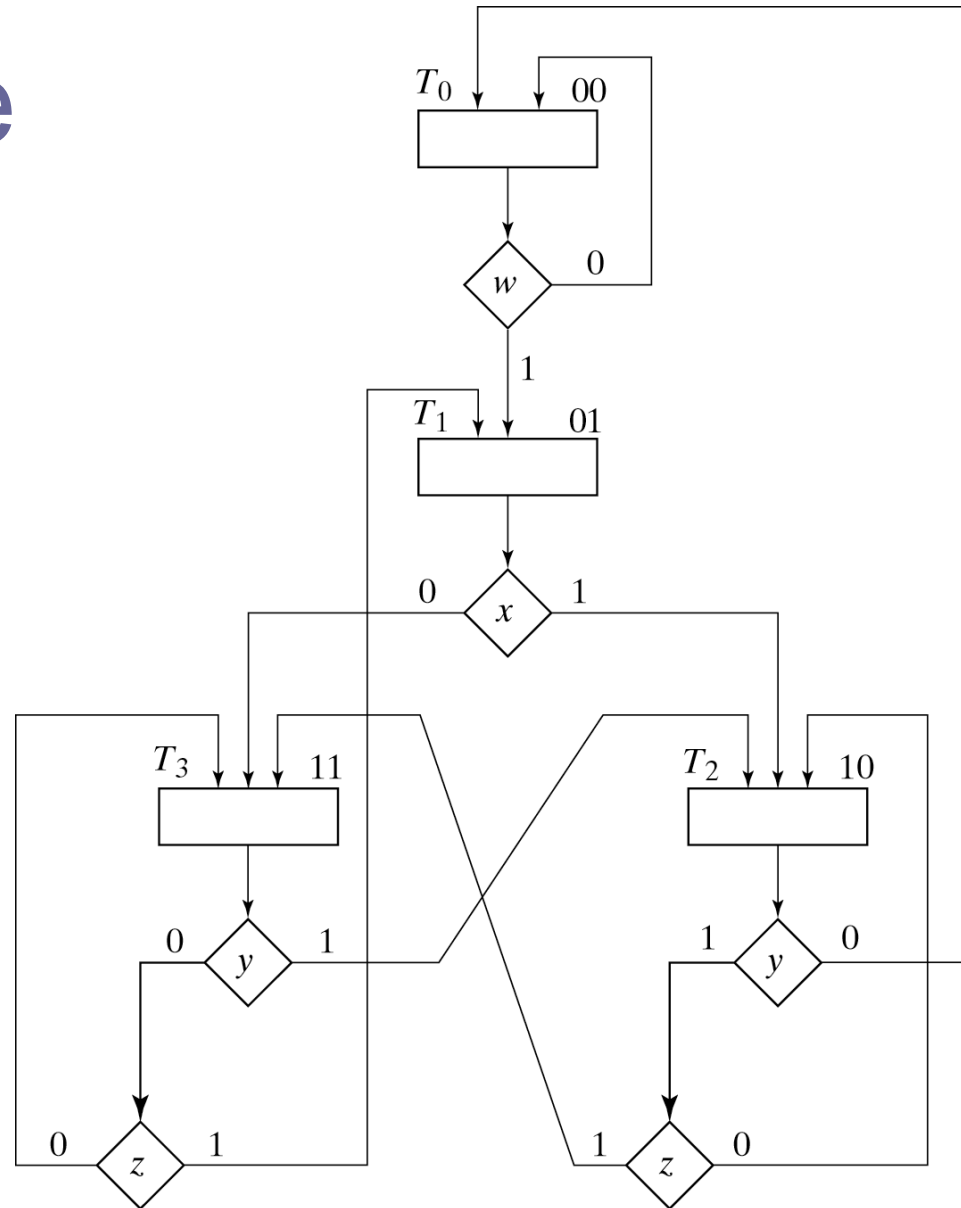

Example of ASM Chart with Four Control Inputs

Example

(2/4)

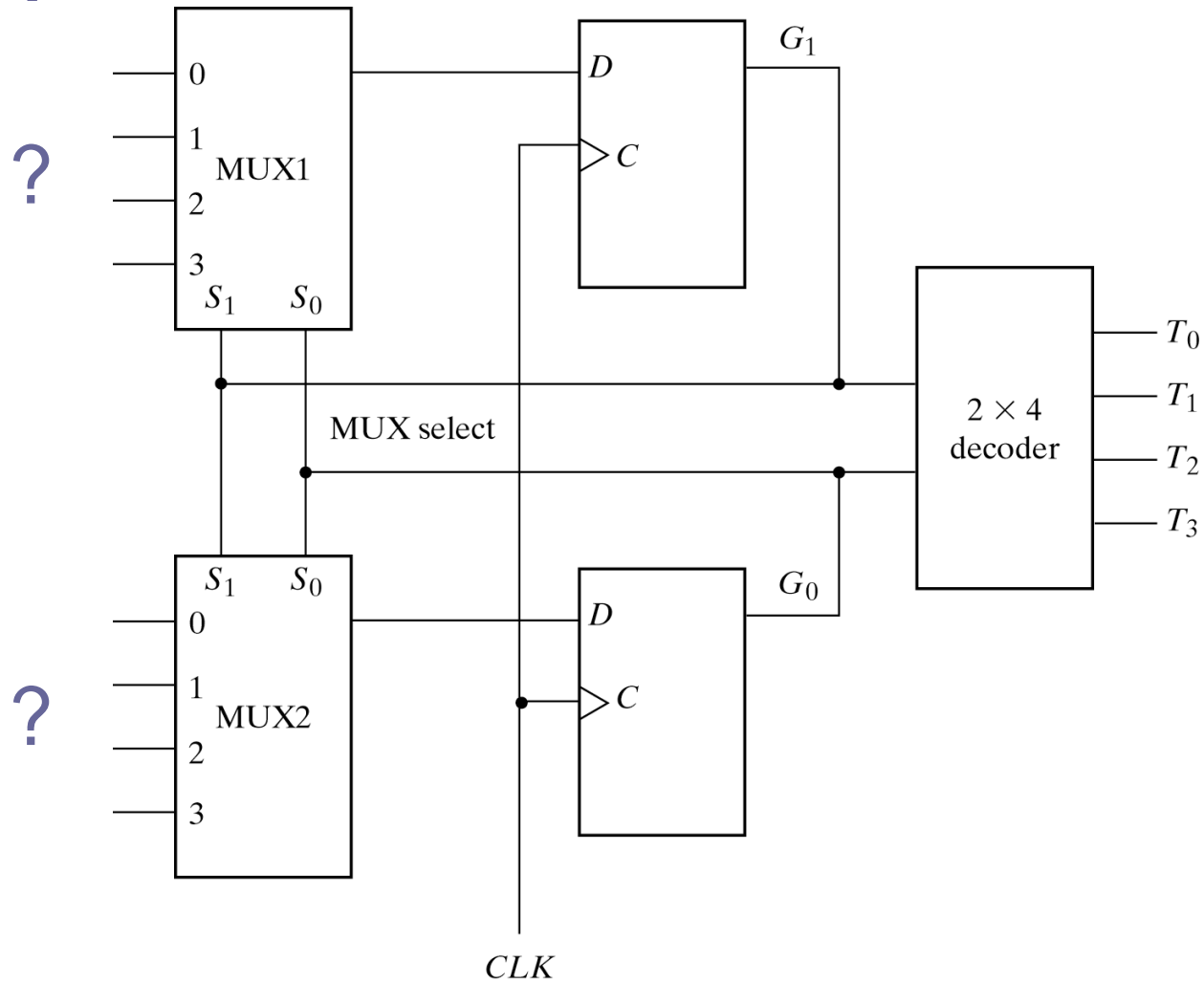


Example

(3/4) – MUX Input Conditions


Present State		Next State		Input Conditions	Inputs	
G_1	G_0	G_1	G_0		MUX1	MUX2
0	0	0	0	w'		
0	0	0	1	w	0	w
0	1	1	0	x		
0	1	1	1	x'	1	x'
1	0	0	0	y'		
1	0	1	0	yz'	$yz' + yz = y$	yz
1	0	1	1	yz		
1	1	0	1	$y'z$		
1	1	1	0	y	$y + y'z' = y + z'$	$y'z + y'z' = y'$
1	1	1	1	$y'z'$		

Example

(4/4)

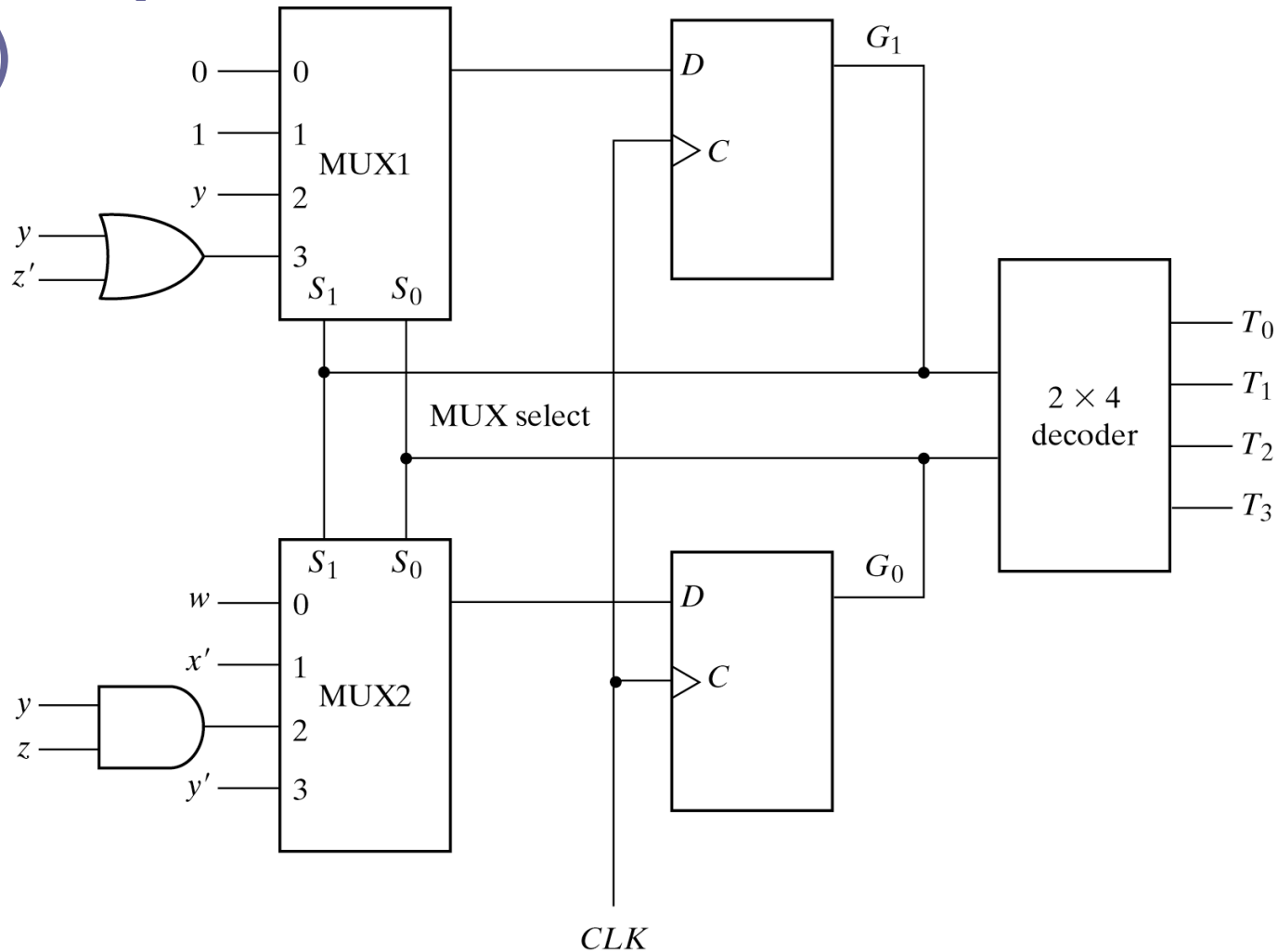


Example – Count the number of 1's

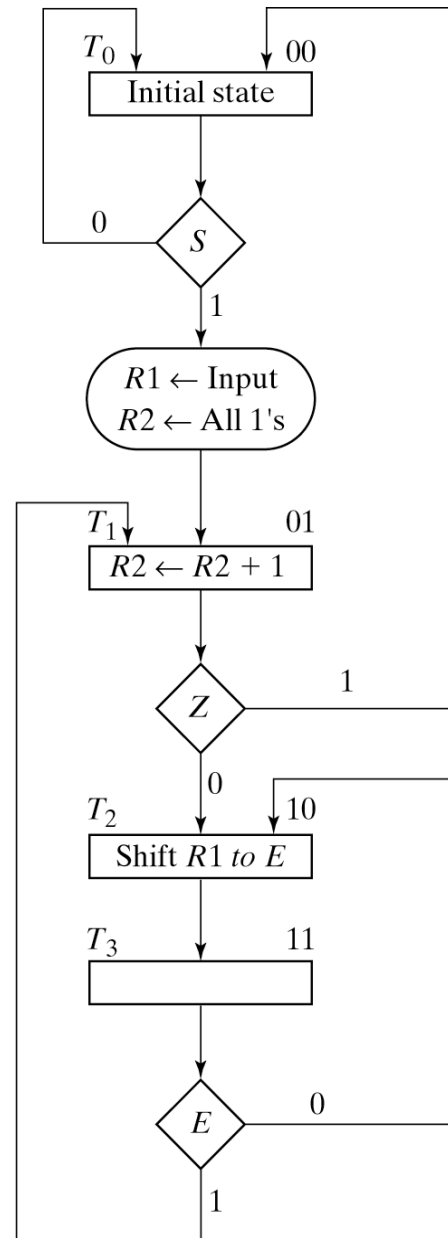


ASM Chart for Count-of-Ones Circuit

Datapath

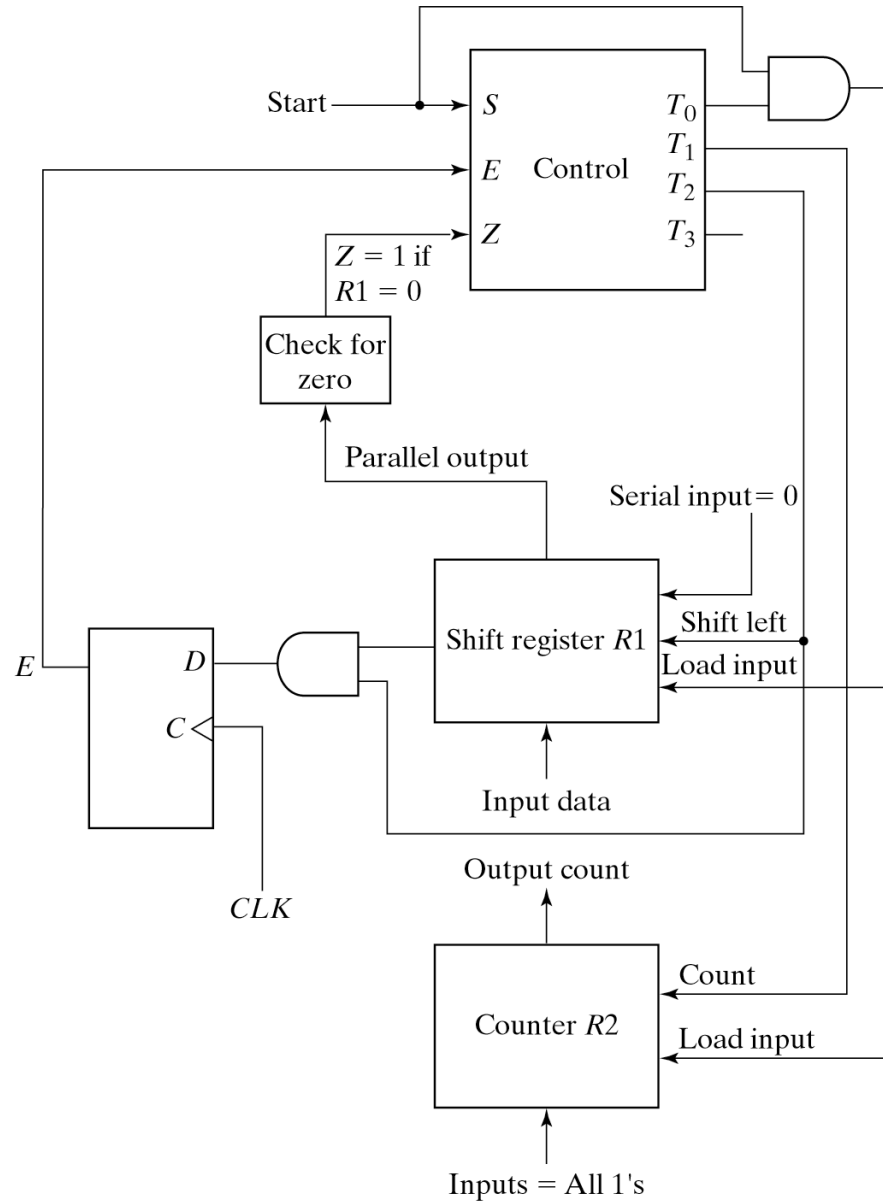

Block Diagram for Count-of-Ones


Control Implementation

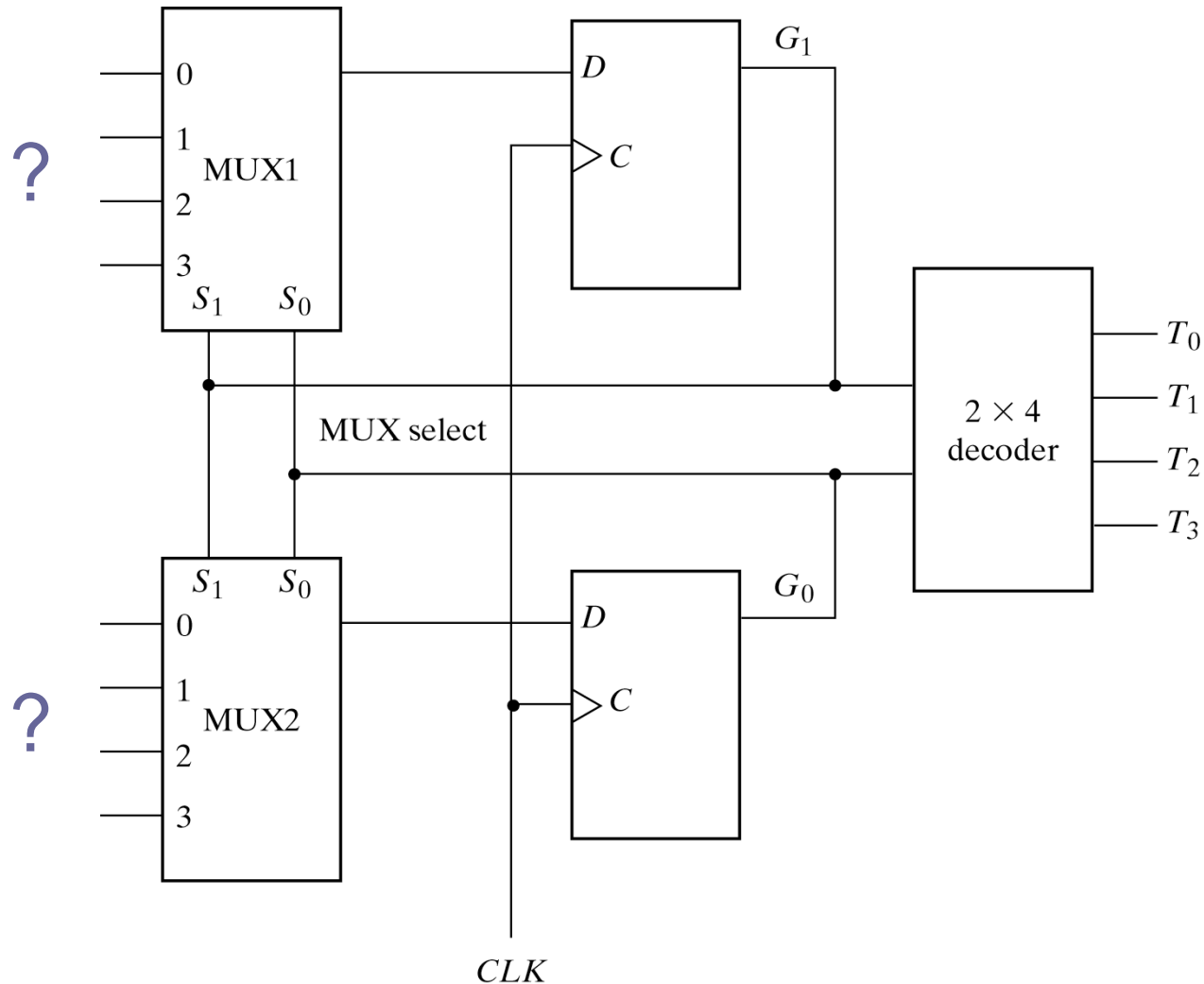

MUX Input Conditions

Present State		Next State		Input Conditions	Inputs	
G_1	G_0	G_1	G_0		MUX1	MUX2
0	0	0	0	S'		
0	0	0	1	S	0	S
0	1	0	0	Z		
0	1	1	0	Z'	Z'	0
1	0	1	1	None	1	1
1	1	1	0	E'		
1	1	0	1	E	E'	E

Control Implementation

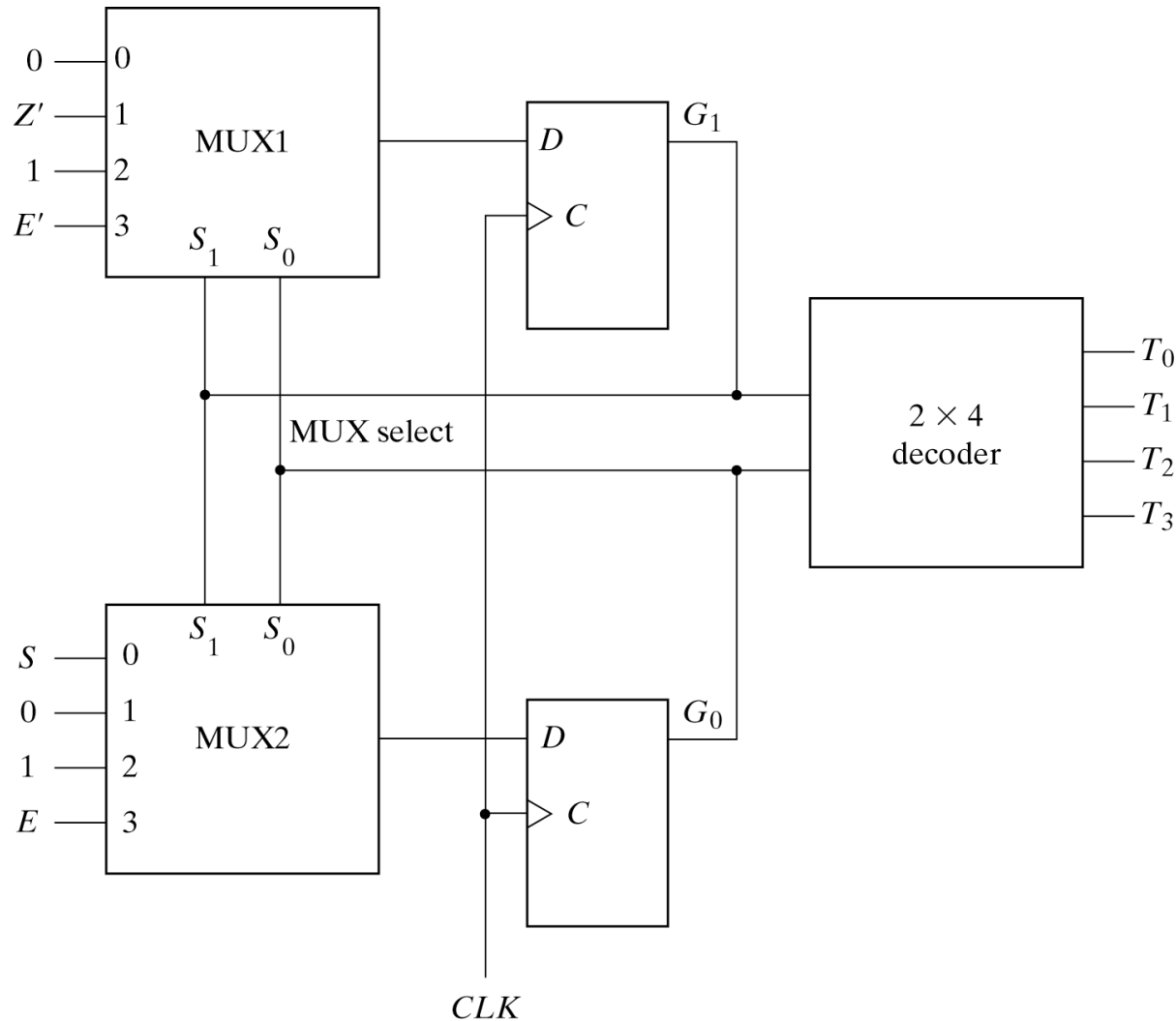

Corresponding Chapter in Textbook

- Chapter 8 (*entire chapter*)
- Reading Assignments
 - Verilog HDL code (behavioral and structural) for the design example(s) given in the lecture (try to implement it yourself)
 - Design Example – Binary Multiplier
 - Design using one-hot assignment

References

- Digital Design, M. Morris, Mano