






EECS 3201: Digital Logic Design Lecture 3

Ihab Amer, PhD, SMIEEE, P.Eng.

Logic Gates


- **Circuit elements**
- A representation of the physical instantiation of a logic function
- Single-input
 - NOT gate, buffer
- Two-input
 - AND, OR, XOR, NAND, NOR, XNOR
- Multiple-input
- Combine these into a **circuit schematic** consisting of graphical symbols

Basic Gates

     

Single-Input Logic Gate


NOT

 

$$Y = \bar{A}$$

A	Y
0	1
1	0

BUF

 

$$Y = A$$

A	Y
0	0
1	1

Two-Input Logic Gates


AND



$$Y = AB$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

OR

 


$$Y = A + B$$

A	B	Y
0	0	
0	1	
1	0	
1	1	



Transistors

 - Logic gates built from transistors
- 3-ported voltage-controlled switch
 - 2 ports connected depending on voltage of 3rd
 - d and s are connected (ON) when g is 1



MOSFET

**NMOS Transistor
(n-channel MOSFET)**

 
 


n-channel

open when voltage at G is low
closed when voltage at G is high

**PMOS Transistor
(p-channel MOSFET)**

poly-crystalline silicon
gate electrode

  


p-channel


closed when voltage at G is low
open when voltage at G is high

Two MOS Transistor Types (CMOS)


nMOS

 




$g = 0$

 

$g = 1$

 


pMOS

 
 
 


Transistor Function


 
- nMOS: passes “good” 0’s, so connect source to GND
- pMOS: passes “good” 1’s, so connect source to V_{DD}



CMOS Basic Logic Gates

   


X	y
0 volts	3 volts
3 volts	0 volts

  

Logic Networks


 
- Larger circuit implemented by network of gates
 - A Logic Network/logic circuit



- One thing you must be able to do is **analyze logic networks**

Network Analysis

 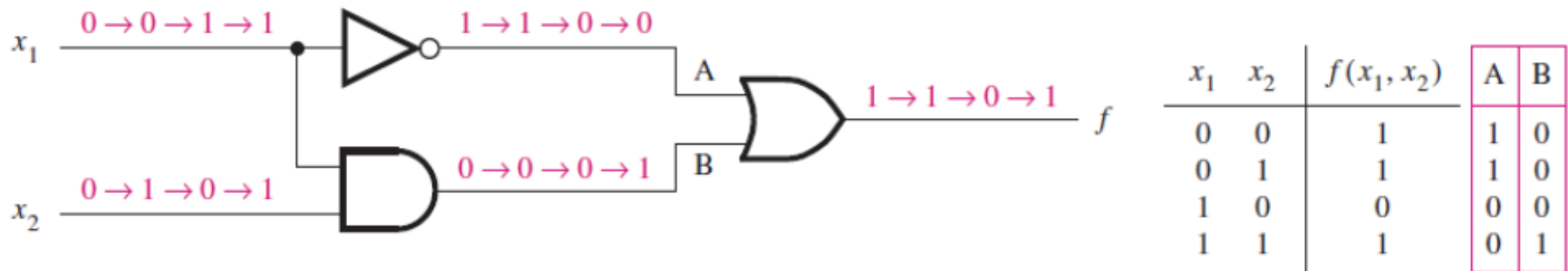- Figuring out what a network does
- Describe with **truth tables** and **timing diagrams**




Network Synthesis


- Another thing you must be able to do is **synthesize logic networks**
- Go from truth tables/timing diagrams to circuits
- Important to **synthesize** networks consisting of optimum arrangement of gates
 - minimize number of gates
 - reduce number of inputs
 - lower interconnect
 - reduce power, etc.

Basic Synthesis

- Synthesize this...

 

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

 

XOR




x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

- $L = y \cdot x' + y' \cdot x$
- $L = y \oplus x$

Polymorphic Mapping

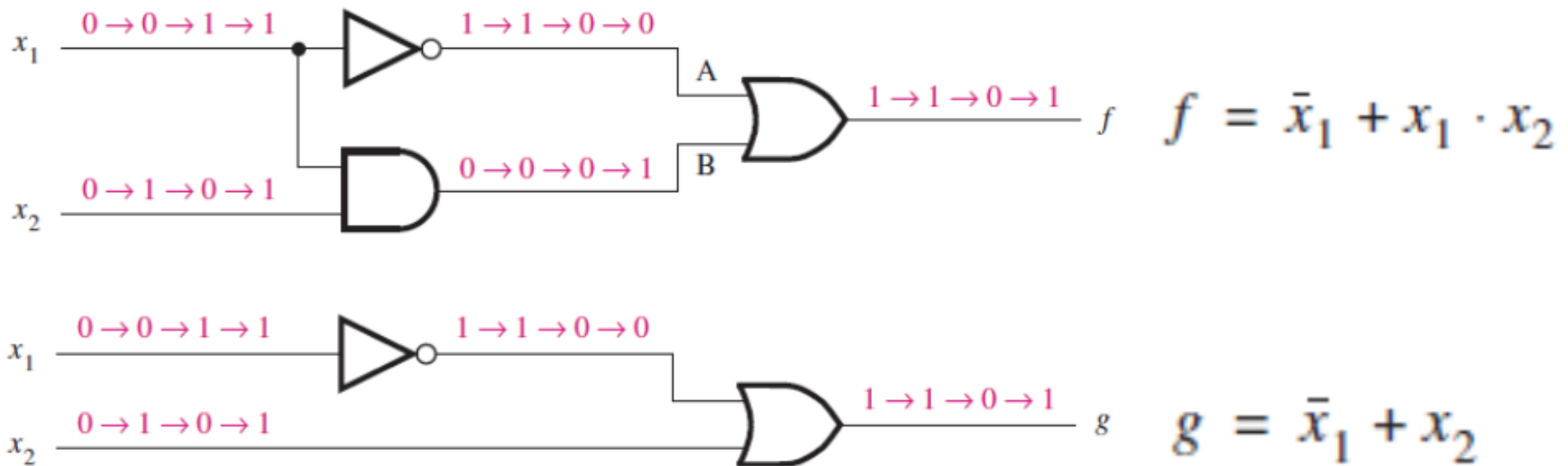- A logic function can be implemented in more than one way




- How do you quickly find the best one?
- Boolean Algebra!

From Previous Lecture(s)

- Modern digital systems use ICs almost exclusively in their designs
- Modern VLSI and ULSI ICs typically contain millions of transistors
- Traditional design approach provides insight and understanding of the problem
- However, it is inadequate for real problems
- Hence, the other design approach (CAD) is an essence for large (real) problems

Basic Design Methodology

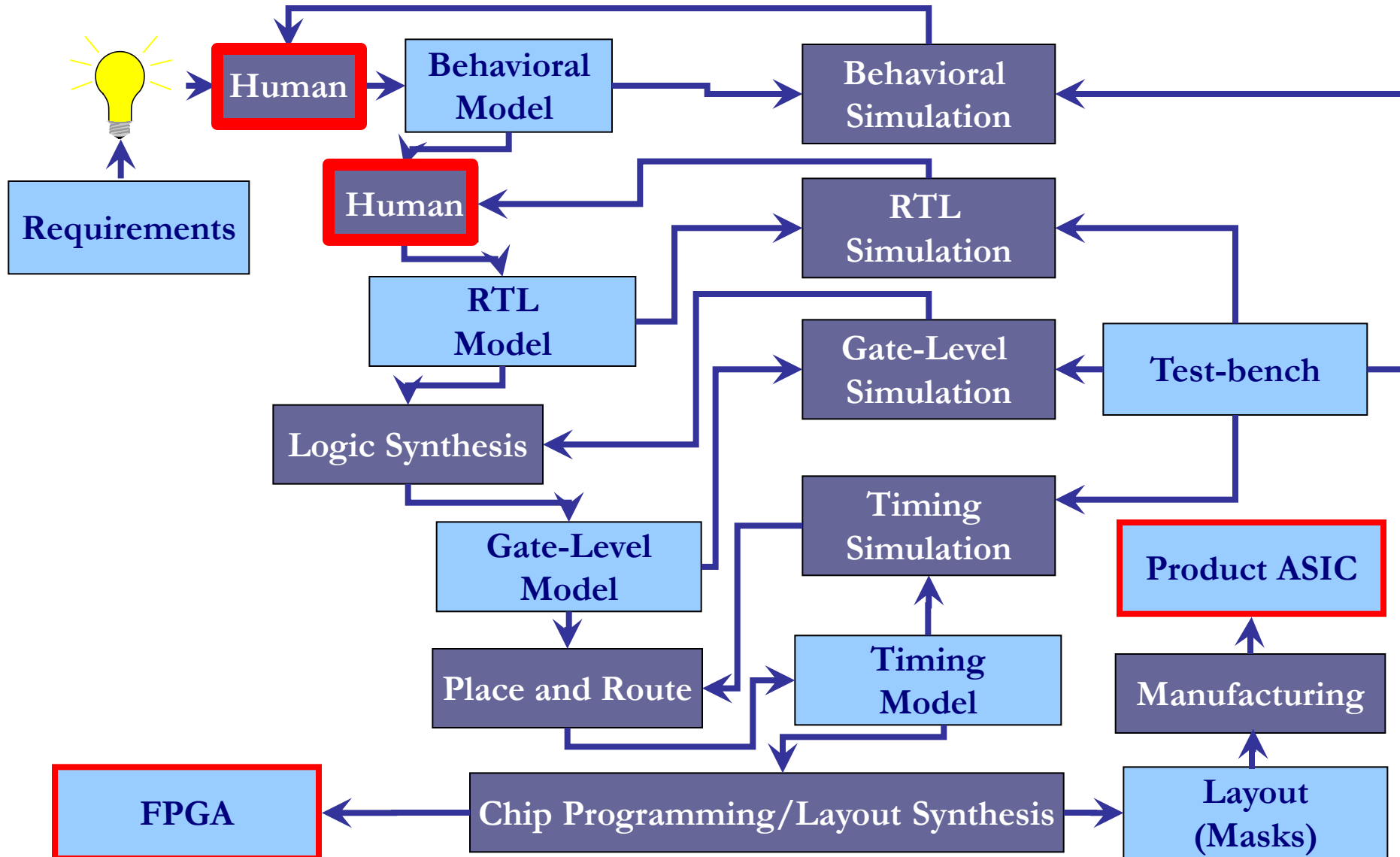

Our Task in the Flow

- *Modeling* the digital system based on the requirements
- Modeling can be at various levels of abstraction (will be discussed later)
- How to perform this modeling?

Using HDL: Hardware Description Language

Reasons for Modeling

- Requirements Specification
- Documentation
- Testing using Simulation
- Synthesis

Goal: Most reliable design process, with minimum cost and time

What is a HDL?

- A high-level computer language that can describe digital systems in textual form
- Two applications of HDL processing:
 - Logic Simulation
 - Logic Synthesis

HDL Applications

□ Logic Simulation

- A simulator translates the HDL description to a readable output such as *timing diagram*
- It predicts how the hardware will work before it is actually fabricated
- Functional errors can be corrected before actual fabrication
- Stimulus that tests the design is called *test-bench* (also written in HDL)

□ Logic Synthesis

- Deriving the *gate-level netlist* from the HDL
- Typically accompanied with optimization, and automated with computer software
- Restrictions on coding style for RTL model
- The outcome (netlist) is tool dependent

References

- Lecture Notes of Dr. Sebastian Magierowski – Fall 2013
- Digital Design, 3rd Edition, M. Morris, Mano
- Digital Design, 4th Edition, John Wakerly
- cpk.auc.dk/education/SSU-2007/mm10/ssu_mm10.pdf
- www.ece.cmu.edu/~thomas/VSLIDES.pdf
- <http://ece.gmu.edu/coursewebpages/ECE/ECE448/S10/>