



EECS 3201: Digital Logic Design Lecture 6

Ihab Amer, PhD, SMIEEE, P.Eng.


Synthesis by Boolean Algebra

- We used a combination of Boolean theorems to implement more efficient circuits
 - not obvious how to apply these
 - often tedious
- Karnaugh Map a much more systematic method
 - a graphical approach
 - a judicious application of the combining property
 - $a \cdot b + a \cdot \bar{b} = a$
 - $(a + b) \cdot (a + \bar{b}) = a$
 - combine terms with complementary variables

Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
- $PA + P\bar{A} = P$ (*combining property*)
- Translate truth table into grid with corresponding
- K-map arranged such that adjacent grids **vary by only one literal**


A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

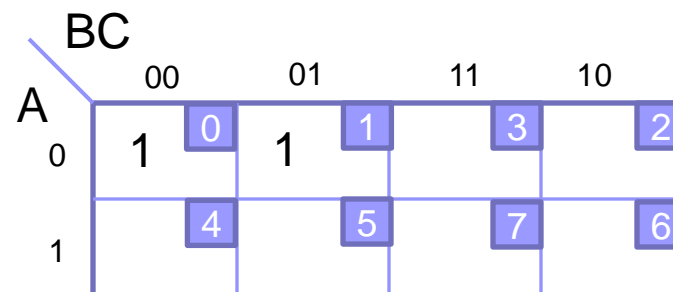

K-Map

- Circle 1's in adjacent squares
- In Boolean expression, include only literals whose true and complement form are **not** in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

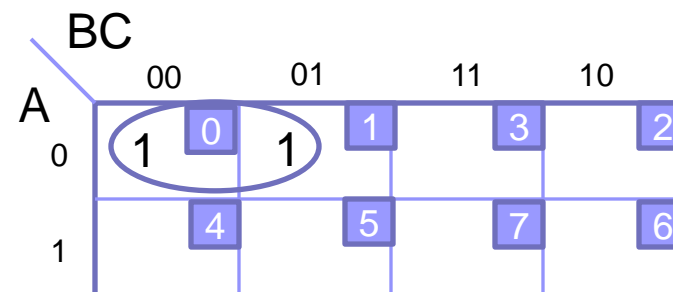

- $Y = \bar{A}\bar{B}$

K-Map Rules

- Every 1 must be circled at least once
- Each circle must span a power of 2 (i.e. 1, 2, 4) squares in each direction
- Each circle must be as large as possible
- A circle may wrap around the edges
- A “don't care” (X) is circled only if it helps minimize the equation


K-Map Minimization Technique

- It is kind of a greedy approach
- Start by circling the largest possible #of 1's (according to the rules)
- Look at the remaining 1's, and circle the largest possible #of remaining 1's (your circle is allowed to cover 1's that were circled before)
- Stop when every 1 is circled at least once

3-Input K-Map

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

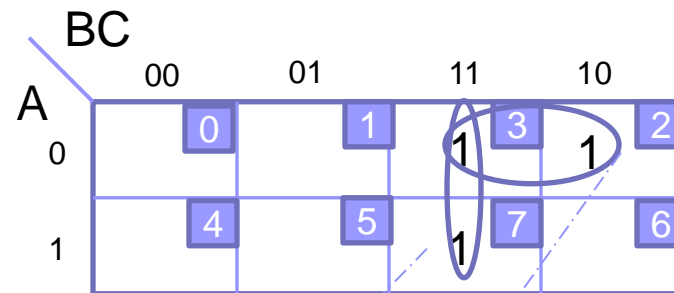


$$Y = BC + \bar{A}B$$

Example

$$f(x_1, x_2, x_3) = \Sigma m(1, 3, 4, 6, 7)$$

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

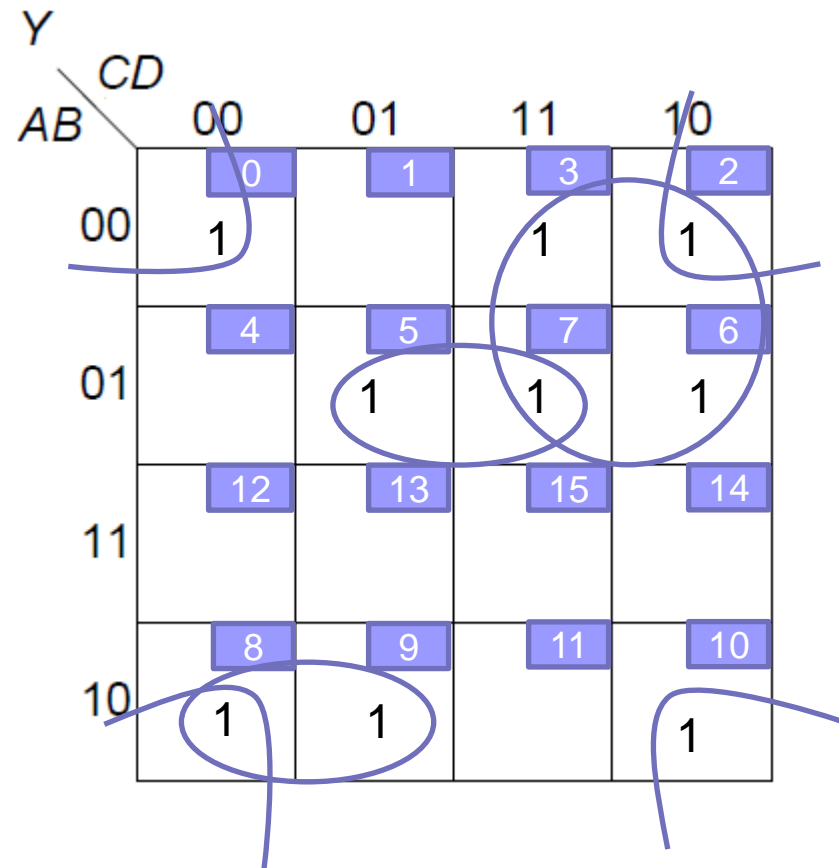

$$Y = \bar{A}C + \bar{B}\bar{D} + \bar{A}BD + A\bar{B}\bar{C}$$

K-Map with Don't Cares


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00				
	01				
	11				
	10				

An Aside on Don't Cares

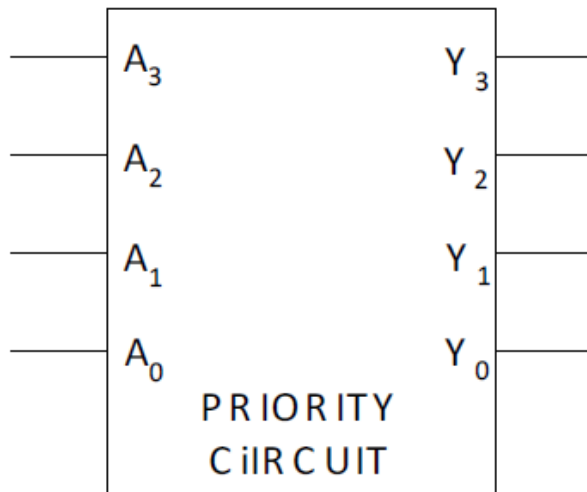- Example: Priority Circuit**

Output asserted
corresponding to
most significant
TRUE input




A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0

An Aside on Don't Cares

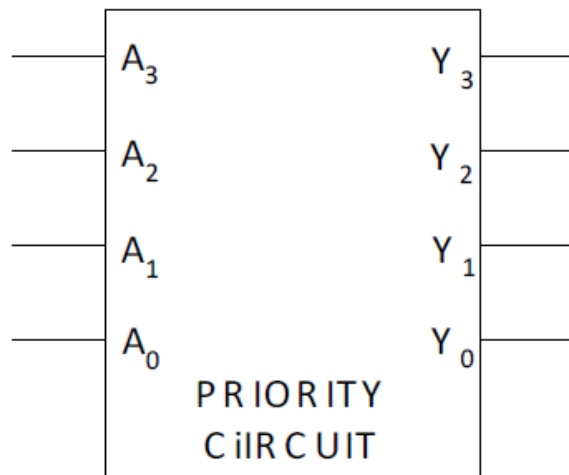
- Example: Priority Circuit**

Output asserted
corresponding to
most significant
TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

5-Variable Map



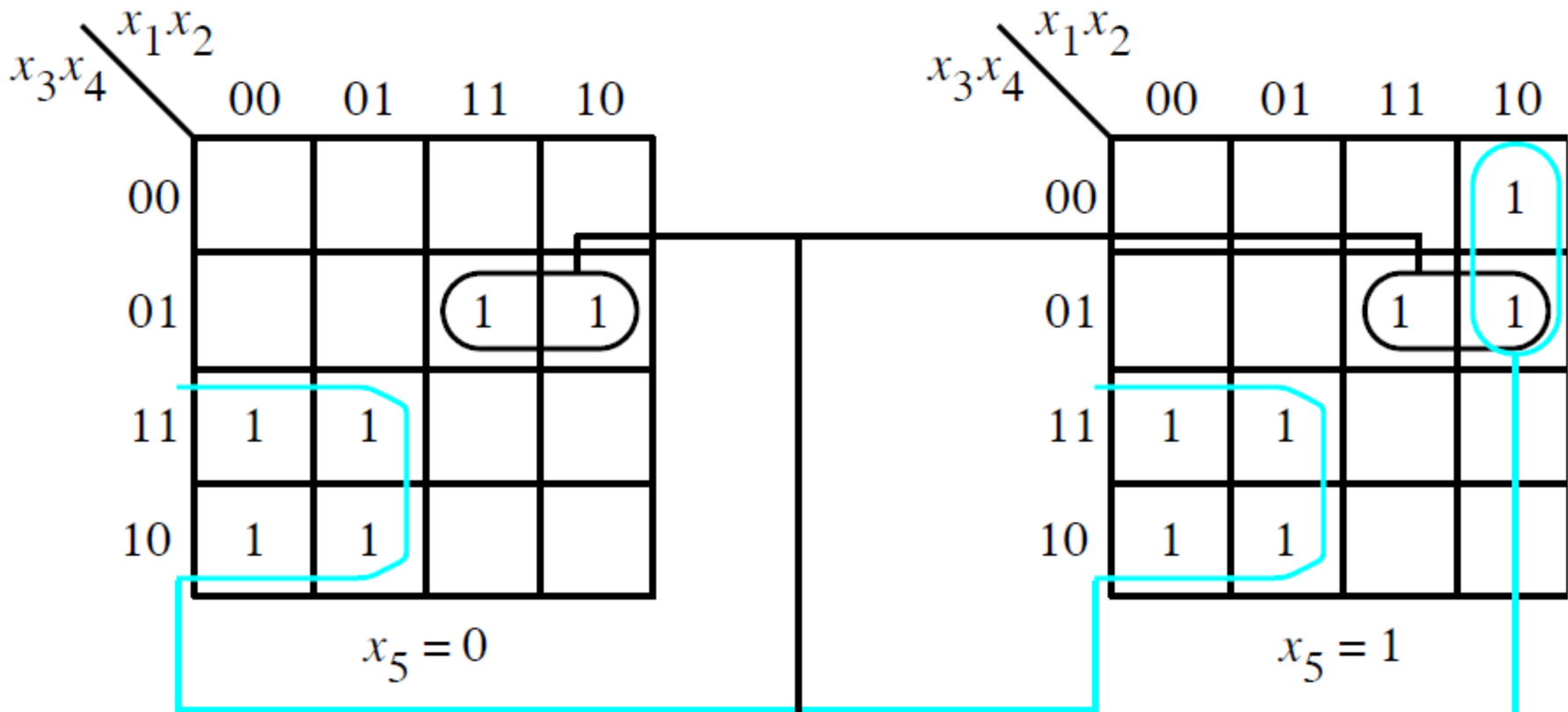


$x_5 = 0$

$x_5 = 1$

$$f_1 = \bar{x}_1x_3 + x_1\bar{x}_3x_4 + x_1\bar{x}_2\bar{x}_3x_5$$

1-bit Addition – The Half Adder

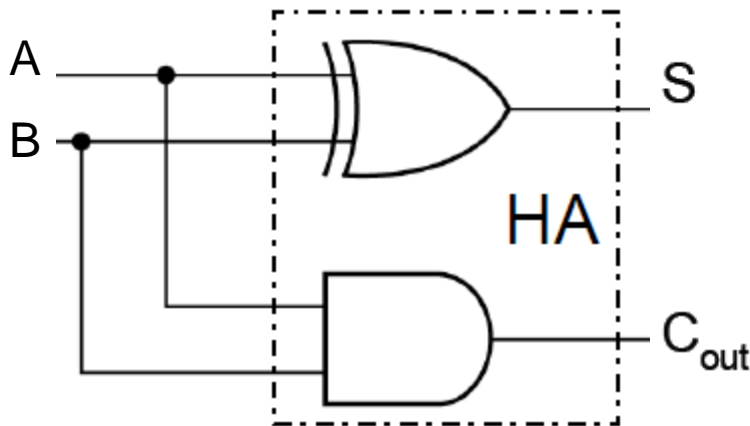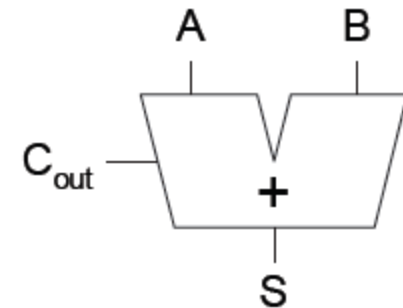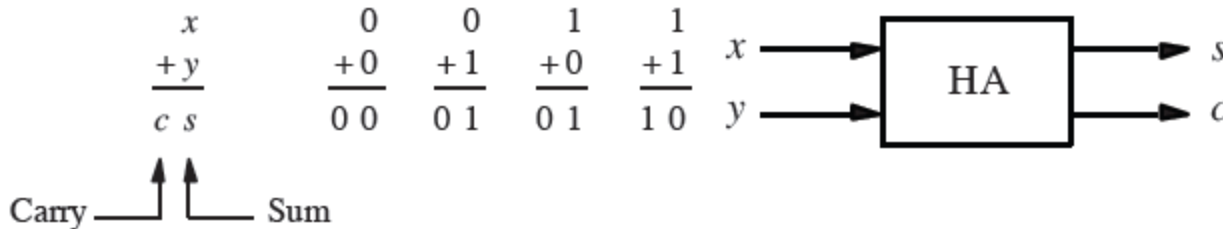

A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		


$$S =$$

$$C_{out} =$$

Multi-Bit Addition


Generated carries \longrightarrow 1 1 1 0
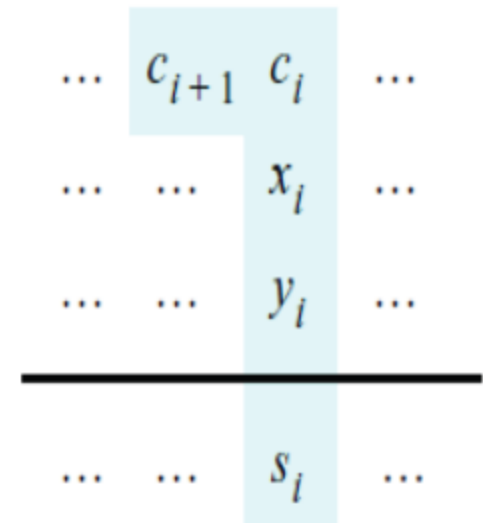
$$\begin{array}{r}
 X = x_4x_3x_2x_1x_0 \quad 01111 \quad (15)_{10} \\
 + Y = y_4y_3y_2y_1y_0 \quad +01010 \quad + (10)_{10} \\
 \hline
 S = s_4s_3s_2s_1s_0 \quad 11001 \quad (25)_{10}
 \end{array}$$



Bit position i

1-bit Addition – The Full Adder

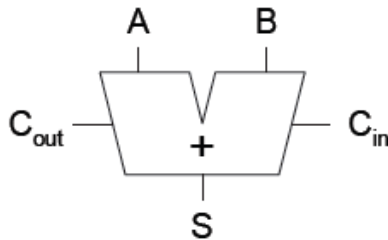


- A straightforward schematic

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S =$$

$$C_{out} =$$

Full Adder with 2 half adders

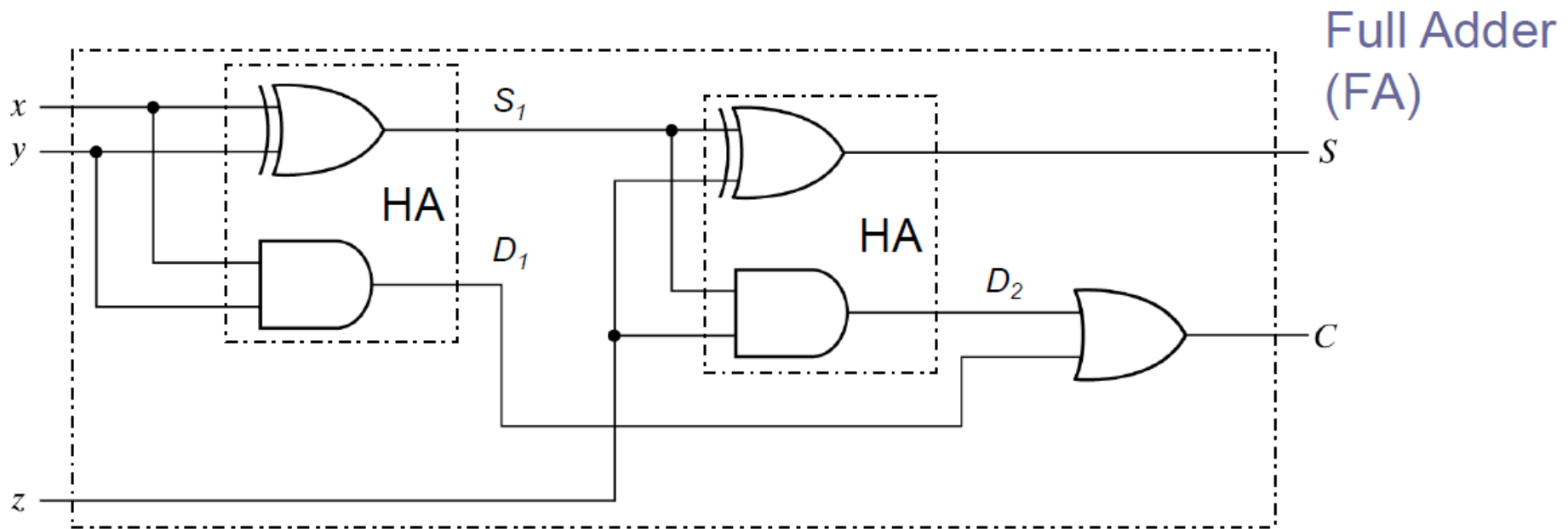


Carry-Ripple Adder

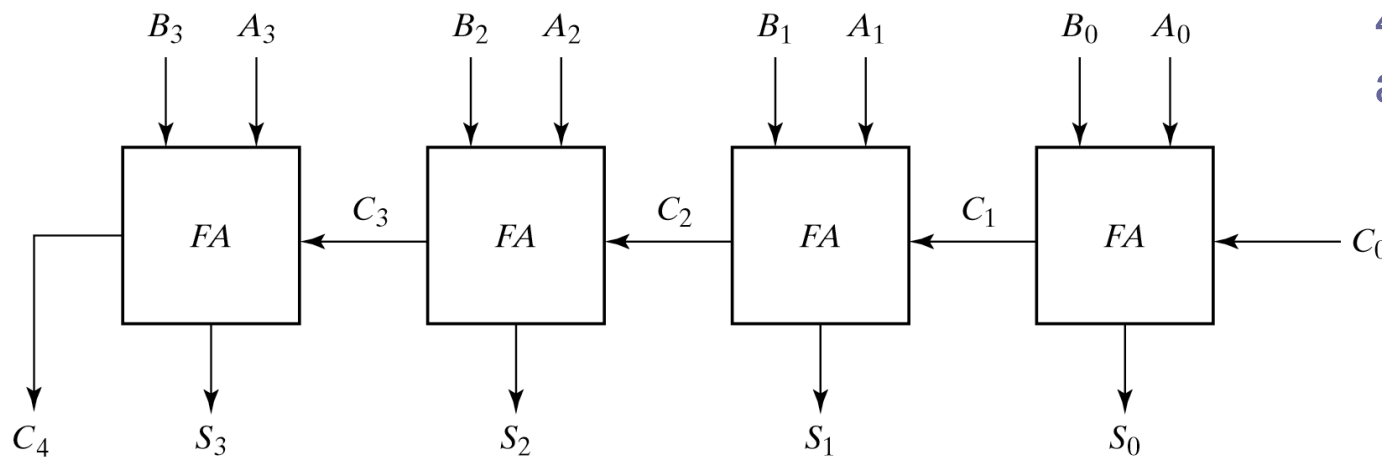

4-bit binary
adder

Adder/Subtractor

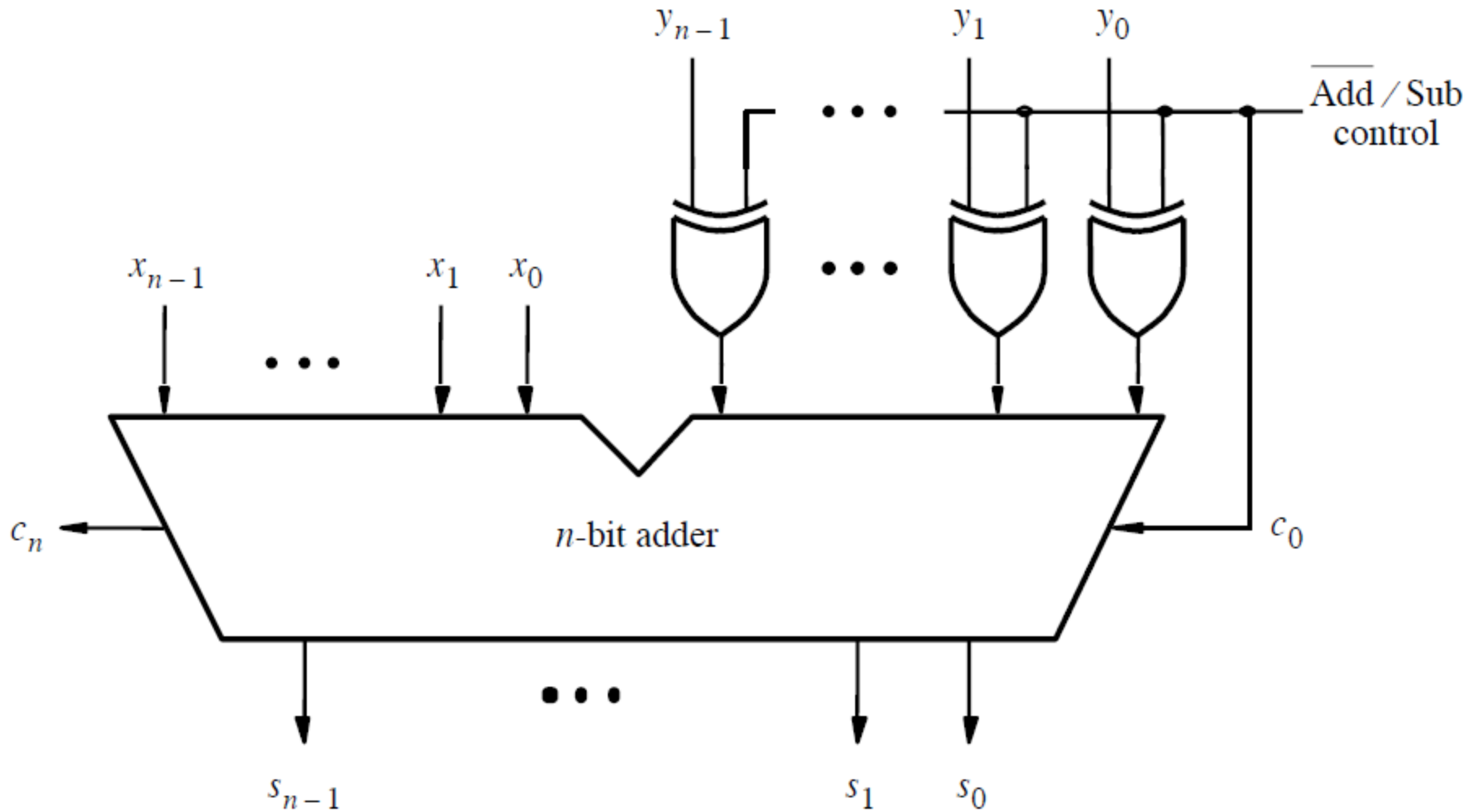

References

- Lecture Notes of Dr. Sebastian Magierowski –
Fall 2013