



EECS 3201: Digital Logic Design Lecture 8

Ihab Amer, PhD, SMIEEE, P.Eng.


Midterm Coming Soon!



- **Midterm** will be on Wednesday, October 22nd, 2014
- Exam will take place during the lecture time
- Exam will include all material of Lectures (1–8). This includes material on website + related material in textbook
- Verilog HDL is part of the content

Read-Only Memory (ROM)

 - A memory device in which permanent binary information is stored
- It is sometimes looked at as a programmable logic device



ROM Block Diagram

Types of ROM


- **Mask ROM:** The *programming* is done by the semiconductor company during the last fabrication process of the unit
- **PROM:** A fused link is burned open during the programming process. Once the PROM is programmed, it cannot be reversed
- **EPROM:** An erasable PROM that can be erased by exposure to UV light
- **EEPROM:** Can be erased and programmed with electrical pulses
- **Flash Memory:** High-density read/write memories that are nonvolatile. They have the ability to retain charge for years with no applied power

Programmable Logic Devices (PLDs)


- An IC with internal logic gates connected through electronic paths
- A logic function can be *programmed* into a PLD after manufacture
- Programming here refers to a hardware procedure, which specifies the bits that are inserted into the hardware configurations of the device

Gate Arrays

 - A typical PLD may have an array of hundreds to millions of gates interconnected through internal paths
- The figure shows the conventional and array logic symbols for a multiple input OR gate






(a) Conventional symbol

 


(b) Array logic symbol

Types of Combinational PLDs

   


Basic Configuration of Three PLDs

PROM Internal Structure

 

Internal Logic of a 32×8 ROM

Programmed PROM

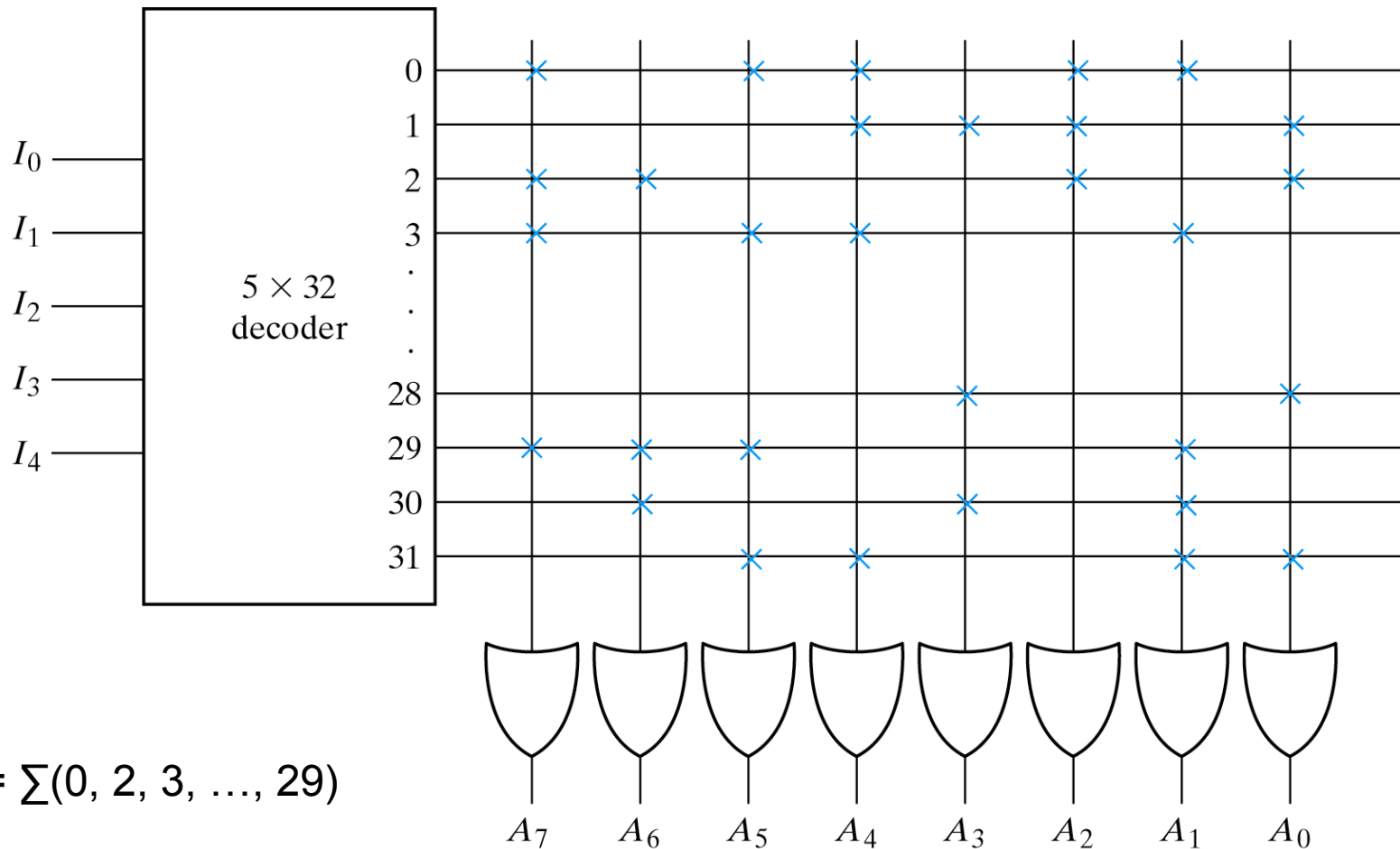


Programming the ROM

Reading Assignment

- Example 7.1 in Mano textbook

PLA

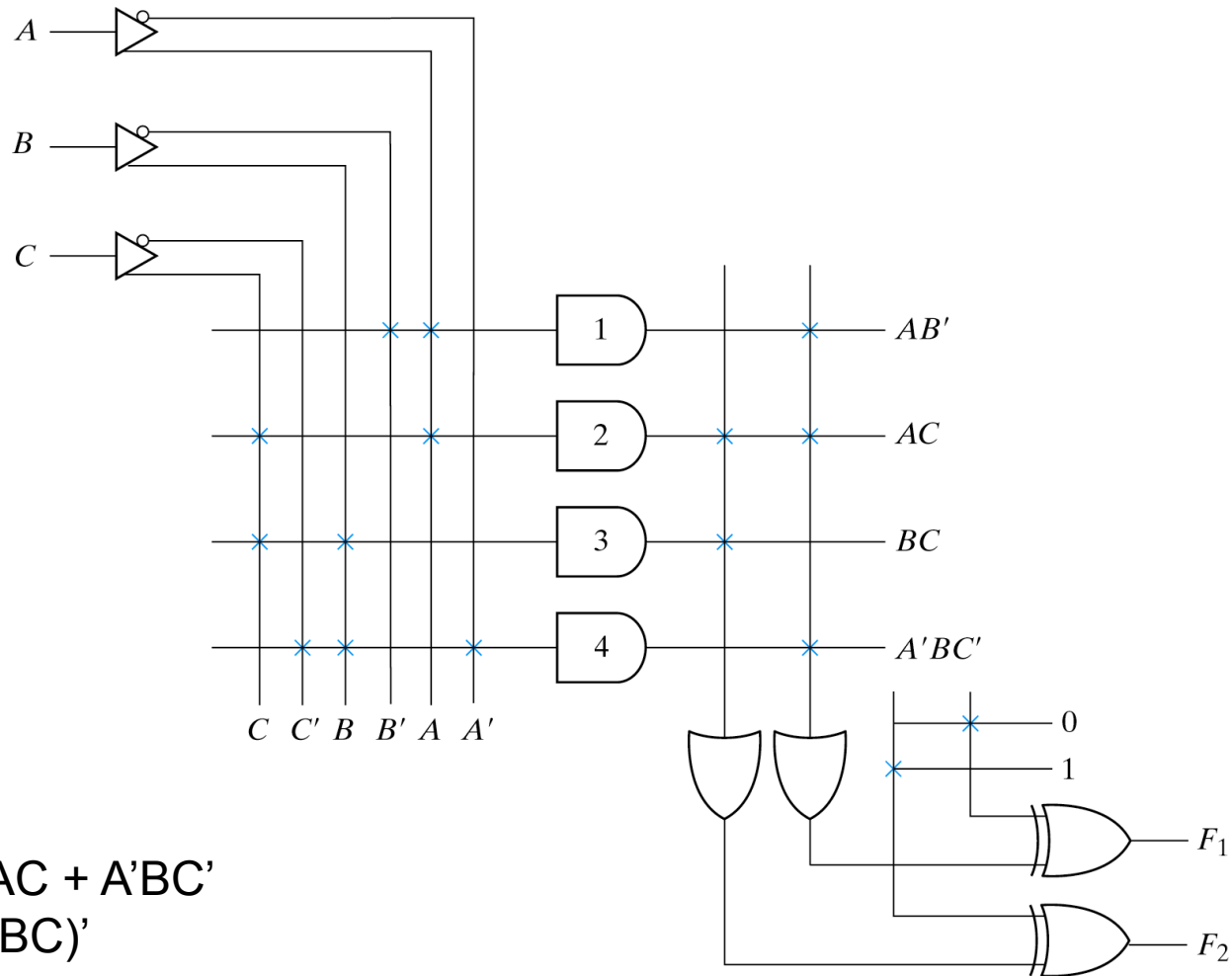

$$F_1 = AB' + AC + A'BC'$$


$$F_2 = (AC + BC)'$$

PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

Reading Assignment

- Refer to Table 7.5 in Mano textbook for the PLA Programming Table
- Example 7.2 in Mano textbook

PAL

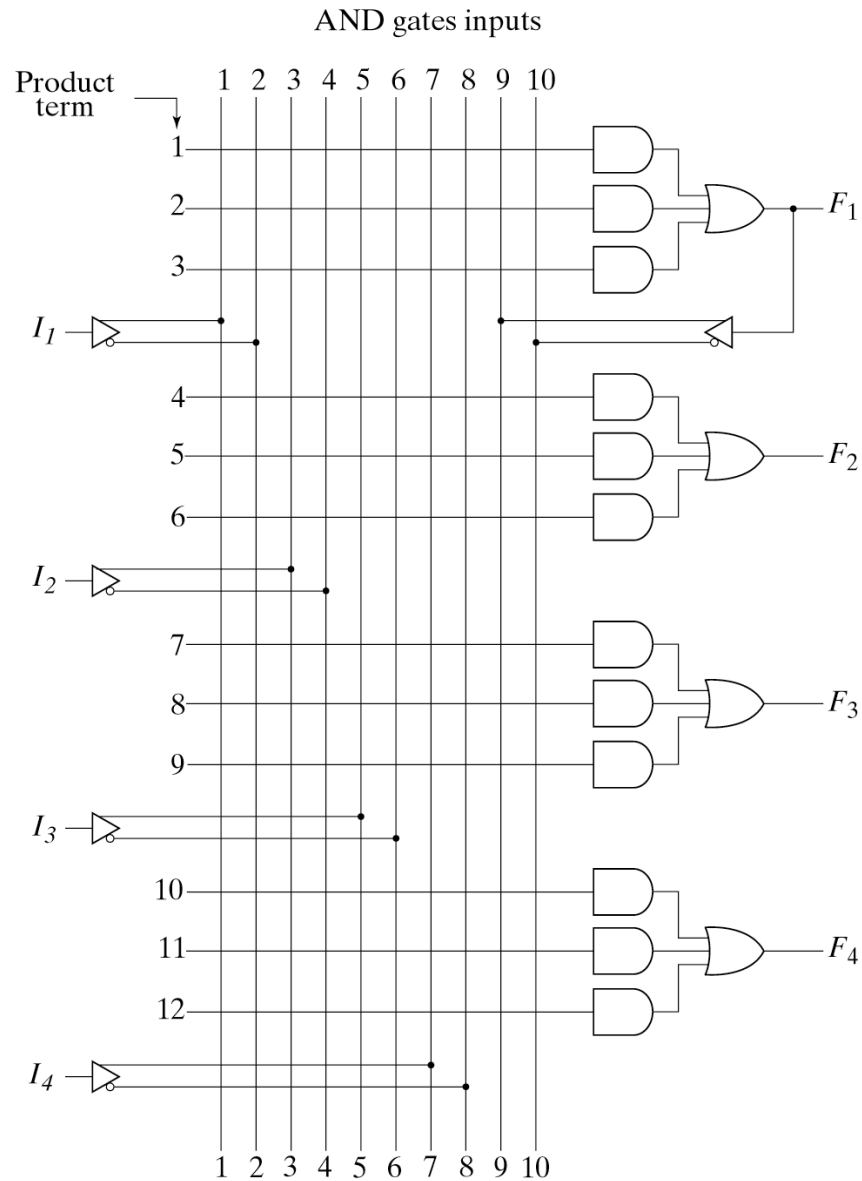

PAL with Four Inputs, Four Outputs, and Three-Wide AND-OR Structure

Programmed PAL


$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

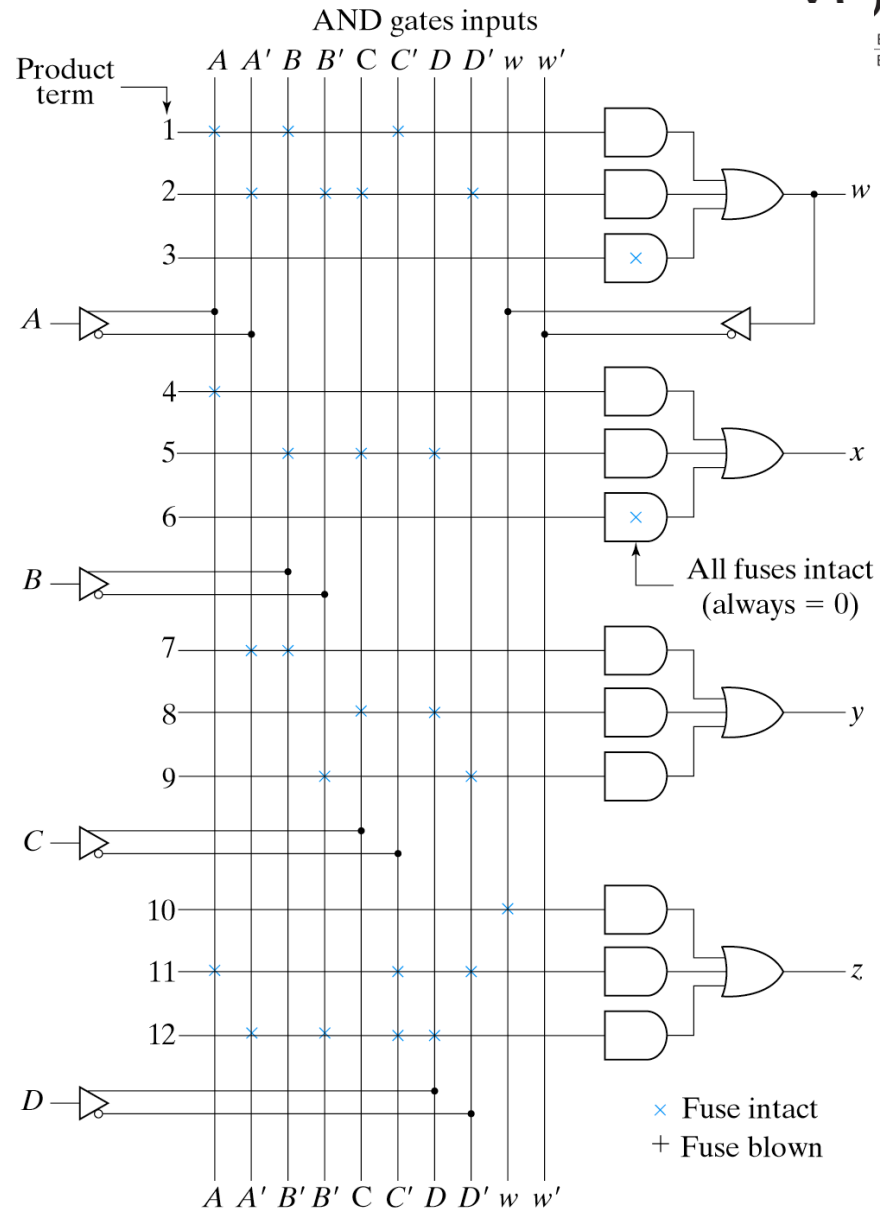

Fuse Map for PAL

Reading Assignment

- Table 7.6 in Mano textbook

Binary Coded Decimal (BCD)

- Using 4 binary numbers to represent decimal digits
- 82 => 1000_0010
- 18 => 1_1000
- How do you add these numbers?
 - If $X + Y = Z < 9$ nothing new
 - What if $Z > 9$?

Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001


BCD Addition

- 4-bit numbers addition is subject to a modulo-16 scheme (values 0-15)
- If they are used to represent numbers 0-9 only, whenever the sum exceeds 9 we have to add 6 to the sum to get the correct BCD representation

$$\begin{array}{r}
 X \quad 0111 \quad 7 \\
 + Y \quad + 0101 \quad + 5 \\
 \hline
 Z \quad 1100 \quad 12 \\
 \quad \quad + 0110 \\
 \hline
 \text{carry} \rightarrow 10010 \\
 \quad \quad \underbrace{\hspace{2cm}} \\
 \quad \quad S = 2
 \end{array}$$

$$\begin{array}{r}
 X \quad 1000 \quad 8 \\
 + Y \quad + 1001 \quad + 9 \\
 \hline
 Z \quad 10001 \quad 17 \\
 \quad \quad + 0110 \\
 \hline
 \text{carry} \rightarrow 10111 \\
 \quad \quad \underbrace{\hspace{2cm}} \\
 \quad \quad S = 7
 \end{array}$$

BCD 1-digit Adder

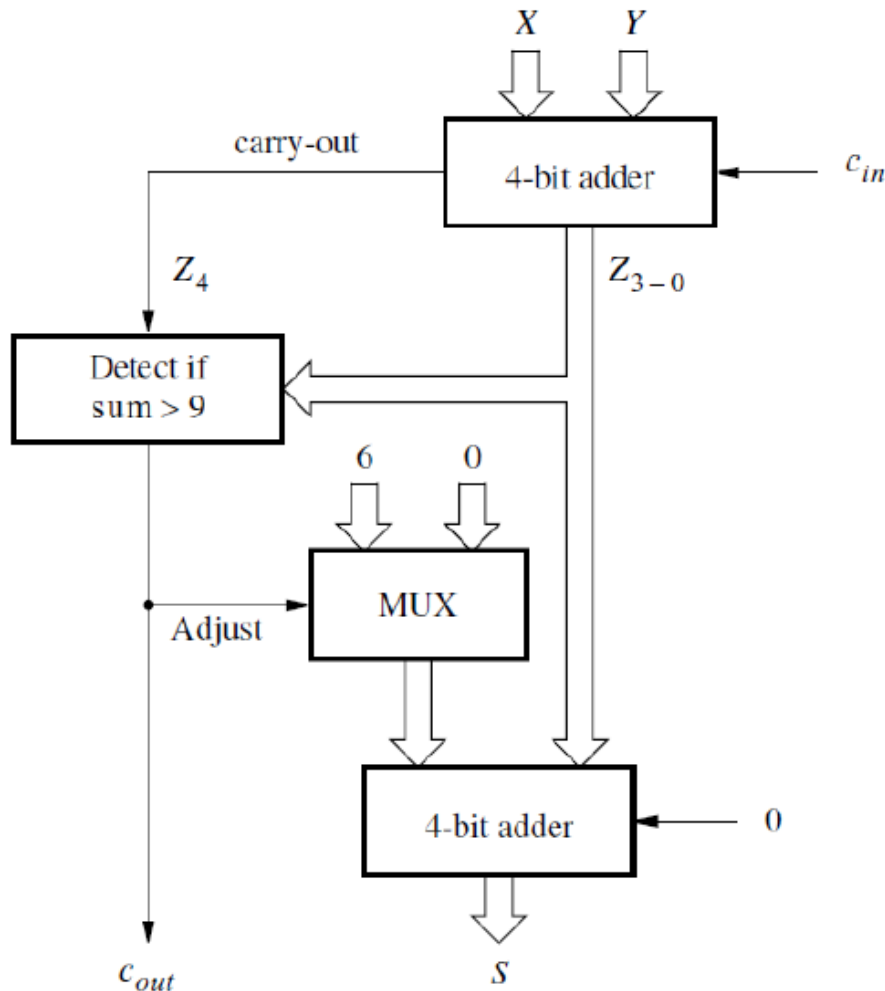

```

module bcdadd(Cin,X, Y, S, Cout);
  input Cin;
  input [3:0] X, Y;
  outputreg [3:0] S;
  outputreg Cout;
  reg [4:0] Z;

```

```

always@ (X, Y, Cin)
begin
  Z = X + Y + Cin;
  if (Z < 10)
    {Cout, S} = Z;
  else
    {Cout, S} = Z + 6;
end

```


```

endmodule


```

Comparator: Equality


Symbol

 

Implementation

 


Arithmetic Logic Unit (ALU)

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

ALU Design

 

$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & \sim B
101	A \sim B
110	A - B
111	SLT


SLT Function

- **slt** function is defined as:

$$A \text{ slt } B = \begin{cases} 000 \dots 001 & \text{if } A < B, \text{ i.e. if } A - B < 0 \\ 000 \dots 000 & \text{if } A \geq B, \text{ i.e. if } A - B \geq 0 \end{cases}$$


- Thus, each 1-bit ALU should have an additional input (called “**Less**”), that will provide results for **slt** function. This input has value 0 for all but 1-bit ALU for the least significant bit.
- For the least significant bit **Less** value should be sign of $A - B$

SLT Example

 

- Configure 32-bit ALU for SLT operation: $A = 25$ and $B = 32$
 - $A < B$, so Y should be 32-bit representation of 1 ($0x00000001$)
 - $F_{2:0} = 111$
 - $F_2 = 1$ (adder acts as subtractor), so $25 - 32 = -7$
 - -7 has 1 in the most significant bit ($S_{31} = 1$)
 - $F_{1:0} = 11$ multiplexer selects $Y = S_{31}$ (zero extended) = $0x00000001$.

4-bit Arithmetic Circuit

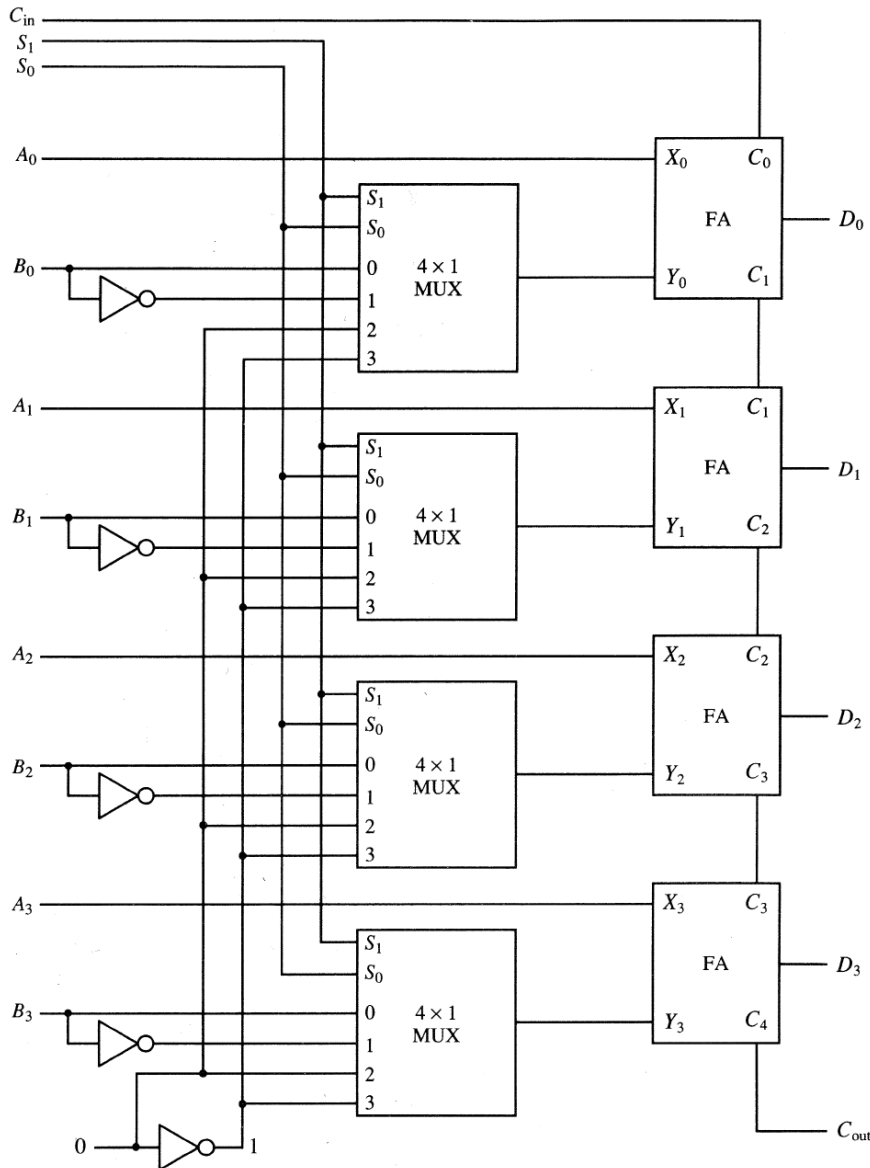

Function Table


Select			Input Y	Output $D = A + Y + C_{in}$	Microoperation
S_1	S_0	C_{in}			
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	\bar{B}	$D = A + \bar{B}$	Subtract with borrow
0	1	1	\bar{B}	$D = A + \bar{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A



Thoughts!

Can you reverse-engineer this circuit?

Hardware Implementation

 

(a) Logic diagram

S_1	S_0	Output	Operation
0	0	$E = A \wedge B$	AND
0	1	$E = A \vee B$	OR
1	0	$E = A \oplus B$	XOR
1	1	$E = \bar{A}$	Complement

(b) Function table

One stage of a logic circuit

References

- Lecture Notes of Dr. Sebastian Magierowski – Fall 2013
- “Digital Design, Morris Mano , Prentice Hall