

EECS2602 Z: Continuous Time Signals and Systems

Instructor: Hui Jiang

Quiz # 2 (12% of the course)

your mark: / 70

Time Allowed: 60 minutes

Name: _____

Student ID Number: _____ York EECS Email: _____

1. (12 points) Write TRUE or FALSE for each of the following statements and justify briefly.

3.1 The system $y(t) = |x(t)|$ is invertible. [**FALSE**]

$y(t) = |x(t)|$ is not one-to-one mapping function

3.2 The system $y(t) = \text{sgn}(x(t))$ is nonlinear. [**TRUE**]

take one example: $x(t) = u(t) \rightarrow y(t)$

take another example: $x'(t) = 2 u(t) \rightarrow y'(t) = y(t) \neq 2 y(t)$

3.3 The system $y(t) = \int_{t-10}^t |x(\tau)| d\tau$ is non-causal. [**FALSE**]

$y(t)$ only depends on $x(t)$ from $t-10$ to t , all of which is history ...

3.4 The system $\frac{dy(t)}{dt} + 2y(t) = 3x(t)$ is always linear. [**FALSE**]


It is not linear if it has non-zero initial conditions.

2. (24 marks) The following electrical circuit consists of two resistors R_1 and R_2 , and a capacitor C .

(i) (8 marks) Determine the differential equation relating the input voltage $v(t)$ to the output voltage $y(t)$.

(ii) (6 marks) Determine whether the system is (a) linear; (b) time-invariant; (c) memory less; (d) causal; (e) invertible; and (f) stable.

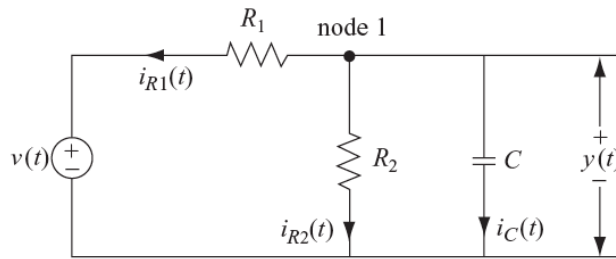(iii) (10 marks) Assume the system is initially rest, $R_1=1$, $R_2=2$, $C=1$, determine the output signal $y(t)$ when the input $x(t) = \cos(t) \cdot u(t)$.



Q2:

(i)

$$i_{R_1}(t) = \frac{y(t) - v(t)}{R_1}$$

$$i_{R_2}(t) = \frac{y(t)}{R_2}$$

$$i_C(t) = C \frac{dy(t)}{dt}$$

$$i_{R_1} + i_{R_2} + i_C = 0 \Rightarrow C \frac{dy(t)}{dt} + \frac{y(t)}{R_2} + \frac{y(t) - v(t)}{R_1} = 0$$

$$\Rightarrow \frac{dy(t)}{dt} + \frac{R_1 + R_2}{CR_1 R_2} y(t) = \frac{1}{CR_1} v(t)$$

iii). $R_1=1$, $R_2=2$, $C=1$.

$$\Rightarrow \frac{dy(t)}{dt} + \frac{3}{2} y(t) = v(t)$$

characteristic equation: $s + \frac{3}{2} = 0$

Homogenous component: $s = -\frac{3}{2}$

$$y_h(t) = A \cdot e^{-\frac{3}{2}t}$$

particular component.

$$x(t) = \cos(t) u(t) \Rightarrow y_p(t) = C_1 \sin t + C_2 \cos t$$

This page is for Q2.

ii) The system can be either linear or nonlinear, depending on the initial conditions.

The system is time-invariant.

The system has memory.

The system is causal.

The system is not invertible if the initial conditions are not zero

The system is stable

$$C_1 \cos t + C_2 \sin t + \frac{3}{2} (C_1 \sin t + C_2 \cos t) = \cos t$$
$$\Rightarrow \begin{cases} C_1 + \frac{3}{2} C_2 = 1 \\ \frac{3}{2} C_1 - C_2 = 0 \end{cases} \Rightarrow C_2 = \frac{3}{2} C_1$$
$$\Rightarrow C_1 + \frac{9}{4} C_1 = 1 \Rightarrow C_1 = \frac{4}{13} \quad C_2 = \frac{6}{13}$$
$$y_p(t) = \frac{4}{13} \sin t + \frac{6}{13} \cos t$$

Complete response

$$y(t) = A \cdot e^{-\frac{3}{2}t} + \frac{4}{13} \sin t + \frac{6}{13} \cos t$$
$$y(0) = A + \frac{6}{13} = 0 \Rightarrow A = -\frac{6}{13}$$


Finally:

$$y(t) = \left[-\frac{6}{13} e^{-\frac{3}{2}t} + \frac{4}{13} \sin t + \frac{6}{13} \cos t \right] u(t)$$

3. (24 marks) Given the following electrical circuit, assume $C = 1$, $R = \frac{1}{2}$, $L = \frac{1}{2}$,

(i) (8 marks) Determine the differential equation relating the input voltage $v(t)$ to the output voltage $y(t)$.

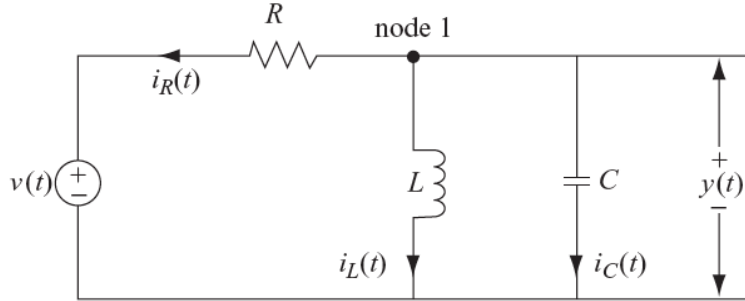(ii) (16 marks) Determine the output signal $y(t)$ when we apply the input signal $v(t) = e^{-2t}$ at the time instance $t = 0$, Assume $y(0^-) = 5$, $y'(0^-) = -2$.



Q3:

$$(i) \quad i_R(t) = \frac{y(t) - v(t)}{R}$$

$$i_C(t) = C \frac{dy(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t y(\tau) d\tau$$

$$i_R + i_L + i_C = 0$$

$$\Rightarrow \frac{y(t) - v(t)}{R} + C \cdot \frac{dy(t)}{dt} + \frac{1}{L} \int_{-\infty}^t y(\tau) d\tau = 0$$

$$\Rightarrow C \cdot \frac{d^2 y(t)}{dt^2} + \frac{1}{R} \cdot \frac{dy(t)}{dt} + \frac{1}{L} y(t) = \frac{1}{R} \frac{dv(t)}{dt}$$

$$\Rightarrow \frac{d^2 y(t)}{dt^2} + \frac{1}{RC} \cdot \frac{dy(t)}{dt} + \frac{1}{Lc} y(t) = \frac{1}{RC} \frac{dv(t)}{dt}$$

$$C = 1, \quad R = \frac{1}{2}, \quad L = \frac{1}{2}$$

$$\frac{d^2 y(t)}{dt^2} + 2 \frac{dy(t)}{dt} + 2 y(t) = 2 \frac{dv(t)}{dt}$$

$$\begin{aligned} x(t) &= 2 \frac{dv(t)}{dt} \\ &= -4 e^{-2t} \end{aligned}$$

ii) homogeneous component.

characteristic equation.

$$s^2 + 2s + 2 = 0 \Rightarrow (s+1)^2 + 1 = 0$$

$$\Rightarrow s = -1 \pm j$$

$$y_h(t) = A_1 e^{-t} \cos t + A_2 e^{-t} \sin t$$

Particular component:

$$x(t) = -4e^{-2t} \Rightarrow y(t) = ce^{-2t}$$

$$\cancel{4c \cdot e^{-2t}} - \cancel{4e^{-2t}} + 2c \cdot e^{-2t} = -4e^{-2t}$$

$$c = -2$$

complete response:

$$y(t) = A_1 e^{-t} \cos t + A_2 e^{-t} \sin t - 2e^{-2t}$$

$$y(0) = A_1 - 2 = 5$$

$$y'(t) = -A_1 e^{-t} \sin t - A_1 e^{-t} \cos t + A_2 e^{-t} \cos t - A_2 e^{-t} \sin t + 4e^{-2t}$$

$$y'(0) = -A_1 + A_2 + 4 = -2 \Rightarrow \begin{cases} A_1 = 7 \\ A_2 = 1 \end{cases}$$

4. (10 marks) Prove: $x(t) = \int_{-\infty}^{+\infty} x(\tau) \cdot \delta(t - \tau) d\tau$.

I) use the property of impulse signals.

$$\begin{aligned} & \int_{-\infty}^{+\infty} x(\tau) \cdot \delta(t - \tau) d\tau \\ &= \int_{-\infty}^{+\infty} x(\tau) \Big|_{\tau=t} \cdot \delta(t - \tau) d\tau \\ &= x(t) \int_{-\infty}^{+\infty} \delta(t - \tau) d\tau \\ &= x(t) \end{aligned}$$

II) use limit to the rectangular approximation.